

ECE 320 - Quiz #7 - Name _____

DC to AC, SCR

DC to AC Converter

1) Assume the Fourier transform for the output of a DC to AC converter driving a 1 Ohms resistor is as follows:

- note: units are Vp (peak voltage)
- $Energy = \frac{1}{2}(a_n^2 + b_n^2)$ *Watts: assumes a 1 Ohm resistive load*

Harmonic	0 (DC)	1	2	3	4	5
an (cosine)	0	Birth Month (1..12)	0	0	0	0
bn (sine)	0	Birth Date (1..31)	0	0	0	0

Determine the following:

Total Energy in the signal Watts	Energy in the 1st harmonic Watts	Efficiency % of energy in the 1st harmonic

DC to AC Converter

2) Assume the Fourier transform for the output of a DC to AC converter driving a 1 Ohms resistor is as follows:

- note: units are Vp (peak voltage)
- *Watts: assumes a 1 Ohm resistive load*
- $Energy = \frac{1}{2}(a_n^2 + b_n^2)$

Harmonic	0 (DC)	1	2	3	4	5
an (cosine)	0	60Vp	0	10Vp	Birth Date (1..31)	0
bn (sine)	0	0	Birth Month (1..12)	0	0	5Vp

Determine the following:

Total Energy in the signal Watts	Energy in the 1st harmonic Watts	Efficiency % of energy in the 1st harmonic


Circuits & Differential Equations

3) Write the differential equation which describes the following circuit. Assume

- L = your birth month (1..12) mH
- $R2$ = your birth date (1..31) Ohms

Note:

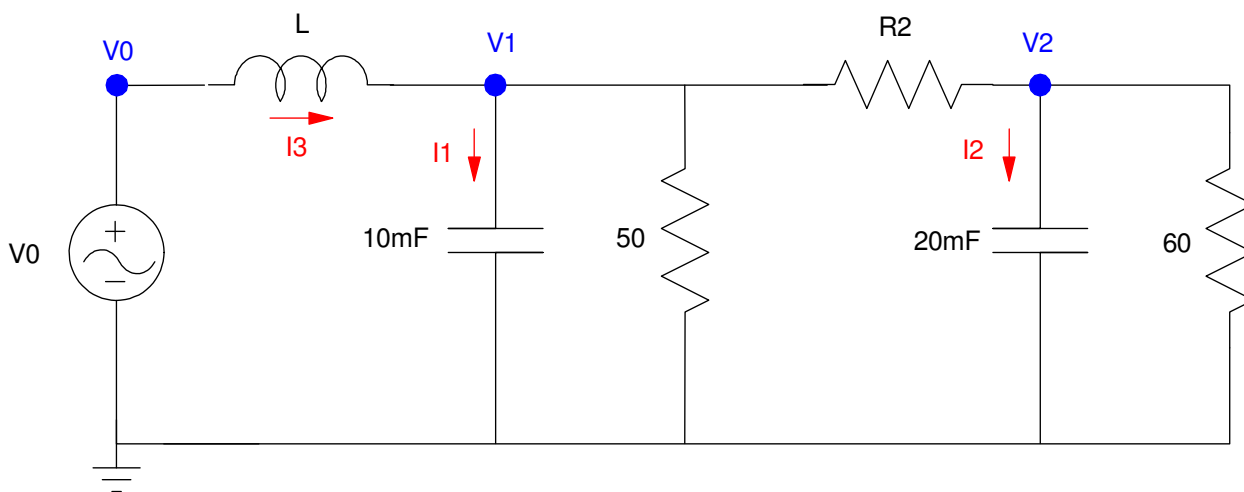- $I = C \frac{dV}{dt}$
- $V = L \frac{dI}{dt}$




SCR (4 diode version)

4) SCR: Analysis. Determine the voltages at V1 and V2 (both DC). Assume

- R1 = your birth month (1..12)
- X = 10 + your birth date (11..41 degree firing angle)

Firing Angle day + 10	V1		V2	
	DC	AC (V1pp)	DC	AC (V2pp)

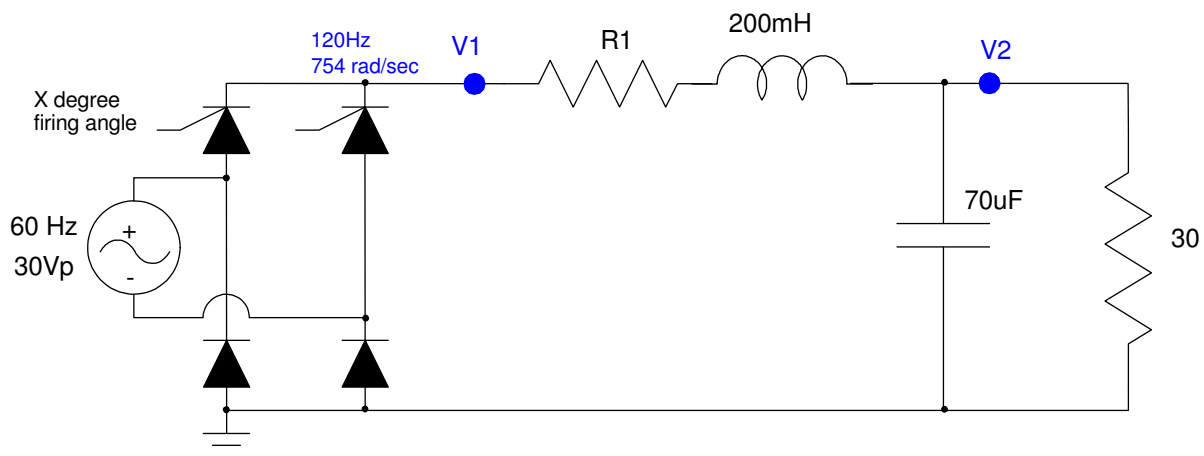


SCR (5 diode version)

5) SCR: Analysis. Determine the voltages at V1 and V2 (both DC). Assume

- $R1 = \text{your birth month (1..12)}$
- $X = 10 + \text{your birth date (11..41 degree firing angle)}$

Firing Angle day + 10	V1		V2	
	DC	AC (V1pp)	DC	AC (V2pp)

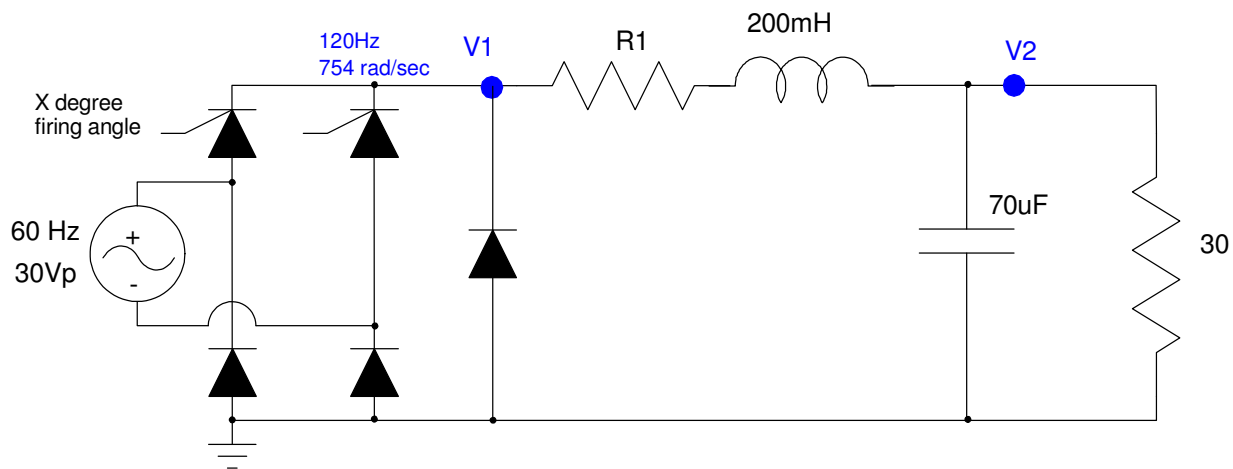

6) SCR Design. Determine the firing angle and C so that

- $V2(\text{DC}) = 10.00\text{V}$
- $V2(\text{AC}) = 1.00\text{Vpp}$
- $R1 = \text{Your Birth Month (1..12)}$

V1(DC)	Firing Angle	C	R1 Month (1..12)

