

ECE 320 - Quiz #8 - Name _____

Boolean Logic, DTL, TTL Logic, MOSFETs.

Boolean Logic

- 1) Design a circuit using NAND gates to implement the following logic

		f(A,B,C,D)			
		CD			
		00	01	11	10
AB	00	x	x	x	1
	01	0	0	0	x
	11	0	1	1	1
	10	1	x	x	x

2) Design a circuit using NOR gates to implement the following logic:


		f(A,B,C,D)			
		CD			
		00	01	11	10
AB	00	x	x	x	1
	01	0	0	0	x
	11	0	1	1	1
	10	1	x	x	x

DTL: 10V Logic Logic

3) Determine the voltges and currents for the following DTL gate. Assume

- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, gain = 100)
- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 900 + 100(\text{Birth Month}) + (\text{Birth Day})$.

R $900 + 100 \cdot \text{mo} + \text{day}$	V_1	I_2	V_3	I_4	V_5

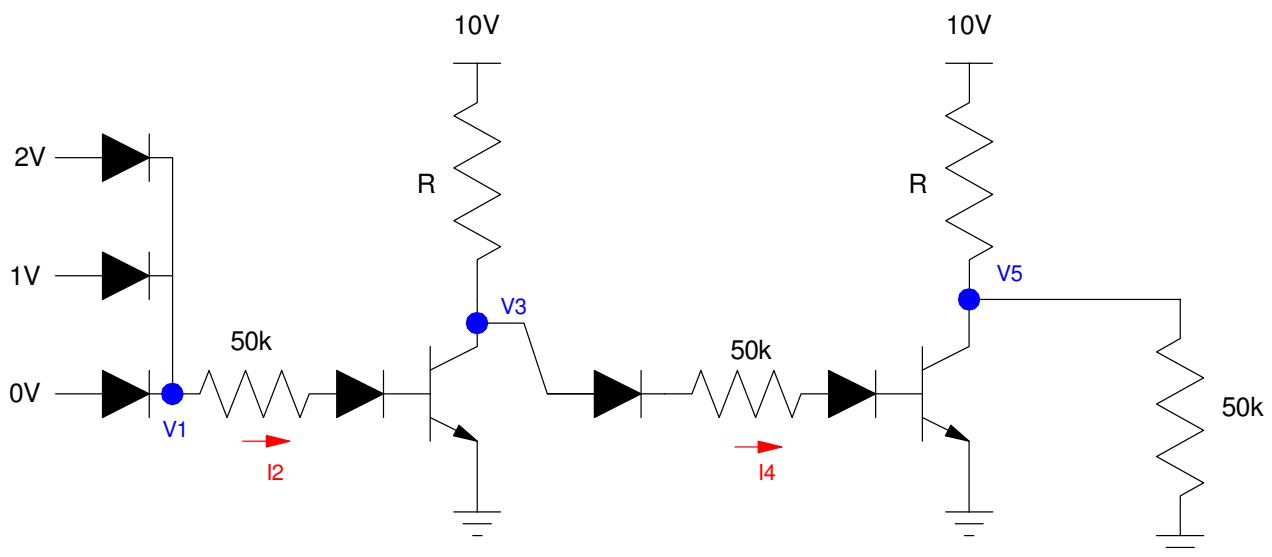


DTL 10V Logic Gate:

4) Determine the voltages and currents for the following DTL gate. Assume

- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, gain = 100)
- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 900 + 100(\text{Birth Month}) + (\text{Birth Day})$.

R $900 + 100 \cdot \text{mo} + \text{day}$	V_1	I_2	V_3	I_4	V_5

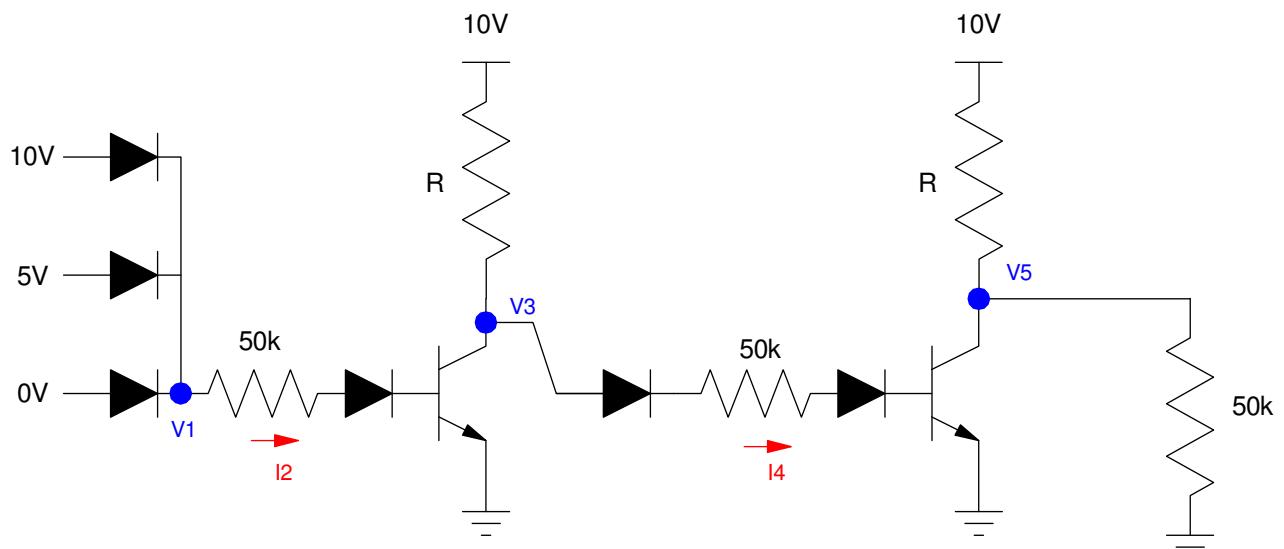


10V Open Collector Logic

5) Determine the voltages and currents for the following circuit. Assume

- Ideal silicon diodes ($V_f = 0.7V$)
- $V_{be} = 0.7V$
- $\beta = 100$
- $R = 900 + 100(\text{Birth Month}) + (\text{Birth Day})$.

R $900 + 100 \cdot \text{mo} + \text{day}$	I_1	I_2	I_3	V_4

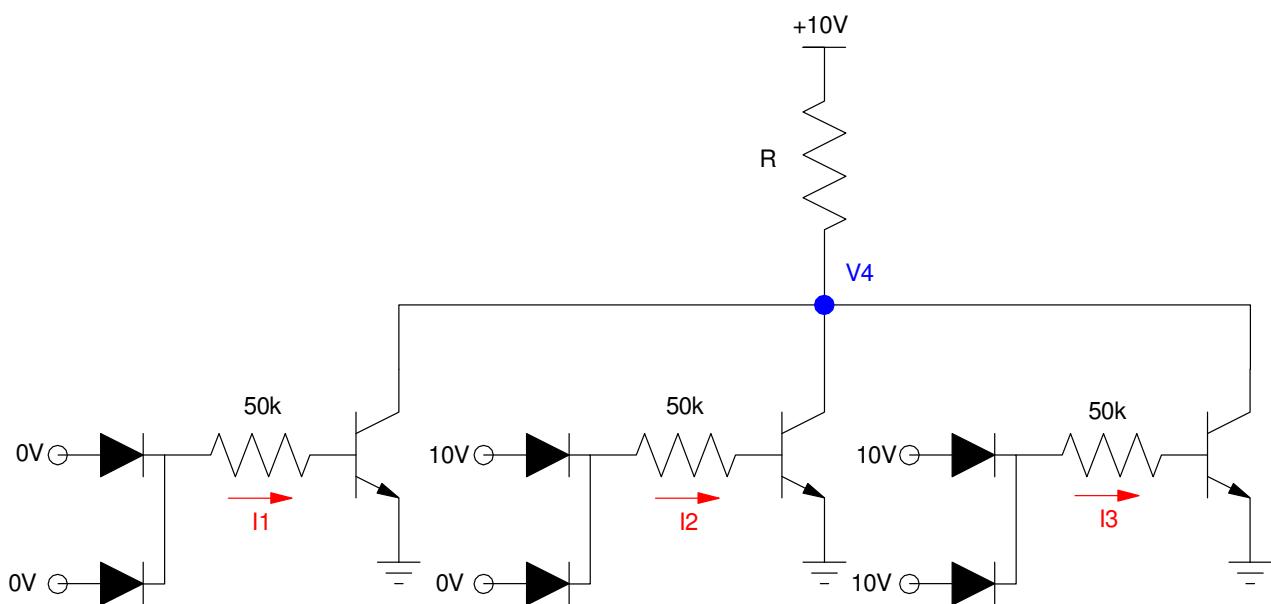

TTL Logic

6) Determine the voltages and currents for the following TTL gate. Assume

- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, $\beta = 100$)
- $R = 900 + 100(\text{Birth Month}) + (\text{Birth Day})$.

R $900 + 100 \cdot \text{mo} + \text{day}$	V_1	V_2	V_3	I_4	I_5

