

ECE 320 - Homework #2

Semiconductors, PN Junction. Due Monday, January 24th

Please make the subject "ECE 320 HW#2" if submitting homework electronically to Jacob_Glower@yahoo.com (or on blackboard)

Semiconductors

1) Why does current flow p-to-n but not n-to-p across a pn junction?

Several ways to answer this (any are OK)

Answer 1)

- When current flows p to n, it uses majority carriers. A large number of carriers means low resistance.
- When current flows n to p, it uses minority carriers. A small number of carriers means high resistance.

Answer 2) A depletion zone exists across the pn junction. This prevents current flow.

- Voltage p to n decreases the depletion zone. When it goes to zero, current flows (about 0.7V for silicon)
- Voltage n to p increases the depletion zone (blocking current flow)

Answer 3) A potential energy barrier is created across the pn junction

- Voltage in excess of this barrier (0.7V for silicon) allows current to flow
- Voltage less than this barrier results in no current

2) What doping of phosphorus (n-type) do you need to make an 1206 resistor have a resistance of 1200 Ohms? The dimensions of an 1206 resistor are

$$L = 3.20\text{mm}, W = 1.60\text{mm}, H = 0.95\text{mm}$$

$$R = \left(\frac{\rho L}{A} \right)$$

$$1200\Omega = \left(\frac{\rho \cdot 0.32\text{cm}}{(0.16\text{cm})(0.091\text{cm})} \right)$$

$$\rho = 54.6\Omega \cdot \text{cm}$$

$$\sigma = \frac{1}{\rho} = 0.01832 \frac{1}{\Omega \cdot \text{cm}} = n_n \cdot q \cdot \mu_n$$

$$0.01832 \frac{1}{\Omega \cdot \text{cm}} = n_n \cdot (1.6 \cdot 10^{-19}) \cdot (1300)$$

$$n_n = 8.805 \cdot 10^{13} \frac{\text{atoms}}{\text{cc}}$$

That seems like a large number, but it's one phosphorus atom for every 1e10 silicon atoms.

3) A thermistor has the following resistance - voltage relationship

$$R = 1000 \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$

where T is the temperature in degrees C. What is the resistance at

0F Recommended temperature of a freezer

- -17.778C
- 8992 Ohms

+40F Recommended temperature of a refrigerator

- 4.444C
- 2640 Ohms

+68F Temperature of cold tap water (varies)

- 20.000C
- 1250 Ohms

+120F Temperature of hot tap water (varies)

- 48.49C
- 378 Ohms

Note that there is a large change in resistance with respect to temperature for thermistors.

Diode VI Characteristics


Assume the VI characteristics for a diode are (1N4004 diode in CircuitLab)

- $n = 1.45$
- $n V_t = 0.0377$
- $I_{dss} = 7.69e-11$

$$V_d = 0.0377 \cdot \ln\left(\frac{I_d}{7.69 \cdot 10^{-11}} + 1\right) \quad I_d = 7.69 \cdot 10^{-11} \left(\exp\left(\frac{V_d}{0.0377}\right) - 1\right)$$

4) For the 1-diode circuit (next page - 100 Ohms is brown - black - brown)

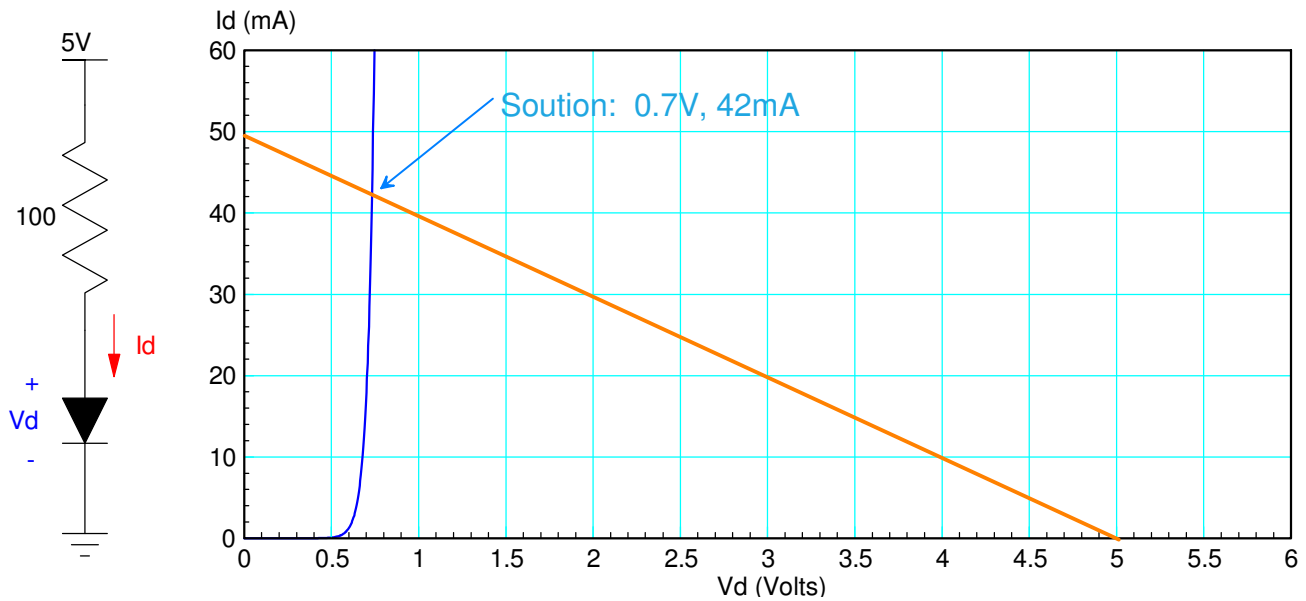- a) Draw the load-line for the following circuit (next page). Determine V_d and I_d from the graph.
- b) Write the voltage node equations and solve for V_d and I_d assuming the VI equations above



Numerical Solution

$$V_d = 0.0377 \cdot \ln\left(\frac{I_d}{7.69 \cdot 10^{-11}} + 1\right)$$


$$V_d + 100I_d = 5$$

Solving:

$$I_d = 42.4117\text{mA}$$


$$V_d = 0.7588\text{V}$$

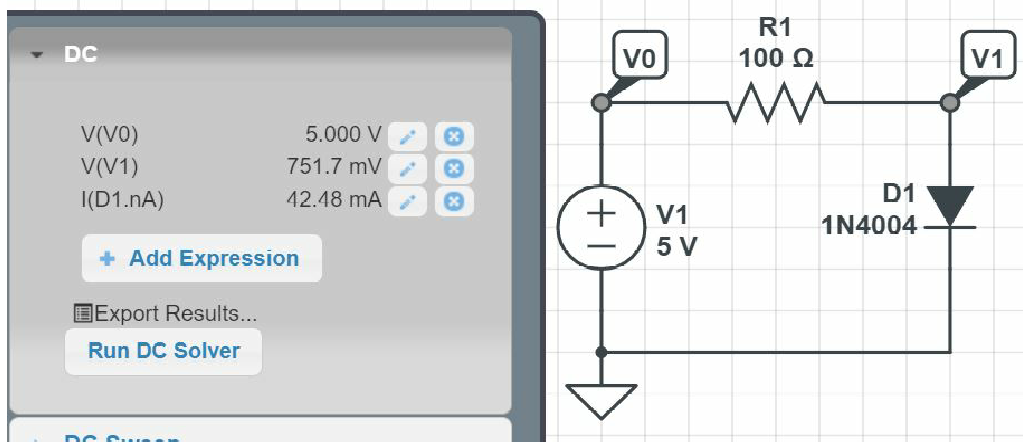5) Build this circuit in CircuitLab and solve for V_d and I_d . (Use a 1N4004 diode)



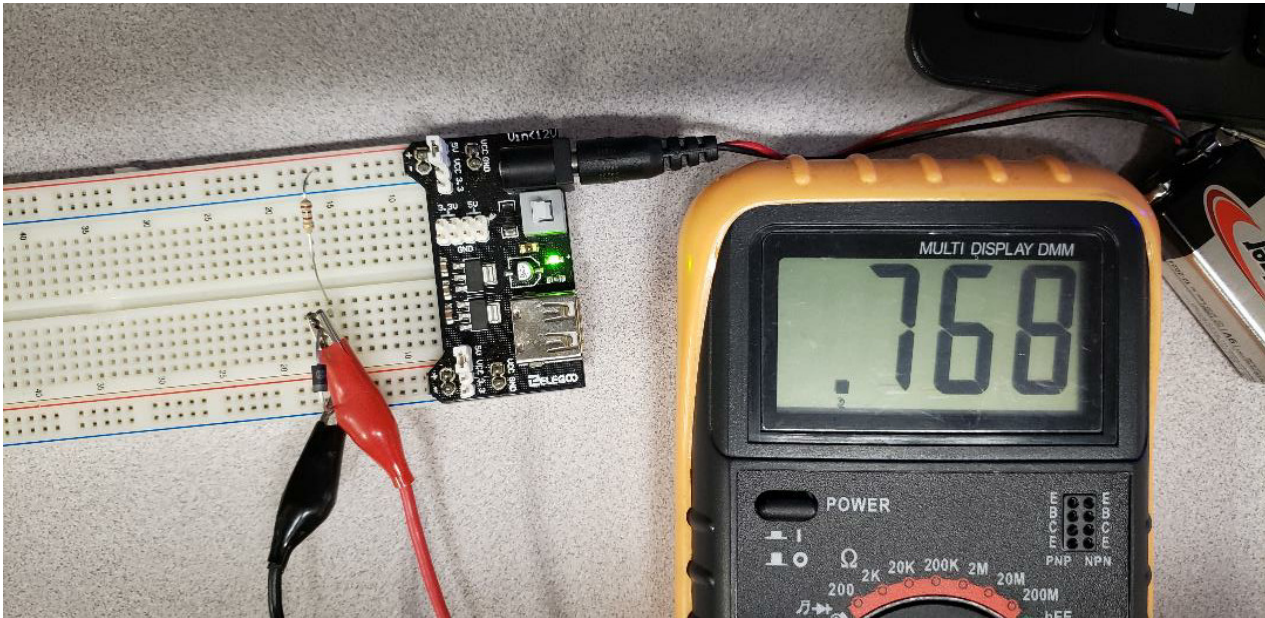6) Build this circuit on your breadboard and measure V_d . From this, compute I_d


- Include a photo to receive credit for this problem



	V_d	I_d
4a) Graphical solution	0.7V	42mA
4b) Numeric Solution	0.7588V	42.4117mA
5) Simulation (CircuitLab)	0.7517V	42.483mA
6) Lab (experimental)	0.768V	42.32mA (calculated from V_d)

Problem 8 - 10: *Note: If you don't have four 100 Ohm resistors (brown - black - brown), replace the resistors with ones you *do* have - ideally all the same and close to 100 Ohms. Do problems 8 - 10 using the resistors you use for the experimental results (problem #10).*

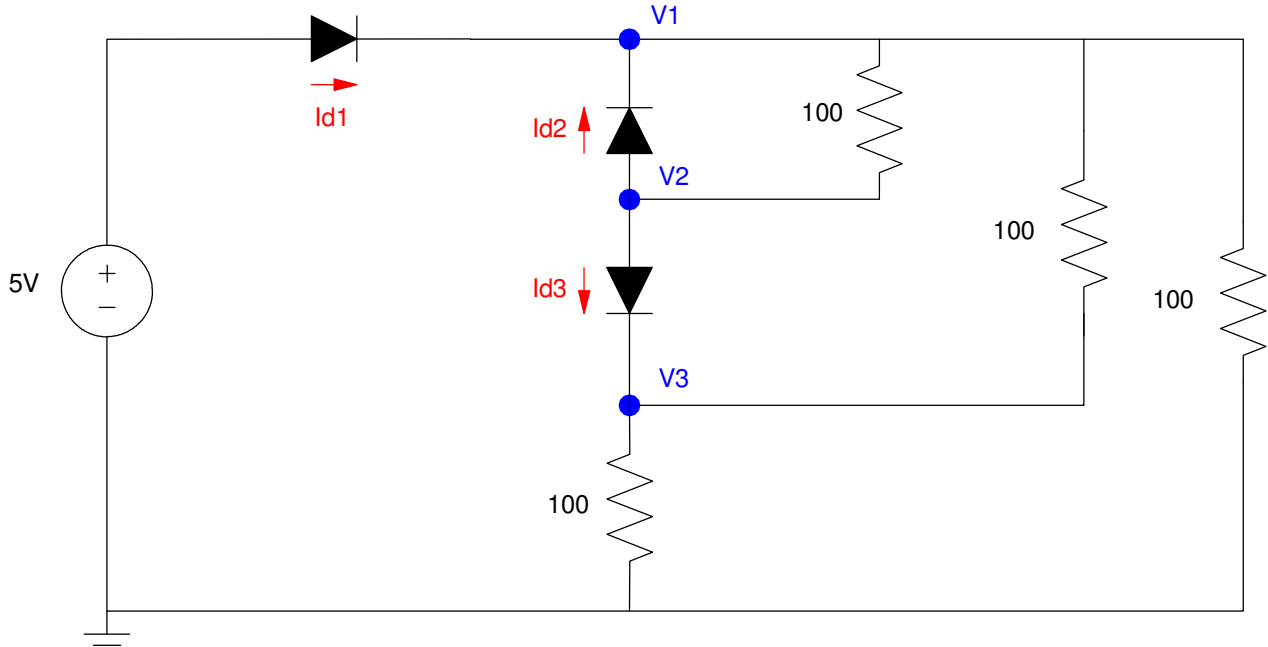8) Write the voltage node equations assuming nonlinear diodes. Solve for {V1, V2, and V3} using Matlab.



$$I_{d1} = 7.69 \cdot 10^{-11} \left(\exp \left(\frac{5-V_1}{0.0377} \right) - 1 \right)$$

$$I_{d2} = 7.69 \cdot 10^{-11} \left(\exp \left(\frac{V_2-V_1}{0.0377} \right) - 1 \right)$$

$$I_{d3} = 7.69 \cdot 10^{-11} \left(\exp \left(\frac{V_2-V_3}{0.0377} \right) - 1 \right)$$

$$-I_{d1} - I_{d2} + \left(\frac{V_1-V_2}{100} \right) + \left(\frac{V_1-V_3}{100} \right) + \left(\frac{V_1}{100} \right) = 0$$

$$I_{d2} + I_{d3} + \left(\frac{V_2-V_1}{100} \right) = 0$$

$$-I_{d3} + \left(\frac{V_3}{100} \right) + \left(\frac{V_3-V_1}{100} \right) = 0$$

Solve in Matlab

Create an m-file where you guess {V1, V2, V3} and it returns how good your guess was

```
function [ J ] = Diode3( z )
V1 = z(1);
V2 = z(2);
V3 = z(3);

Idss = 7.69e-11;
nVt = 0.0377;

Id1 = Idss* exp( (5 - V1)/nVt - 1 );
Id2 = Idss* exp( (V2 - V1)/nVt - 1 );
Id3 = Idss* exp( (V2 - V3)/nVt - 1 );

e1 = -Id1 - Id2 + (V1-V2)/100 + (V1-V3)/100 + V1/100;
e2 = Id2 + Id3 + (V2-V1)/100;
e3 = -Id3 + V3/100 + (V3-V1)/100;

J = (e1)^2 + (e2)^2 + (e3)^2;

disp([V1, V2, V3, log10(J)])
pause(0.1)

end
```

Solve using fminsearch()

```
>> [Z,e] = fminsearch('Diode3',[3,2,1])
    3.0000    2.0000    1.0000   138.9076
    3.1500    2.0000    1.0000   135.4790
    :
    :
    4.1861    3.2828    2.5446  -10.9365
    4.1861    3.2829    2.5447  -12.3080


Z =      V1      V2      V3
     4.1861     3.2829     2.5447

e =

    4.9206e-013

>>
```

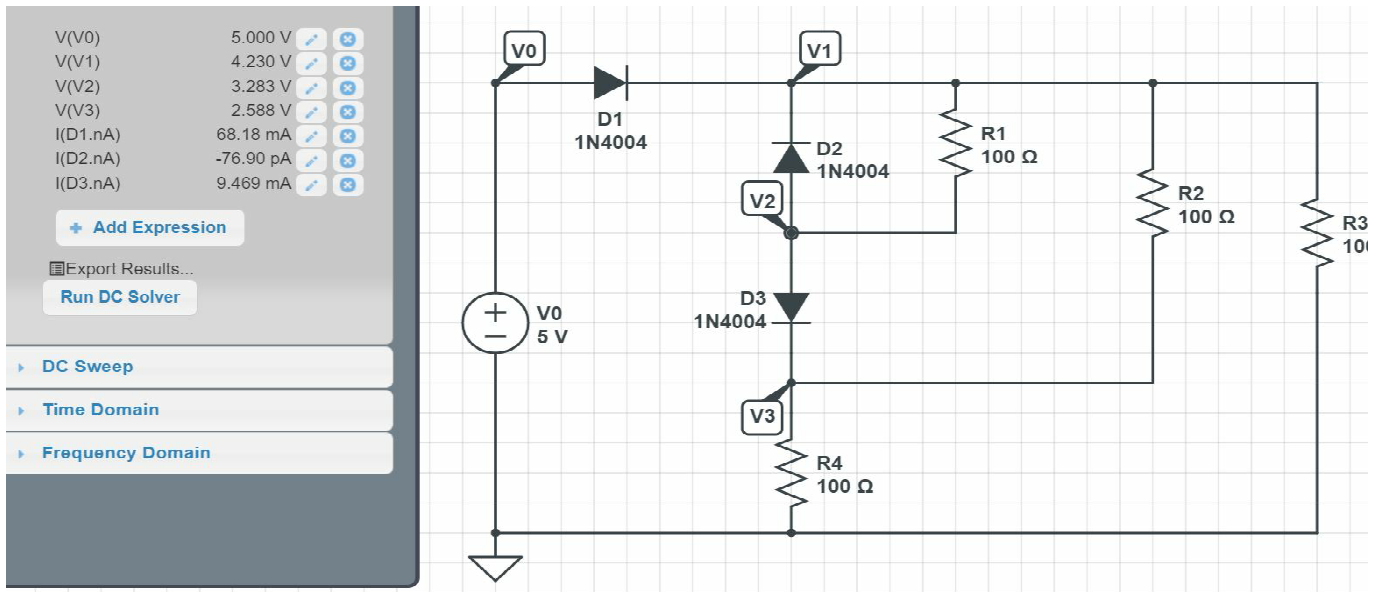
9) Simulate this circuit in CircuitLab to determine {V1, V2, and V3}




10) Build this circuit with your breadboard and measure {V1, V2, V3} +5V V1 V2 V3 gnd

- Include a photo to receive credit for problem #10

	V1	V2	V3
8) Numeric Solution	4.1861 V	3.2829 V	2.5447 V
9) Simulation (CircuitLab)	4.230 V	3.283 V	2.588 V
10) Lab (experimental)	4.17 V	3.25 V	2.55 V

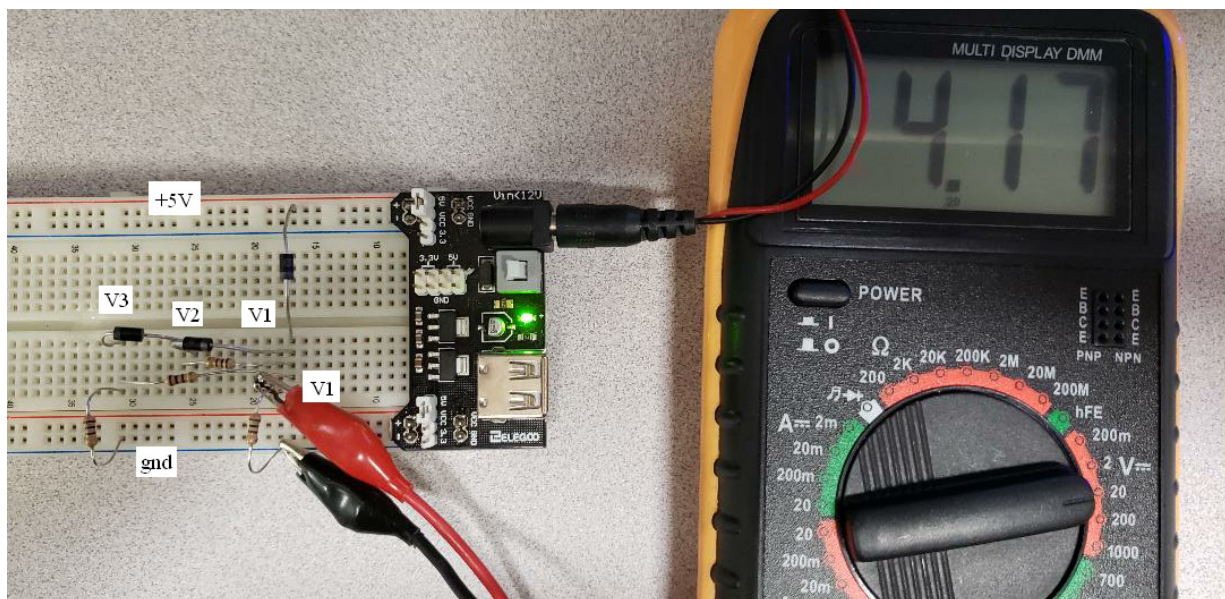

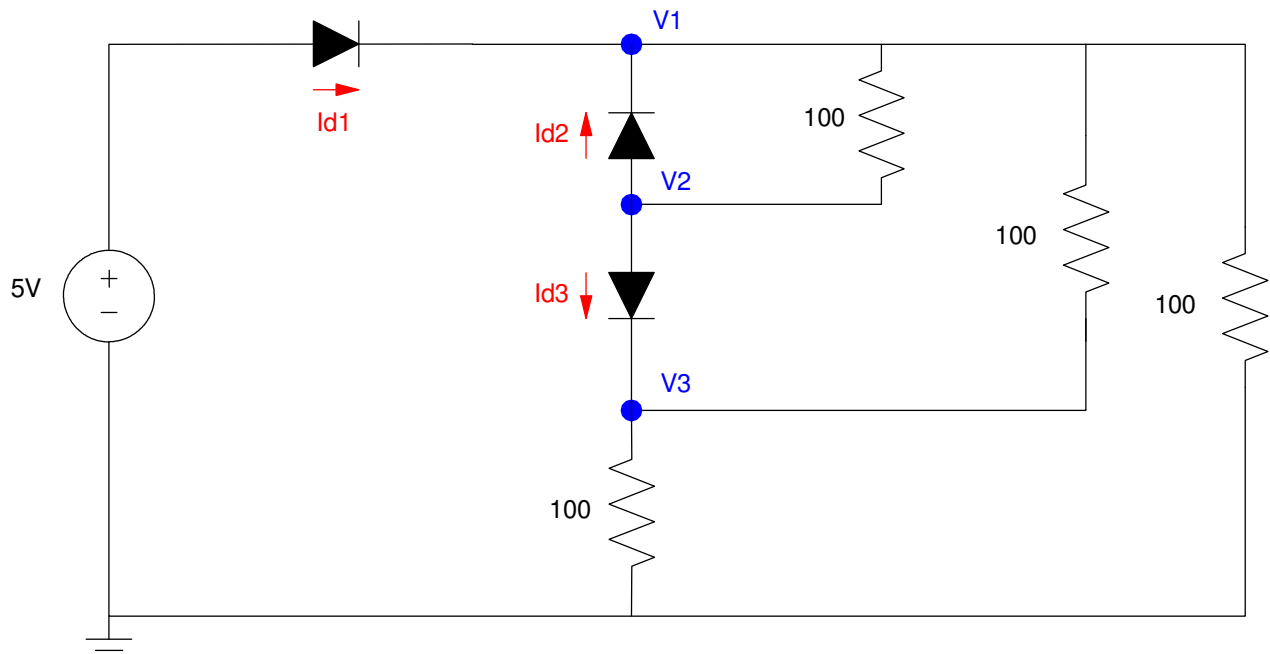

Problem 8-11. Change the resistors if you don't have four 100 Ohm resistors available