

ECE 320 - Homework #5

555 Timers, Transistors used as a Switch, Schmitt Triggers. Due Monday, February 14th

Assume a 3904 transistor (NPN) and 3906 (PNP) (\$0.04 each)

$$b = 100 \quad \min(|V_{ce}|) = 0.2V \quad \max(I_c) = 200mA$$

Assume a thermistor with

$$R = 1000 \exp \left(\frac{3905}{T+273} - \frac{3905}{298} \right) \text{ W}$$

555 Timers

1) Determine the on and off times for the voltage at V2 for following 555-timer circuit

On-Time: charge through R1 and R2

$$T_{on} = (R_1 + R_2) \cdot C \cdot \ln(2)$$

$$T_{on} = (10k + 20k) \cdot 0.1\mu F \cdot \ln(2)$$


$$T_{on} = 2.079ms$$

Off-Time: discharge through R2

$$T_{off} = R_2 \cdot C \cdot \ln(2)$$

$$T_{off} = 1.386ms$$

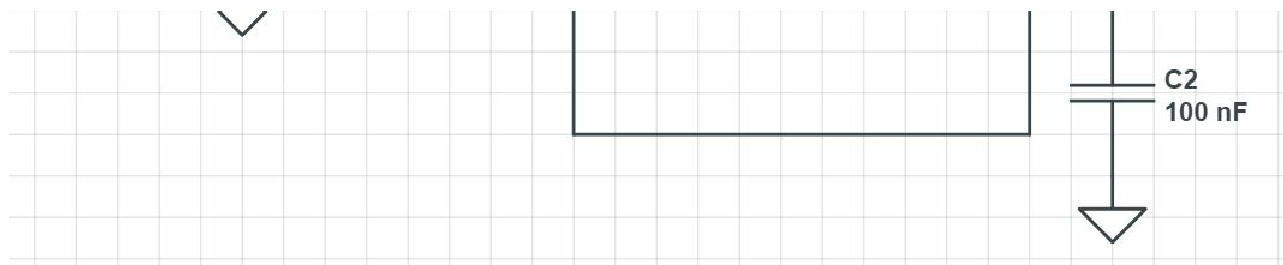2) Simulate this circuit in CircuitLab and verify the on and off times





Transistor Switch

3) Determine the voltages $\{V_b, V_c\}$ and currents $\{I_b, I_c\}$ when

When $V_2 = 0V$ (off)

- $V_b = 0V$
- $V_c = 5V$

When $V_2 = 5V$

- $V_b = 0.7V$ (ideal diode)
- $V_c = 0.2V$ (saturated)


4) Verify your calculations using CircuitLab

When $V_2 = 0V$

- $V_b = 0V$
- $V_c = 5V$

When $V_2 = 5V$

- $V_b = 0.8361V$
- $V_c = 0.2417V$

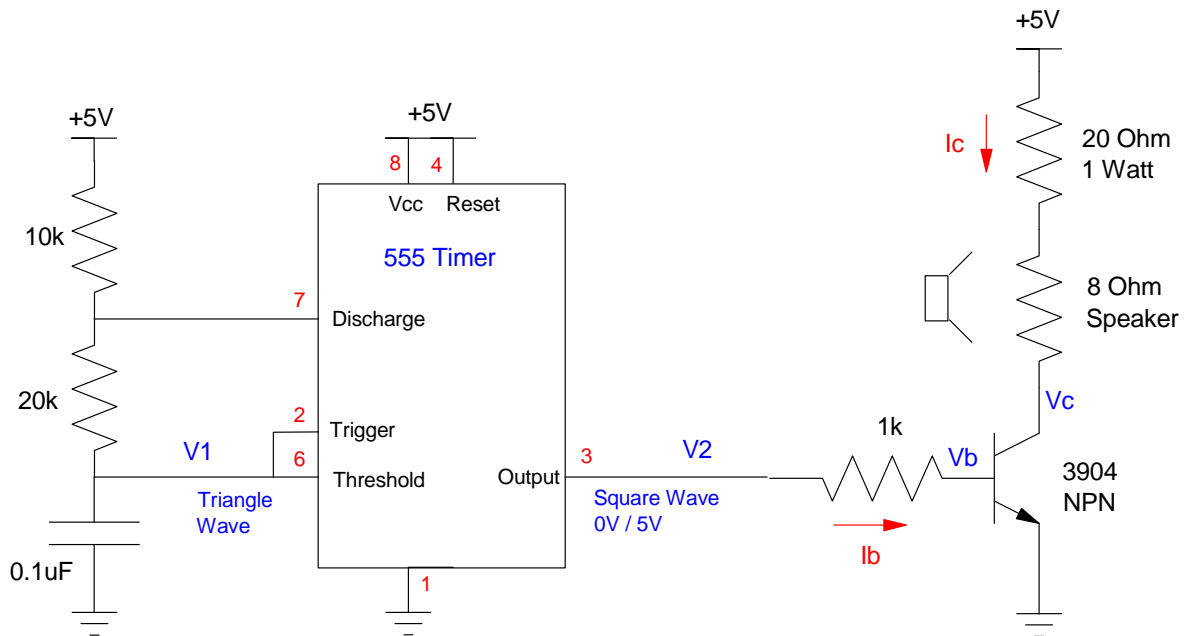

Comparator

Add an electronic switch to turn the speaker on and off

$$R = 1000 \exp \left(\frac{3905}{T+273} - \frac{3905}{298} \right) \text{ W}$$

5) Design a comparator (shown in blue - don't add the red resistors (they are for a Schmitt trigger)) to

- Turn on the speaker ($V_3 = 5V$) when $T > 40C$, and
- Turn off the speaker ($V_3 = 0V$) when $T < 40C$

At 40C



$$R = 533.66 \text{ ohms}$$

$$V_5 = 1.740V$$

Make $V_6 = 1.740V$ so that the comparator switches at 40C (create 1.740V with a voltage divider)

Connect the thermistor (V_5 thermistor) to the minus input so that

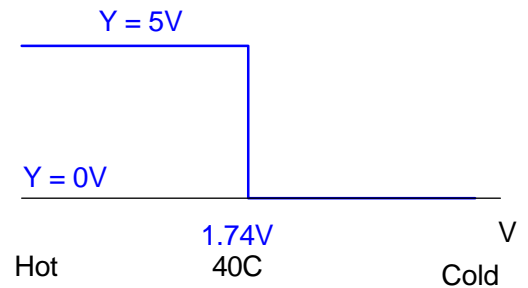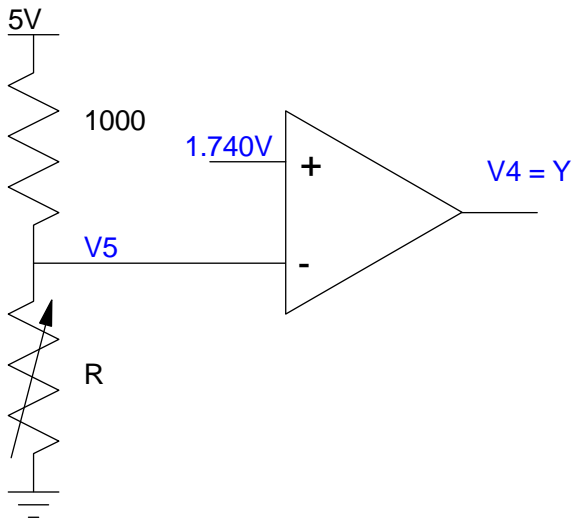- As temperature goes up, $R(\text{thermistor})$ goes down
- V_5 goes down
- V_4 goes up (V_4 is 5V when it's hot)




6) Simulate the comparator in CircuitLab to verify the on / off temperature (or resistance or voltage)

- use a voltage source (V4) to simulate the voltage at the voltage divider)




When V4 his high, the speaker plays (V3 oscillates as the transistors turn on and off with the 555 timer)

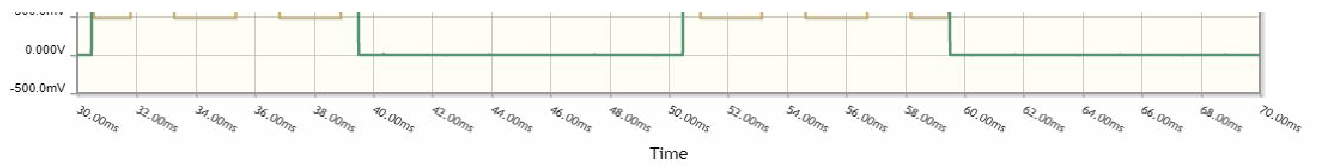When V4 is low, the speaker is off (V3 is a constant 5.00V meaning the transistors are off)



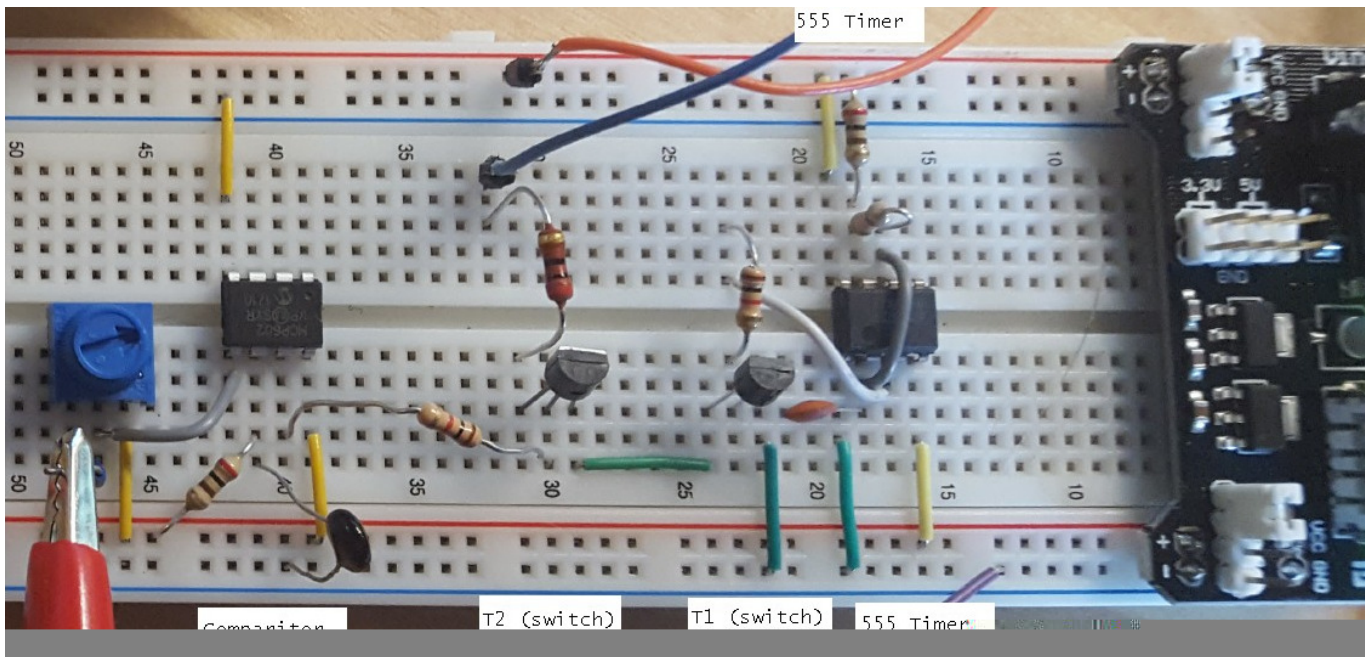7) Build this circuit and verify it s on and off temperature (or voltage or resistance. Replace R with a potentiometer for test purposes)



$V_p = 2.00V$ (set with a potentiometer)

- Turns on at 1.99V
- Turns off at 2.08V

Note that for a comparotor, $V(\text{on}) = V(\text{off})$ (approximately)

Schmitt Trigger

Add an electronic switch to turn the speaker on and off

8) Design a Schmitt Trigger (modify section in blue) to

- Turn on the speaker ($V3 = 5V$) when $T > 45C$, and
- Turn off the speaker ($V3 = 0V$) when $T < 40C$

$$R = 1000 \exp \left(\frac{3905}{T+273} - \frac{3905}{298} \right) \text{ W}$$

At 40C

- $R = 533.66 \text{ Ohms}$
- $V5 = 1.74V$
- $V4 = 0V$

At 45V

- $R = 438.61 \text{ Ohms}$
- $V5 = 1.524V$
- $V4 = 5V$



As $V5$ goes down, $V4$ goes up. Connect the voltage divider to the minus input

$V4$ is set when $V5 = 1.524V$. Make the offset 1.524V

The gain needed is

$$\text{gain} = \frac{\text{change in output}}{\text{change in input}} = \frac{5V - 0V}{1.74V - 1.524V} = 23.21$$

Make the resistors in a 23.31 : 1 ratio

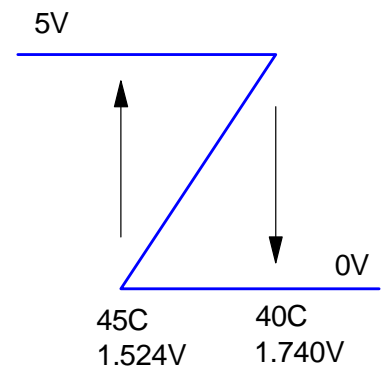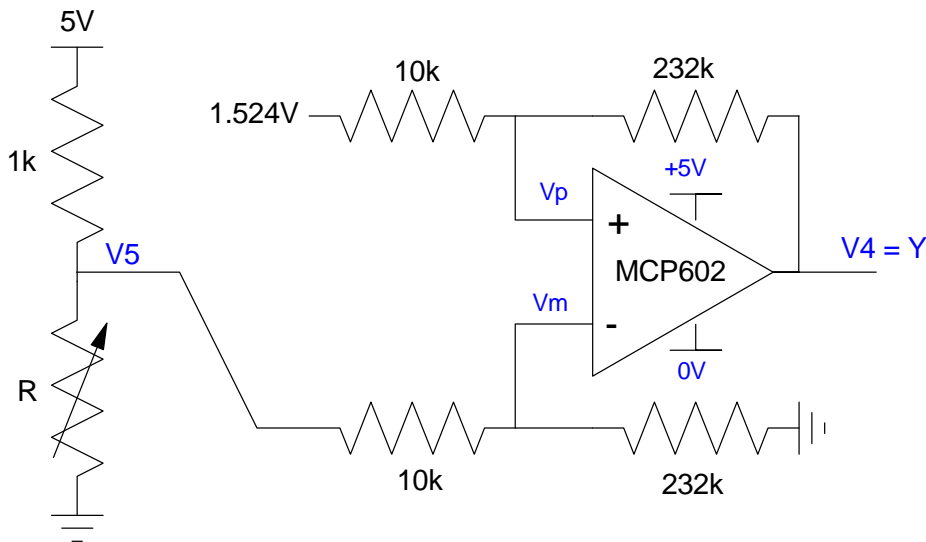

- 9) Simulate the comparator in CircuitLab to verify the on / off temperature (or resistance or voltage)
- use a voltage source (V4) to simulate the voltage at the voltage divider)

Time