

# ECE 320 - Homework #7


DC to AC, SCR. Due Monday, February 28th


## DC to AC

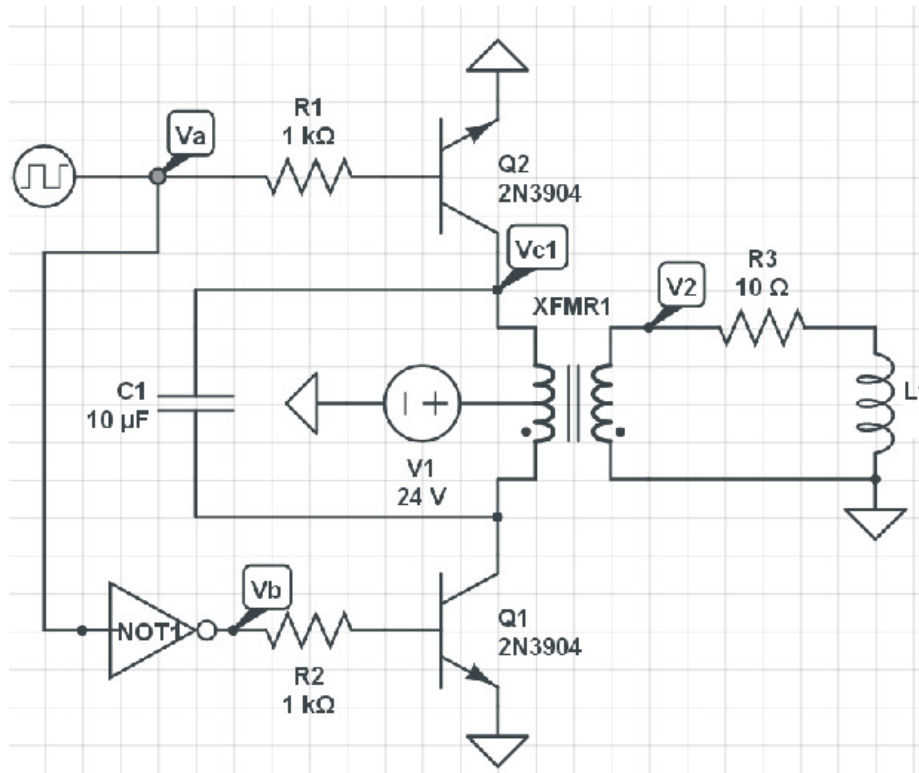1) Let  $L1 = 200\text{mH}$

- $V_a = 0\text{V} / 5\text{V}$  square wave, 60Hz, 0 degree time delay
- $V_b = 0\text{V} / 5\text{V}$  square wave, 60Hz, 180 degree time delay
- $C1 = 10\mu\text{F}$

Determine using CircuitLab the voltage  $V2$  (i.e. the voltage across a DC motor, modeled as a 10 Ohm & 100mH load)



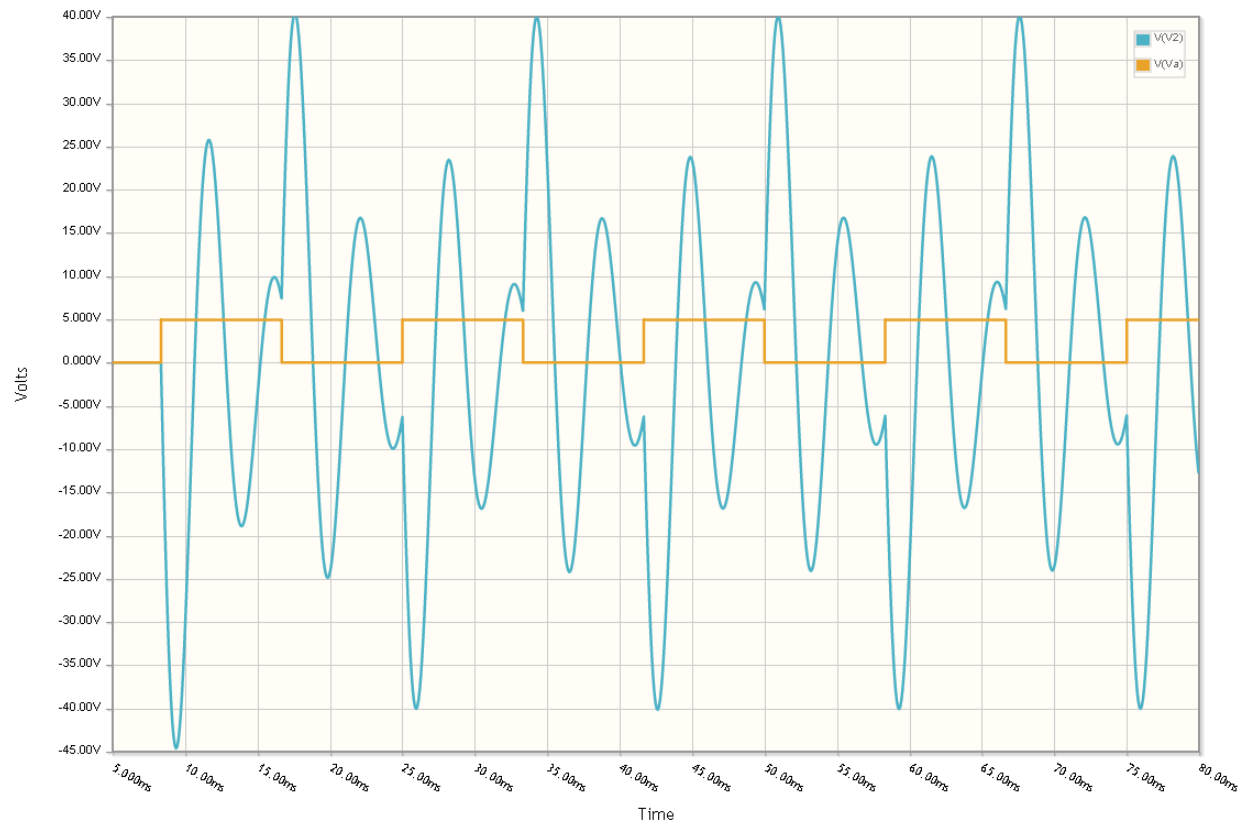

2) Adjust C1 so that the voltage across the motor is as close to a sine wave as possible (trial and error)

For resonance, ideally

$$\left(\frac{1}{LC}\right) = \omega_0^2$$


$$\left(\frac{1}{(0.1H)(C)}\right) = (2\pi \cdot 60Hz)^2$$

$$C = 70.3\mu F$$

Trial and error adjustment results in


$$C = 100\mu F$$

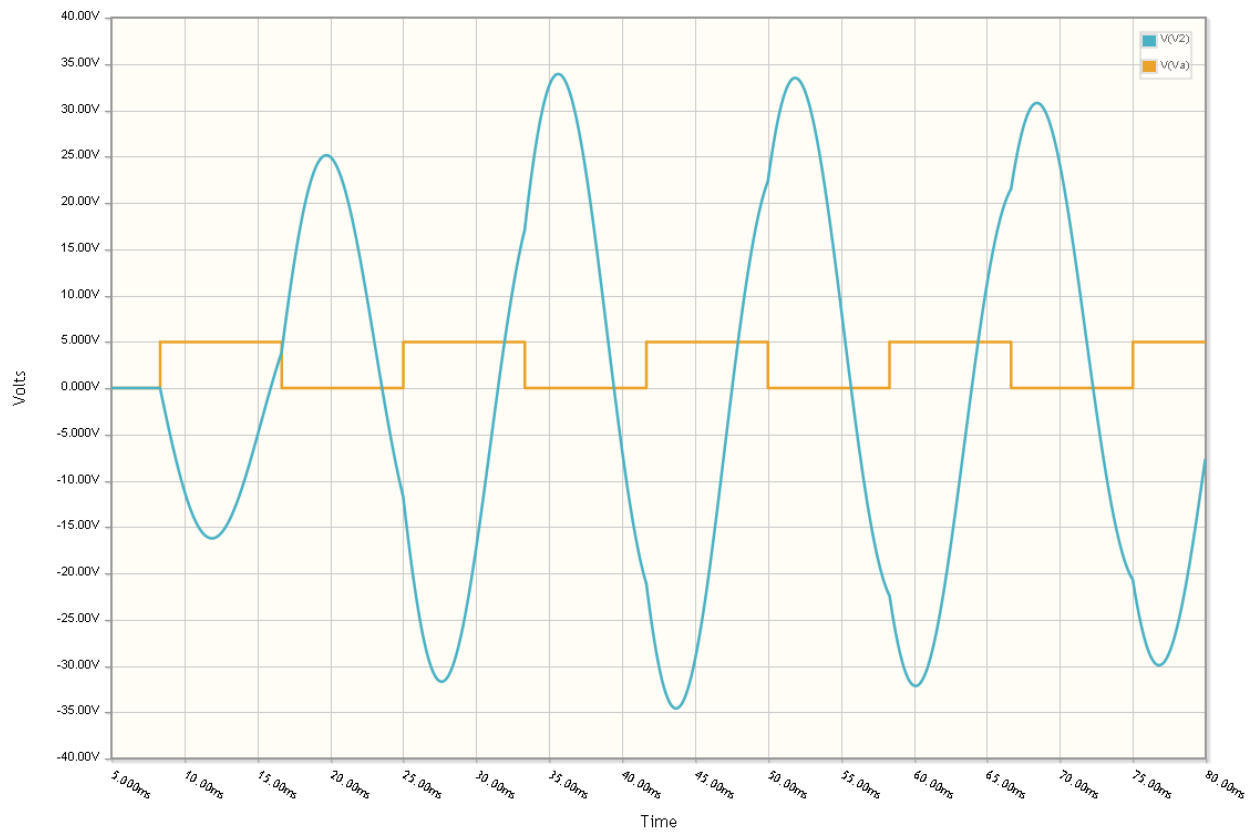This isn't a perfect sine wave at V2, but it's pretty close (meaning the harmonics are fairly small)



## Circuits and Differential Equations

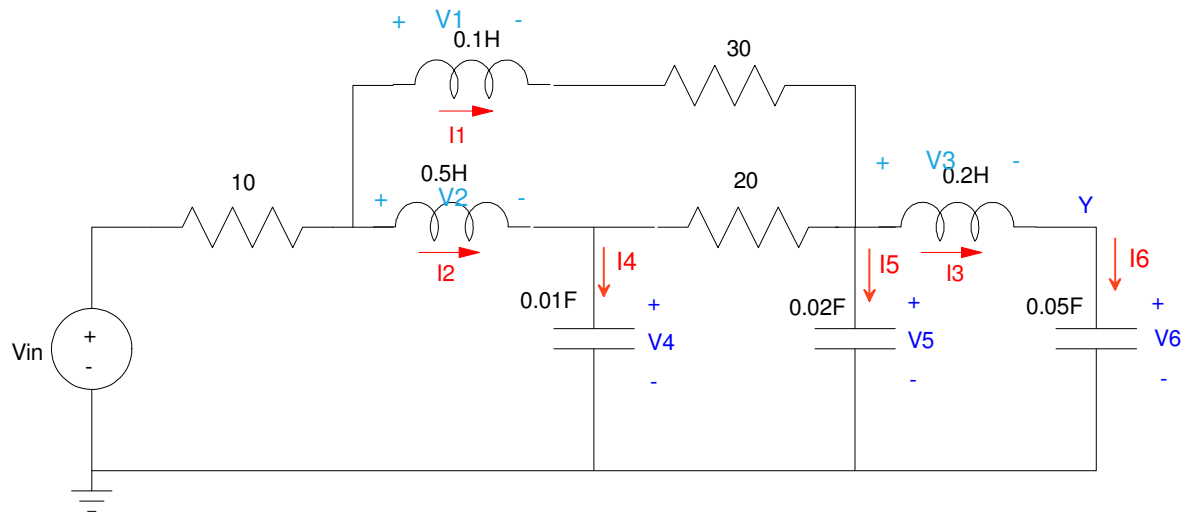3) Write the differential equations that describe the following circuit



$$V_1 = 0.1 \dot{I}_1 = V_{in} - 10(I_1 + I_2) - 30I_1 - V_5$$

$$V_2 = 0.5 \dot{I}_2 = V_{in} - 10(I_1 + I_2) - V_4$$

$$V_3 = 0.2 \dot{I}_3 = V_5 - V_6$$


$$I_4 = 0.01 \dot{V}_4 = I_2 - \left( \frac{V_4 - V_5}{20} \right)$$

$$I_5 = 0.02 \dot{V}_5 = \left( \frac{V_4 - V_5}{20} \right) + I_1 - I_3$$

$$I_6 = 0.05 \dot{V}_6 = I_3$$

## SCR

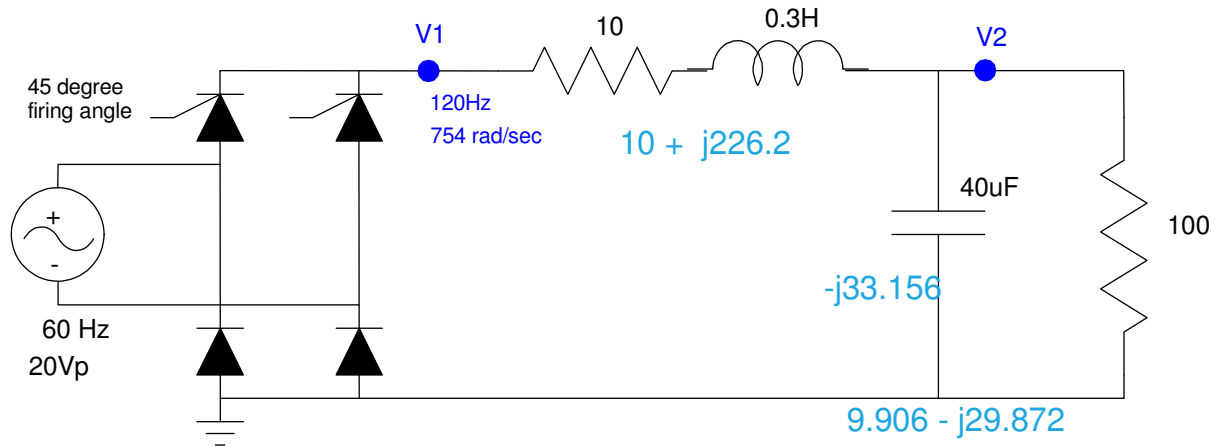4) Assume a firing angle of 45 degrees. Determine the voltage at V1 and V2 (both DC and AC).



SCR: Problem 4 - 6

DC Analysis

$$V_1(DC) = \left( \frac{2V_p \cos \theta}{\pi} \right) - 1.4 \quad \text{correct equation}$$

$$V_1(DC) = \left( \frac{2 \cdot 20 \cdot \cos(45^\circ)}{\pi} \right) - 1.4$$

$$V_1(DC) = 7.603V$$

$$V_2(DC) = \left( \frac{100}{100+10} \right) \cdot 7.603V$$

$$V_2(DC) = 6.911V$$

AC Analysis

$$V_1(AC) = 20V \cdot (1 + \sin(45^\circ))$$

$$V_1(AC) = 34.142V_{pp}$$

$$V_2(AC) = \left( \frac{9.906 - j29.872}{(9.906 - j29.872) + (10 + j226.2)} \right) \cdot 34.142V_{pp}$$

$$V_2(AC) = 5.445V_{pp}$$

5) Change this circuit so that

- The voltage at V2 is 9.00V (DC)
- With a ripple of 1.00Vpp

$$V_2(DC) = \left( \frac{100}{100+10} \right) V_1(DC)$$

$$V_1(DC) = \left( \frac{110}{100} \right) 9.00V$$

$$V_1(DC) = 9.9V$$

For the firing angle

$$V_1(DC) = 9.9V = \left( \frac{2 \cdot 20 \cdot \cos \theta}{\pi} \right) - 1.4$$

$$\theta = 27.439^\circ$$

For the ripple

$$V_1(AC) = 20V \cdot (1 + \sin(27.439^\circ))$$

$$V_1(AC) = 29.216V_{pp}$$

If C = 0, the ripple is

$$V_2(AC) = \left( \frac{100}{(100)+(10+j226.2)} \right) \cdot 29.216V_{pp}$$

$$V_2(AC) = 11.615V_{pp}$$


For a ripple of 1.00Vpp

$$\left| \frac{1}{j\omega C} \right| = \left( \frac{1V_{pp}}{11.615V_{pp}} \right) 100\Omega = 8.61\Omega$$

$$C = 154\mu F$$

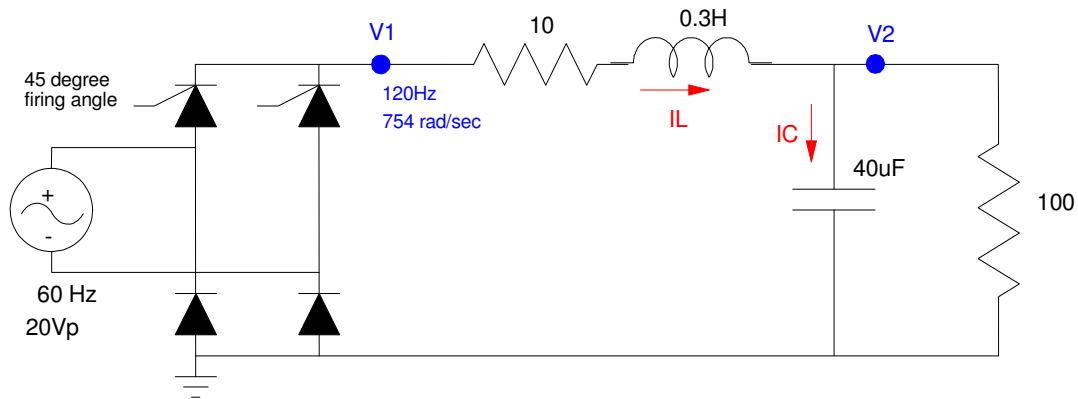6) Simulate this circuit in Matlab by

- Writing the differential equations which describe this circuit ( state variables:  $I_L$  and  $V_c$  )
- Specify  $V_1(t)$  as a full-wave rectified sine wave, clipped at 45 degrees (from problem #4)
- Use numerical integration to find  $V_2(t)$



$$V_L = L \dot{I}_L = V_1 - 10I_L - V_c$$

$$I_c = C \dot{V}_c = I_L - \left( \frac{V_c}{100} \right)$$

Matlab Code

```

t = [0:0.001:1]';
V1 = 20*sin(t*pi + 45*pi/180) - 1.4;
VC = 0*t;
IL = 0*t;
npt = length(t);

t = t/120;
dt = t(2) - t(1);

C = 40e-6;
R = 100;
L = 0.3;

for n=1:40

    VC(1) = VC(npt);
    IL(1) = IL(npt);

    for i=1:npt-1
        dVC = ( IL(i) - VC(i)/R ) / C;
        dIL = ( V1(i) - 10*IL(i) - VC(i) ) / L;


        VC(i+1) = VC(i) + dVC * dt;
        IL(i+1) = IL(i) + dIL * dt;
    end

    plot(t, V1, t, VC);
    pause(0.1);
end

plot(t*1000, V1, 'b', t*1000, VC, 'r');
xlabel('Time (ms)');
ylabel('Volts');

```

## Simulation Results: Problem #4

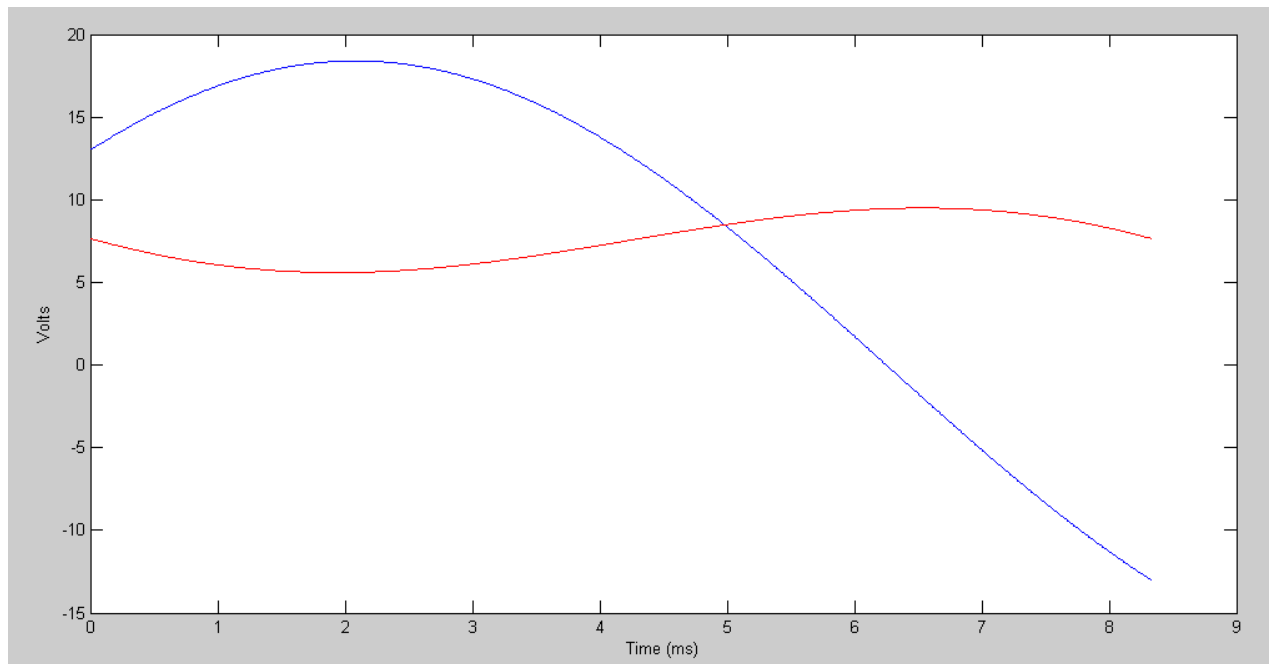

```
>> DC = mean(VC)
```


```
DC = 6.9249 V vs 6.911V calculated
```

```
>> AC = max(VC) - min(VC)
```

```
AC = 4.2487 Vpp vs. 5.445Vpp calculated
```



## Simulation Results (problem #5)

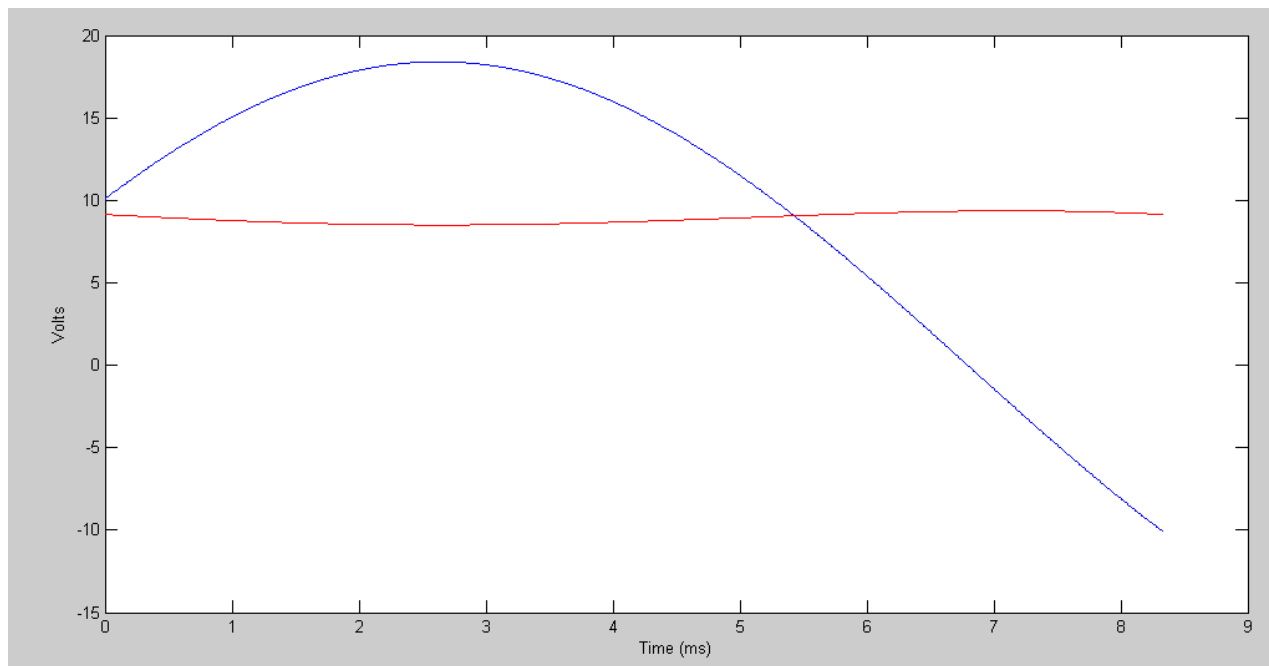

## Simulation Results for Vc:

```
>> mean (VC)
```

```
ans =    9.0087           vs. 9.00V calculated
```

```
>> max (VC) - min (VC)
```

```
ans =    0.8589 Vpp       vs. 1.00Vpp calculated
```