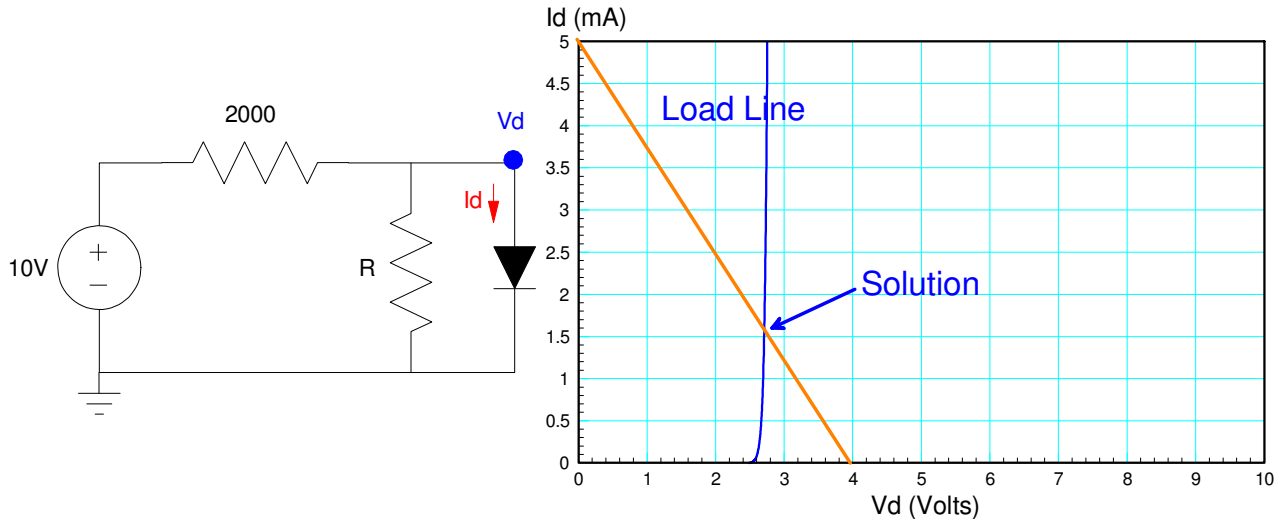


# ECE 320 - Final (pt 1) - Name \_\_\_\_\_

Semiconductors & Diodes - Spring 2023

1) Load Lines: Assume the VI characteristics for the diode is as shown in the graph. Draw the load line for the following circuit and determine  $I_d$  and  $V_d$ . Assume  $R = 800 + 100 * (\text{your birth month}) + (\text{your birth date})$ .



R 800 + 100*mo + day	Load Line x-intercept (volts)	Load Line y-intercept (mA)	$V_d$ Volts	$I_d$ mA
<b>1314</b>	<b>3.965V</b>	<b>5.00mA</b>	<b>2.7V</b>	<b>1.6mA</b>

Convert to a Thevenin equivalent:

$$V_{th} = \left( \frac{1314}{1314+2000} \right) 10V = 3.965V$$

$$R_{th} = 2000 || 1314 = 793.0\Omega$$

The load line is then

$$X_{int} = V_{th} = 3.965V$$

$$Y_{int} = V_{th} / R_{th} = 5.00mA$$


2) Nonlinear equations: Diode circuit

Assume the VI characteristics for the diodes shown below are

$$V_d = 0.038 \ln(10^{11} \cdot I_d + 1) \quad I_d = 10^{-11} \cdot \left( \exp\left(\frac{V_d}{0.038}\right) - 1 \right)$$

Write 6 equations to solve for 6 unknowns:  $\{V_1, V_2, V_3, V_4, I_{d1}, I_{d2}, I_{d3}\}$ .

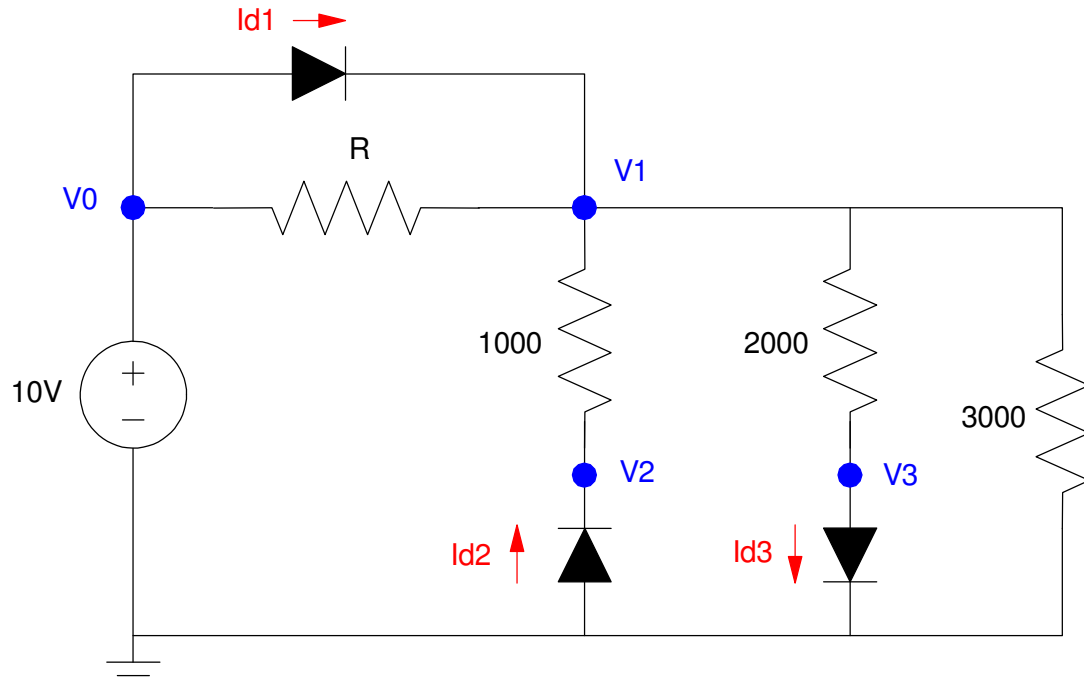- Note: you do not need to solve.
- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{birth date})$ .



Start with the diode equations

$$I_{d1} = 10^{-11} \cdot \left( \exp\left(\frac{V_0 - V_1}{0.038}\right) - 1 \right)$$

$$I_{d2} = 10^{-11} \cdot \left( \exp\left(\frac{0 - V_2}{0.038}\right) - 1 \right)$$

$$I_{d3} = 10^{-11} \cdot \left( \exp\left(\frac{V_3 - 0}{0.038}\right) - 1 \right)$$

$$V_0 = 10$$


$$-I_{d1} + \left(\frac{V_1 - V_0}{1314}\right) + \left(\frac{V_1 - V_2}{1000}\right) + \left(\frac{V_1 - V_3}{2000}\right) + \left(\frac{V_1}{3000}\right) = 0$$

$$\left(\frac{V_2 - V_1}{1000}\right) - I_{d2} = 0$$

$$\left(\frac{V_3 - V_1}{2000}\right) + I_{d3} = 0$$

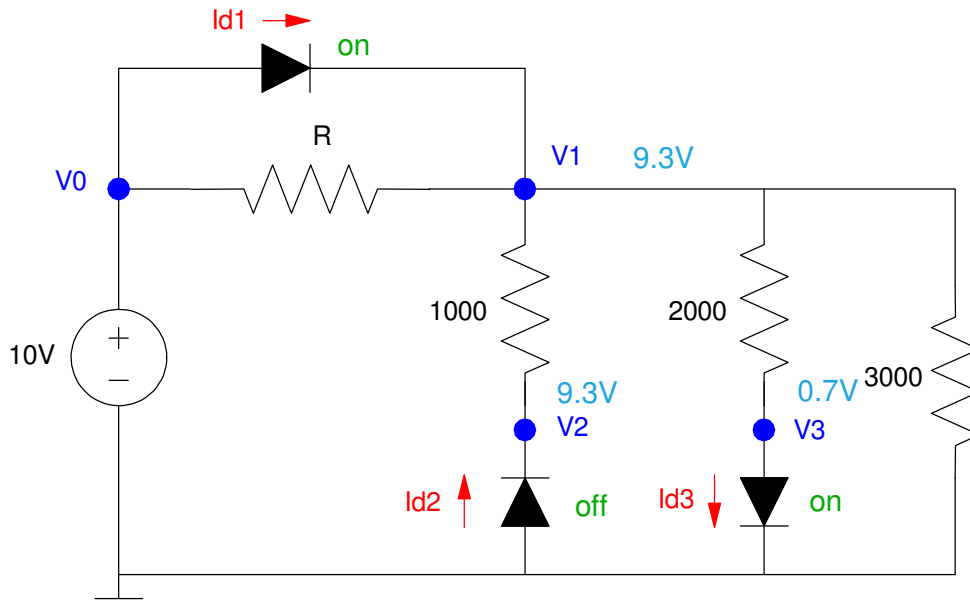3) Ideal Silicon Diodes. Assume the diodes in this circuit are ideal silicon diodes:

- $V_d = 0.7V$        $I_d > 0$
- $I_d = 0$              $V_d < 0.7V$
- $R = 800 + 100 * (\text{your birth month}) + (\text{birth date})$ .




R 800 + 100*mo + day	$I_{d1}$	$I_{d2}$	$I_{d3}$
<b>1314</b>	<b>6.867mA</b>	<b>0mA</b>	<b>4.30mA</b>
	V1	V2	V3
	<b>9.30V</b>	<b>9.30V</b>	<b>0.70V</b>

$I_{d1}$ : Current In = Current Out

$$I_{d1} = \left( \frac{V_1 - V_0}{1314} \right) + 0 + \left( \frac{V_1 - V_3}{2000} \right) + \left( \frac{V_1}{3000} \right)$$

$$I_{d1} = 6.867mA$$

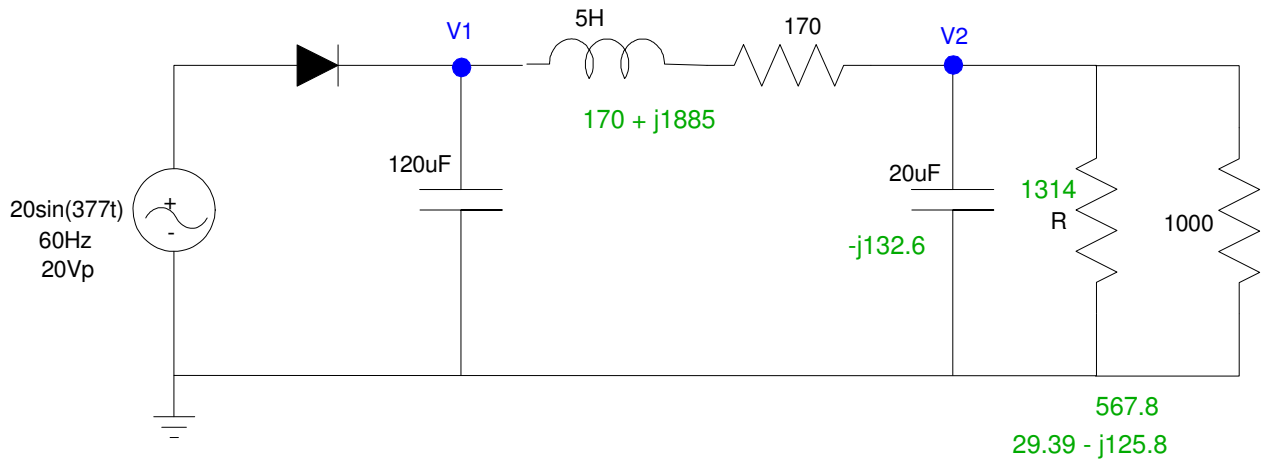4) AC to DC: Analysis: Determine V1 and V2 (both DC and AC) for the following AC to DC converter



R 800 + 100*mo + day	V1		V2	
	DC	AC	DC	AC
<b>1314</b>	<b>17.48V</b>	<b>3.633Vpp</b>	<b>13.46V</b>	<b>0.265Vpp</b>

$$I \approx \left( \frac{19.3V}{170+567.8} \right) = 26.16mA$$

$$I = C \frac{dV}{dt}$$

$$26.16mA = 120\mu F \cdot \frac{dV}{1/60s}$$

$$dV = V_1(AC) = 3.633V_{pp}$$

$$V_1(DC) = 19.3V - \frac{1}{2}V_{1pp} = 17.48V$$


$$V_2(DC) = \left( \frac{567.8}{567.8+170} \right) V_1(DC) = 13.46V$$

$$V_2(AC) = \left( \frac{(29.39-j125.8)}{(29.39-j125.8)+(170+j1885)} \right) V_1(AC)$$

$$|V_1(AC)| = 0.265V_{pp}$$

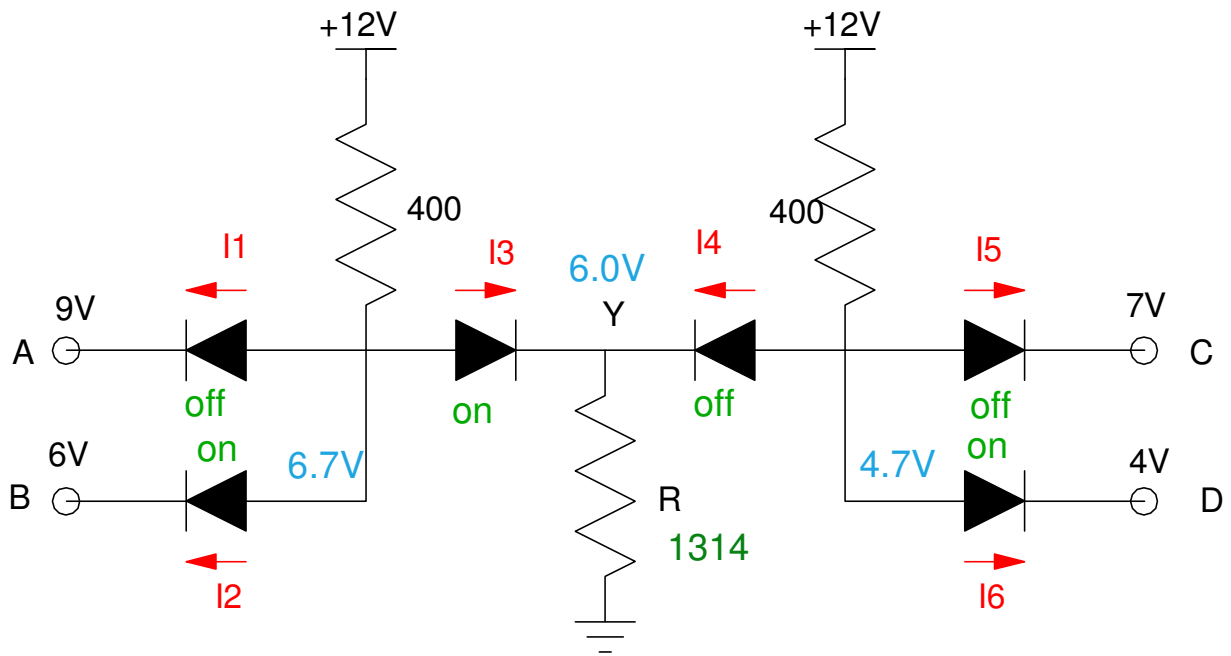5) Max/Min Circuits. Determine the currents I1 .. I6. Assume

- Ideal silicon diodes ( $V_f = 0.7V$ )
- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{birth date})$



R 800 + 100*mo day	I1	I2	I3	I4	I5	I6
<b>1314</b>	<b>0mA</b>	<b>8.684mA</b>	<b>4.566mA</b>	<b>0mA</b>	<b>0mA</b>	<b>18.25mA</b>

$$I_6 = \left( \frac{12V - 4.7V}{400\Omega} \right) = 18.25mA$$

$$I_3 = \left( \frac{6V}{1314\Omega} \right) = 8.684mA$$

$$I_2 + I_3 = \left( \frac{12V - 6.7V}{400\Omega} \right) = 13.25mA$$












- 
- 
- 

b

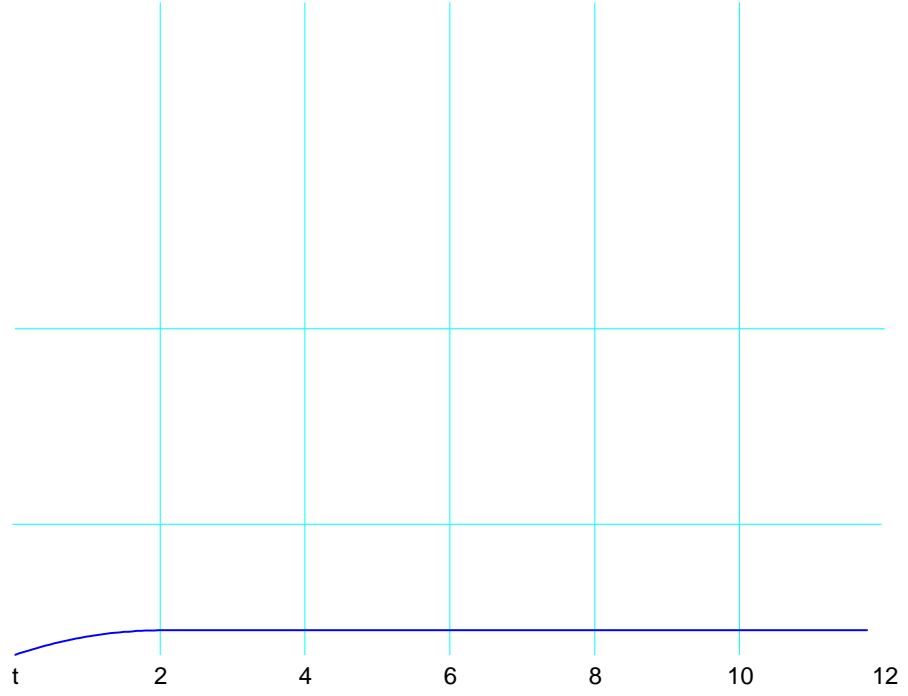



		D			
		0	0	1	0
B	0	1	0	1	1
	0	x	0	x	1
	1	1	0	0	x
	0	1	1	0	0

B

$$\bar{Y} = AC + BD + \bar{A}\bar{C}\bar{D}$$

5/1

$$Y = (\bar{A} + \bar{C})(\bar{B} + \bar{D})(A + C + \bar{D})$$

