








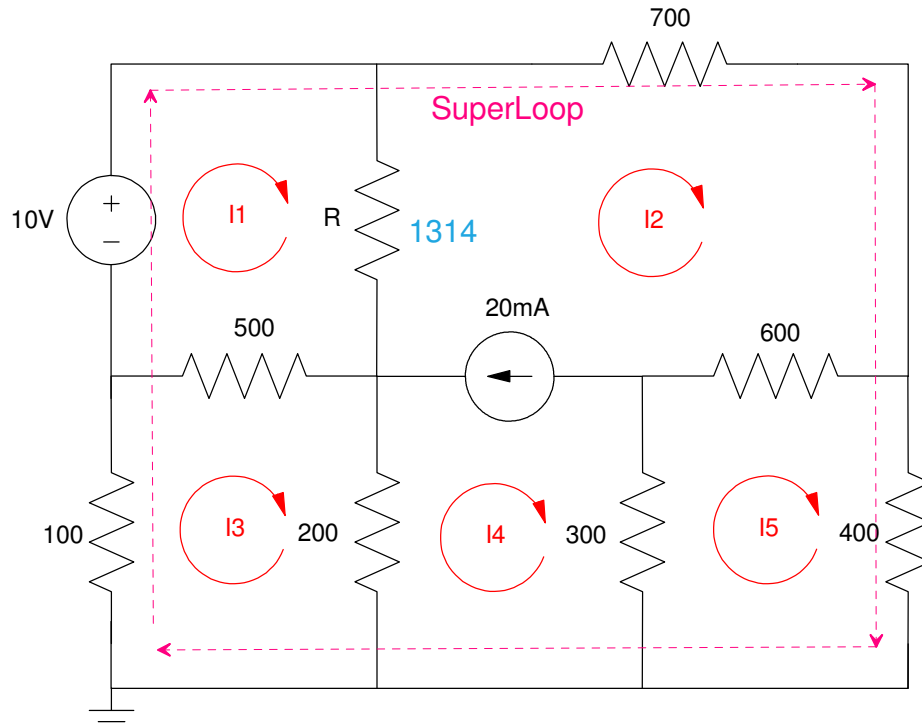4) Give N current loop equations to solve for the N unknown currents. Assume

- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$ . For example, May 14th would give  $R = 1314$



Start with the current source

$$I_2 - I_4 = 20mA$$

Write the loop equations

$$-10 + 1314(I_1 - I_2) + 500(I_1 - I_3) = 0$$

$$100I_3 + 500(I_3 - I_1) + 200(I_3 - I_4) = 0$$


$$300(I_5 - I_4) + 600(I_5 - I_2) + 400I_5 = 0$$

Superloop

$$100I_3 - 10 + 700I_2 + 400I_5 = 0$$

5) Signals X and Y are displayed on an oscilloscope. Give the phasor representation for these two voltages

Frequency (Hz)	X		Y	
	Amplitude	Phase	Amplitude	Phase
<b>75.7 Hz</b>	<b>2.8V</b>	<b>-122 deg</b>	<b>4.4V</b>	<b>-87 deg</b>

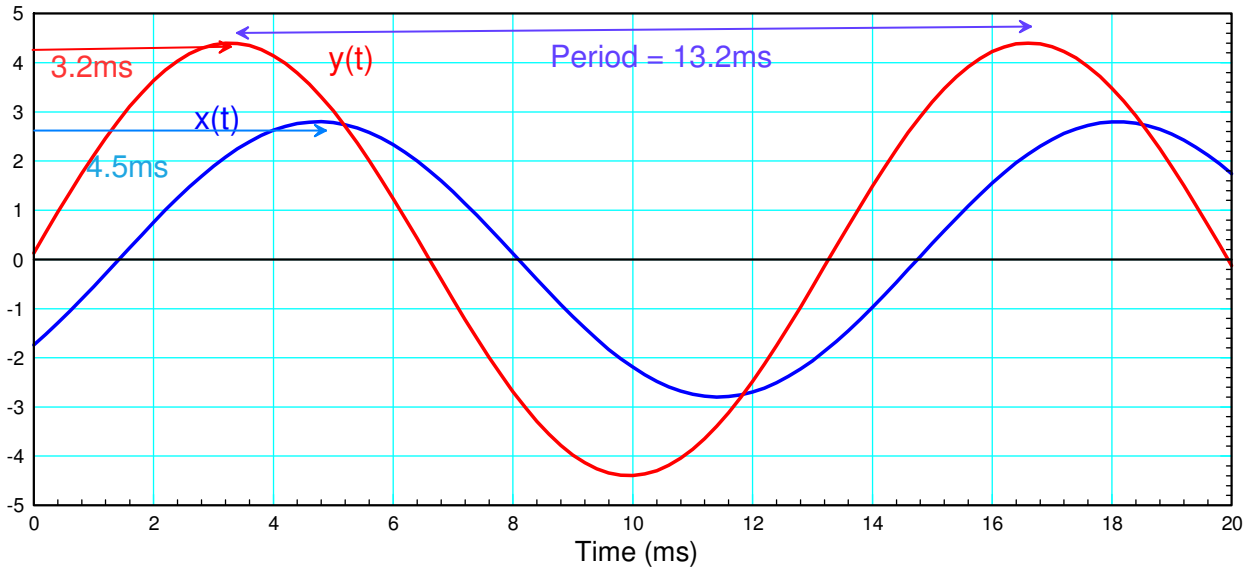

1 cycle = 13.2ms

$$f = \frac{1}{\text{period}} = \frac{1}{13.2\text{ms}} = 75.7\text{Hz}$$

Phase for X

$$\theta_x = -\left(\frac{4.5\text{ms delay to peak}}{13.2\text{ms period}}\right) 360^\circ = -122^\circ$$

Phase for Y

$$\theta_y = -\left(\frac{3.2\text{ms delay to peak}}{13.2\text{ms period}}\right) 360^\circ = -87^\circ$$


6) Determine  $V_2(t)$  assuming

$$V_1(t) = 12 + 13 \sin(\omega t)$$

$\omega = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$ . For example, May 14th would give  $\omega = 1314$

$\omega$ (rad/sec) 800 + 100*mo + day	$V_2(t)$
<b>1314</b>	$10.08 - 8.493 \cos(1314t) + 9.700 \sin(1314t)$

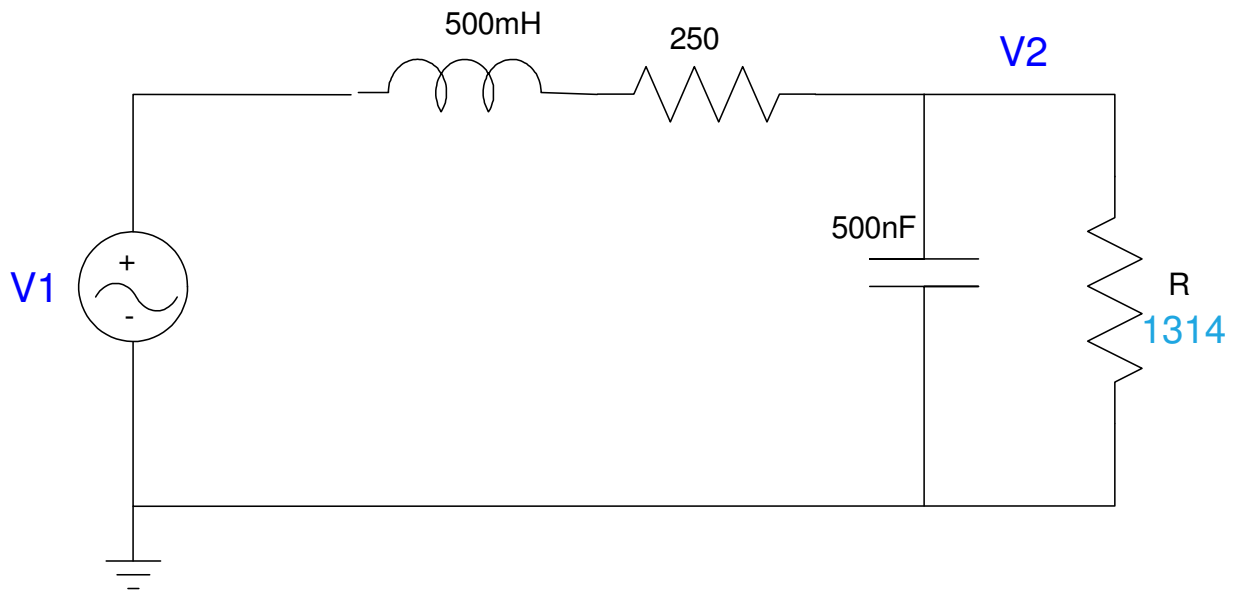Let  $R = 1314$  (or any value from 800 to 2000 Ohms)



DC:

$$V_2 = \left( \frac{1314}{1314+250} \right) 12V$$

$$V_2 = 10.08$$

AC:

$$V_1 = -j13$$

$$L \rightarrow j\omega L = j657\Omega$$

$$C \rightarrow \frac{1}{j\omega C} = -j1522\Omega$$

$$C \parallel R = 752 - j649\Omega$$

$$V_2 = \left( \frac{(752-j649)}{(752-j649)+(250+j657)} \right) (-j13) = -8.493 - j9.700$$

