


ECE 320 - Quiz #3 - Name _____

Ideal Diodes, LEDs, AC to DC Converters - Spring 2023

1) Determine the voltages for the following circuit.

- Assume ideal silicon diodes ($V_d = 0.7V$ when on)

V1	V2	V3	V4
9.3V	8.6V	7.771V	7.771V

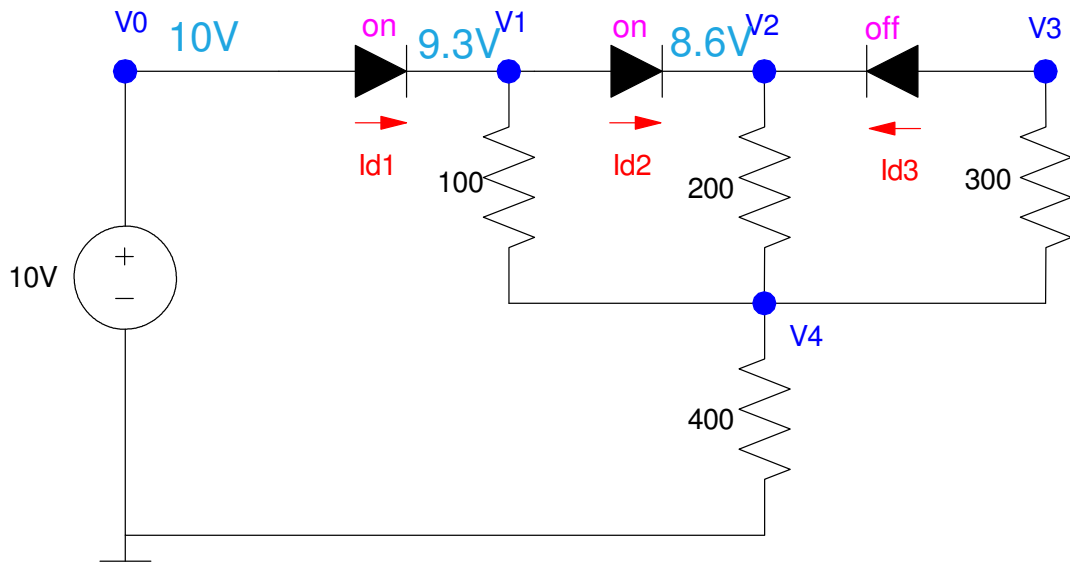

To solve for V4

$$\left(\frac{V_4 - 9.3V}{100}\right) + \left(\frac{V_4 - 8.6V}{200}\right) + \left(\frac{V_4}{400}\right) = 0$$


$$\left(\frac{1}{100} + \frac{1}{200} + \frac{1}{400}\right) V_4 = \left(\frac{9.3V}{100}\right) + \left(\frac{8.6V}{200}\right)$$

$$V_4 = 7.771V$$

2) Determine the voltages for the following circuit. Assume

- Assume ideal silicon diodes ($V_d = 0.7V$ when on)

V1	V2	V3	V4
5.773V	5.073V	5.073V	0V

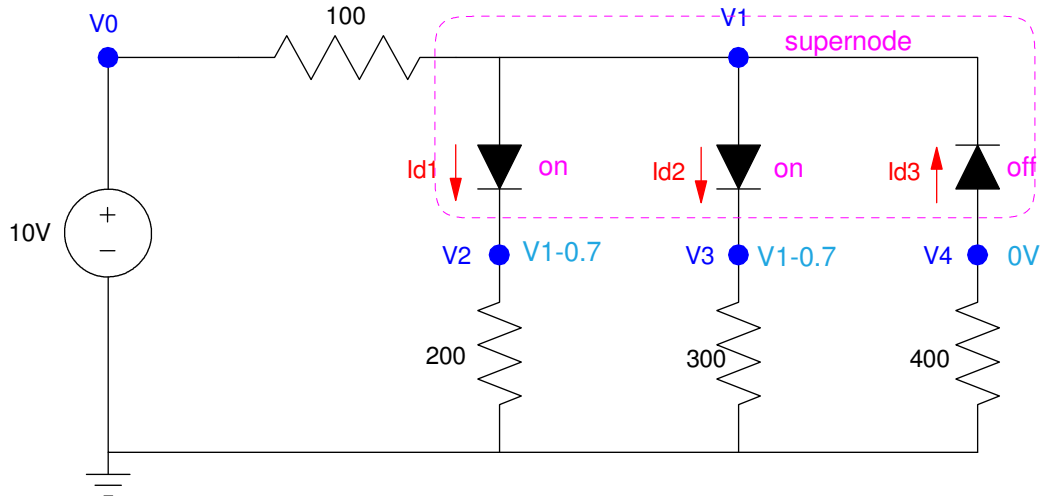

Writing the supernode equation

$$\left(\frac{V_1-10}{100}\right) + \left(\frac{V_1-0.7}{200}\right) + \left(\frac{V_1-0.7}{300}\right) = 0$$

$$\left(\frac{1}{100} + \frac{1}{200} + \frac{1}{300}\right) V_1 = \left(\frac{10}{100}\right) + \left(\frac{0.7}{200}\right) + \left(\frac{0.7}{300}\right)$$


$$V_1 = 5.773V$$

$$V_2 = V_1 - 0.7 = 5.0733V$$

3) A red and green are connected to a 10V source. Determine the current and brightness of each LED. Assume

- R is $800 + 100 \cdot (\text{your birth month}) + (\text{your birthday})$.
- Red LED: $V_f = 1.9V @ 100mA$ $5000 \text{ mcd} @ 100mA$
- Green LED: $V_f = 3.0V @ 100mA$ $5000 \text{ mcd} @ 100mA$

R $800 + 100 \cdot \text{mo} + \text{day}$	V1 Volts	Red LED		Green	
		I_r	mcd	I_g	mcd
1314	1.9V	14.26mA	713.2 mcd	0	0

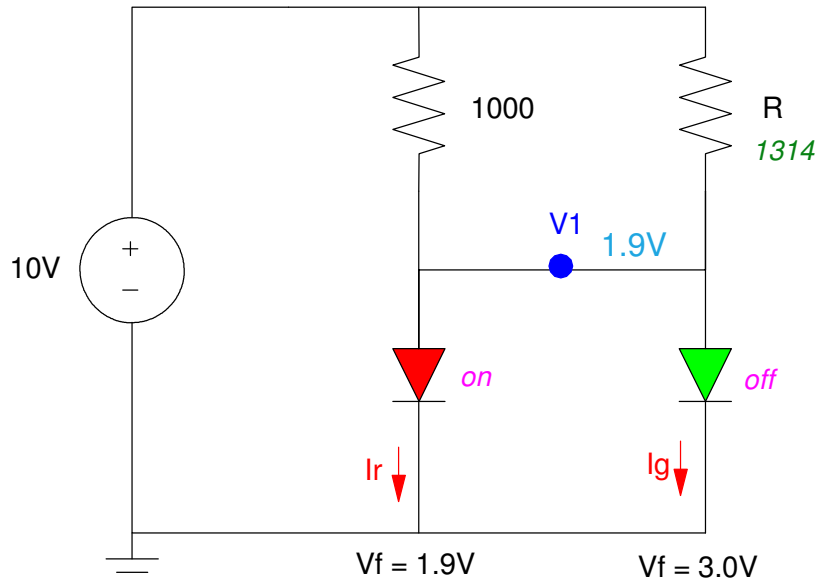

$$R \parallel 1000 = 567.84 \text{ Ohms}$$


$$I_r = \left(\frac{10V - 1.9V}{567.84\Omega} \right) = 14.264mA$$

mcd

$$\left(\frac{14.264mA}{100mA} \right) 5000mcd = 713.2mcd$$

4) The following waveform is found using CircuitLab for an AC to DC converter. Determine the following

Frequency (Hz)	Voltage	
	DC (average)	AC (Vpp)
307 Hz	8.0V	6.0Vpp

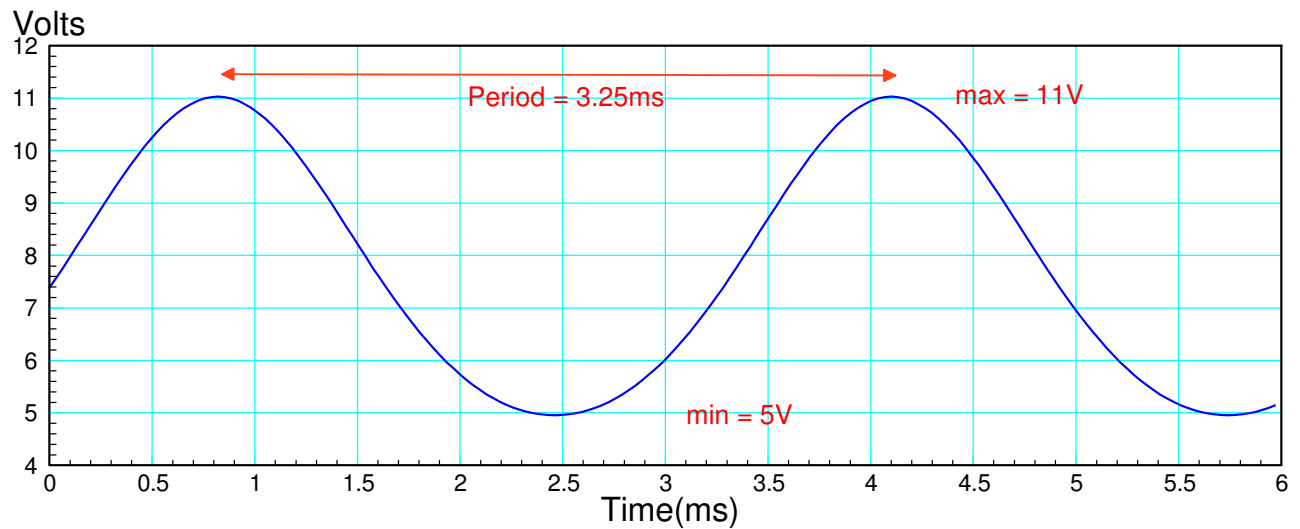

$$frequency = \frac{1}{period} = \frac{1}{0.00325s} = 307Hz$$

$$DC \approx \left(\frac{max+min}{2} \right) = 8.0V$$

$$AC \approx (max-min) = 6.0V_{pp}$$

