

# ECE 320 - Quiz #5 - Name \_\_\_\_\_

555 Timers, Transistor Switch, Comparitors, Schmitt Triggers - Spring 2023


1) 555 Timers. Determine R1 and R2 so that the 555 timer outputs a 20% duty cycle 100Hz square wave:

$$t_{on} = (R_1 + R_2) \cdot C \cdot \ln(2) = 2.000ms$$

$$t_{off} = R_2 \cdot C \cdot \ln(2) = 8.000ms$$

Let C be your birthday day in microfarads (800 + 100\*Month + Day) uF

R1	R2	C ( 800 + 100*Month + Day ) uF

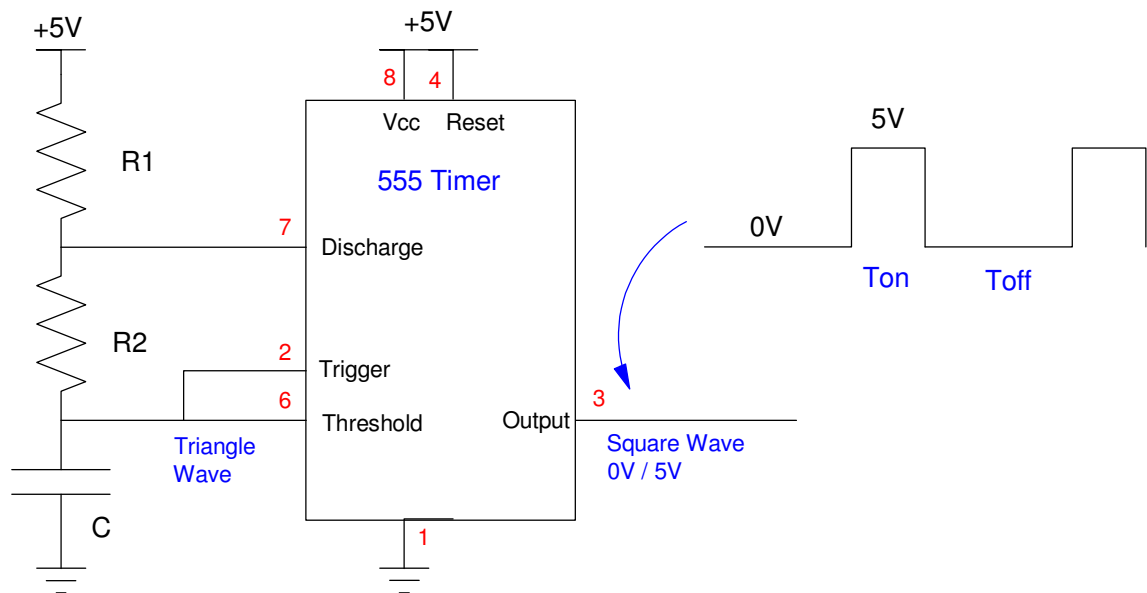


2) Transistor Switch: Design. Specify R1 and R2 so that when  $V_{in} = 5.00V$ ,

- $I_c = ( 800 + 100 * \text{Birth Month} + \text{Birth Day} ) \text{ mA}$ .
- The transistor is saturated, and
- $I_b < 25\text{mA}$  (the maximum output of a 555 timer)

Assume 6144 transistors

- $|V_{be}| = 0.7V$
- $|V_{ce}| = 0.2V$  when saturated
- $\beta = 200$

$I_c$ (mA) $800 + 100 * (\text{Mo}) + (\text{Day})$	$R_c$	min value of $R_b$	max value of $R_b$

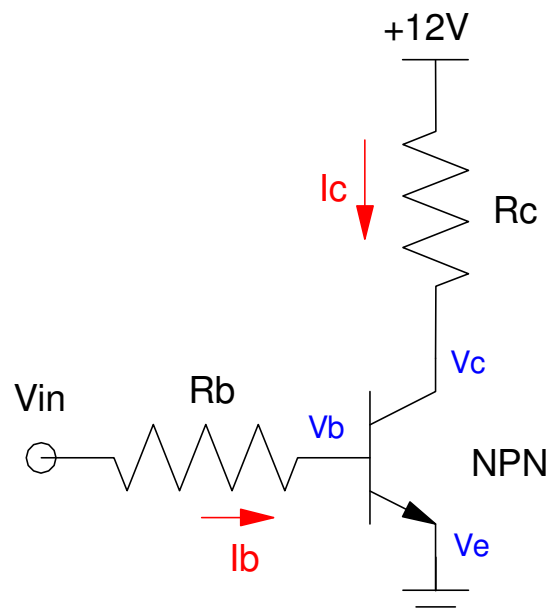


3) Darlington Pair (analysis). Assume two 6144 NPN transistors are connected as a Darlington pair.

- $|V_{be}| = 0.7V$
- $|V_{ce}| = 0.2V$  when saturated
- $\beta = 200$

Let  $R_b$  be  $800 + 100(\text{Birth Month}) + \text{Birth Day}$ . Find the currents and voltages.



$R_b$ $800 + 100 * Mo + Day$	$I_1$	$I_2$	$I_3$
	$V_1$	$V_2$	$V_3$

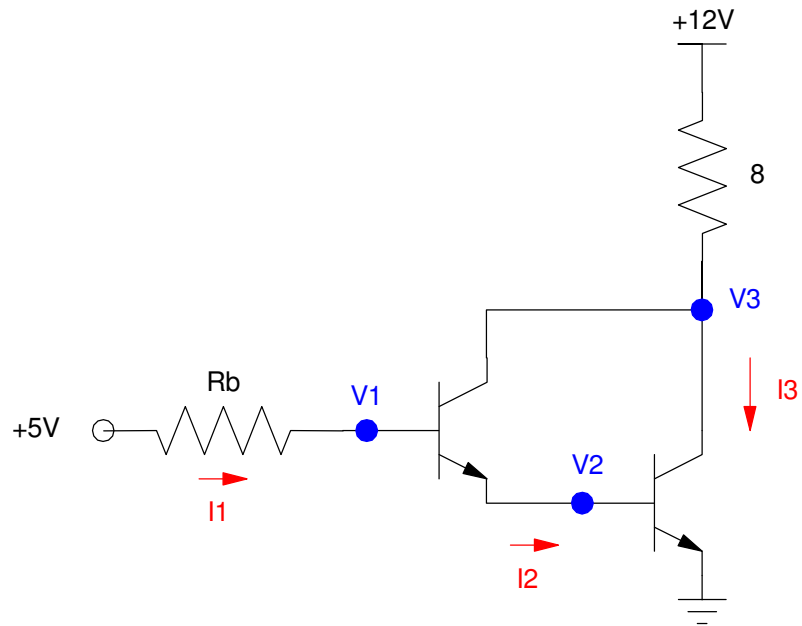

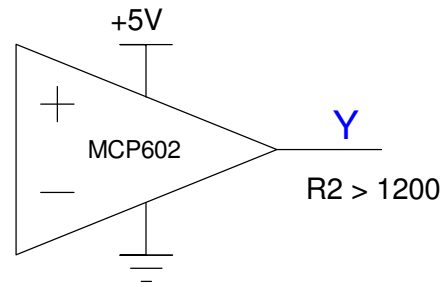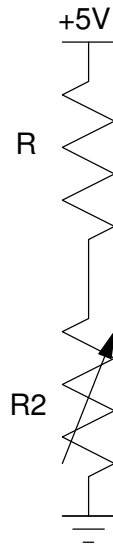4) Comparitor: Design a circuit which output

- 5V when  $R2 > 1200$  Ohms
- 0V when  $R2 < 1200$  Ohms



where  $R = 800 + 100 * (\text{Birth Month}) + (\text{Birth Day})$ .



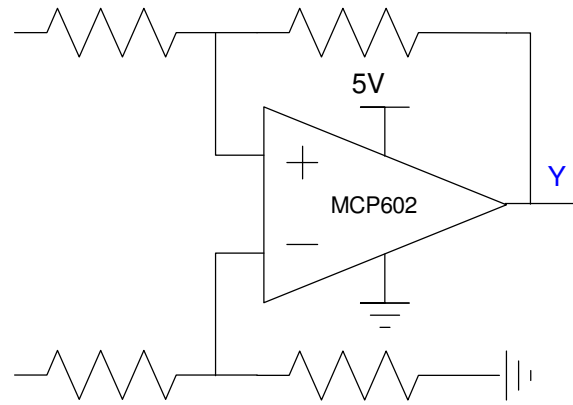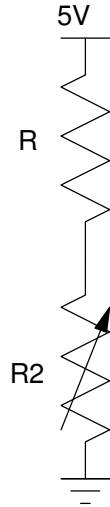5) Schmitt Trigger: Design a circuit which output

- 5V when  $R2 < 1200$  Ohms
- 0V when  $R2 > 1300$  Ohms
- No change for  $1200 < R2 < 1300$  Ohms

Let R be  $800 + 100(\text{Birth Month}) + (\text{Birth Date})$ .



6) Schmitt Trigger: Analysis. Determine the voltages and resistance where the following Schmitt trigger turns on and off. Assume R is  $800 + 100 * (\text{Birth Month}) + (\text{Birth Day})$ .

R $800 + 100 * \text{Mo} + \text{Day}$	On ( $V_2 = +5V$ )		Off ( $V_2 = 0V$ )	
	V1	R2	V1	R2

