

# ECE 320 - Quiz #6 - Name \_\_\_\_\_

Spring 2023 - H Bridges, DC to DC, SCR, Fourier Transforms, Boolean Logic


## H-Bridge Analysis:

Determine the voltages and currents for the following H-bridge. Assume ideal transistors:

- $|V_{be}| = 0.7V$
- $|V_{ce}| = 0.2V$  when saturated
- Current gain =  $\beta = 60$

Let  $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$

R 800 + 100*mo + day	I1	I2	I3	V4	V5

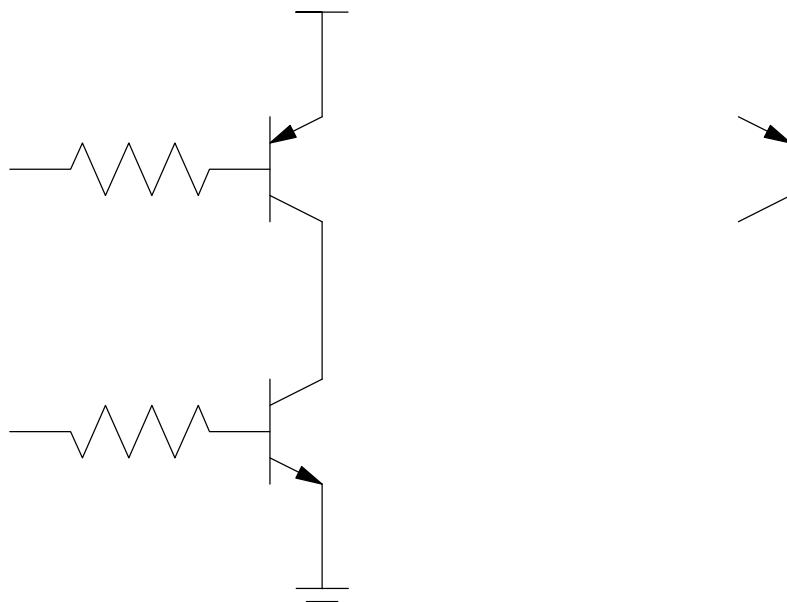


## DC to DC Converter: Analysis

Determine the voltages at V1 and V2 (both DC and AC). Assume

- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$

R 800 + 100*mo + day	V1		V2	
	DC	AC (V1pp)	DC	AC (V2pp)

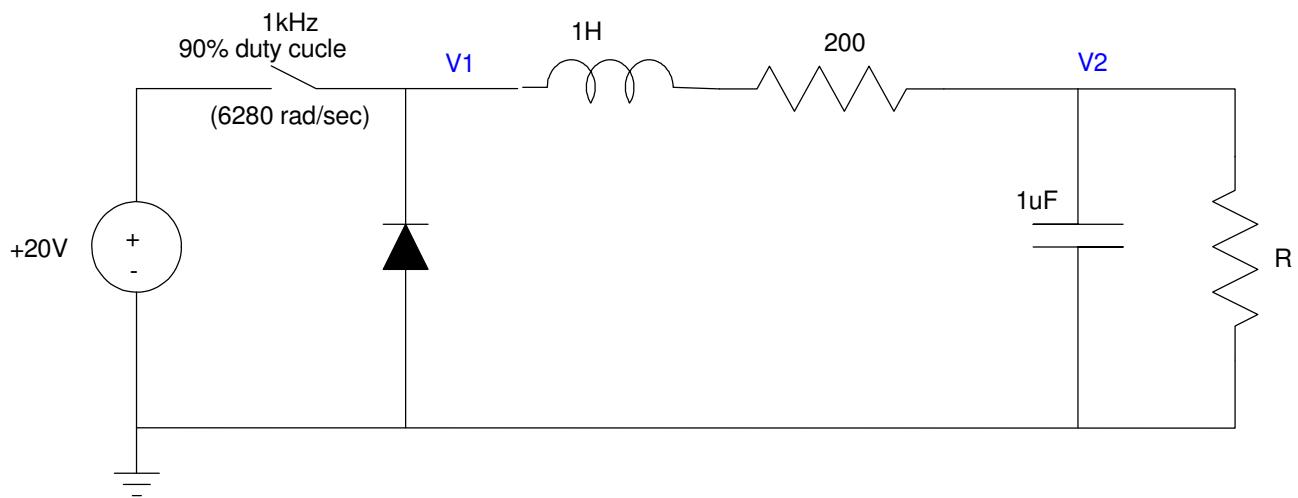


## DC to DC Converter: Design

Determine the duty cycle and C so that

- V<sub>2</sub>(DC) is 11.0V and
- V<sub>2</sub>(AC) = 250mVpp
- R = 800 + 100\*(your birth month) + (your birth date)

R 800 + 100*mo + day	Duty Cycle (X) %	C

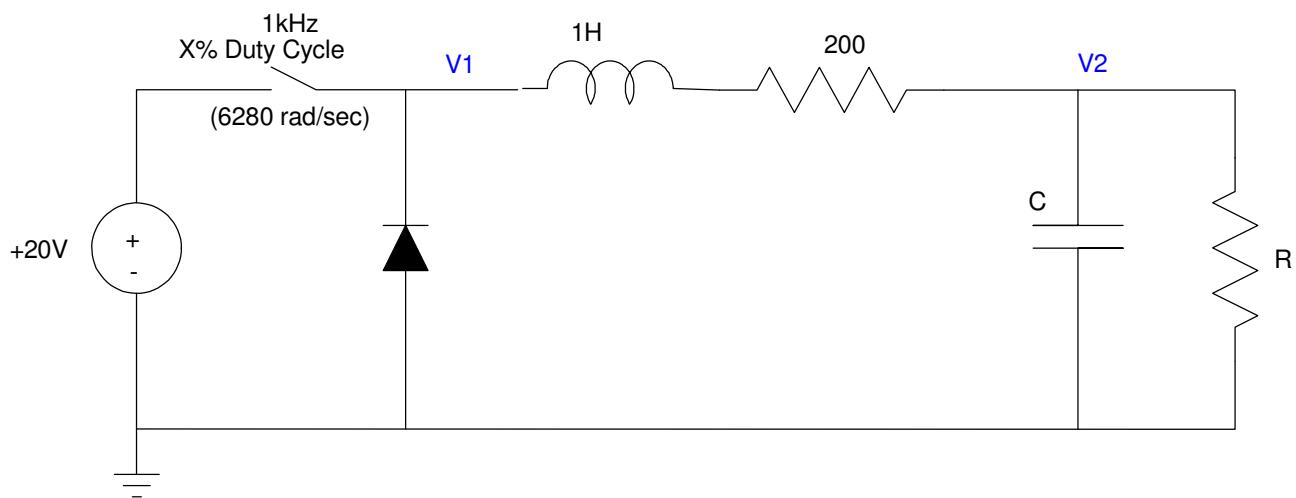


## SCR

Determine the voltages at V1 and V2 (both DC and AC). Assume

- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$
- 17 degree firing angle
- 20Vp 60Hz sine wave as the input

R 800 + 100*mo + day	V1		V2	
	DC	AC (V1pp)	DC	AC (V2pp)

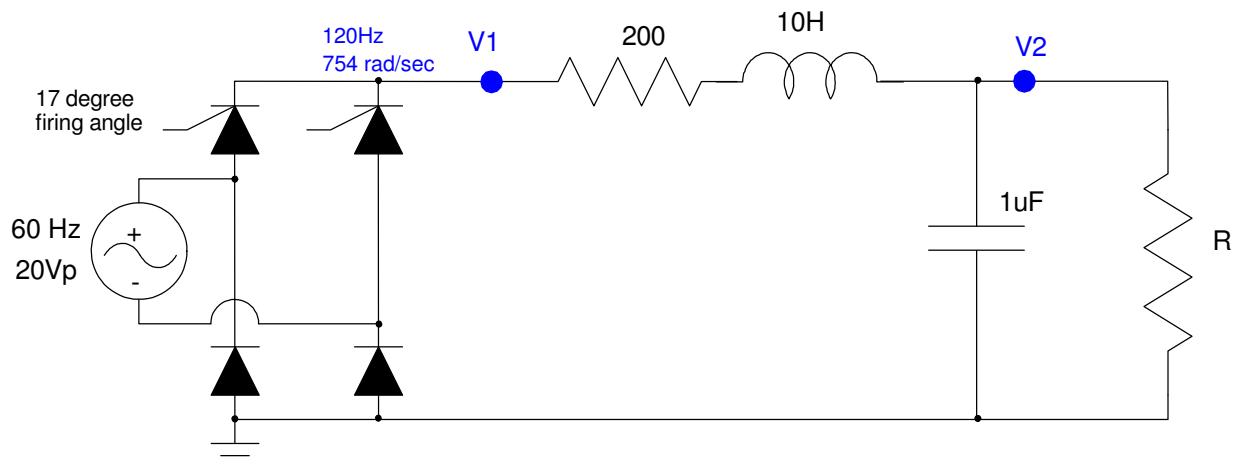


## Fourier Transform

Determine  $y(t)$  given that

$$x(t) = 24 + 5 \sin(50t) + 2 \cos(100t)$$

- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$

R 800 + 100*mo + day	y(t)

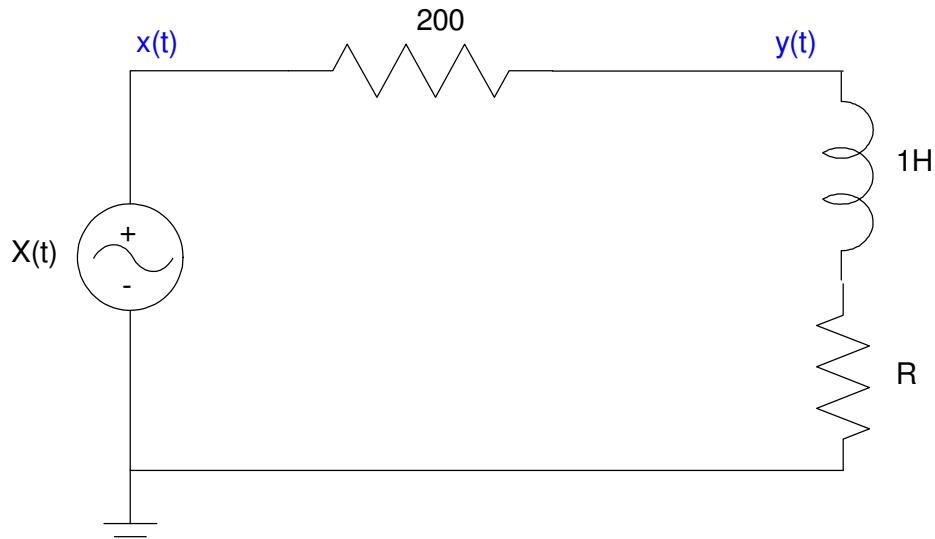

## Boolean Logic

Design a circuit using NOR gates to implement  $Y(A,B,C,D)$

		CD				
		00	01	11	10	
		00	x	0	1	1
AB		01	1	1	1	x
		11	x	x	0	0
		10	x	1	x	0