







## TTL Logic

4) Determine the voltges and currents for the following TTL gate. Assume

•



## DTL Logic

6) Determine the voltages and currents when  $V_0 = 1V$ . Assume

- Ideal transistors ( $V_{be} = 0.7V$ ,  $V_{ce(sat)} = 0.2V$ , gain = 100)
- Ideal silicon diodes ( $V_f = 0.7V$ )
- $R = 800 + 100(\text{Birth Month}) + (\text{Birth Day})$ .

$R$ $800 + 100 \cdot \text{mo} + \text{day}$	$V_1$	$V_2$	$V_3$	$I_4$	$I_5$
<b>1314</b>	<b>5.00V</b>	<b>1.40V</b>	<b>0.20V</b> saturated: 0.2V active: $5 - 20 \cdot I_5$	<b>2.74mA</b>	<b>240mA</b> $\min(I_4 \cdot 100, 240\text{mA})$ active / saturated

