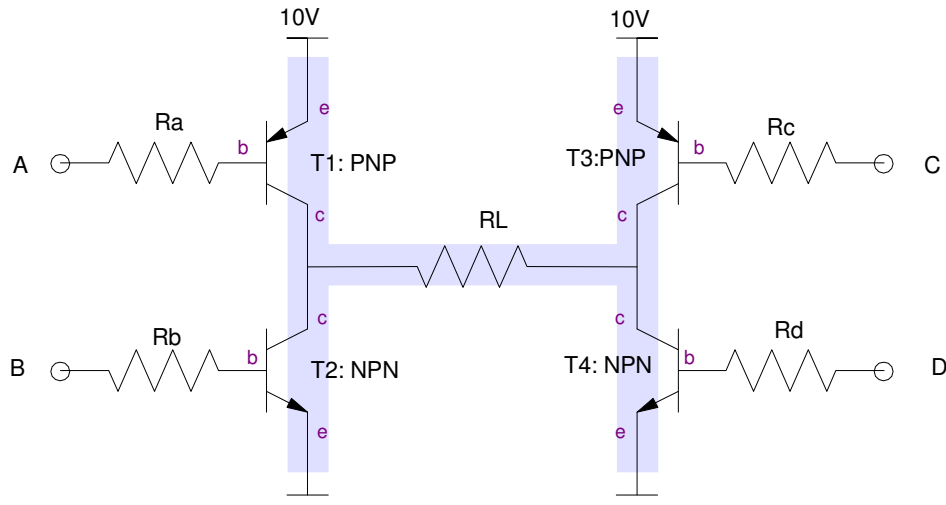


H-Bridges

With a single NPN transistor, you can turn a motor on and off. If the motor only spins in one direction, that's all you need. If you want to design a motor that can spin forward and backwards, you need an H-bridge.

To build an H-bridge, you need two NPN and two PNP transistors and four inputs. The connection to the load looks like the letter 'H' - hence the name H-bridge



H-Bridge

There are four modes of operation with an H-bridge:

- Forward: T1 & T4 on
- Reverse: T2 & T4 on
- Brake: T2 & T4 on
- Coast: all transistors off

There's actually a fifth mode:

- Smoke: All transistors on

When all transistors are on, you short power to ground. This tends to create lots of smoke and burns out components.


H-Bridge Analysis:

Given a circuit, determine the voltages and currents.

Assume TIP transistors

- $|V_{be}| = 1.4V$
- $\min(|V_{ce}|) = 0.9V$
- $\beta = 1000$

Forward: Determine the voltages and currents for the following H-bridge.

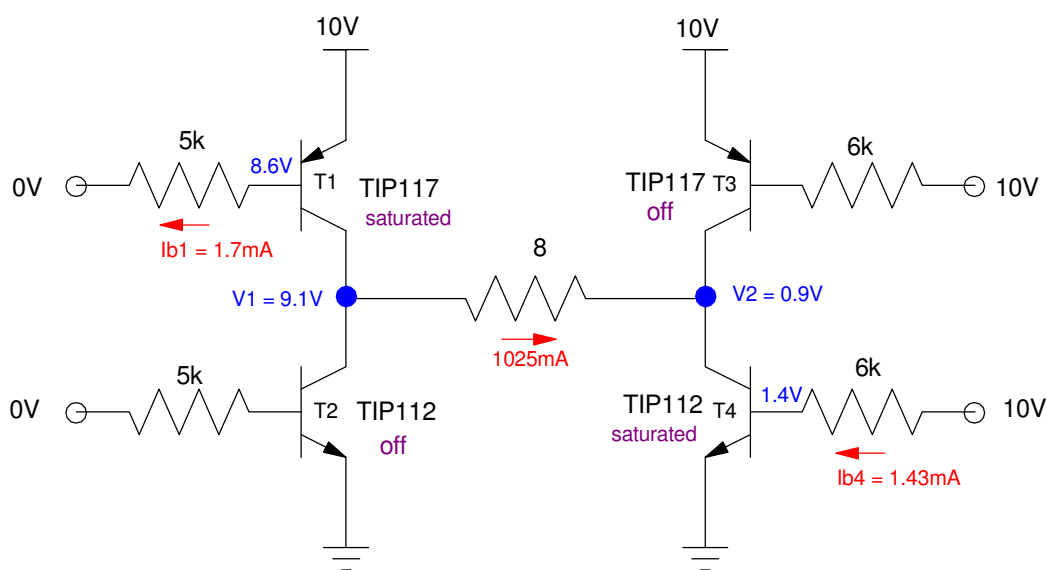

Case 1: Forward ($V_L = +8.2V$)

To analyze this, determine the current. It will be the minimum of

$$I_L = \min\left(\beta I_{b1}, \frac{10V - 0.9V - 0.9V}{8\Omega}, \beta I_{b4}\right)$$

Transistor T1 limits the current to 1.72A (βI_b)

$$I_{b1} = \left(\frac{10 - 1.4}{5k}\right) = 1.72mA$$

Transistor T4 limits the current to 1.433A

$$I_{b4} = \left(\frac{10 - 1.4}{6k}\right) = 1.433mA$$

The 8-Ohm resistor limits the current to

$$I_{\max} = \left(\frac{10 - 0.9 - 0.9}{8} \right) = 1.025A$$

The current is the minimum of these three

$$I = \min(\beta I_{b1}, \beta I_{b4}, I_{RL})$$


$$I = \min(1.72A, 1.433A, 1.025A)$$

Since RL limits the current, the transistors are saturated ($\beta I_b > I_c$) and


- V1 = 9.1V
- V2 = 0.9V
- I = 1.025A

Reverse: Flip the voltages to turn on T2 and T3. This results in

- V1 = 0.9V
- V2 = 9.1V
- I = -1.025A

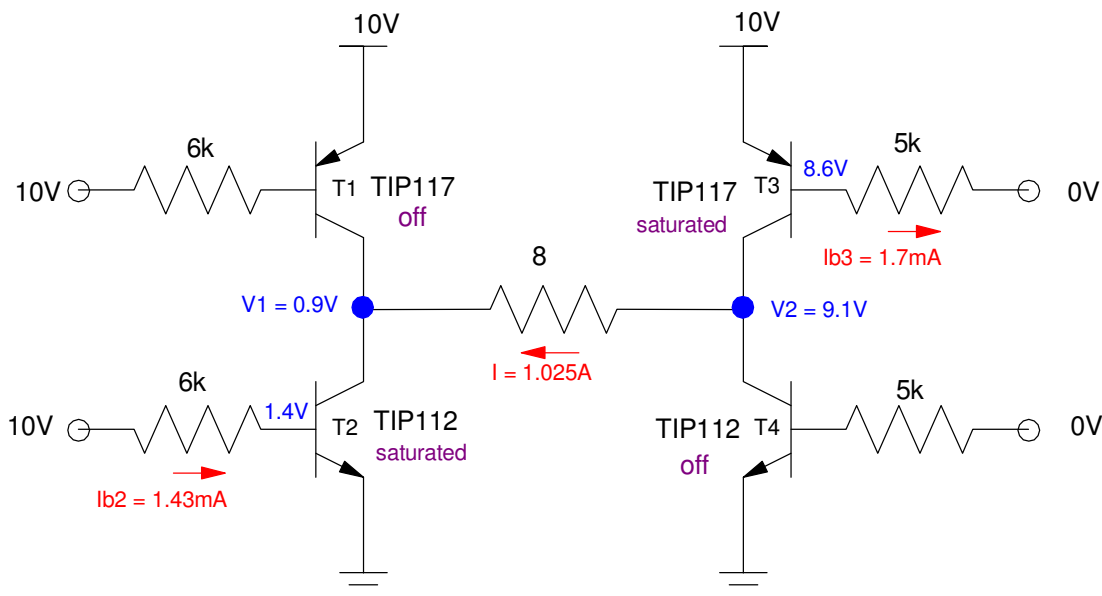


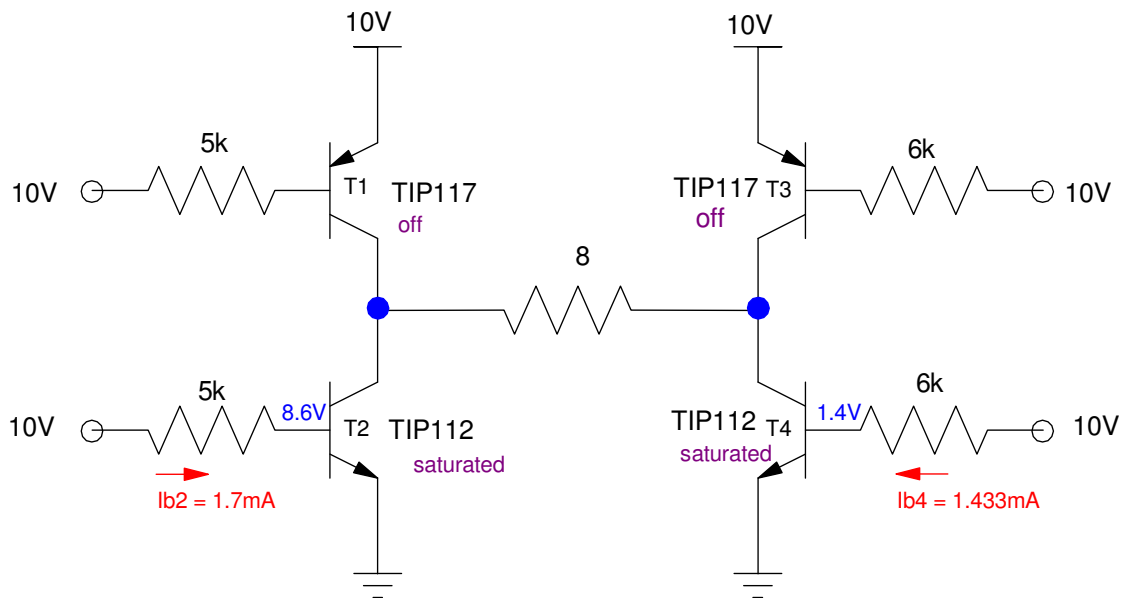Braking: Turn on T2 and T4. This shorts the load out. If it's a motor, the motor acts as a generator, producing current which gets turned into heat as I^2R . This turns the kinetic energy into heat



Braking Mode: Short out the load


Coast: All transistors off.

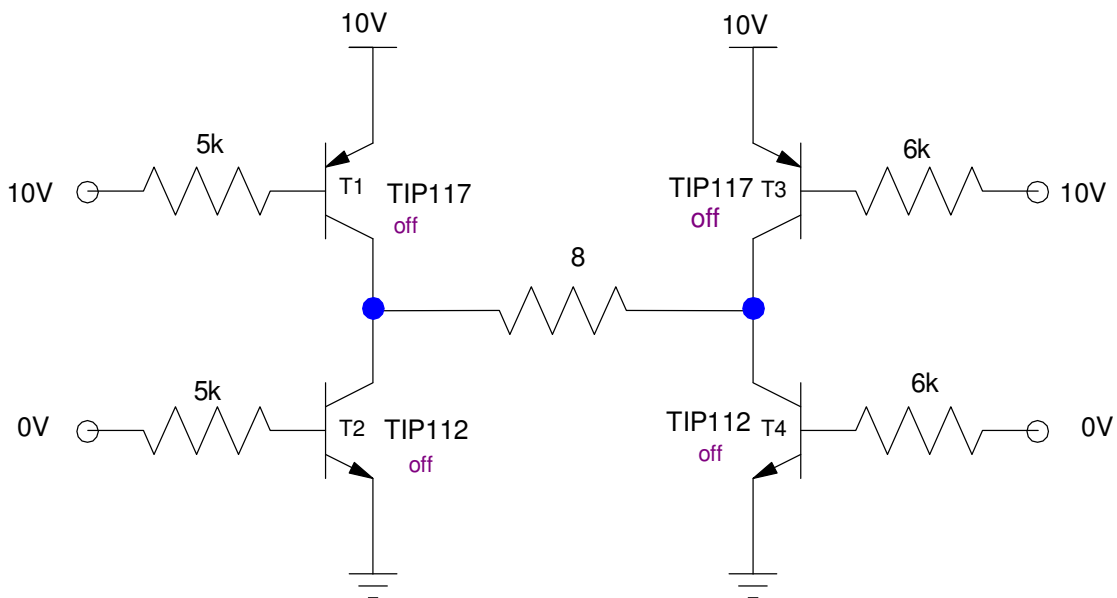

Coast: All transistors off

H-Bridge Analysis (take 2)

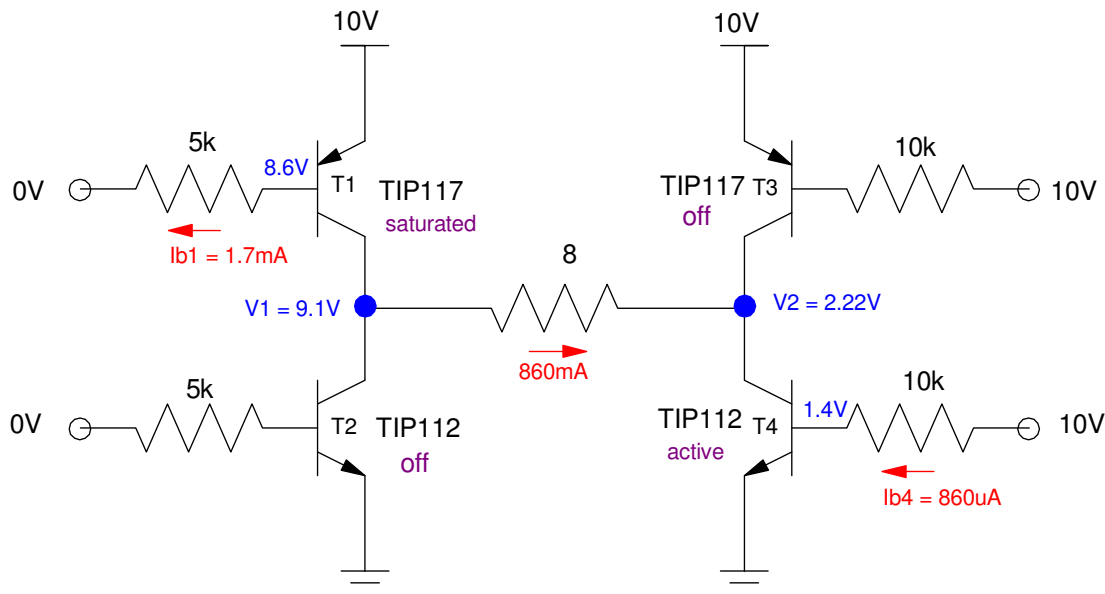If you do it wrong, a transistor will be in the active region. For example, find the voltages and currents



Solution: First find the base currents

$$I_{b1} = \left(\frac{10 - 1.4}{5k} \right) = 1.720mA$$

$$I_{b4} = \left(\frac{10 - 1.4}{10k} \right) = 860\mu A$$

The currents is then

$$I_L = \min \left(\beta I_{b1}, \left(\frac{10 - 1.8}{8} \right), \beta I_{b4} \right)$$

$$I_L = \min (1.73A, 1.025A, 860mA)$$

Since transistor 4 wins, it limits the current and is operating in the active region.

T1 is saturated

- $\beta I_b = 1.74A > 860mA$
- $V_{ec} = 0.9V$
- $V_1 = 9.1V$

V2 is harder to find since T4 is in the active region. This tells you that $0.9V < V_{ce} < 12V$ (i.e. doesn't help). To find V2, back into it

$$V_L = 8\Omega \cdot 860mA = 6.88V$$

$$V_2 = V_1 - 6.88V = 2.22V$$

This is actually a bad design: you want the transistors to saturate. Since you're trying to push 1.025A through the 8 Ohm load, I_b should be

$$\beta I_b > I_c$$

$$I_b > \frac{I_c}{\beta} = \frac{1.025A}{1000} = 1.025mA$$

Let $I_b = 2mA$. Then



$$R_b = \left(\frac{10V - 1.4V}{2mA} \right) = 4300\Omega$$

Make all four resistors 4.3k (give or take) and this H-bridge will be able to drive the load at

- +8.2V T1 and T4 on
- -8.2V T2 and T3 on
- 0V all transistors off

1/2 H-Bridge on a Chip: TLE5205:

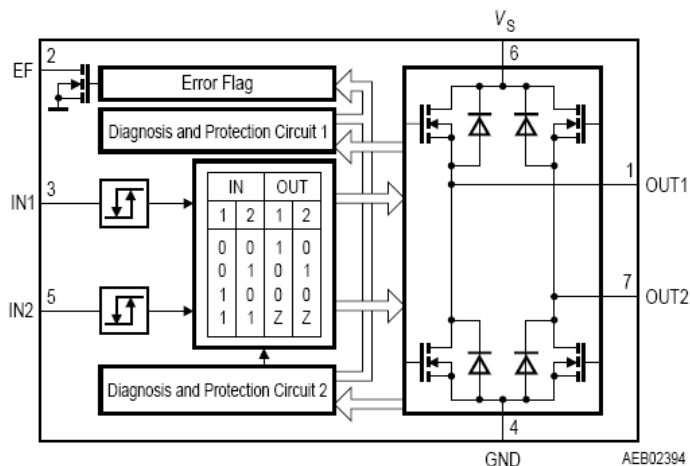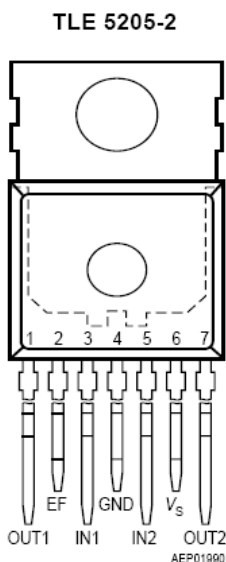H-Bridges are kind of useful. Not surprisingly, there are H-bridges on a chip.




TLE5205 (\$7.16 from Digikey)

This chip lets a PIC drive a motor at up to +40VDC, +5A using TTL levels. The logic from the PIC is:

Functional Truth Table				
IN1	IN2	OUT1	OUT2	Comments
L	L	H	L	Motor turns clockwise
L	H	L	H	Motor turns counterclockwise
H	L	L	L	Brake; both low side transistors turned-ON
H	H	Z	Z	Coast: no current through the motor

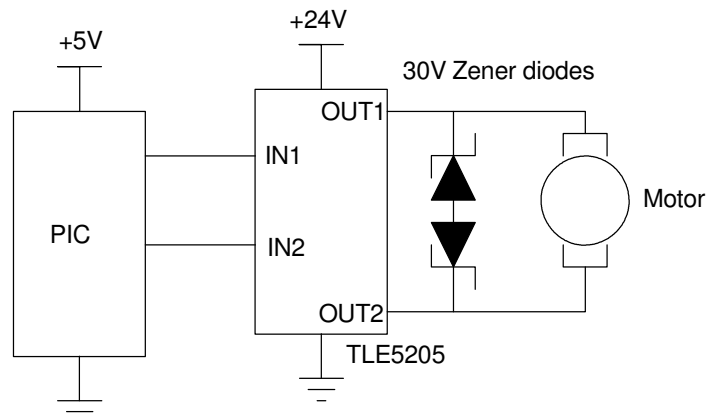note: You need to use zener diodes to protect the chip at the output. Use zener diodes slightly larger than the voltage driving the motor.



Dual H-Bridges: L298N

A third option is to use a ready-built H-bridge like the one shown below.

Stepper Motor Drive Controller Board Module L298N Dual H Bridge
 🔥 Top selling product ★★★★★ 1 product rating

Item condition: **New**

Quantity: More than 10 available
 121 sold / See feedback

Price: **US \$1.99** [Buy It Now](#)

[Add to cart](#)

13 watching [Add to watch list](#)
[Add to collection](#)

121 sold | Experienced seller | 30-day returns

Shipping: **\$3.00** Standard Shipping | [See details](#)
 Item location: Bensenville, Illinois, United States
 Ships to: United States | [See exclusions](#)

Delivery: Estimated on or before **Mon, Aug. 28** to 58104 📍

Payments: [PayPal](#) [VISA](#) [MasterCard](#) [Discover](#) [American Express](#)
 Credit Cards processed by PayPal

Dual H-Bridge from ebay (search: Arduino H Bridge)

This chip actually contains two H-bridges, each capable of


- Voltage Range: 5V .. 35V
- Current Range: Up to 2A per channel
- Max Power: 25W:

The board contains two H-bridges

- { IN-1, IN-2 } control voltage V_{ab}
- { IN-3, IN-4 } control voltage V_{cd}

IN-1	IN-2	V_{ab}	IN-3	IN-4	V_{cd}
0V	0V	0 V	0V	0V	0 V
0V	5V	+ V_{cc}	0V	5V	+ V_{cc}
5V	0V	- V_{cc}	5V	0V	- V_{cc}
5V	5V	0 V	5V	5V	0 V

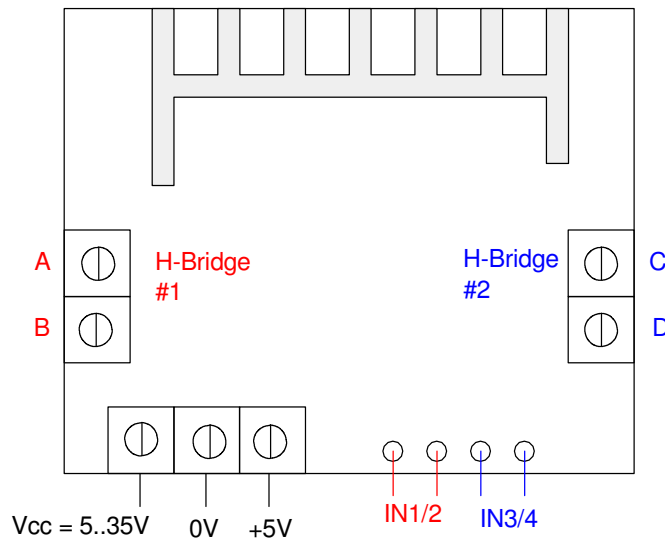If you're trying to demonstrate knowledge of electronics and H-bridges, I'd build an H-bridge at the transistor level. If you're trying to demonstrate something else, I'd use an L298N board. They're inexpensive, they're easy to use, and they work.



Wiring for a L298N board IN1 and IN2 control the voltage V_{AB} . IN3 and IN4 control the voltage V_{CD} .