
Circuits I Review

ECE 320 Electronics I (Digital)

Jake Glower - Lecture #1

Circuits I Review

EE 206 Circuits I covers steady-state analysis of circuits with DC inputs.

Three techniques are used:

- Current Loops
- Voltage Nodes
- Thevenin Equivalent


All of these techniques are used in Electronics I and II. There are shortcuts we'll introduce in this course - but you can analyze pretty much any circuit just using these techniques.

Resistors in Series and Parallel:

Resistors in series add:


$$R = 100 + 200 + 300$$

$$R = 600\Omega$$

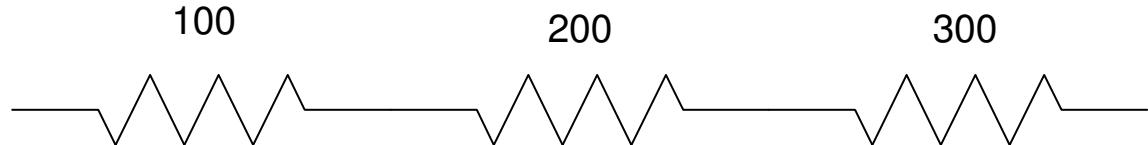


Resistors in parallel add as the sum of the inverses inverted.
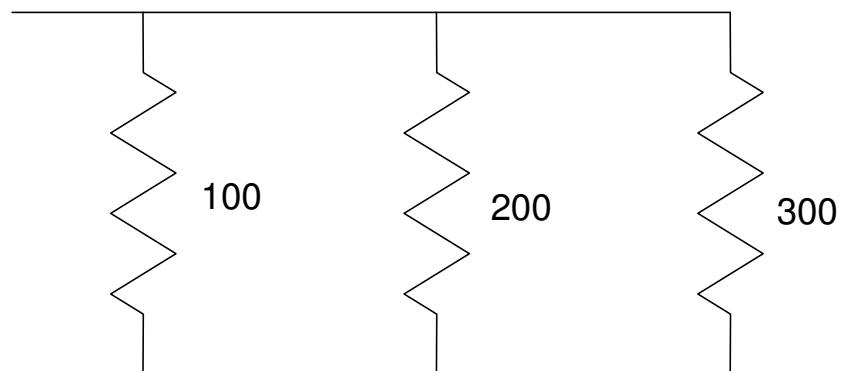
$$R = \left(\frac{1}{100} + \frac{1}{200} + \frac{1}{300} \right)^{-1} = 54.54\Omega$$



Example (Handout)

Find R_{ab}

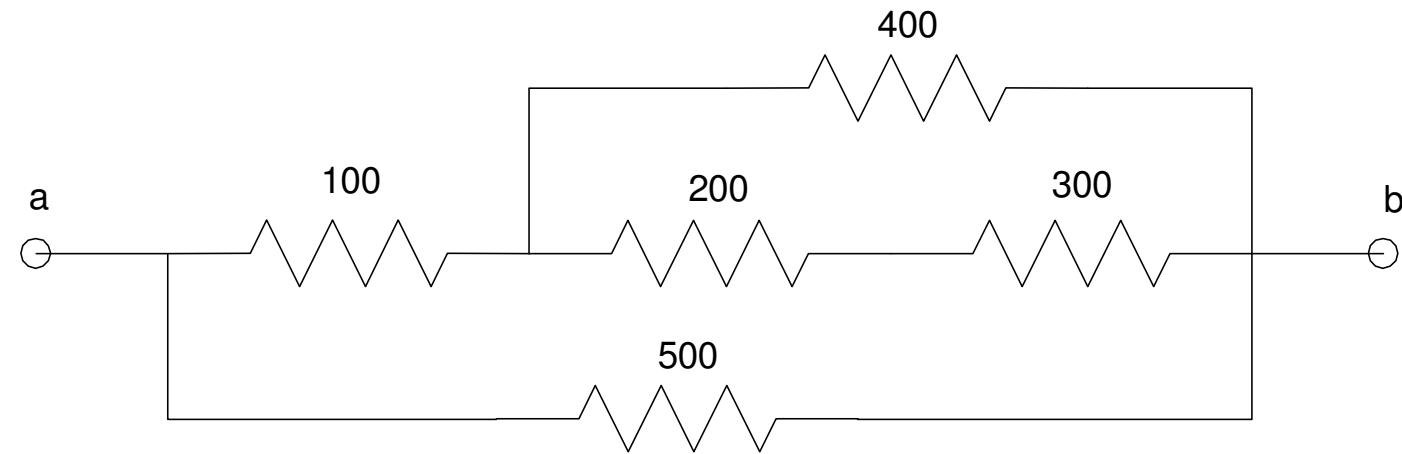


Current Loops

Conservation of Voltage:

- The sum of the voltages around any closed path must be zero.

Step 1: Determine the number of "windows" the circuit has. This is how many loop equations you'll need to write.

- $N = 3$

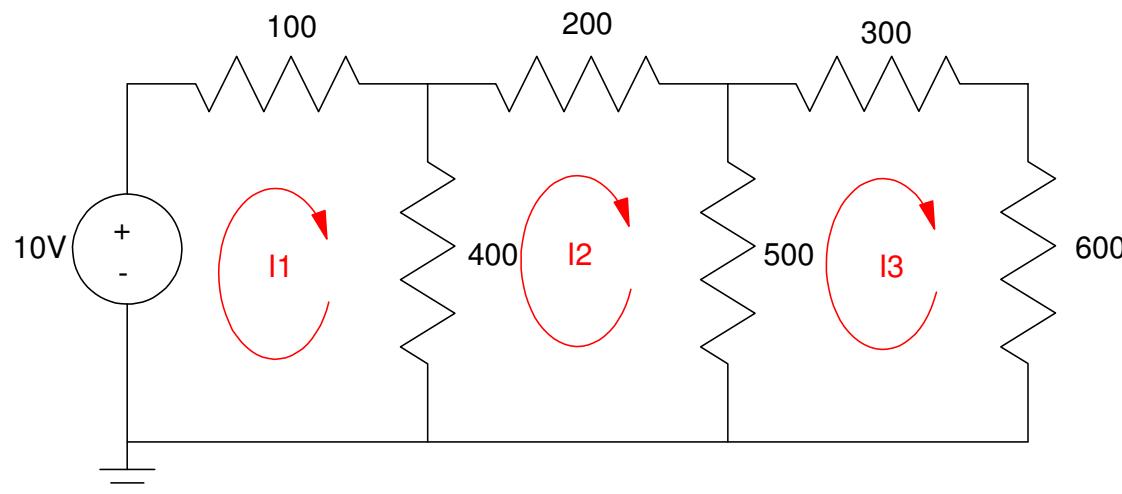


Step 2: Define the currents. I prefer to place a current in each window, each going clockwise. (shown in red).

Step 3) Write 3 equations for 3 unknowns:

$$-10 + 100I_1 + 400(I_1 - I_2) = 0$$

$$400(I_2 - I_1) + 200I_2 + 500(I_2 - I_3) = 0$$

$$500(I_3 - I_2) + 300I_3 + 600I_3 = 0$$

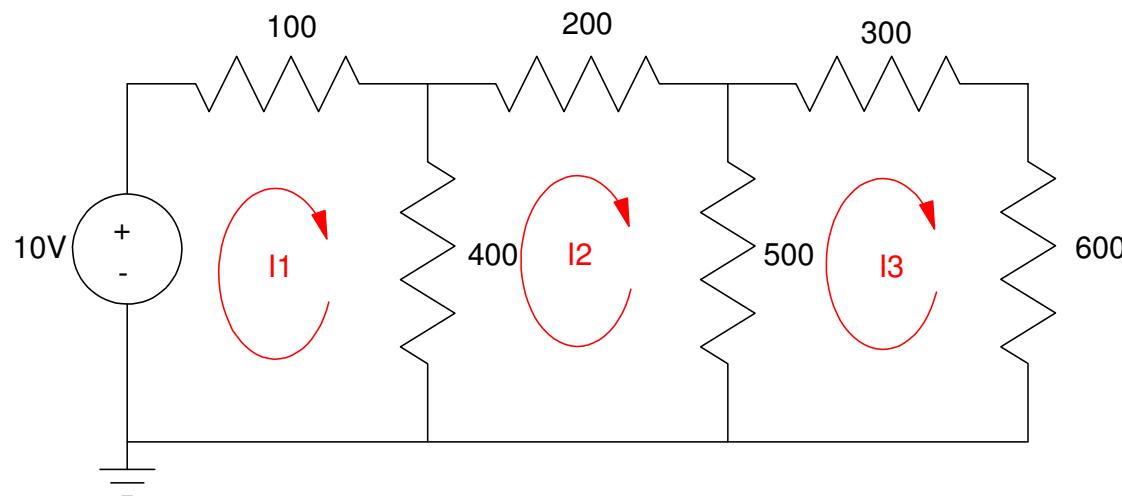

Step 4: Solve. First group terms:


$$500I_1 - 400I_2 = 10$$

$$-400I_1 + 1100I_2 - 500I_3 = 0$$

$$-500I_2 + 1400I_3 = 0$$

Put in matrix form:
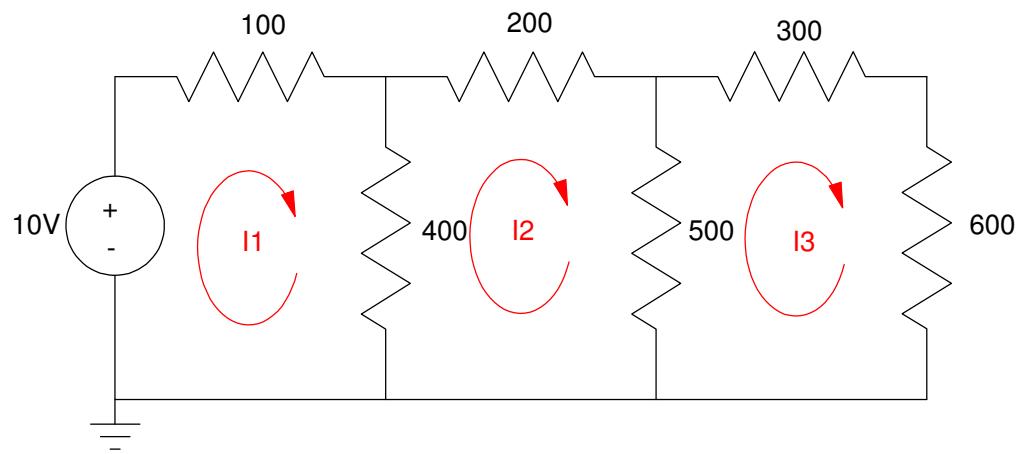
$$\begin{bmatrix} 500 & -400 & 0 \\ -400 & 1100 & -500 \\ 0 & -500 & 1400 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$



Solve in Matlab:

$$A = [500, -400, 0 ; -400, 1100, -500 ; 0, -500, 1400]$$

$$\begin{matrix} 500 & -400 & 0 \\ -400 & 1100 & -500 \\ 0 & -500 & 1400 \end{matrix}$$

$$B = [10; 0; 0]$$


$$\begin{matrix} 10 \\ 0 \\ 0 \end{matrix}$$

$$I = \text{inv}(A) * B$$

$$I_1 = 0.0306$$


$$I_2 = 0.0133$$

$$I_3 = 0.0048$$

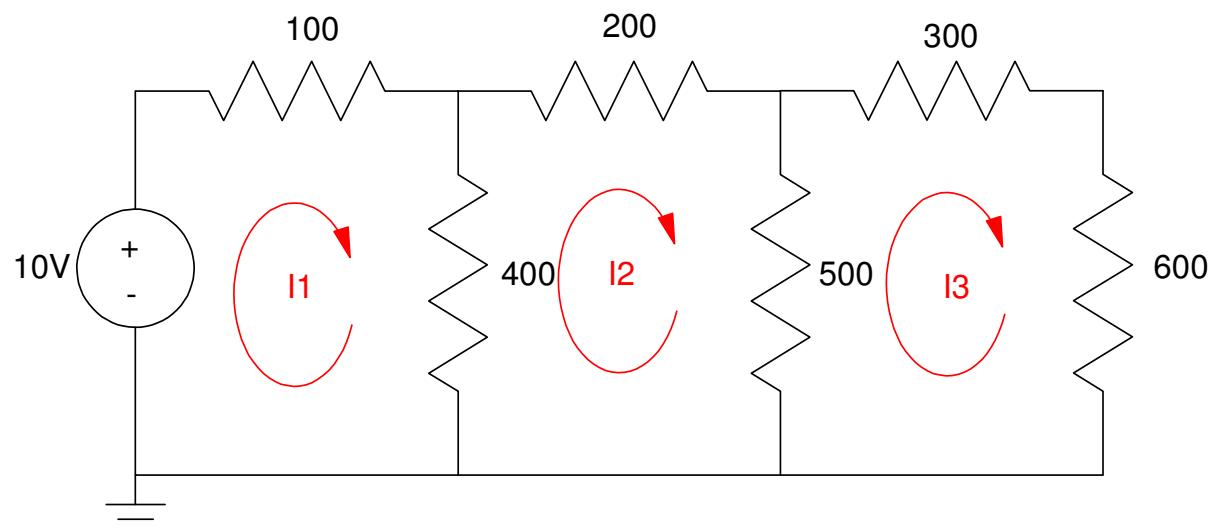

Testing (CircuitLab)

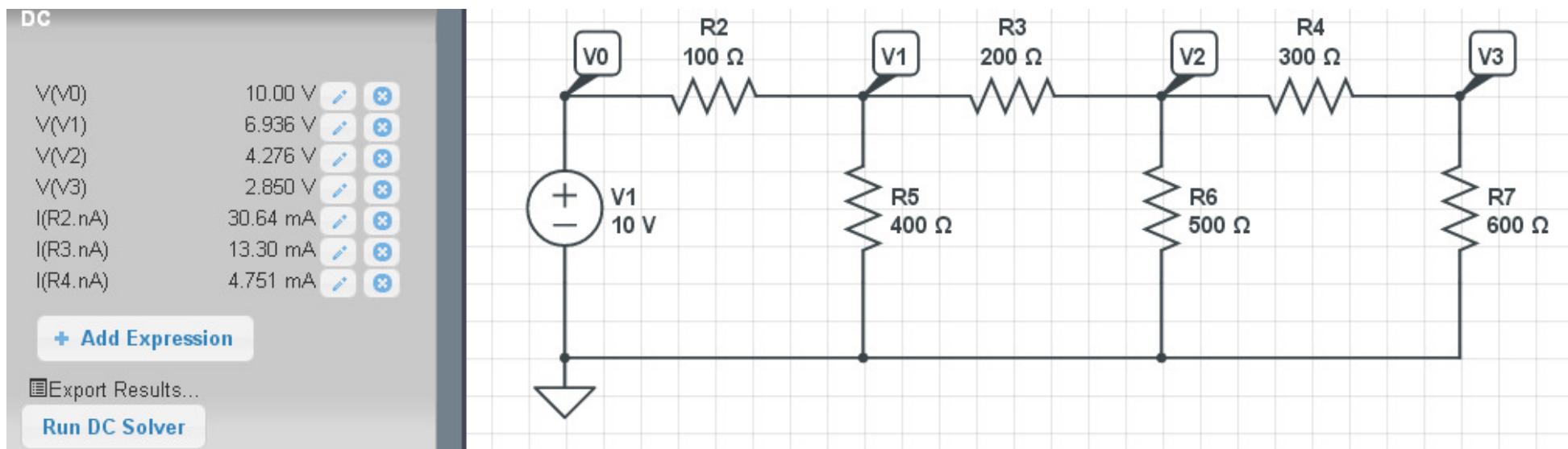- Add Expression
- Click on the left side of each resistor.



SuperLoops

- If you need more equations, choose another closed path
- A path which passes over several loops is called a *superloop*

Example:


Step 1: $N = 3$ (3 windows)

Step 2: Define currents

Step 3: Write N equations for N unknowns.

$$I_3 - I_2 = 2$$

$$-10 + 100I_1 + 400(I_1 - I_2) = 0$$

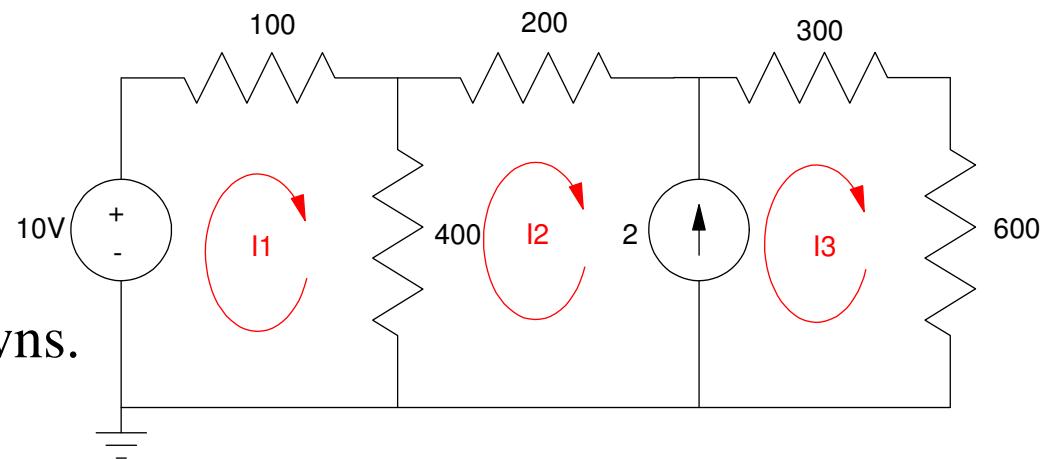

SuperLoop: Outer Loop

$$-10 + 100I_1 + 200I_2 + 300I_3 + 600I_3 = 0$$

Step 4: Solve N equations for N unknowns.

Group terms:


$$I_3 - I_2 = 2$$

$$500I_1 - 400I_2 = 10$$

$$100I_1 + 200I_2 + 900I_3 = 10$$

Put in matrix form:
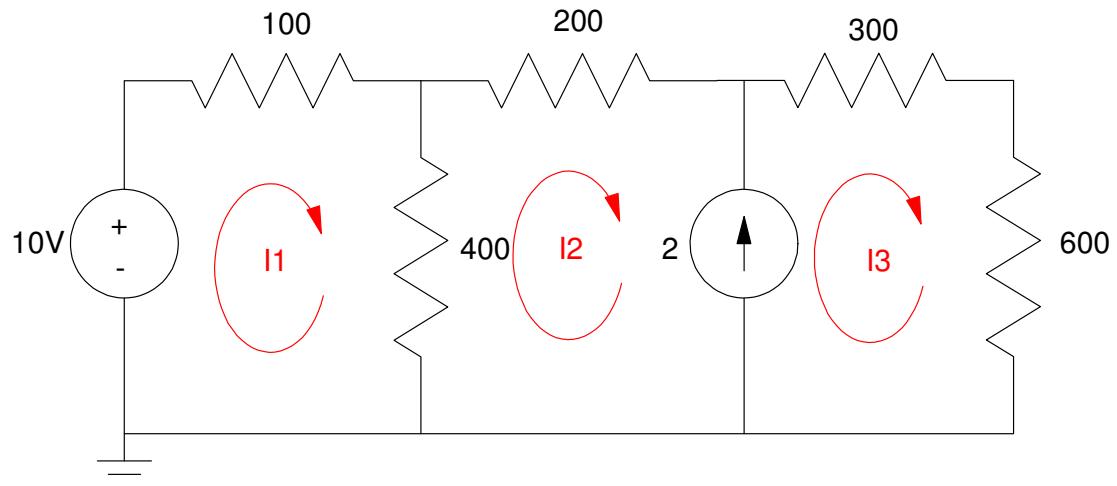
$$\begin{bmatrix} 0 & -1 & 1 \\ 500 & -400 & 0 \\ 100 & 200 & 900 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 2 \\ 10 \\ 10 \end{bmatrix}$$



Solve in Matlab:

```
>> A = [0, -1, 1 ; 500, -400, 0 ; 100, 200, 900]
```


$$\begin{matrix} 0 & -1 & 1 \\ 500 & -400 & 0 \\ 100 & 200 & 900 \end{matrix}$$

```
>> B = [2;10;10]
```

$$\begin{matrix} 2 \\ 10 \\ 10 \end{matrix}$$


```
>> I = inv(A)*B
```
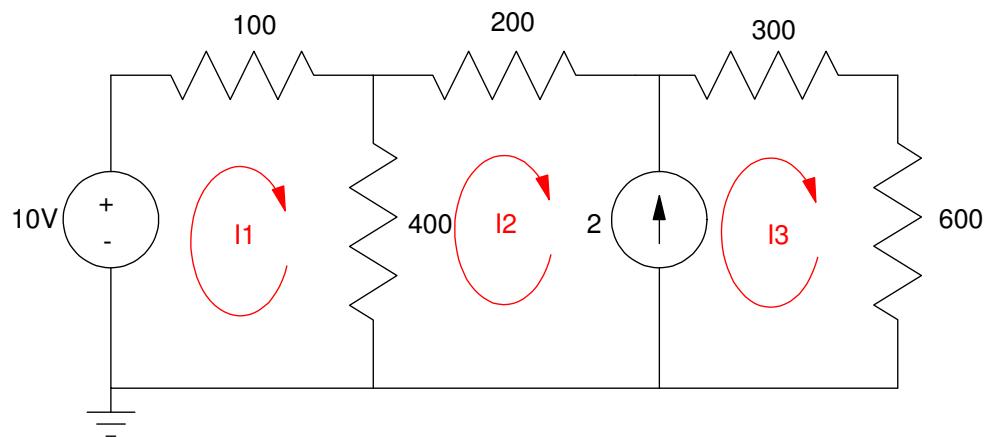
$$\begin{matrix} I_1 = -1.1949 \\ I_2 = -1.5186 \\ I_3 = 0.4814 \end{matrix}$$



Example (Handout)

Write the current loop equations

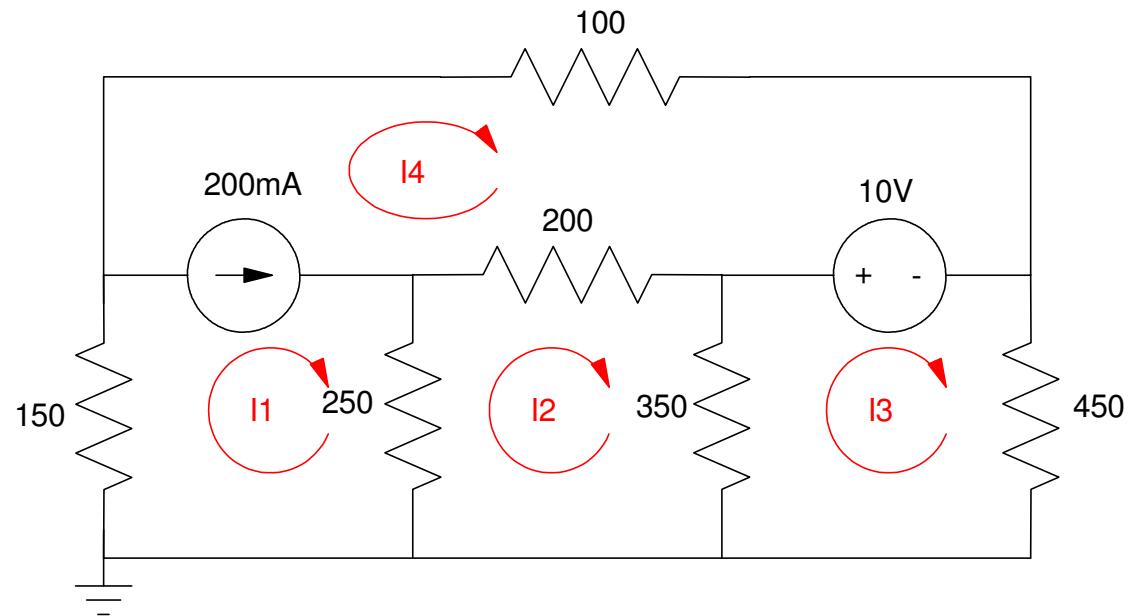

Voltage Nodes:

Conservation of Current

- The total current flowing to a node must be zero
- For N unknown voltages, write N voltage node equations

Step 1: Define circuit ground.

Step 2: Define the remaining N voltage nodes.


Step 3: Write N equations for N unknowns

$$V_1 = 10$$

$$\left(\frac{V_2-V_1}{100}\right) + \left(\frac{V_2}{400}\right) + \left(\frac{V_2-V_3}{200}\right) = 0$$

$$\left(\frac{V_3-V_2}{200}\right) + \left(\frac{V_3}{500}\right) + \left(\frac{V_3-V_4}{300}\right) = 0$$
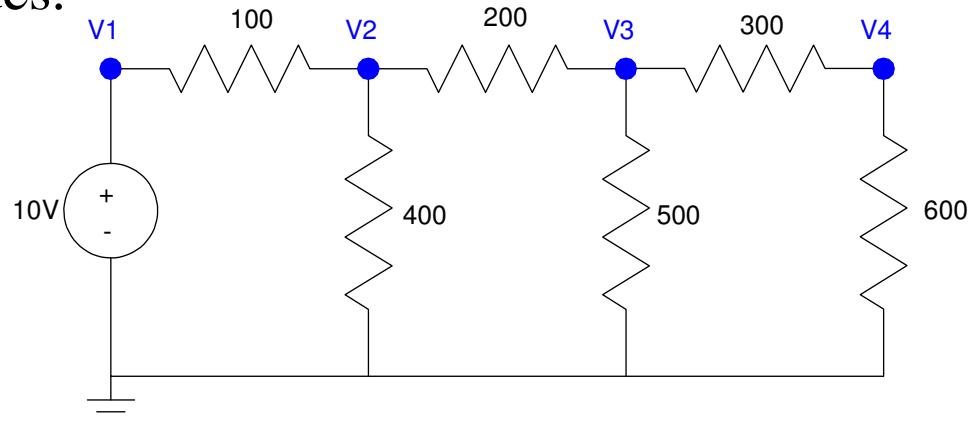
$$\left(\frac{V_4-V_3}{300}\right) + \left(\frac{V_4}{600}\right) = 0$$



Step 4: Solve. Group terms:

$$V_1 = 10$$

$$\left(\frac{-1}{100}\right)V_1 + \left(\frac{1}{100} + \frac{1}{400} + \frac{1}{200}\right)V_2 + \left(\frac{-1}{200}\right)V_3 = 0$$

$$\left(\frac{-1}{200}\right)V_2 + \left(\frac{1}{200} + \frac{1}{500} + \frac{1}{300}\right)V_3 + \left(\frac{-1}{300}\right)V_4 = 0$$

$$\left(\frac{-1}{300}\right)V_3 + \left(\frac{1}{300} + \frac{1}{600}\right)V_4 = 0$$

Place in matrix form:

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{100}\right) \left(\frac{1}{100} + \frac{1}{400} + \frac{1}{200}\right) & \left(\frac{-1}{200}\right) & 0 & 0 \\ 0 & \left(\frac{-1}{200}\right) & \left(\frac{1}{200} + \frac{1}{500} + \frac{1}{300}\right) & \left(\frac{-1}{300}\right) \\ 0 & 0 & \left(\frac{-1}{300}\right) & \left(\frac{1}{300} + \frac{1}{600}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve in Matlab

```
A = [1,0,0,0 ; -1/100, 1/100+1/400+1/200,-1/200,0];  
A = [A ; 0,-1/200,1/200+1/500+1/300,-1/300 ; 0,0,-1/300,1/300+1/600]
```


$$\begin{matrix} 1.0000 & 0 & 0 & 0 \\ -0.0100 & 0.0175 & -0.0050 & 0 \\ 0 & -0.0050 & 0.0103 & -0.0033 \\ 0 & 0 & -0.0033 & 0.0050 \end{matrix}$$

```
B = [10;0;0;0]
```


$$\begin{matrix} 10 \\ 0 \\ 0 \\ 0 \end{matrix}$$

```
V = inv(A) *B
```
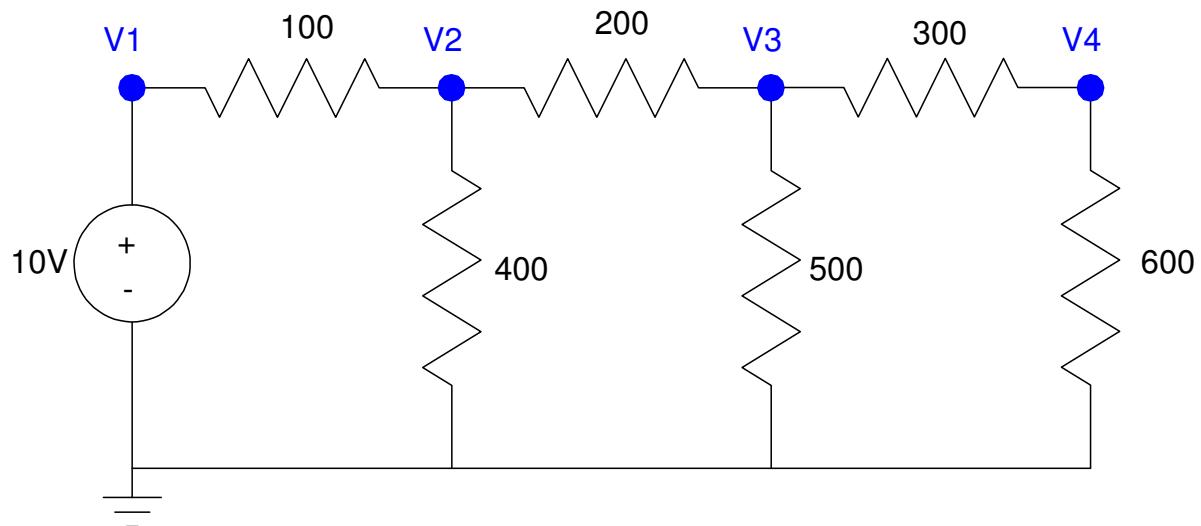
$$\begin{matrix} V1 & 10.0000 \\ V2 & 6.9359 \\ V3 & 4.2755 \\ V4 & 2.8504 \end{matrix}$$



Testing: Check with CircuitLab

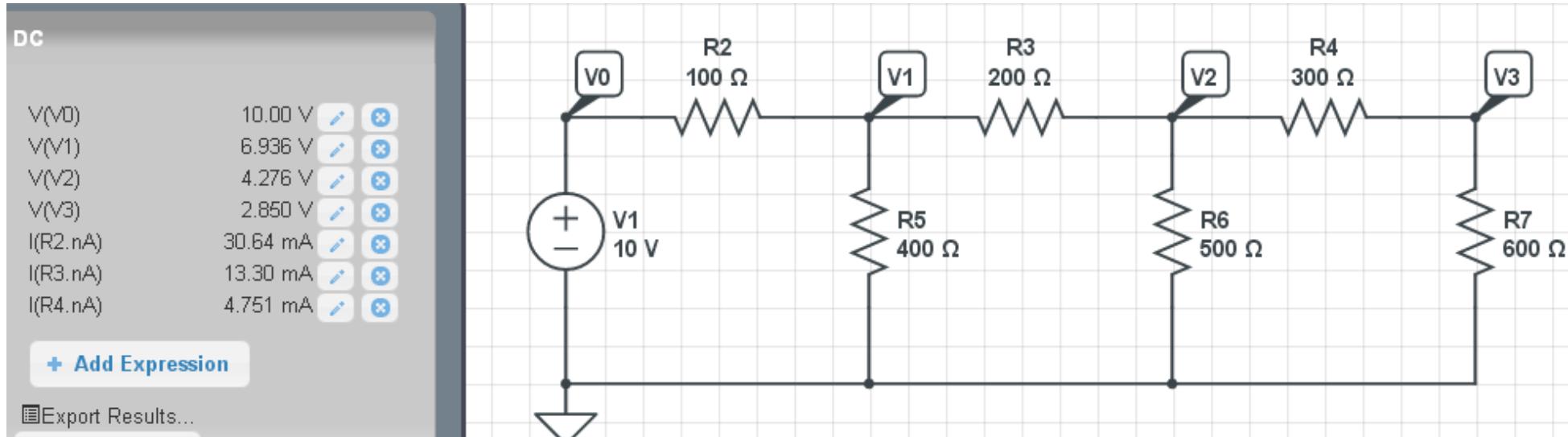

Super-Nodes:

- The current coming out of any closed-path must be zero
- Paths which enclose several nodes are called *supernodes*

Example:

Step 1&2: 4 Nodes

- Need 4 equations for 4 unknowns


Step 3:

$$V_1 = 10$$

$$V_3 - V_4 = 2$$

$$\left(\frac{V_2-V_1}{100}\right) + \left(\frac{V_2}{400}\right) + \left(\frac{V_2-V_3}{200}\right) = 0$$
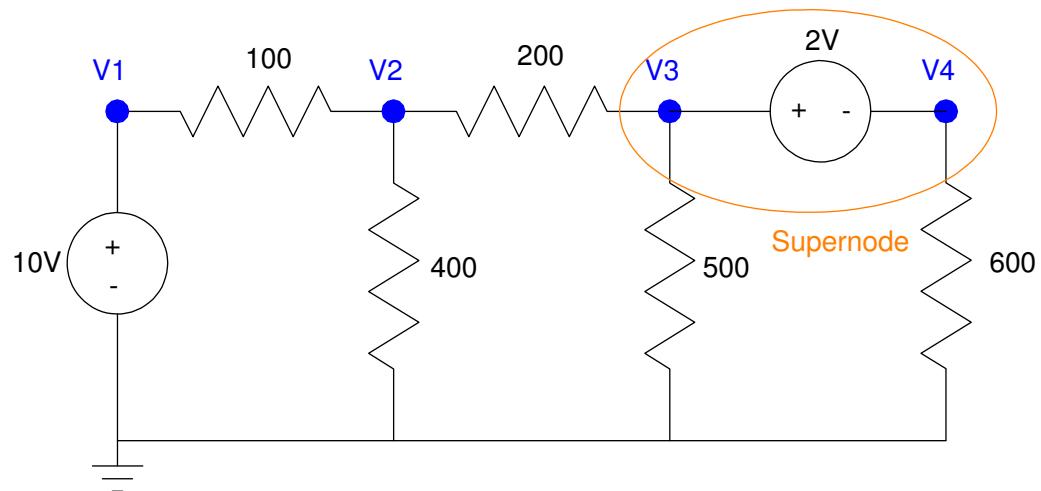
$$\left(\frac{V_3-V_2}{200}\right) + \left(\frac{V_3}{500}\right) + \left(\frac{V_4}{600}\right) = 0 \quad \text{supernode}$$



Step 4: Solve. Group terms

$$V_1 = 10$$

$$V_3 - V_4 = 2$$

$$\left(\frac{-1}{100}\right)V_1 + \left(\frac{1}{100} + \frac{1}{400} + \frac{1}{200}\right)V_2 + \left(\frac{-1}{200}\right)V_3 = 0$$

$$\left(\frac{-1}{200}\right)V_2 + \left(\frac{1}{200} + \frac{1}{500}\right)V_3 + \left(\frac{1}{600}\right)V_4 = 0$$

Place in matrix form:

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 \\ \left(\frac{-1}{100}\right) \left(\frac{1}{100} + \frac{1}{400} + \frac{1}{200}\right) & \left(\frac{-1}{200}\right) & 0 & \\ 0 & \left(\frac{-1}{200}\right) & \left(\frac{1}{200} + \frac{1}{500}\right) & \left(\frac{1}{600}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 10 \\ 2 \\ 0 \\ 0 \end{bmatrix}$$

Solve in Matlab:

```
A = [1,0,0,0;0,0,1,-1;-1/100,1/100+1/400+1/200,-1/200,0;0,-1/200,1/200+1/500,1/600]
```


$$\begin{matrix} 1.0000 & 0 & 0 & 0 \\ 0 & 0 & 1.0000 & -1.0000 \\ -0.0100 & 0.0175 & -0.0050 & 0 \\ 0 & -0.0050 & 0.0070 & 0.0017 \end{matrix}$$

```
B = [10;2;0;0]
```


$$\begin{matrix} 10 \\ 2 \\ 0 \\ 0 \end{matrix}$$

```
V = inv(A)*B
```
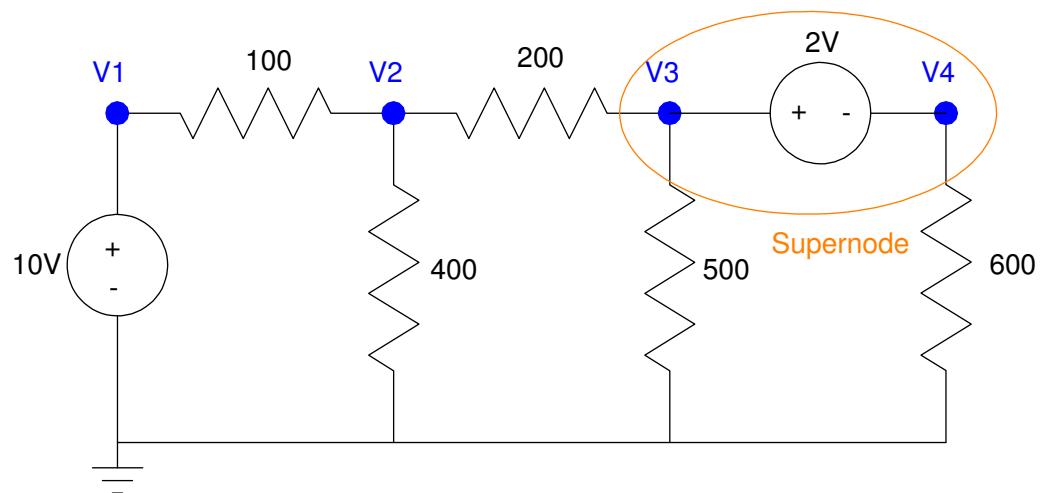
$$\begin{matrix} V1 & 10.0000 \\ V2 & 6.9737 \\ V3 & 4.4079 \\ V4 & 2.4079 \end{matrix}$$




Checking in Circuitlab

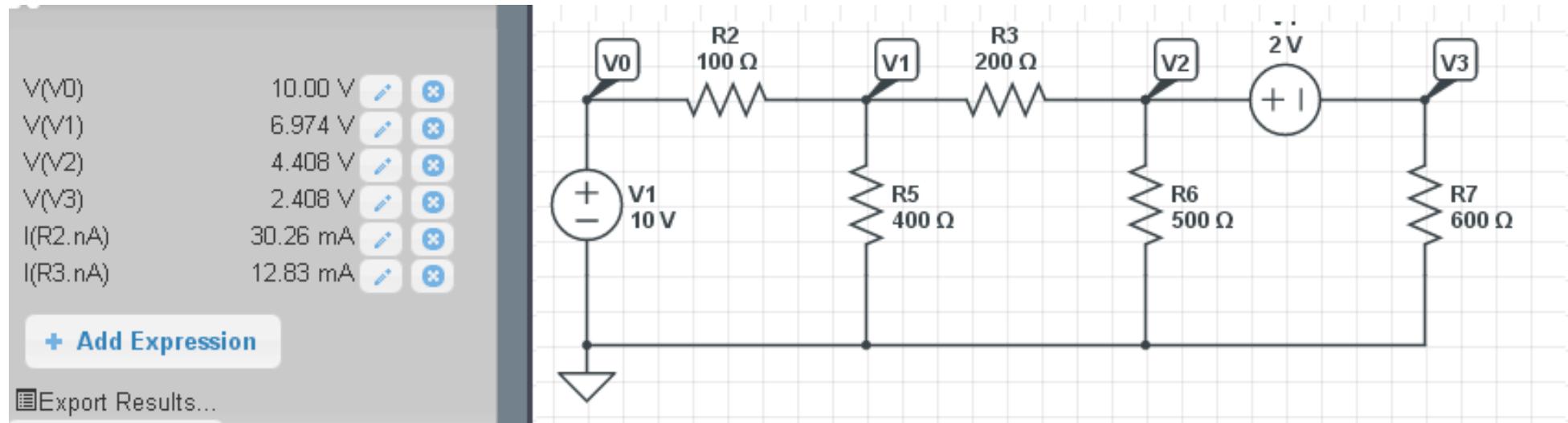


Example: (handout)

Write the voltage node equations

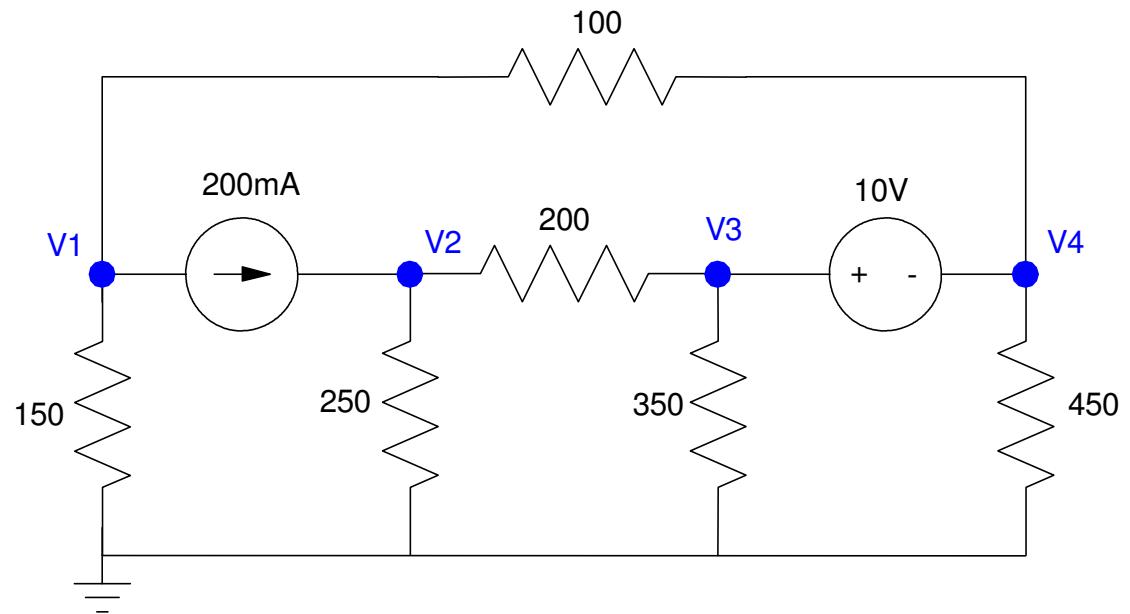

Thevenin Equivalents

- If a circuit is linear (i.e. only contains sources, resistors, capacitors, and inductors), its voltage / current relationship will follow a straight line, termed the load line.
- Any circuit which has the same load line is indistinguishable from the original circuit.
- The simplest circuits which produce a load line are a voltage source and resistor (Thevenin equivalent) and a current source and a resistor (Norton equivalent).

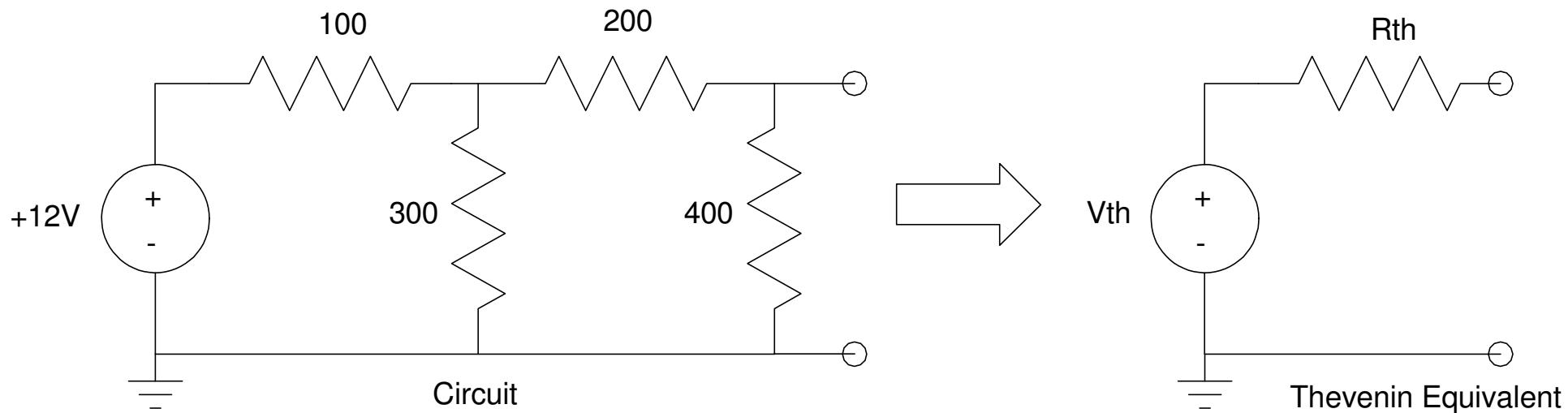


Since the two circuits are equivalent, whatever test you do on the circuit to the right to find V_{th} and R_{th} , do the same test to the original circuit.

V_{th} : Measure the open-circuit voltage.

- The original circuit gives 5.33V
- The Thevenin equivalent gives V_{th}


So $V_{th} = 5.33V$

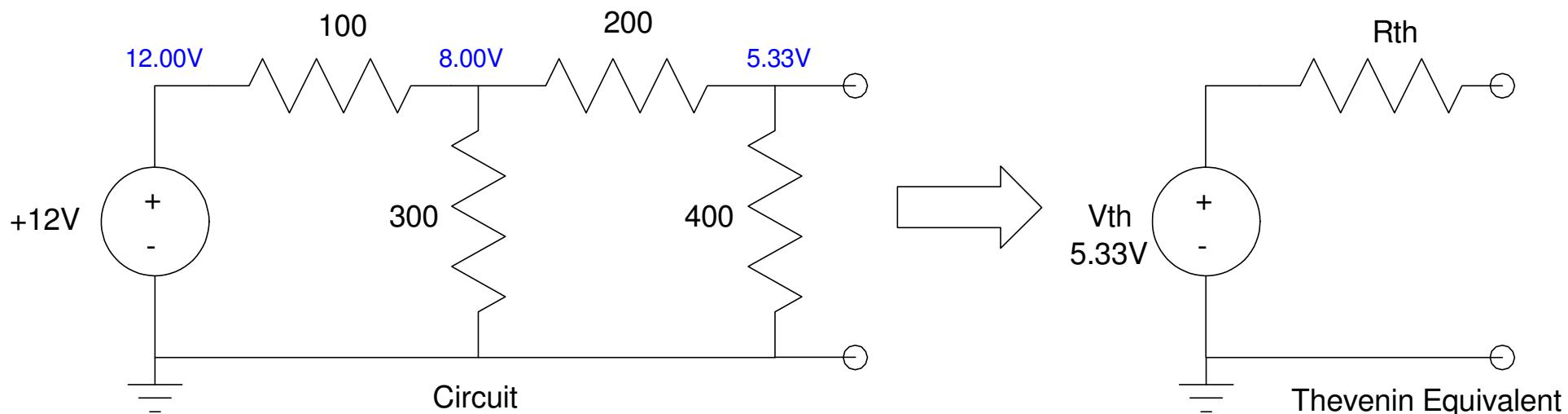

R_{th}: Turn off the source and measure the resistance looking in. This gives

- R = 162.96 Ohms (original circuit)
- R = R_{th} (circuit to the right)

so R_{th} = 162.96 Ohms.

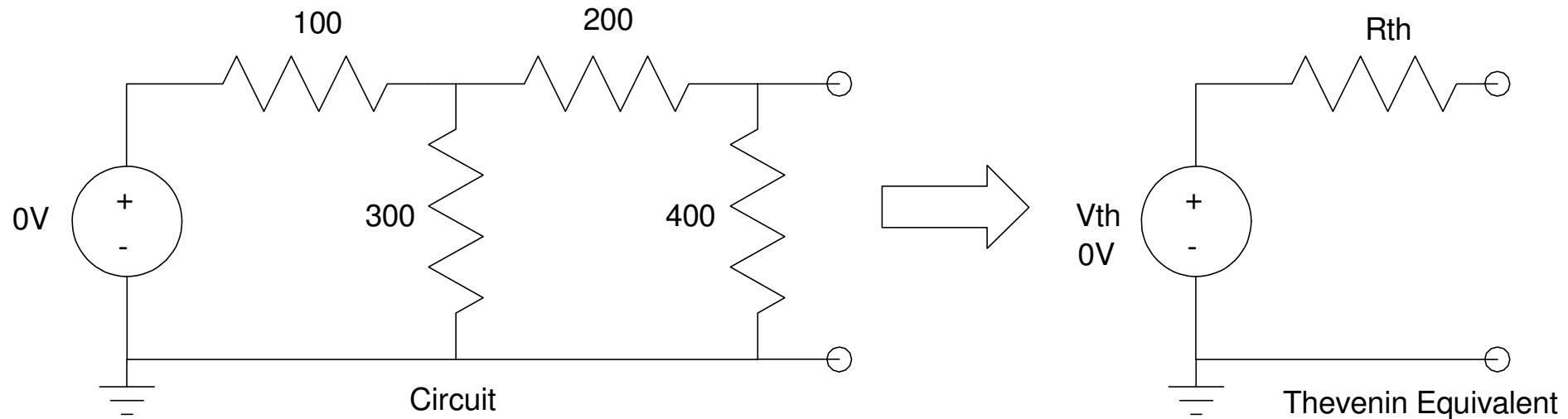

R_{th} (take 2): Sometimes the resistance looking in isn't obvious. In that case, apply a 1V test voltage and compute the current. The Thevenin resistance is then


$$R_{th} = 1V / I_{in}$$

For example with this circuit

$$I_{in} = 6.136mA$$

meaning
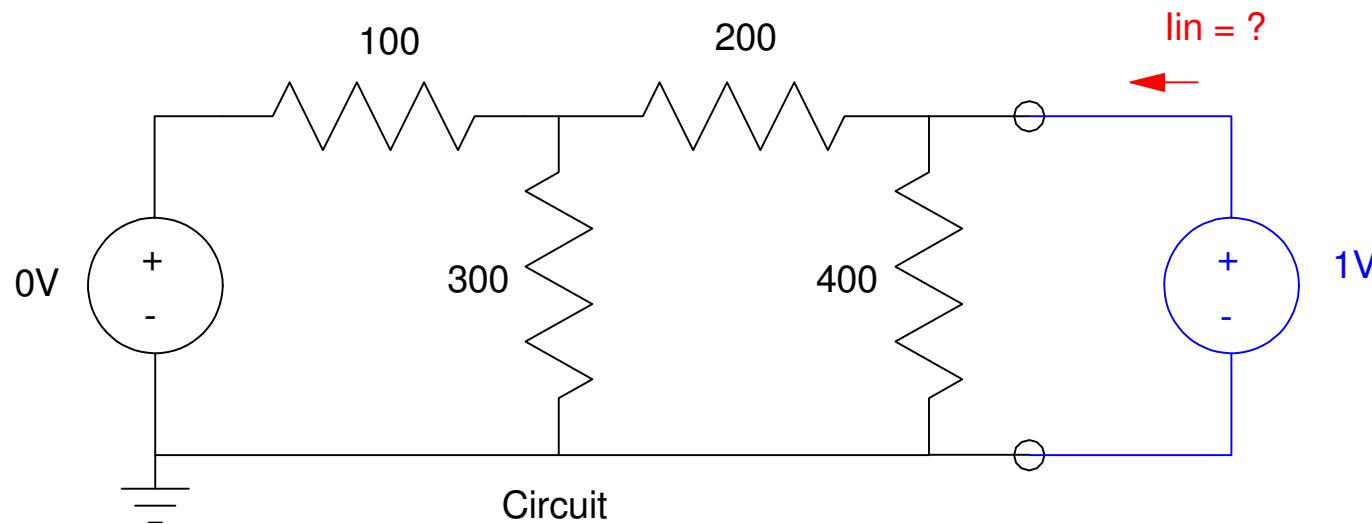
$$R_{th} = 1V / 6.136mA = 162.96 \text{ Ohms}$$



Summary

Resistors

- Add in series
- Add as $\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots\right)^{-1}$ in parallel

Current Loops

- The total current coming from a closed area must be zero
- Write N equations for N unknown currents

Voltage Nodes

- The voltages around a closed path must sum to zero
- Write N equations for N unknown voltages

Thevenin Equivalents

- Replace a circuit with a simpler circuit that has the same load line
-