
H-Bridges

ECE 320 Electronics I

Jake Glower - Lecture #13

Please visit [Bison Academy](#) for corresponding lecture notes, homework sets, and solutions

Transistor Switch (Review)


A transistor is an electronic switch

With it you can turn on and off

- Motors
- LEDs
- Speakers
- etc.

Two variations:

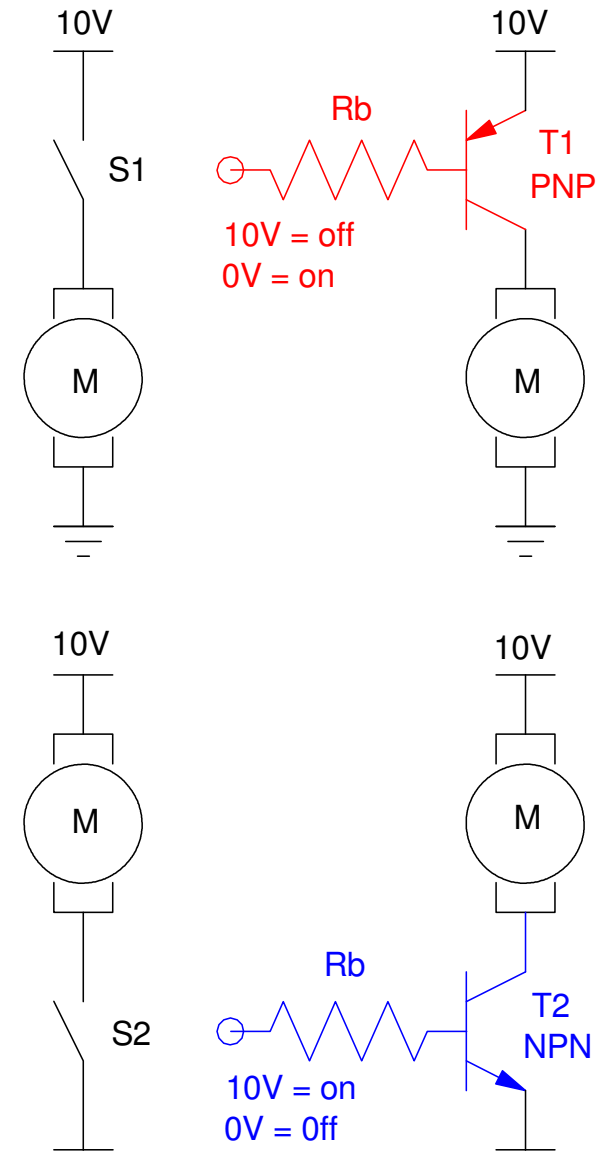- PNP: Switch connected to power
- NPN: Switch connected to ground



Problem:



- How to you make a motor spin forward and reverse
- Using a single power supply?

Solution: Use four switches

- Forward: Close S1 & S4
- Reverse: Close S2 & S3

Replace each switch with a transistor

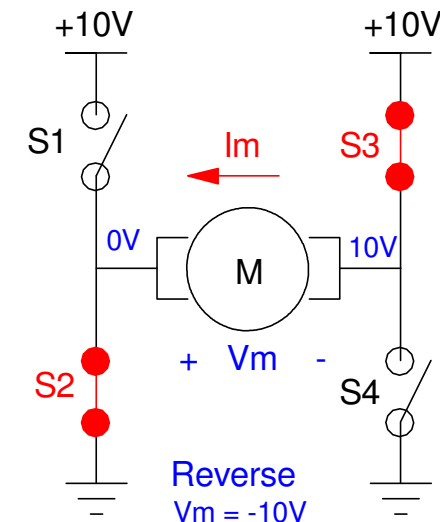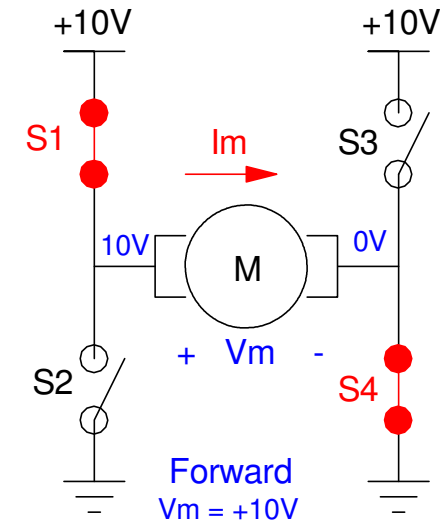
- PNP connected to power
- NPN connected to ground



H-Bridges

4 modes of operation

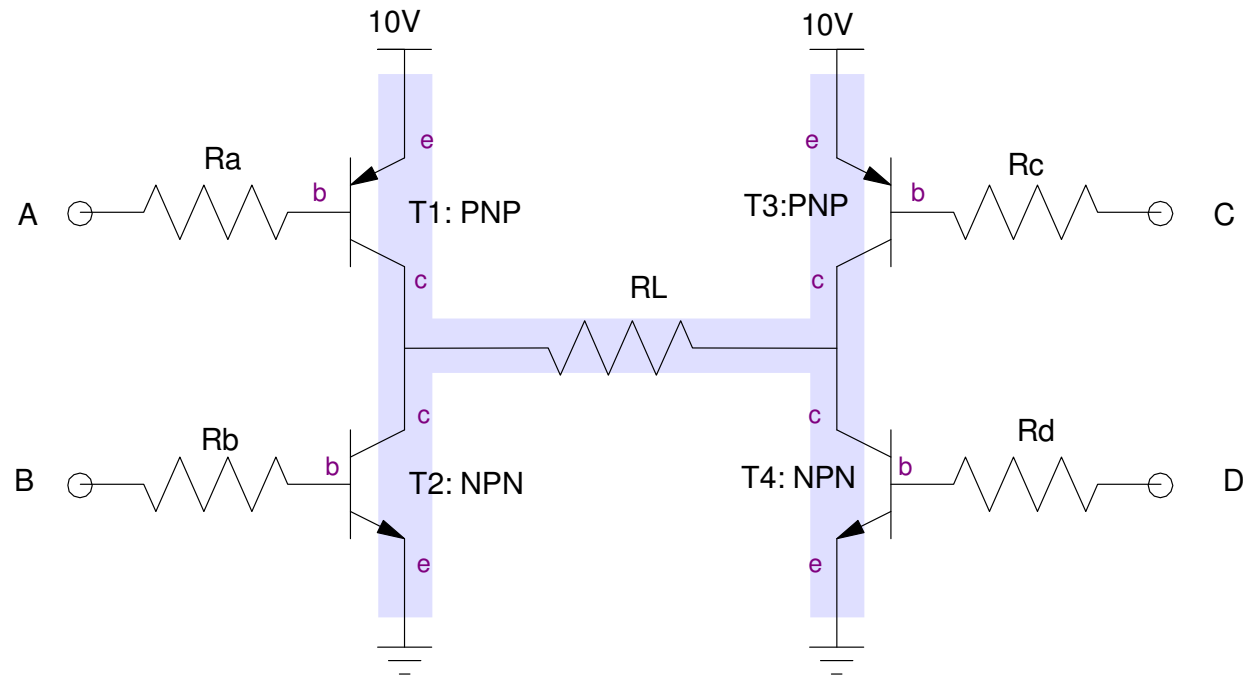- Forward: T1 & T4 on
- Reverse: T2 & T3 on
- Brake: T2 & T4 on
- Coast: all transistors off
- Smoke: All transistors on



H-Bridge Analysis: Forward

Assume TIP transistors ($V_{be} = 1.4V$, $V_{ce(sat)} = 0.9V$)


Transistors are current limiters

$$I = \min\left(\beta I_{b1}, \frac{10V - 0.9V - 0.9V}{8\Omega}, \beta I_{b4}\right)$$

$$I = \min(1.72A, 1.025A, 1.433A)$$

$\beta I_b > I_c$: Transistors are saturated

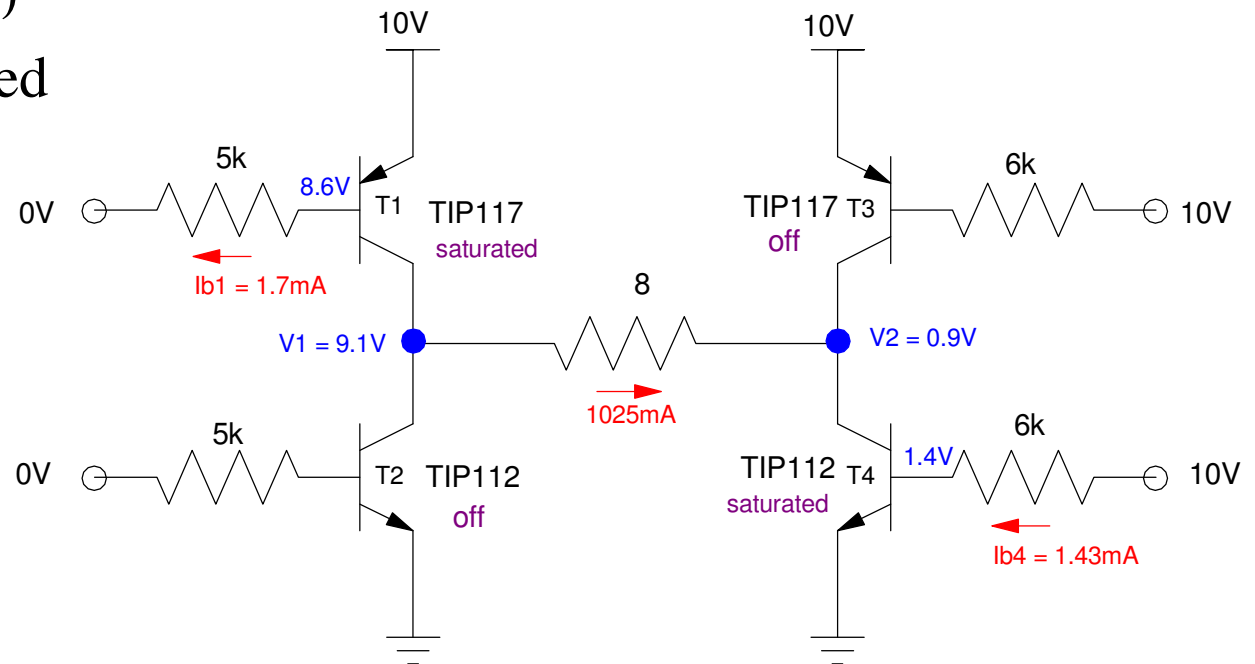- $V_1 = 9.1V$
- $V_2 = 0.9V$
- $I = 1.025A$




CircuitLab (take 1)

Build a Darlington pair using two transistors

- Similar to TIP112 & TIP117
- Use TIP31/32 to handle the current

Results:

- $V1 = 9.265V$
9.1V calculated
- $V2 = 0.860V$
0.9V calculated
- $Q31.b = 1.314V$
1.4V calculated
- $Q10.b = 8.498V$
 $|V_{be}| = 1.502V (1.4V)$
- **$V12 = +8.405V$**
 $I6 = +1.051A$

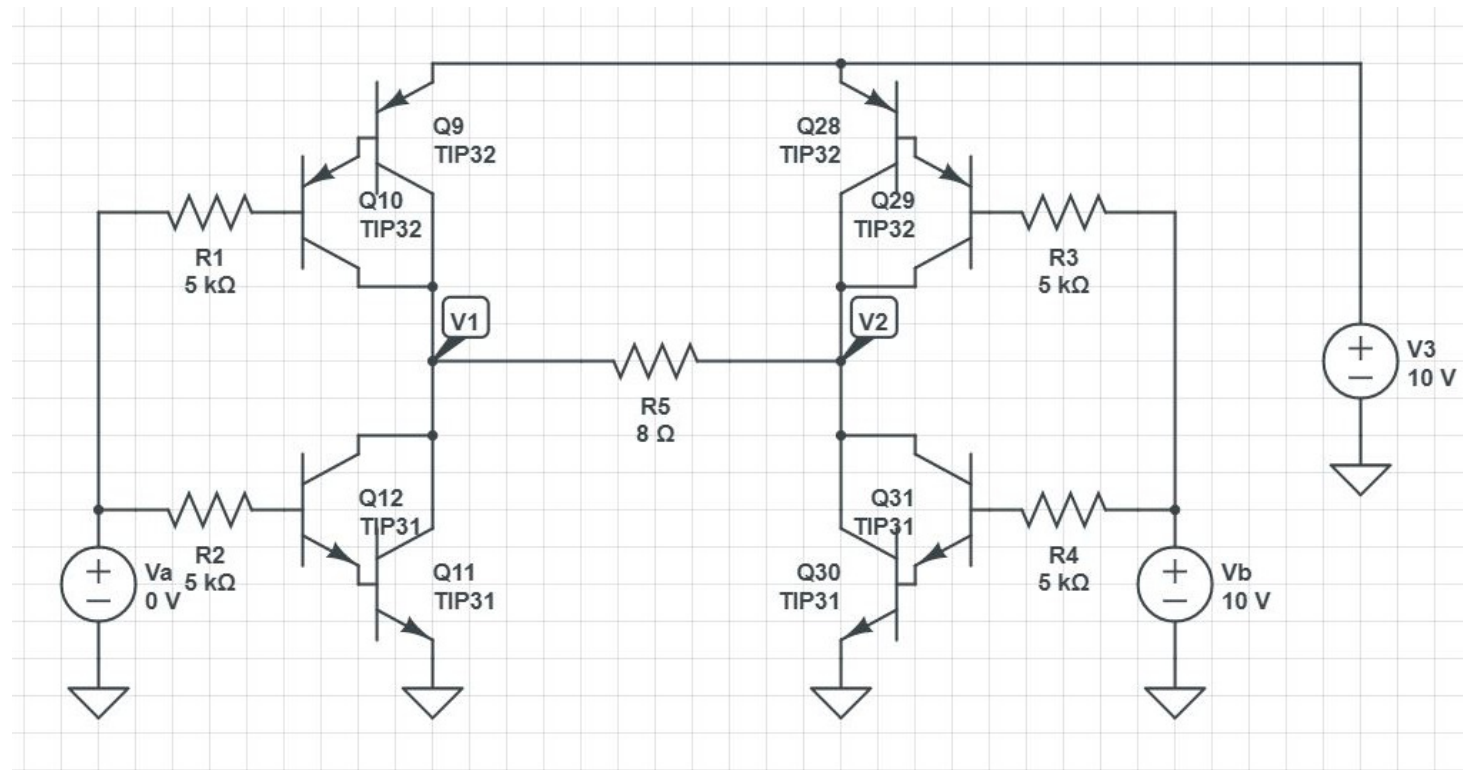

CircuitLab (take 2)

Use a single transistor


- TIP41/TIP42
- Adjust gain to be 1000

Similar to a Zetex 1051a

- \$1 each

Result


- $V1 = 9.842V$
0.158V drop means Q9 is saturated
- $V2 = 0.252V$
Q30 is saturated
- $Q30.b = 0.746V$
0.7V calculated
- $Q9.b = 9.264V$
 $|V_{be}| = 0.736V$ (0.7V)
- **$V12 = +9.590V$**
 $I5 = 1.199A$

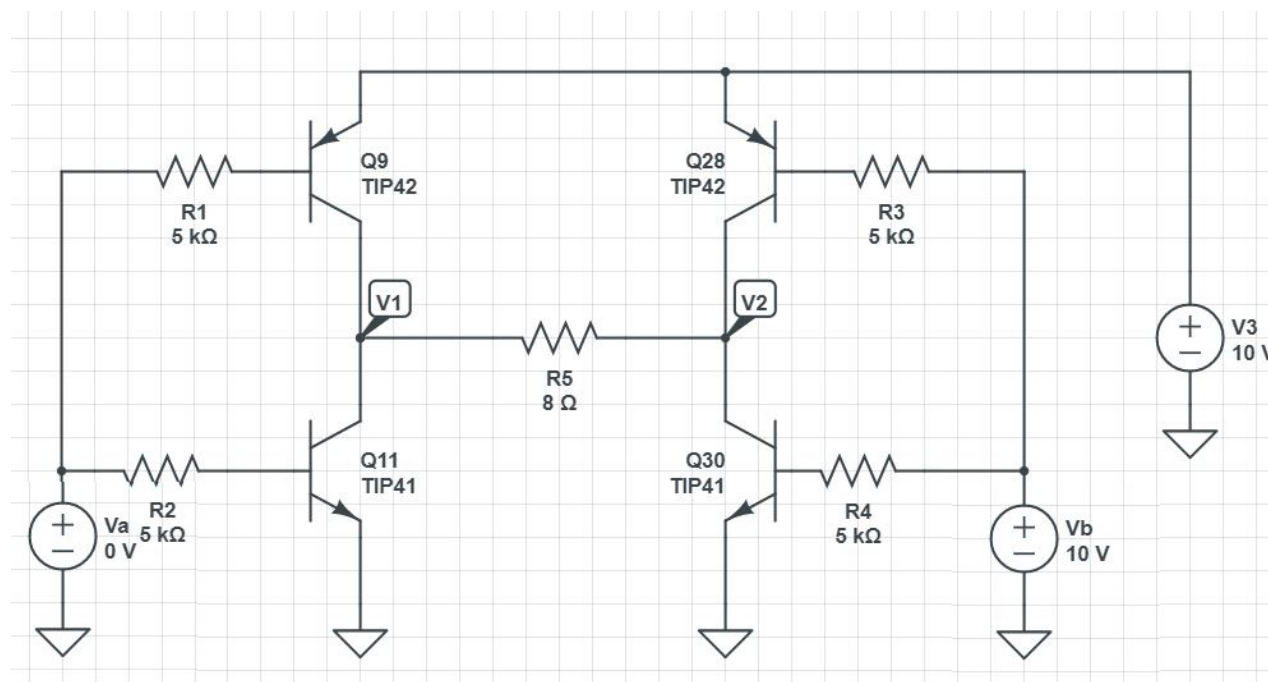

H-Bridge: Reverse


Flip the voltages to turn on T2 and T3. This results in

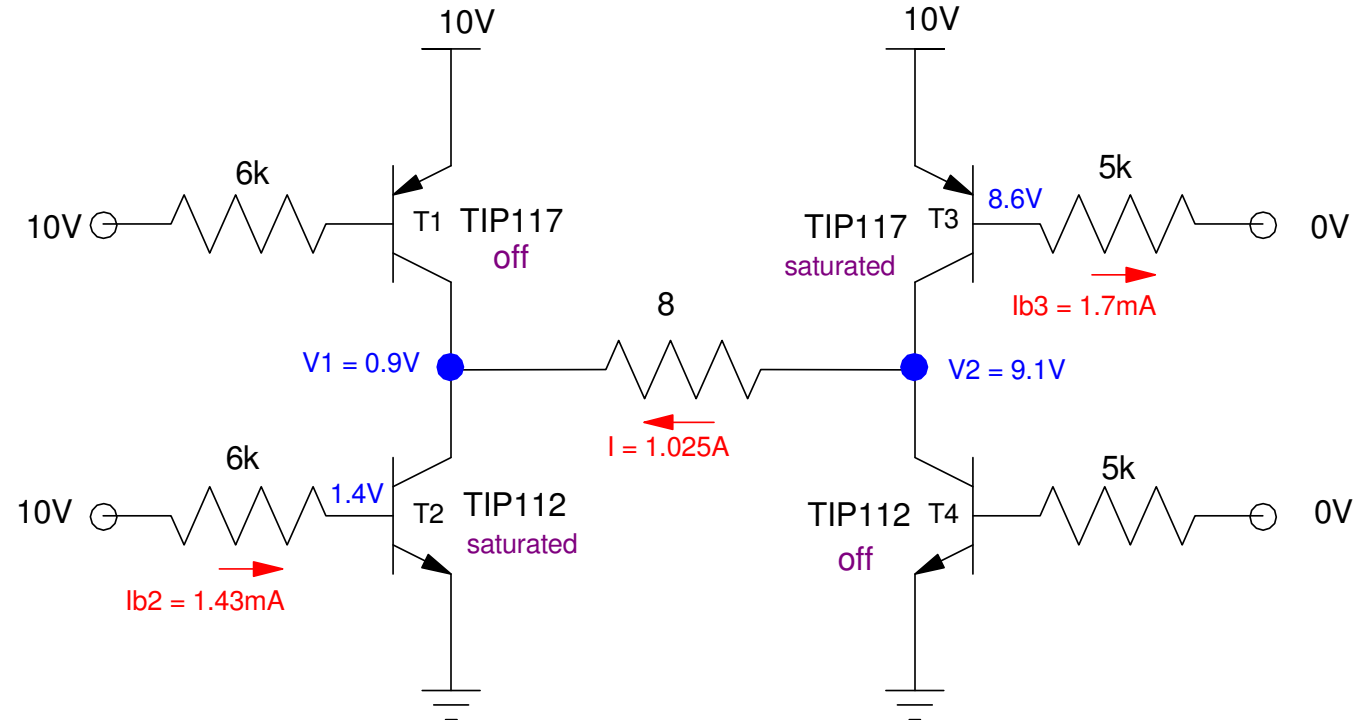- $V1 = 0.9V$
- $V2 = 9.1$
- $V12 = -8.20V$
- $I = -1.025A$




CircuitLab

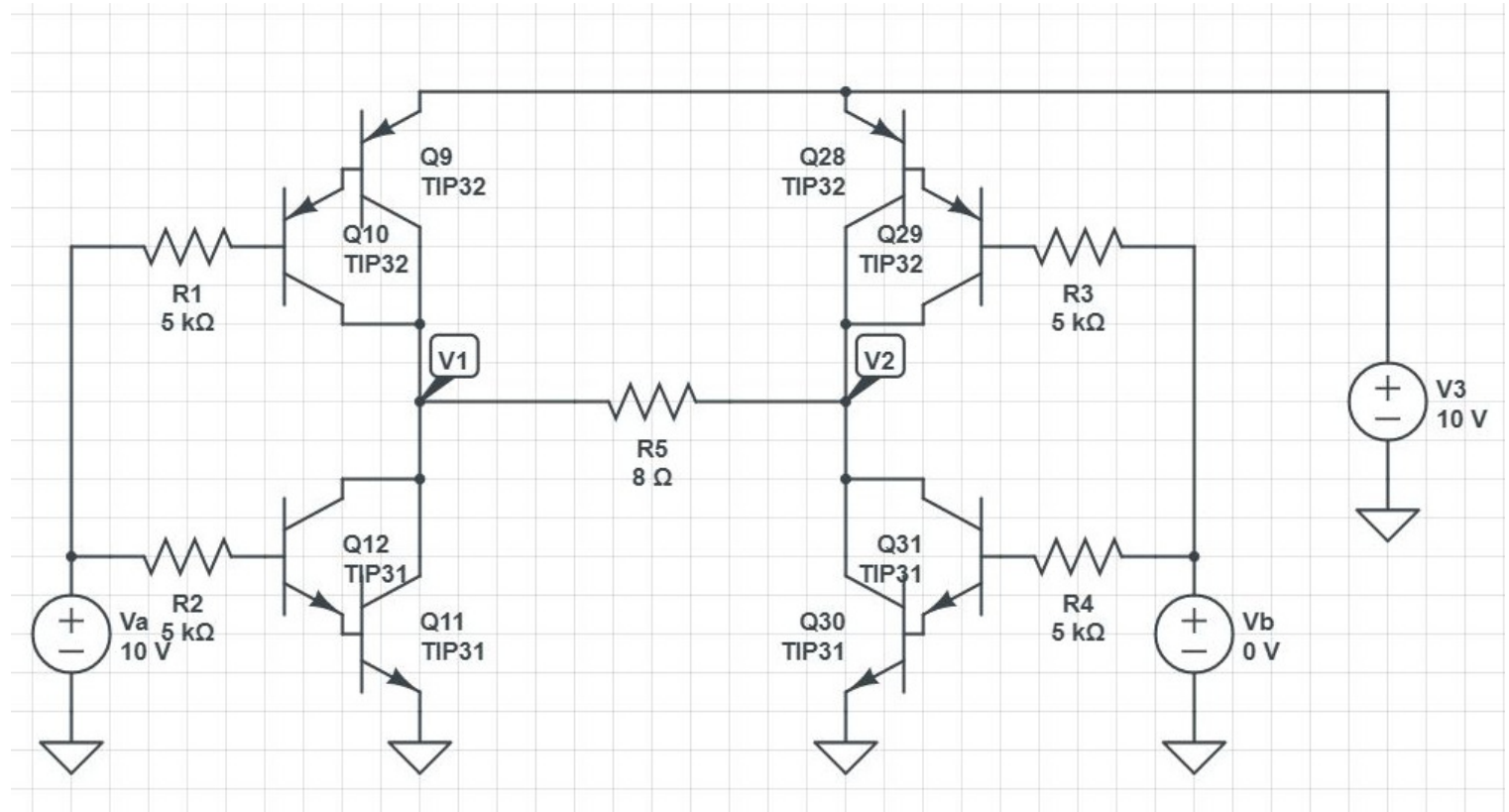- $V1 = 0.860V$
- $V2 = 9.266V$
- **$V12 = -8.406V$**
-8.2V calculated




H-Bridge: Brake

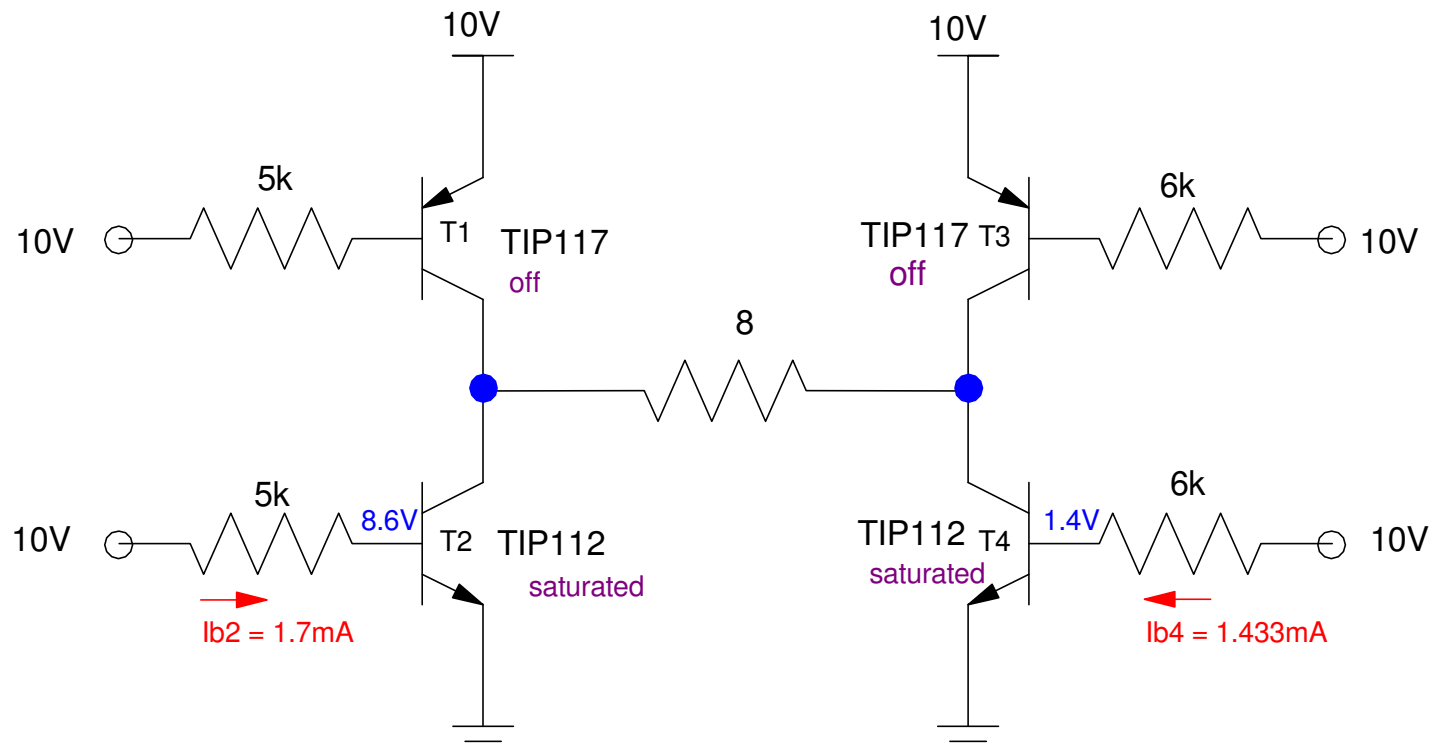- T2 and T4 on
- Motor acts as a generator (kinetic energy converted to heat)



H-Bridge: Coast

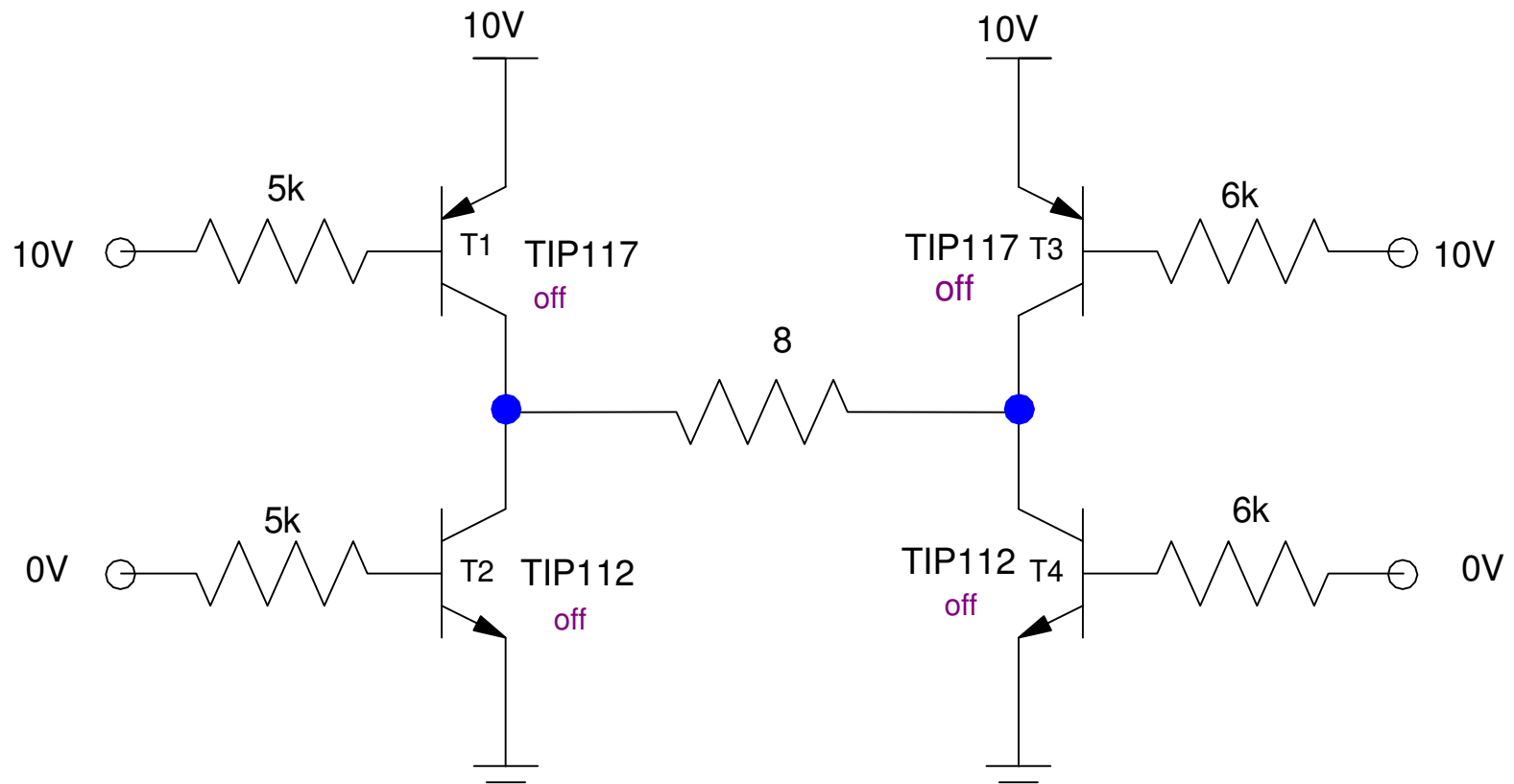- All transistors off
- Motor spins freely



H-Bridge Analysis (take 2)

If you do it wrong, a transistor will be in the active region.

$$I_{b1} = \left(\frac{10 - 1.4}{5k} \right) = 1.720mA$$


$$I_{b4} = \left(\frac{10 - 1.4}{10k} \right) = 860\mu A$$

I is:

$$I = \min \left(\beta I_{b1}, \left(\frac{10 - 1.8}{8} \right), \beta I_{b4} \right)$$

$$I = \min (1.73A, 1.025A, 860mA)$$

T4 is in the active region (bad)

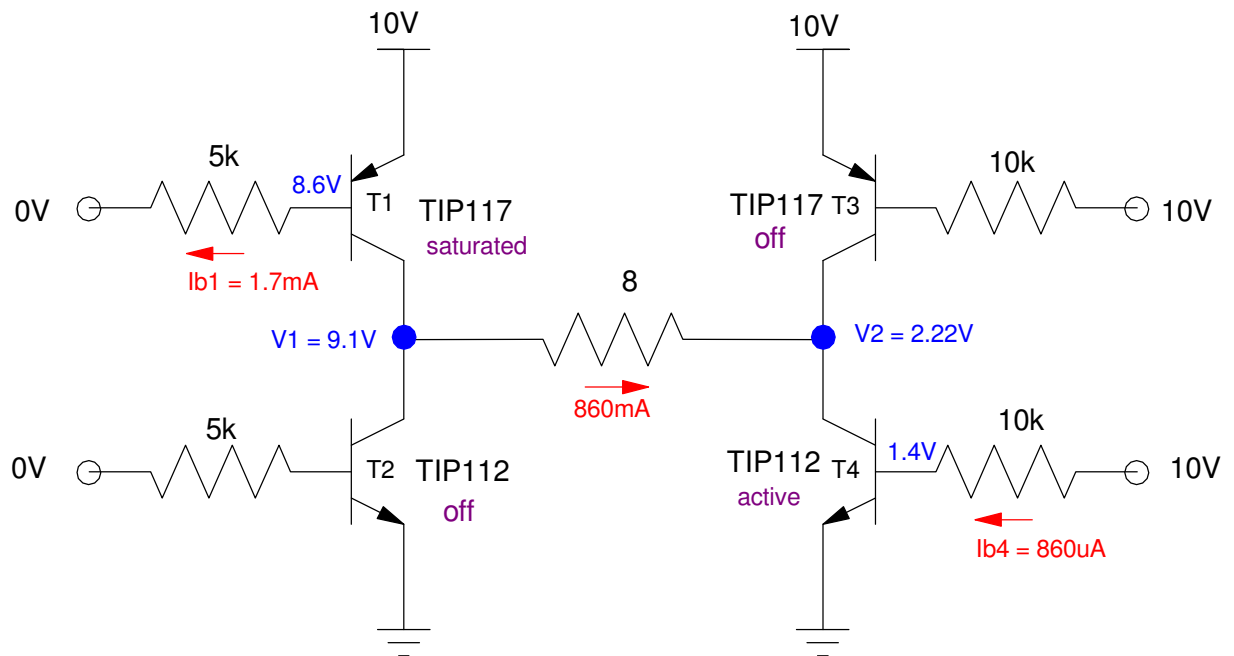

Fix: Make sure transistors are saturated


Since you're trying to push 1.025A through the 8 Ohm load, I_b should be

$$\beta I_b > I_c$$

$$I_b > \frac{I_c}{\beta} = \frac{1.025A}{1000} = 1.025mA$$

Let $I_b = 2mA$. Then
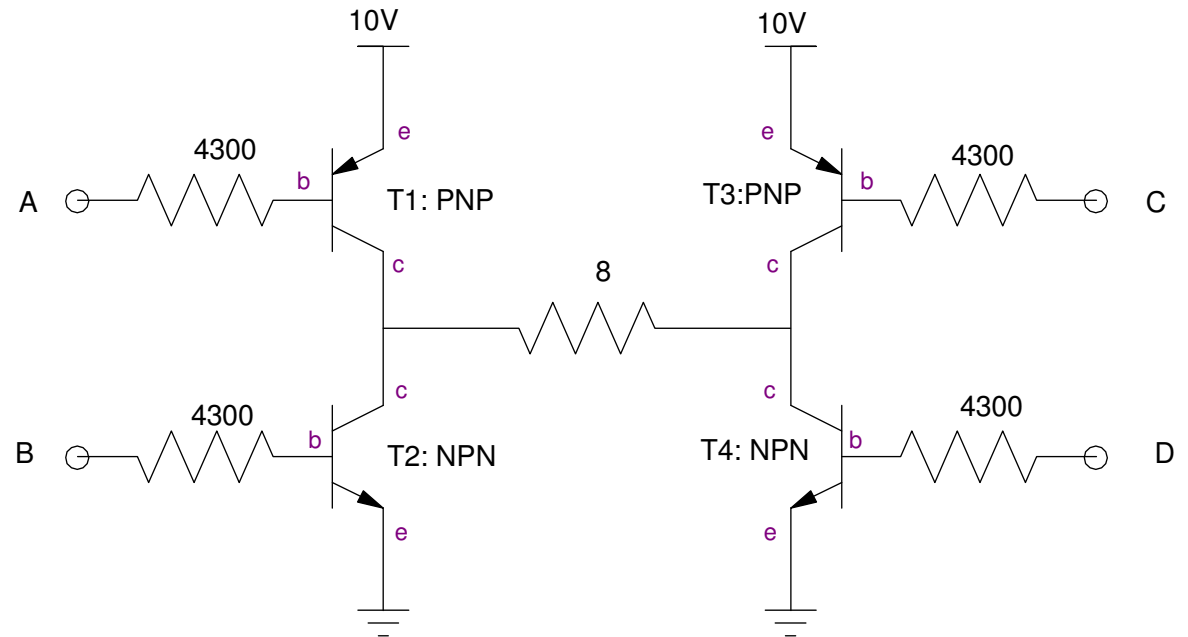
$$R_b = \left(\frac{10V - 1.4V}{2mA} \right) = 4300\Omega$$




Handout

Find the voltages and currents.

Assume

- $|V_{be}| = 0.7V$
- $|V_{ce}| > 0.2V$
- $\beta = 100$

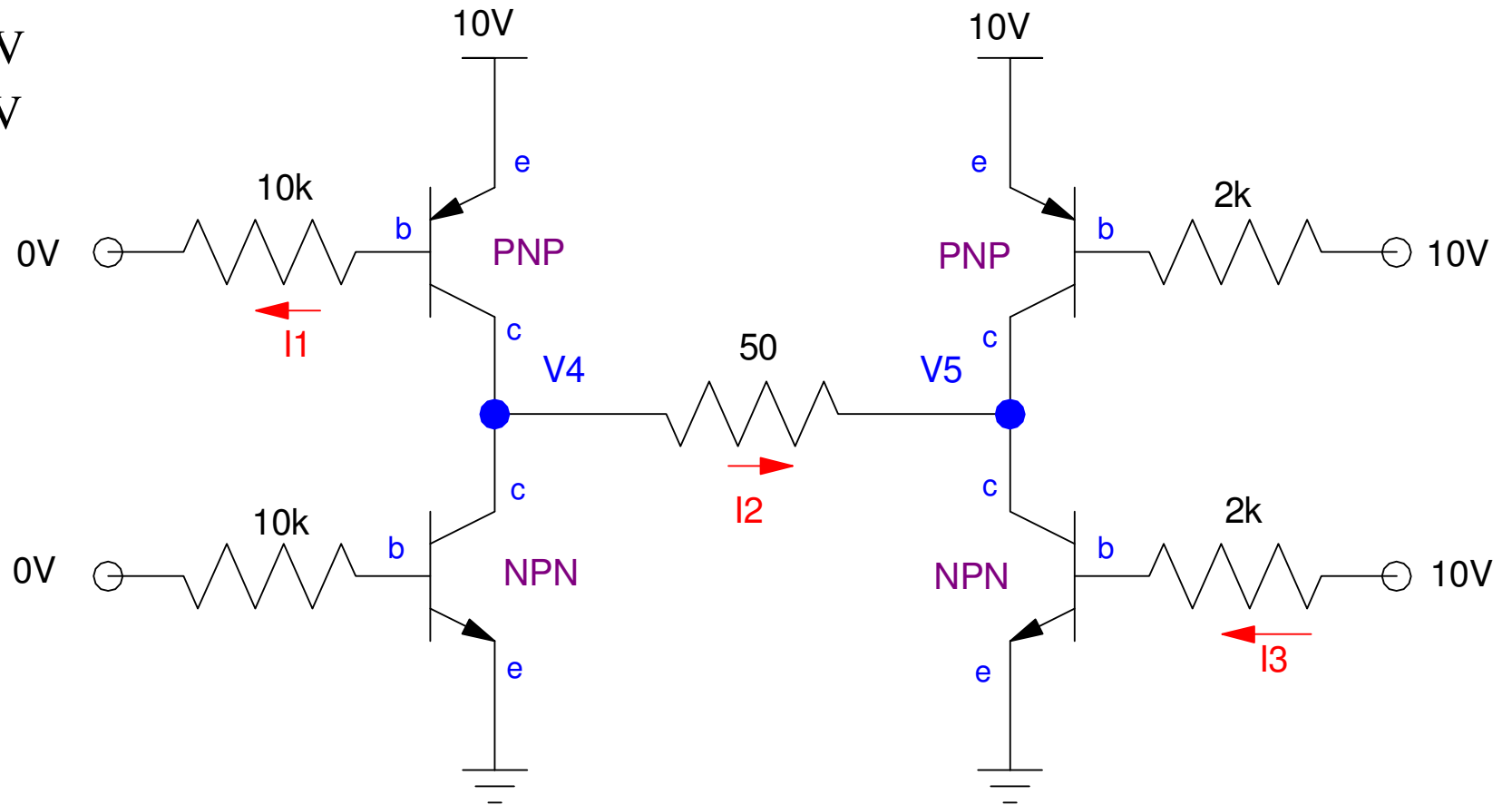

1/2 H-Bridge on a Chip: TLE5205:



H-Bridges are kind of useful.

- Available from Digikey (\$7.16 each)

Functional Truth Table


IN1	IN2	OUT1	OUT2	Comments
L	L	H	L	Motor turns clockwise
L	H	L	H	Motor turns counterclockwise
H	L	L	L	Brake:
H	H	Z	Z	Coast:

TLE 5205-2

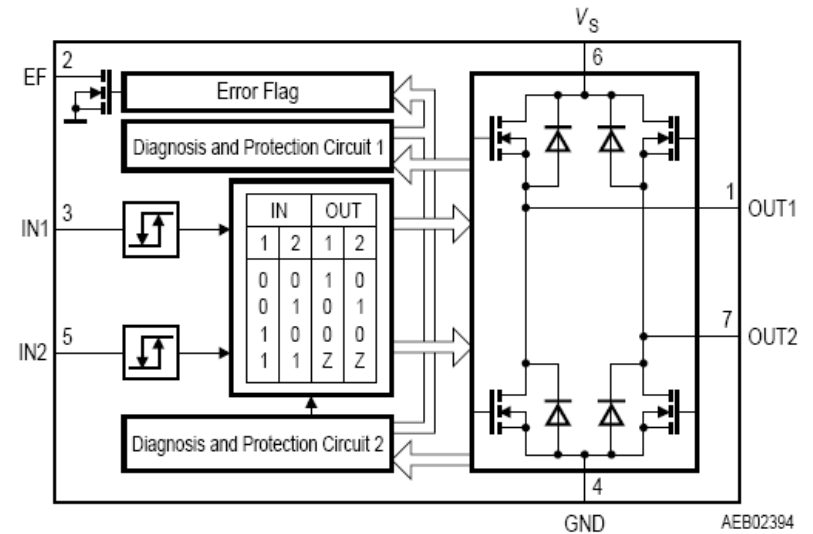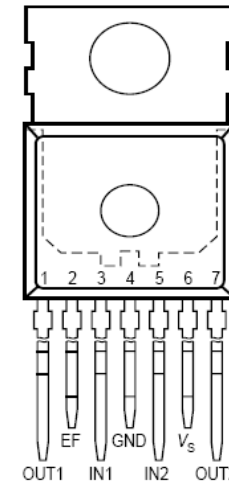

Dual H-Bridges: L298N

A third option is to use a ready-built H-bridge like the one shown below.



Stepper Motor Drive Controller Board Module L298N Dual H Bridge
🔥 Top selling product ★★★★★ 1 product rating

Item condition: **New**

Quantity: More than 10 available
121 sold / See feedback

Price: **US \$1.99**

[Buy It Now](#)

[Add to cart](#)

13 watching

- [Add to watch list](#)
- [Add to collection](#)

121 sold	Experienced seller	30-day returns
-----------------	--------------------	----------------

Shipping: **\$3.00** Standard Shipping | [See details](#)
Item location: Bensenville, Illinois, United States
Ships to: United States | [See exclusions](#)

Delivery: Estimated on or before **Mon. Aug. 28** to 58104 📍


Payments: [PayPal](#) [VISA](#) [MasterCard](#) [AMERICAN EXPRESS](#) [DISCOVER](#)
Credit Cards processed by PayPal

Dual H-Bridge from ebay (search: Arduino H Bridge)

This chip actually contains two H-bridges

- Voltage Range: 5V .. 35V
- Current Range: Up to 2A per channel
- Max Power: 25W:

IN-1	IN-2	Vab	IN-3	IN-4	Vcd
0V	0V	0 V	0V	0V	0 V
0V	5V	+ Vcc	0V	5V	+ Vcc
5V	0V	- Vcc	5V	0V	- Vcc
5V	5V	0 V	5V	5V	0 V

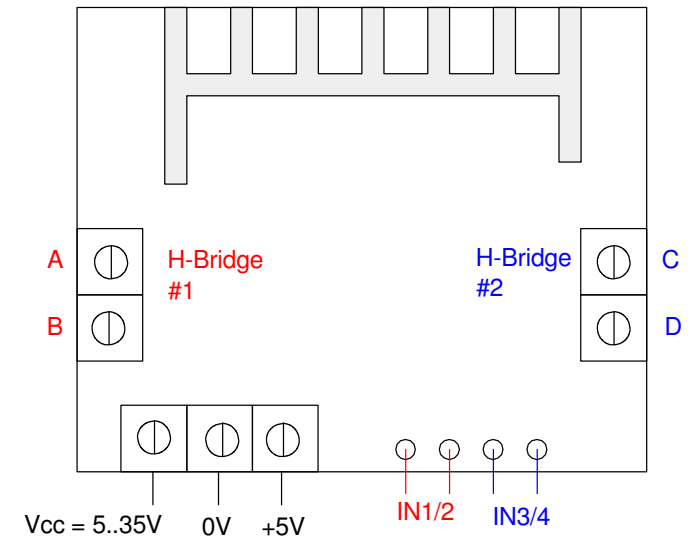

Goal: Demonstrate knowledge of H-bridges

- Build an H-bridge at the transistor level

Goal: Anything else

- Use an L298N board
-

H-Bridge Demo

With a single +5V power supply,

Drive a DC motor

- Forward
- Stop
- Reverse

Drive a speaker

- Forward
 - 0V
 - Reverse
-

Summary

A transistor allows you turn turn a device

- On and
- Off

An H-bridge gives more options

- Forward
- Reverse
- Coast
- Brake

Ideally, all transistors are either

- Off, or
 - Saturated
-

