
555 Timers

ECE 320 Electronics I

Jake Glower - Lecture #25

Please visit [Bison Academy](#) for corresponding lecture notes, homework sets, and solutions

555 Timers

- Common
- Inexpensive
- Easy to use (been used since 1972)


Easy way to generate waveforms

- Square Wave
- PWM
- Triangle Wave

Applications


- Voltage controlled oscillator (siren)
- Temperature controlled oscillator (sensor)
- One-Shot (buzz a door if left open)

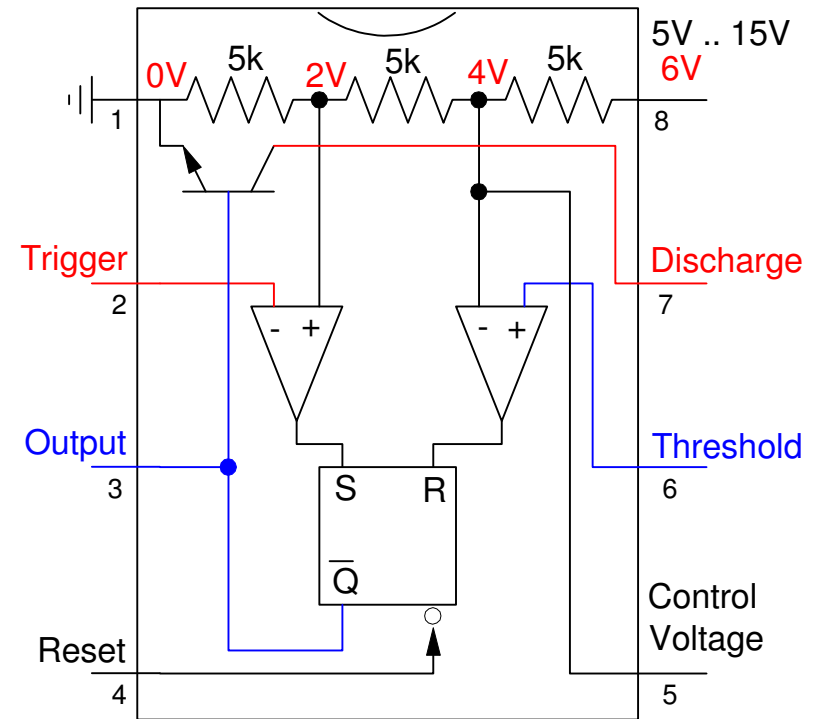No software to write, no program to crash



555 Timer:

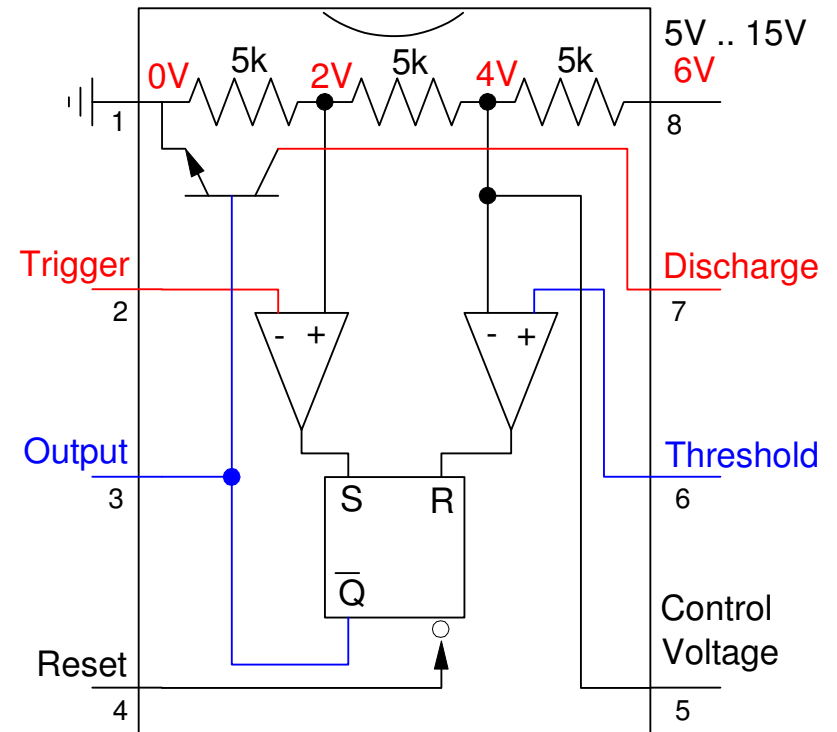- Power and Ground: 5V to 15V.
- Trigger: When Trigger < 2V
 - SR flip-flop sets
 - Output goes high.
- Threshold: When Threshold > 4V
 - SR flip flop clears
 - Output goes low
- Control Voltage:
 - Adjust threshold voltage from 4V
- Discharge: When 0V
 - Ground pin 7





555 Oscillator (take 1):

- Charge C through R1 & R2
- Discharge C through R2

Resulting Waveform

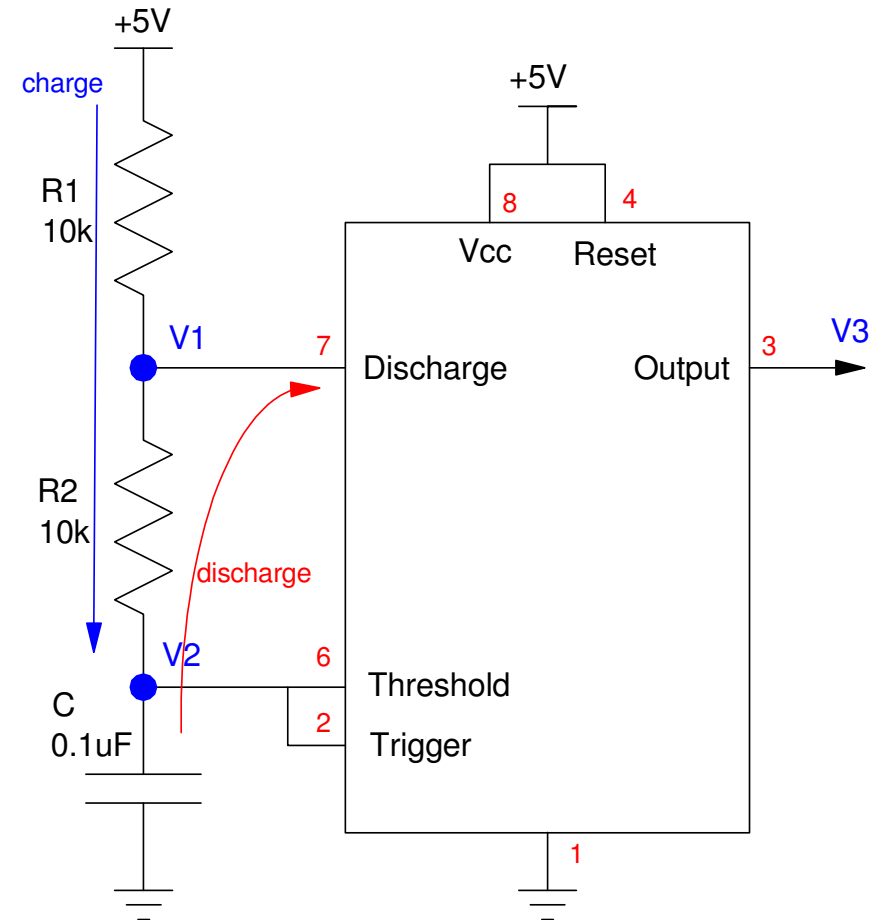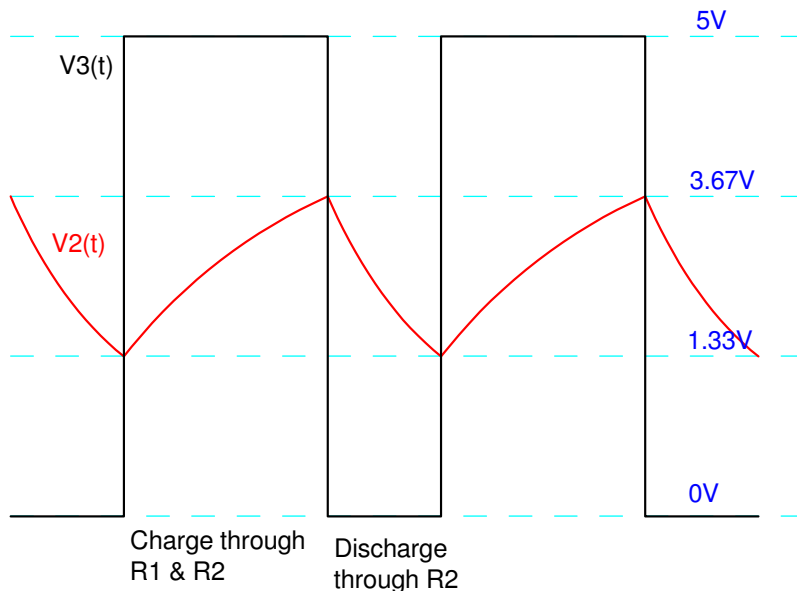- Square Wave at V3
- Triangle Wave at V2



Calculations

On-Time: (charge)

- $t_{on} = (R_1 + R_2) \cdot C \cdot \ln(2)$
- $t_{on} = 1.386ms$

Off-Time: (discharge)


- $t_{off} = R_2 \cdot C \cdot \ln(2)$
- $t_{off} = 0.693ms$

Period & Frequency

- $T = (R_1 + 2R_2) \cdot C \cdot \ln(2)$
- $f = \frac{1}{T} = 480.9Hz$



Duty Cycle

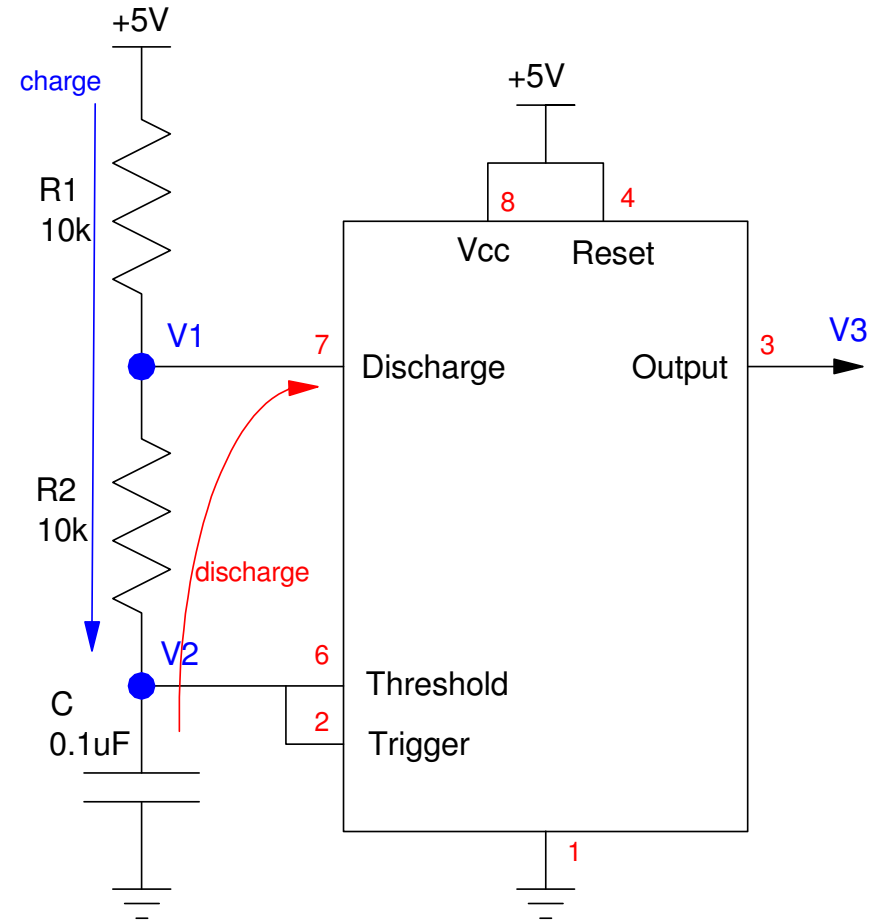- $d = \left(\frac{R_1 + R_2}{R_1 + 2R_2} \right) = 66.7\%$




CircuitLab Simulation

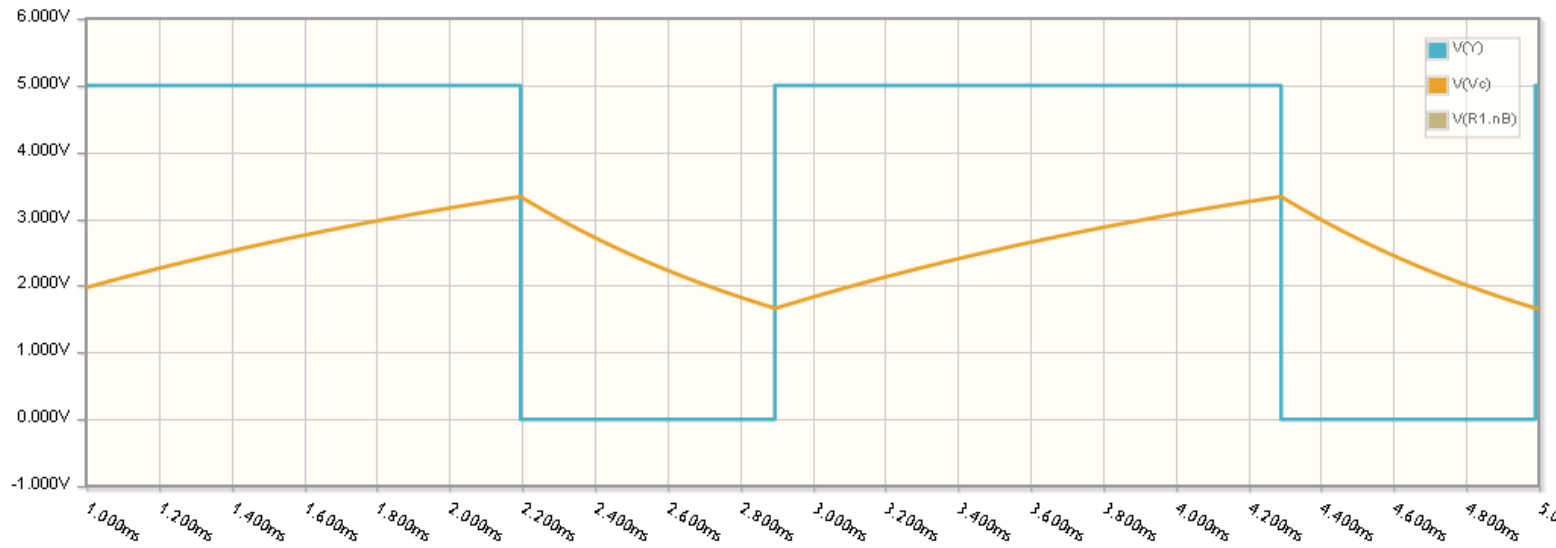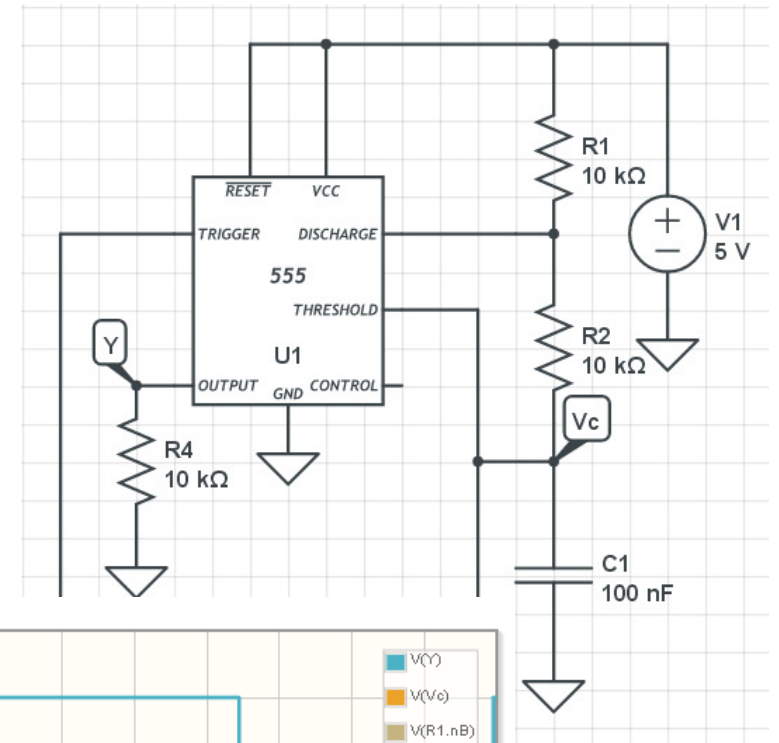- On Time: 1.396ms
 - 1.386ms calculated
- Off Time: 0.702ms
 - 0.693ms calculated
- Frequency: 476.6Hz
 - 480.9Hz calculated
- Duty Cycle: 66.5%
 - 66.7% calculated



Experimental (Hardware)

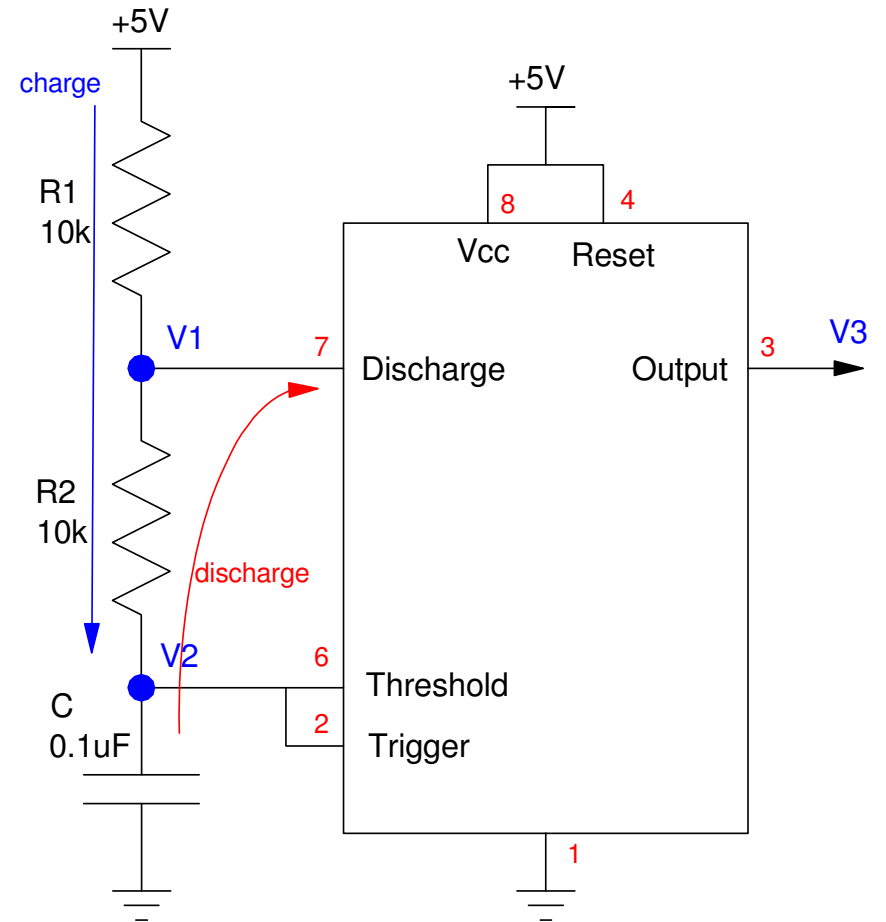- Build the circuit on your breadboard
 - Should match with calculations
 - Should match with simulations




Breadboards (Front & back)

Edges are used for power & ground

- Two separate nodes
- Shorted horizontally along length of board


Middle is used for signals

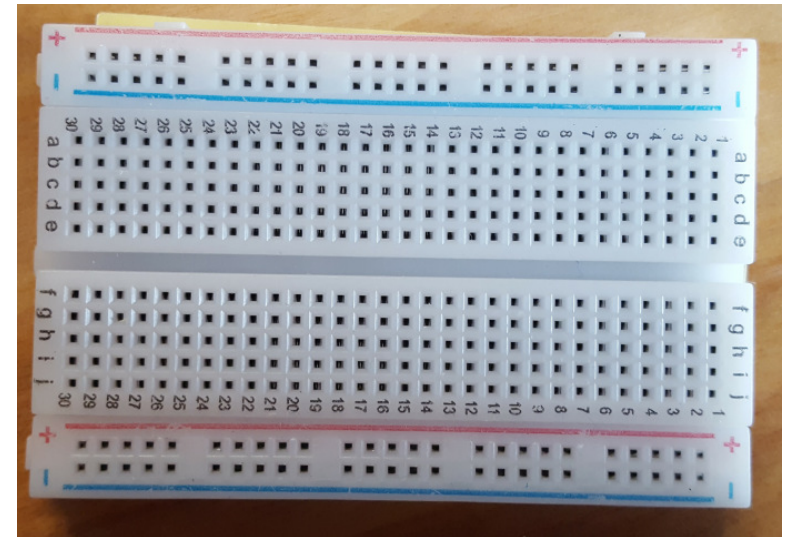- 30 nodes (top)
- 30 nodes (bottom)
- Each is shorted vertically





Electronics Kits: Powered Breadboard

+5V
0V
inner pins
shorted
up / down

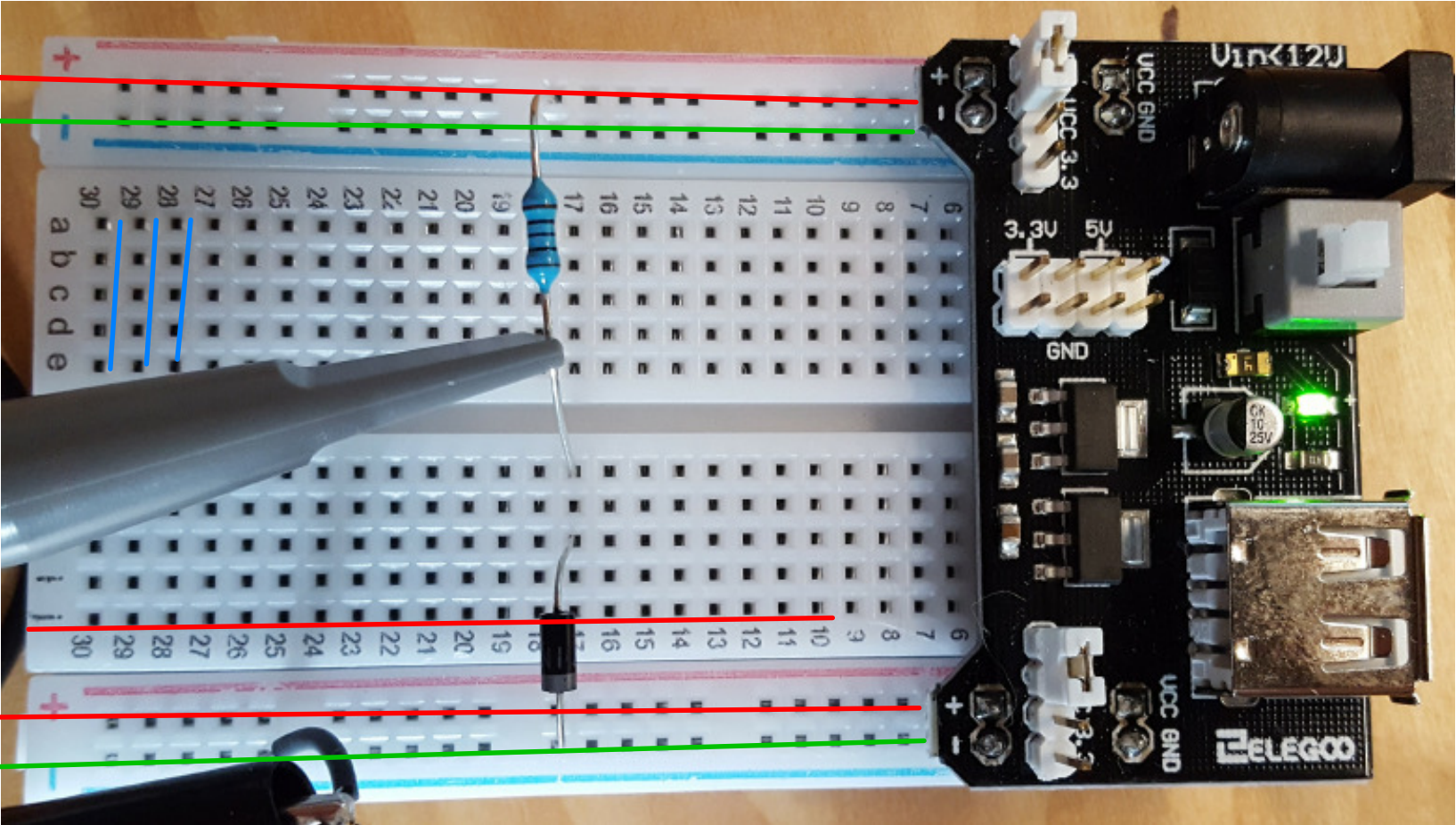

555 Timer on a Breadboard

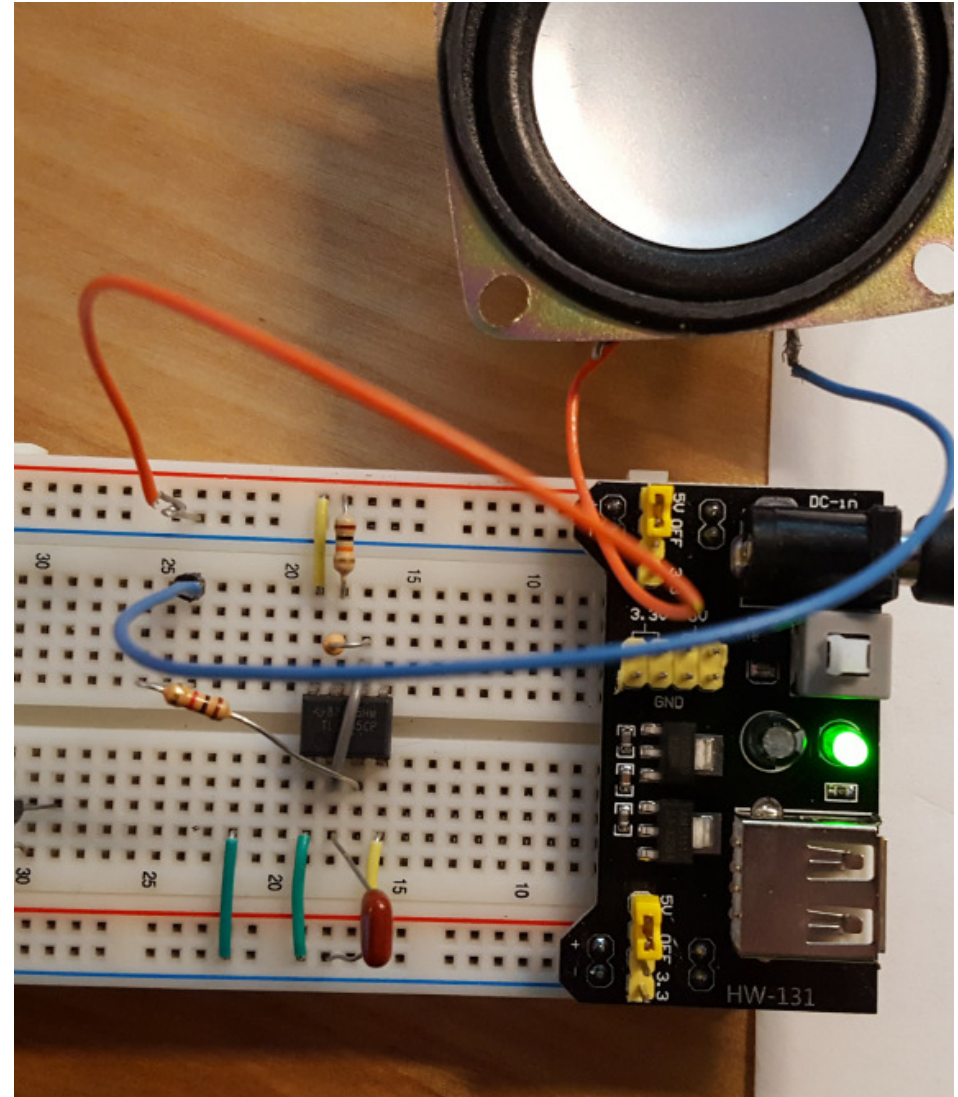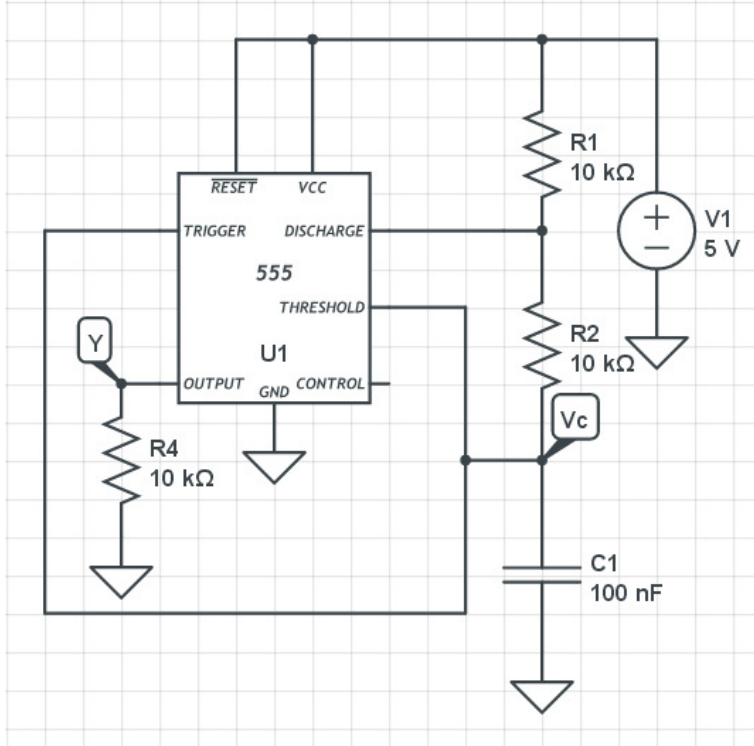- 1 = ground
- 2 = Trigger
- 3 = Output
- 4 = Reset
- 5 = Control
- 6 = Threshold
- 7 = Discharge
- 8 = Power




Experimental Results (With an Oscilloscope)

Vout (blue)

- DC = 3.33V
 - Average = DC
 - Duty cycle (67%)
- Freq = 462Hz
 - 480Hz calculated
 - 476Hz simulated
 - Changes with temperature

Vc (red)

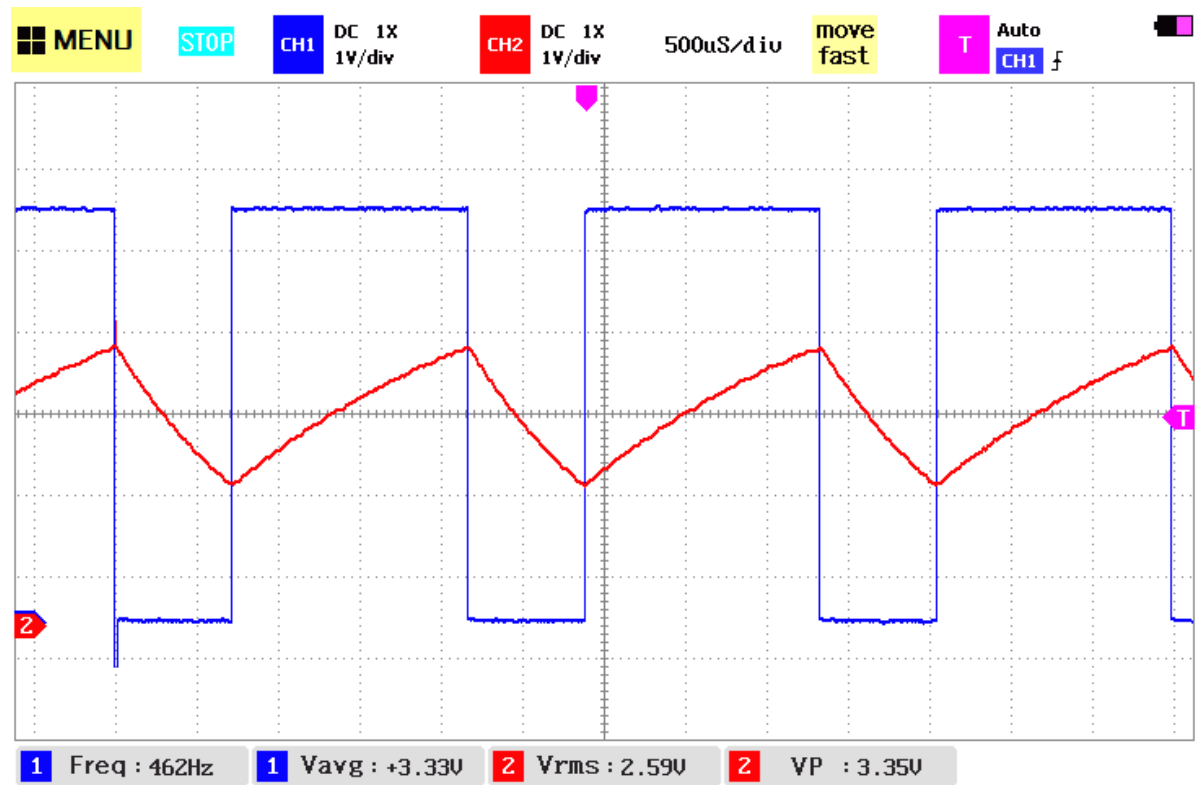- 3.35Vpp
 - 3.33Vpp calculated
 - 3.33Vpp simulated




Experimental Results (Without an Oscilloscope)

Multi-Meter

- $V_{out} = 3.33V$ (DC)
 - Duty Cycle = 66%

Piano Tuner (free cell phone app)

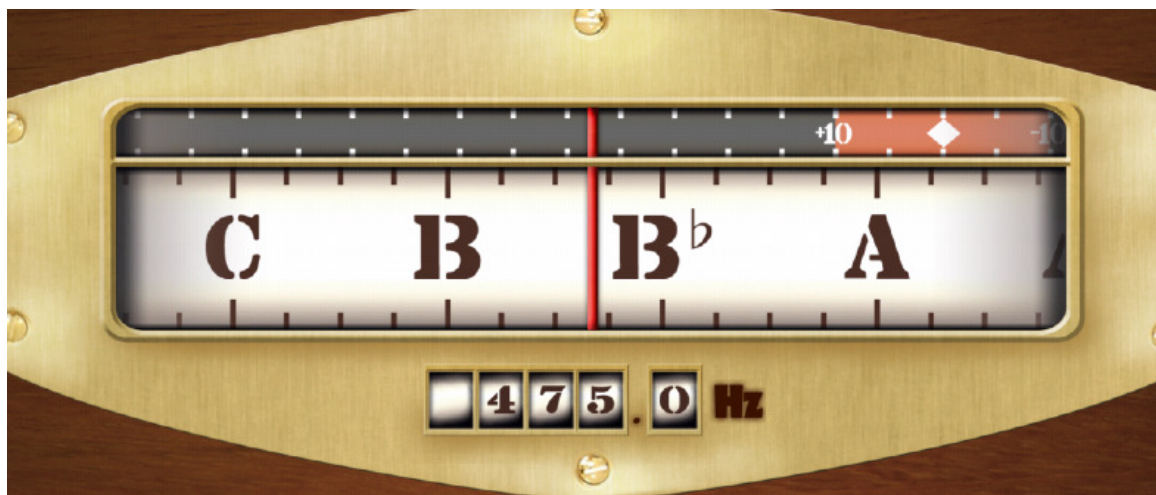- Connect Output to an 8 Ohm speaker through a 200 Ohm resistor
- Limits the current to 20mA
- Measure the frequency with Piano Tuner app





555 Oscillator: Adjustable on/off times

Charge through R1 & D2

- $t_{on} = R_1 C \ln(2.58) = 948\mu s$



Discharge through R2

- $t_{off} = R_2 C \ln(2) = 693\mu s$

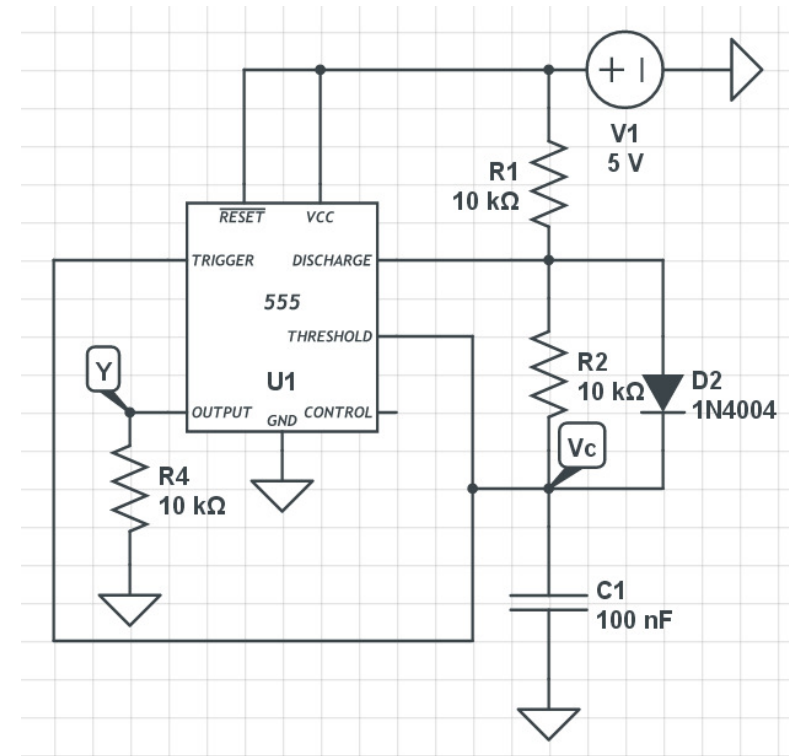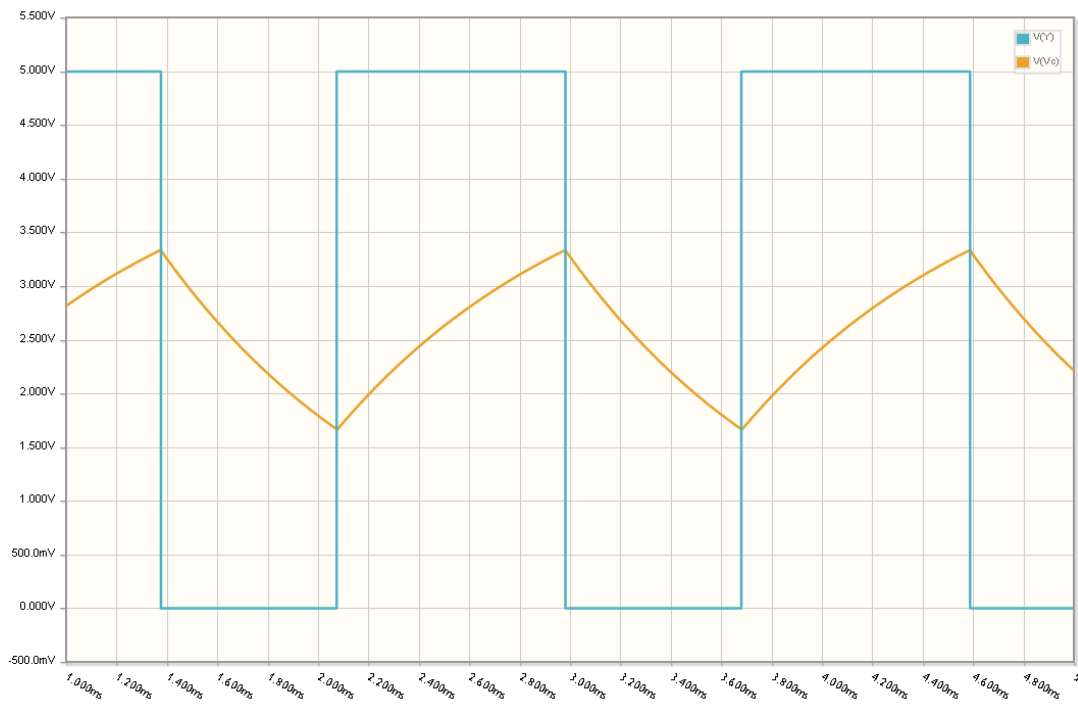



555 Oscillator: Sawtooth Wave

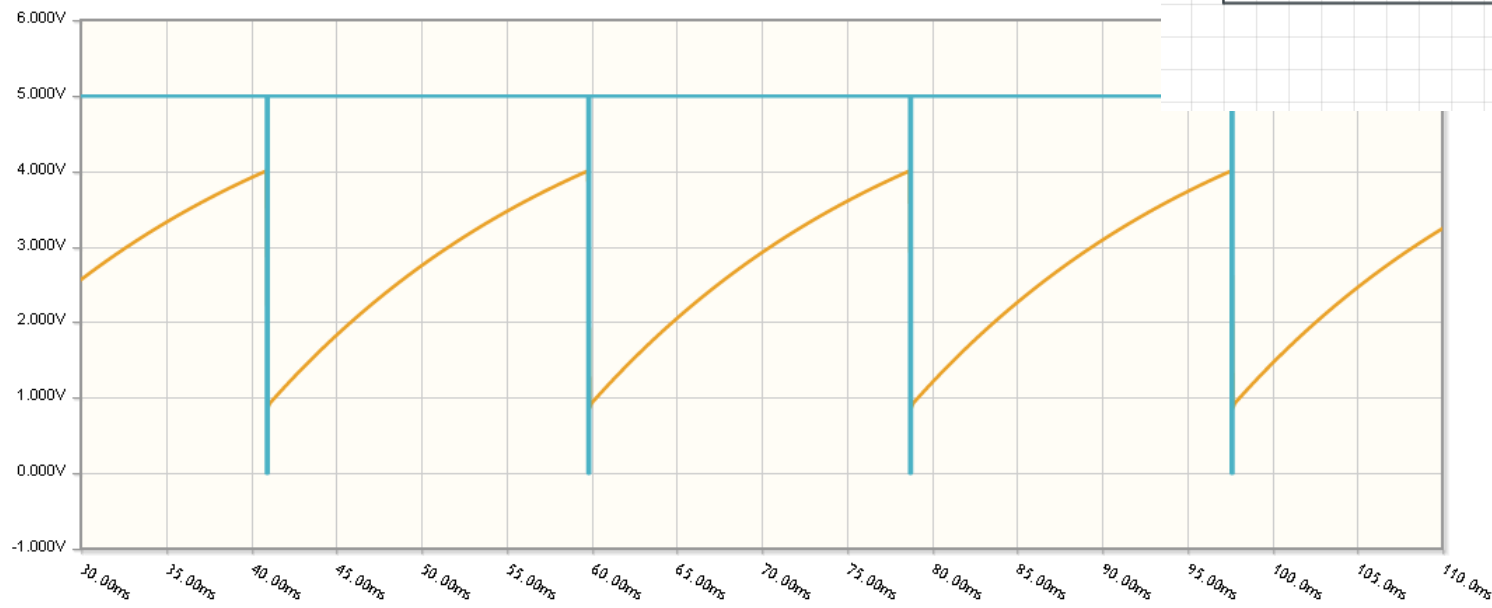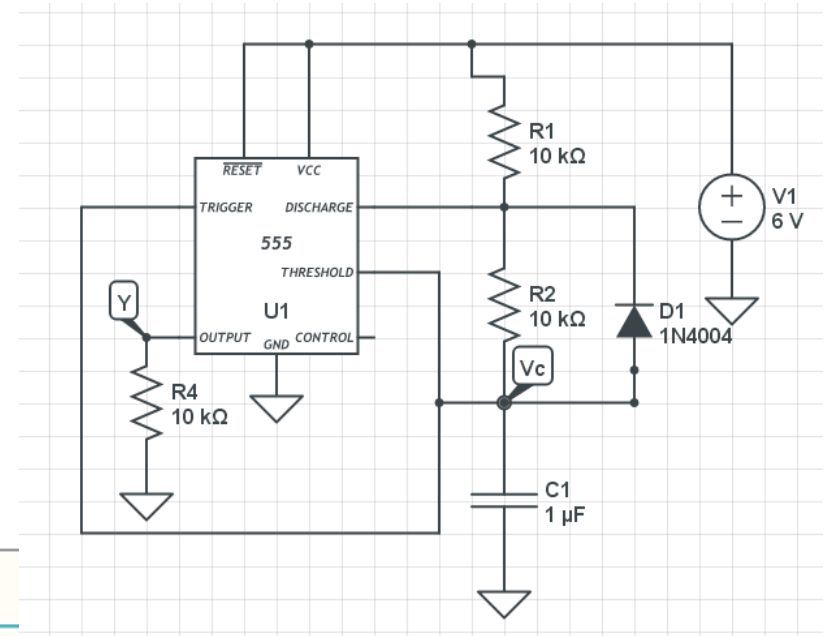- Flip the diode
- $t_{on} = (R_1 + R_2) \cdot C \cdot \ln(2)$
- $t_{off} \approx 0$




555 Timer: Voltage Controlled Oscillator

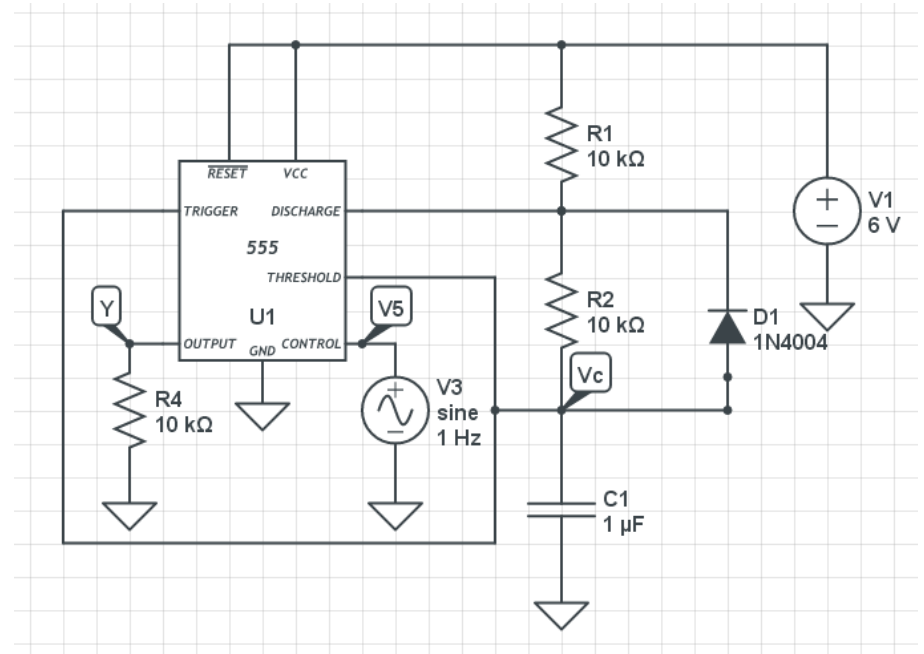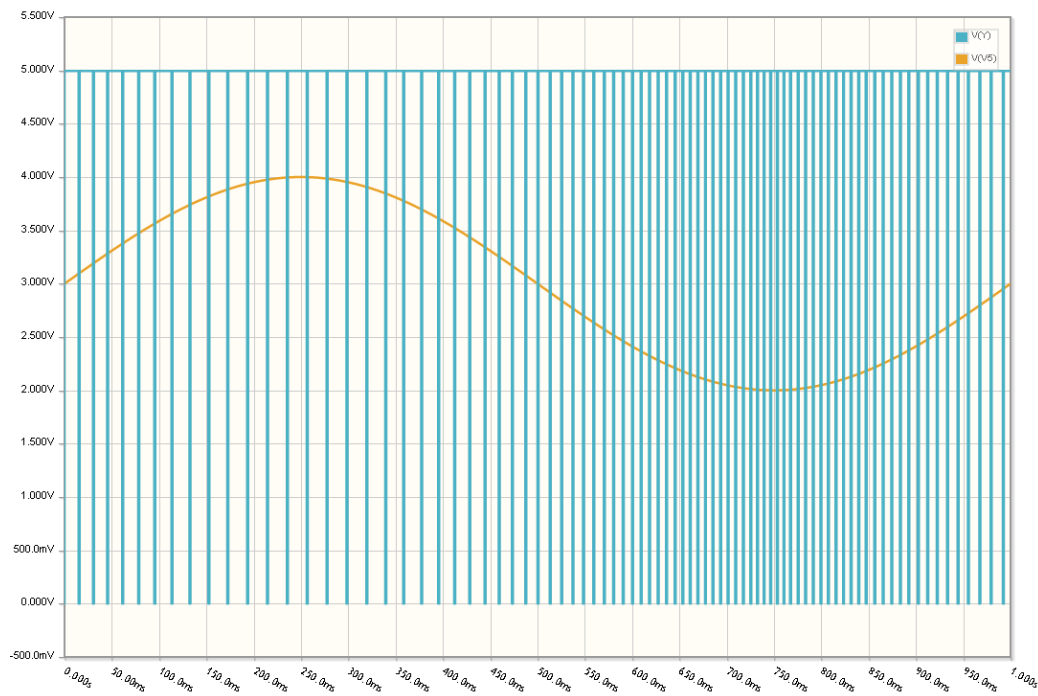
- Voltage goes to pin 5 (Control Voltage)
- Also serves as a sensor
 - Voltage divider to produce V5
 - Frequency = $f(R)$



Siren

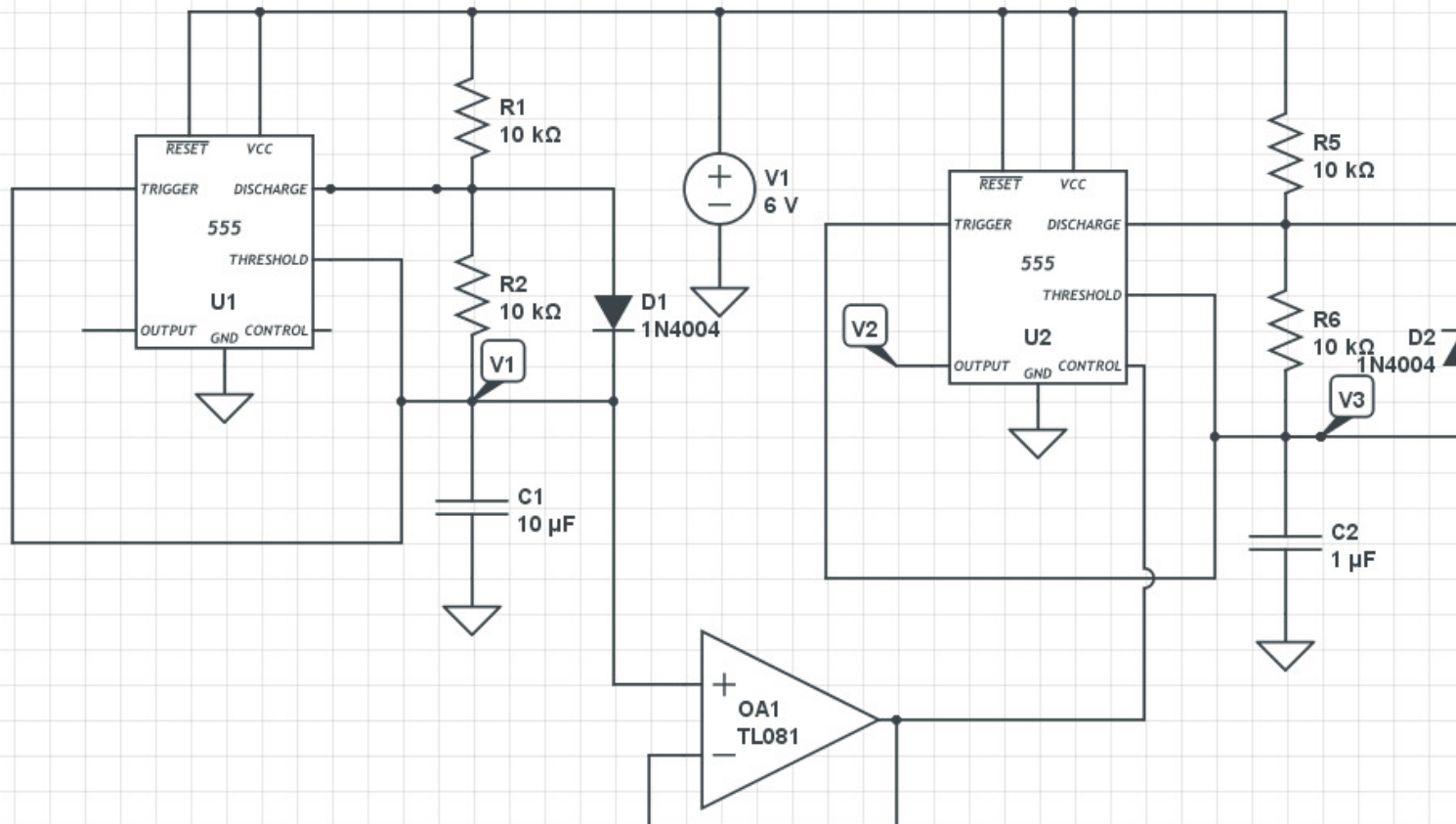- 555 #1 outputs a triangle wave
- 555 #2 is a voltage-controlled oscillator



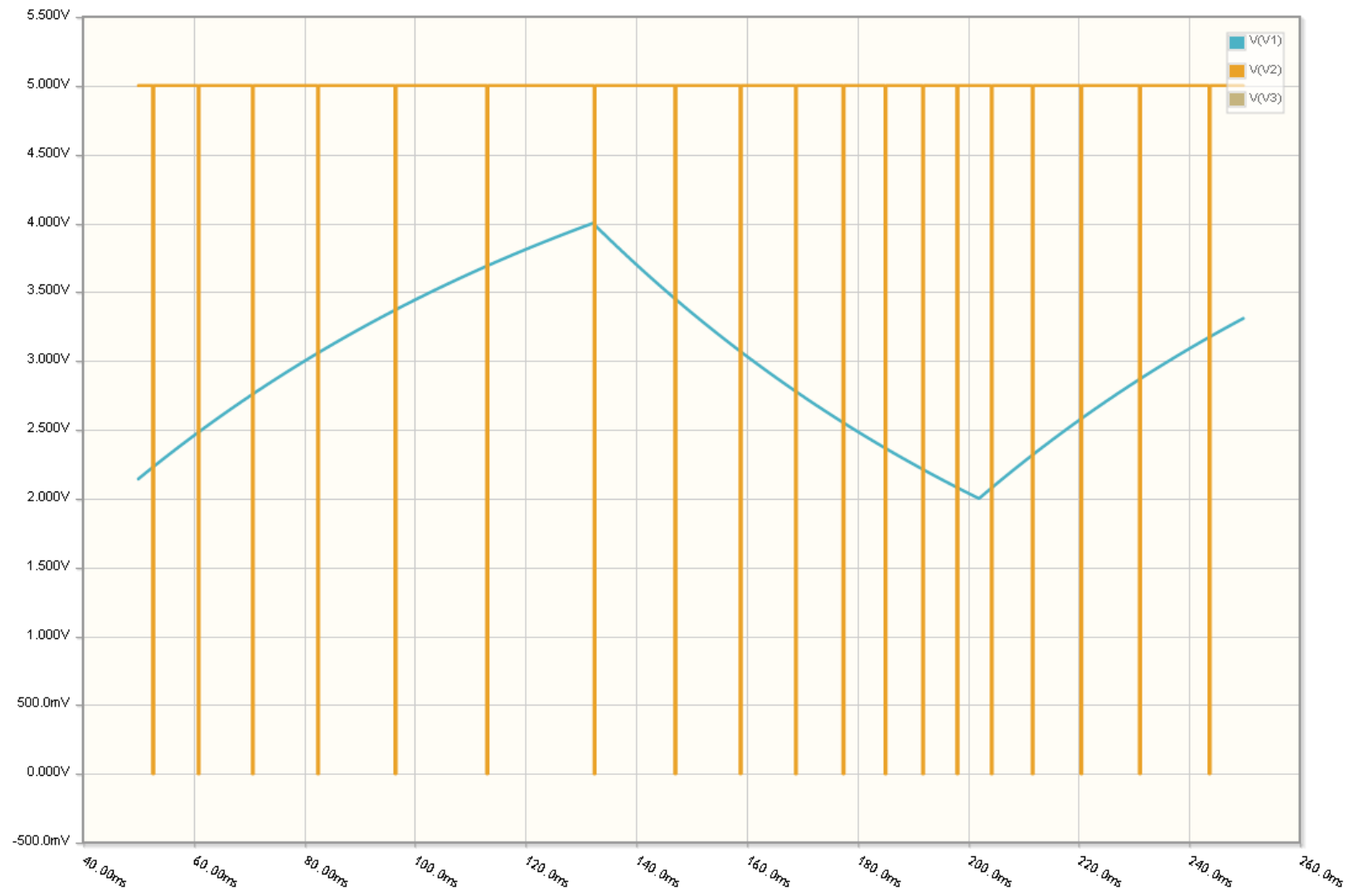

Summary

555 Timers are useful for generating

- Square waves
- Triangle waves
- Sawtooth waves

The frequency depends upon resistors and capacitors

- Allows you to convert resistance to frequency
- Allows you to convert capacitance to frequency

This in turn allows you to build

- Temperature-controlled oscillators
- Light-controlled oscillators
- Voltage controlled oscillators

