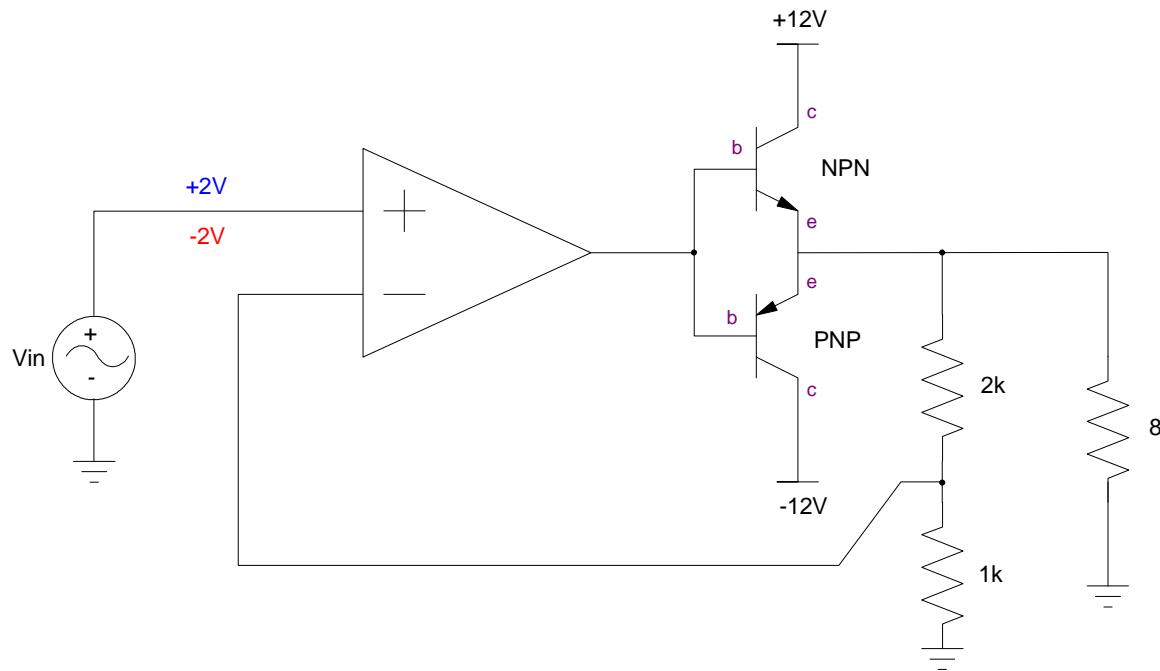


ECE 321: Handout #3


Push-Pull Amplifiers

Assume TIP transistors: $|V_{be}| = 1.4V$, $\beta = 1000$


Voltage Amplifier: Find the voltages and currents for $V_{in} = \{ +2V, -2V \}$



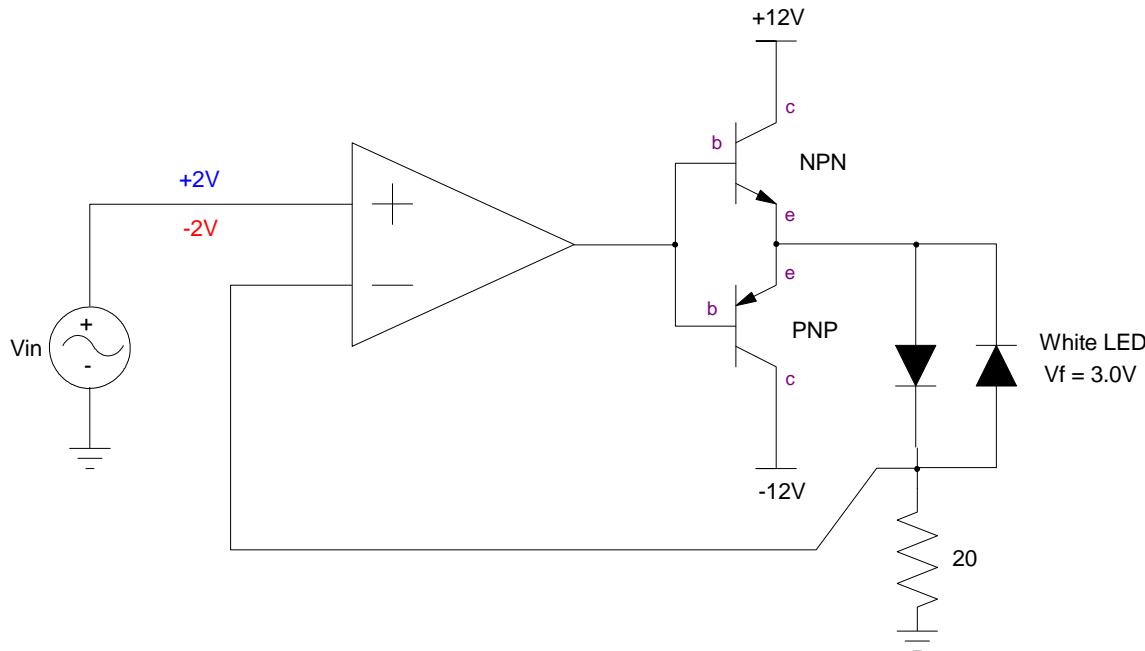
Current Amplifier: Find the voltages and currents for $V_{in} = \{ +2V, -2V \}$




Voltage Amplifier: Vin = +2V (push)

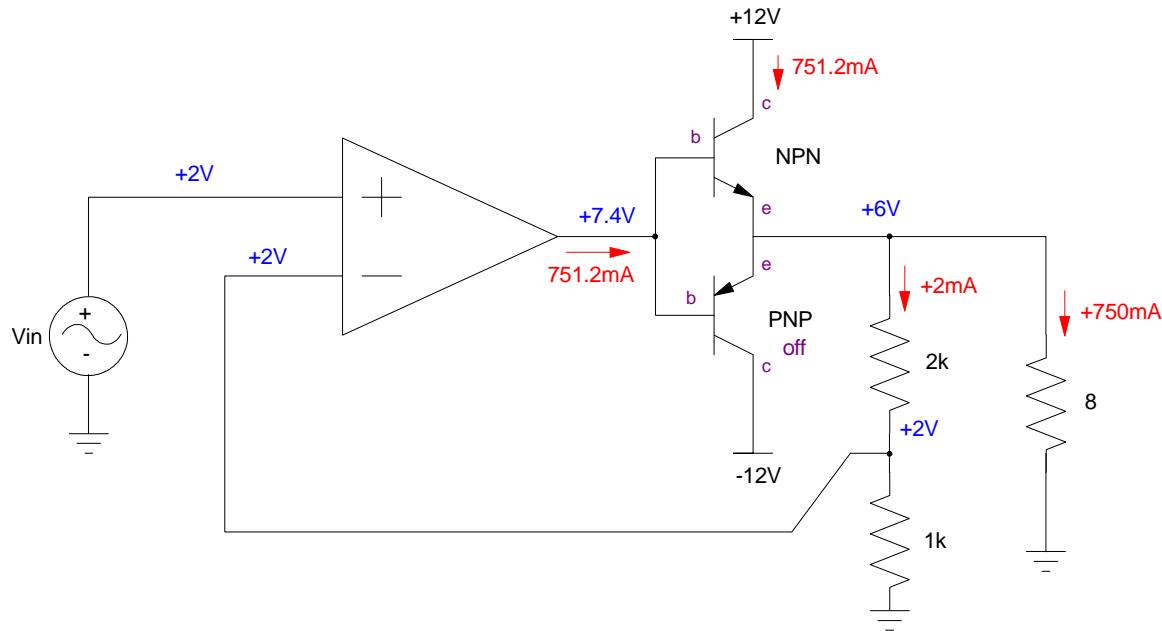

Voltage Amplifier: Vin = -2V (pull)

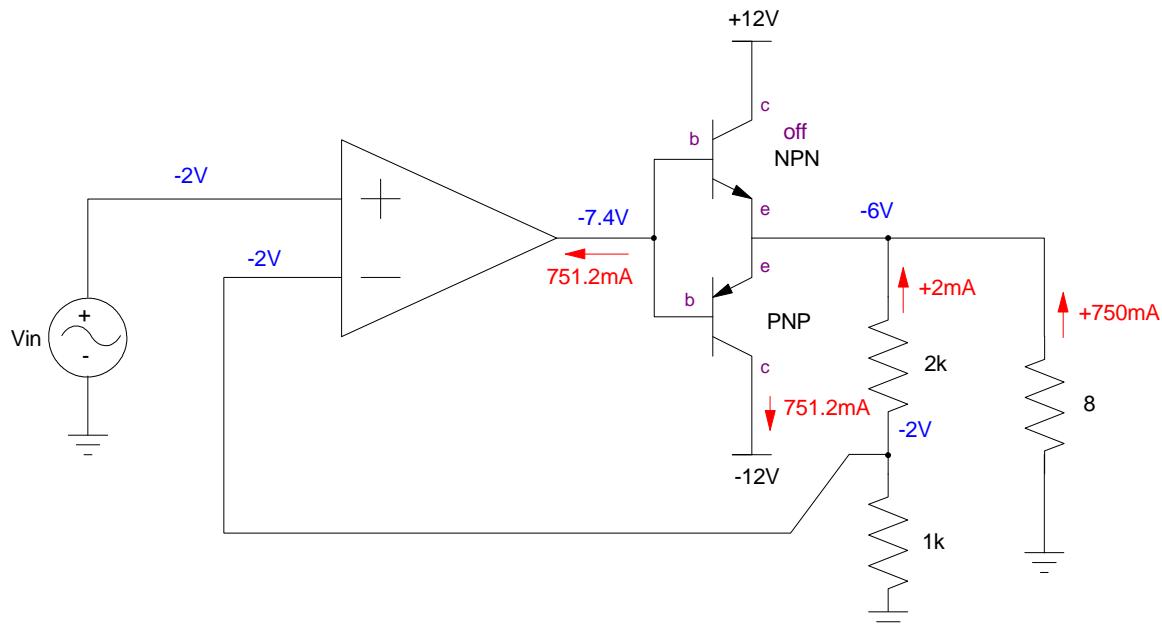

Current Amplifier: Vin = +2V

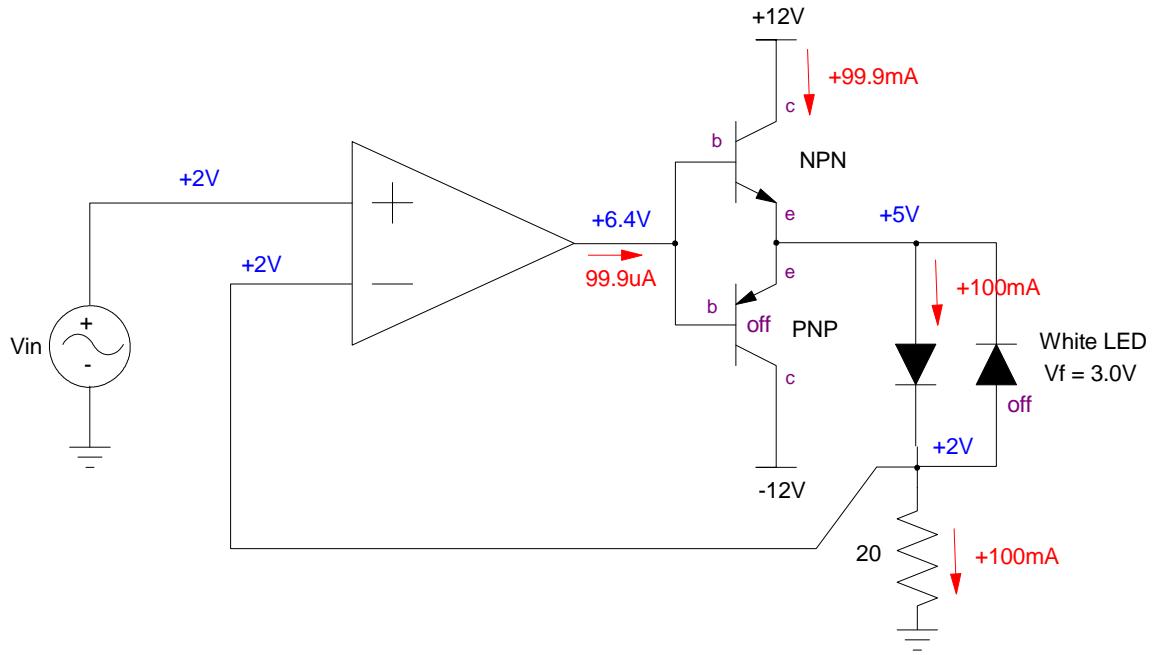

Current Amplifier: Vin = -2V

