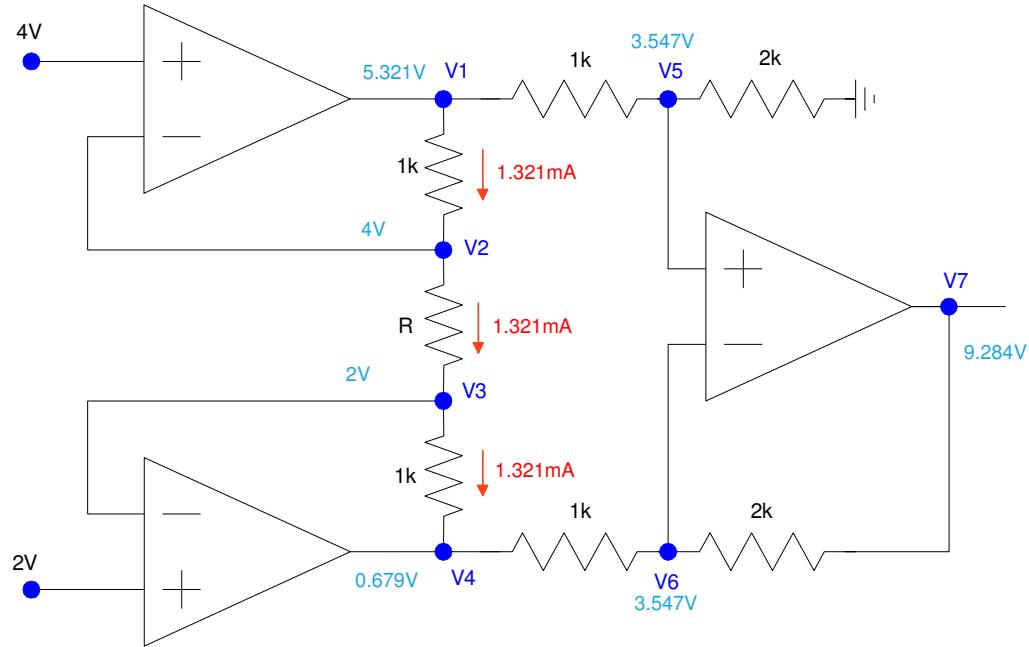


4) Determine the voltages V1..V7 for the following circuit.

- Assume ideal op-amps.
- Assume $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$. For example, May 14th gives $R = 1514$.

V1	V2	V3	V4	V5	V6	V7
5.321V	4V	2V	0.679V	3.547V	3.547V	9.294V



With negative feedback, $V_p = V_m$

- $V_2 = 4V$
- $V_3 = 2V$
- $V_5 = V_6$

The current from V_2 to V_3 is

$$I = \frac{4V - 2V}{1514} = 1.321mA$$

$$V_1 = V_2 + 1k \cdot I = 5.321V$$

$$V_4 = 2 - 1k \cdot I = 0.679V$$

$$V_5 = \frac{2}{3} V_1 = 3.547V$$

To find V_7 , two approaches

$$\frac{V_6 - V_4}{1k} + \frac{V_6 - V_7}{2k} = 0$$

or note that the last stage is an instrumentation amplifier with a gain of 2

$$V_7 = 2(V_1 - V_4)$$


5) Design a circuit to implement

$$Y = 2X - 4$$

Many solutions. If you use an instrumentation amplifier, rewrite as

$$Y = 2(X - 2)$$

$$Y = \frac{R_1}{R_2} (A - B)$$


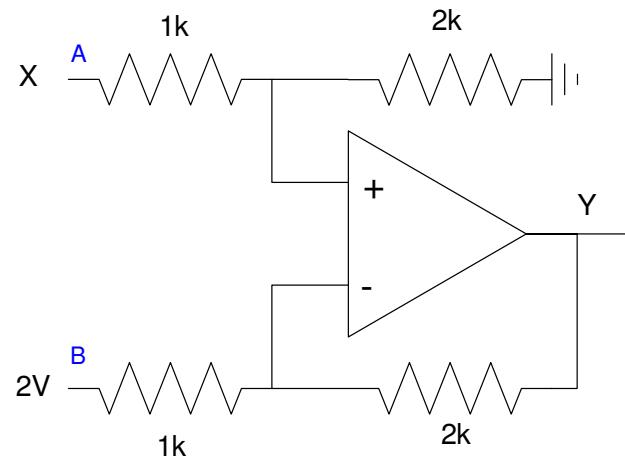


6) Design a circuit to implement

$$Y = 2A - 3B$$

There are many solutions. Using an instrumentation amplifier

$$Y = 3 \frac{2}{3}A - B$$

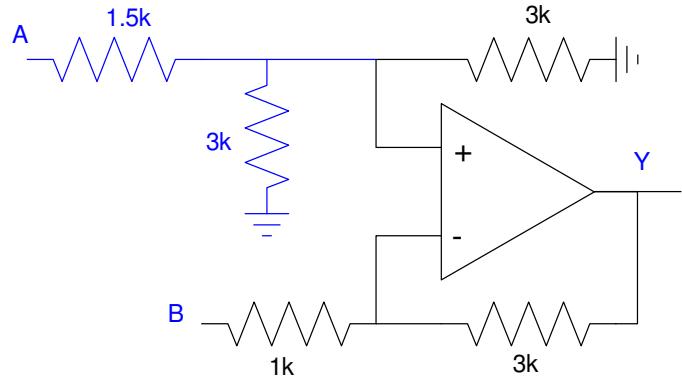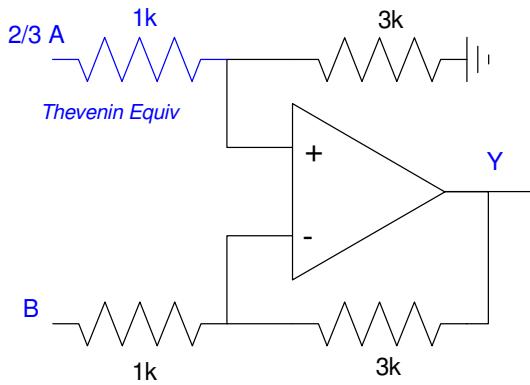

Using inverting amplifiers

