

ECE 321 - Homework #1

Op Amp Amplifiers & Mixers. Due Wednesday, April 7th

Please make the subject "ECE 321 HW#1" if submitting homework electronically to Jacob_Glower@yahoo.com (or on blackboard)

For all problems, assume you are using

- MCP602 Op Amps (2.7V - 6.0V, max current = 22mA)
- 2SC6144 transistors
- $\beta = 200$, 10A max, $|V_{be}| = 0.7V$

555 Timer


Problem 1) Design a circuit using a 555 timer so that it outputs a 500hz triangle wave

The period is


$$T = (R_1 + 2R_2) \cdot C \cdot \ln(2) = 2ms$$

Let

- $T = 2ms$
- $R_1 = 1k$
- $R_2 = 3.3k$
- $C = 0.379\mu F$

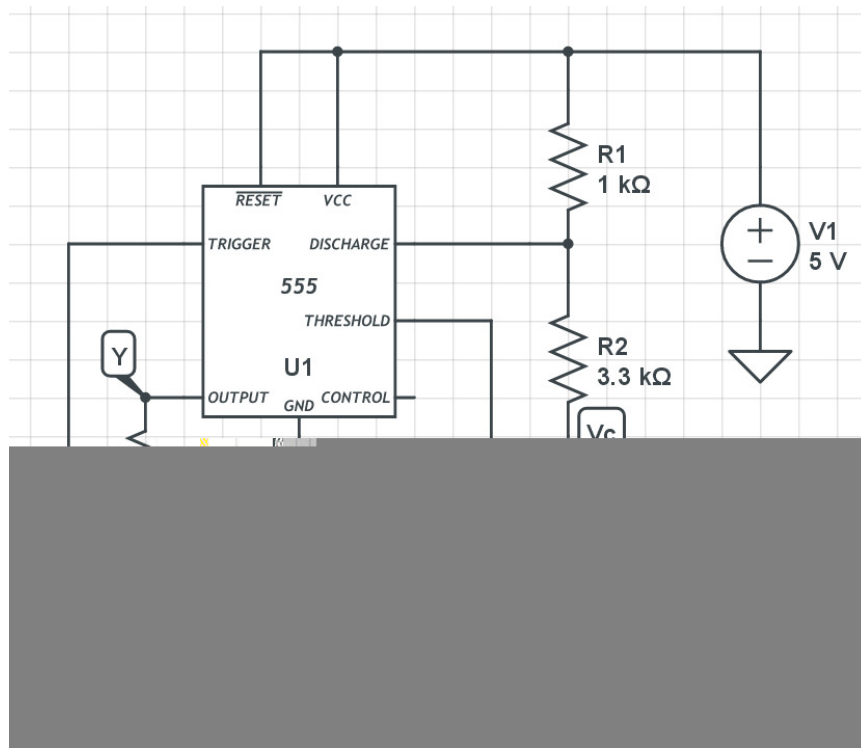

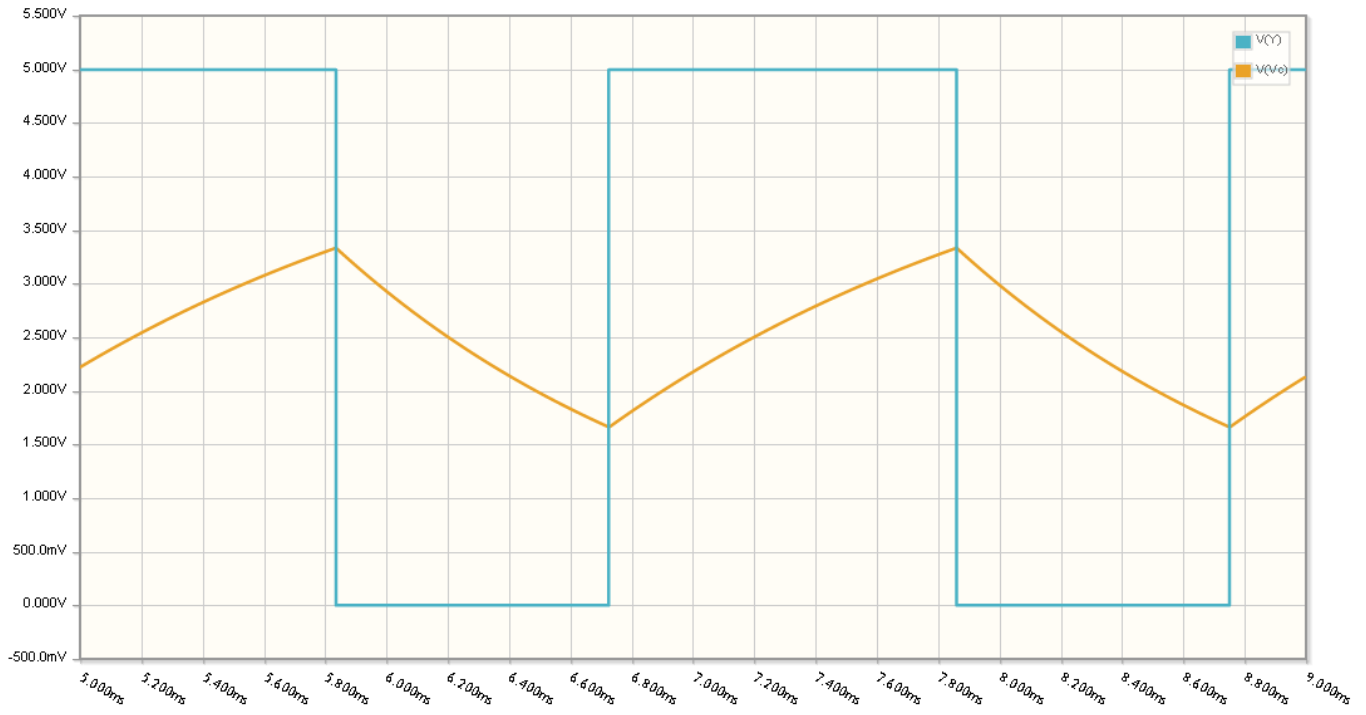Problem 2) Verify your design in CircuitLab



Period = 2.045ms (489Hz)

Problem 3) Build this circuit in hardware and verify its operation

- Using two $0.18\mu\text{F}$ capacitors in parallel (what I could scrounge up - $0.36\mu\text{F}$ total)




Voltage Amplifier & Mixer:

Problem 4) Design a circuit to mix two audio signals


- A = the output of your 555 timer: (1.66Vpp triangle wave, 500Hz)
- B = the output of your cell phone (1Vpp, 20-20kHz sine wave)


$$Y = 2A + 5B$$

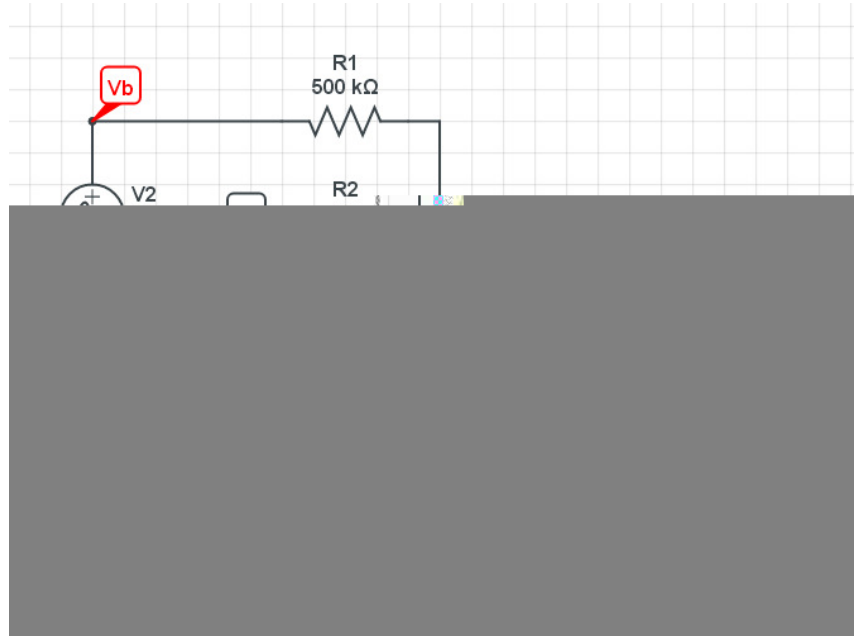

Problem 5) Verify the operation of your mixer in CircuitLab

Use superposition

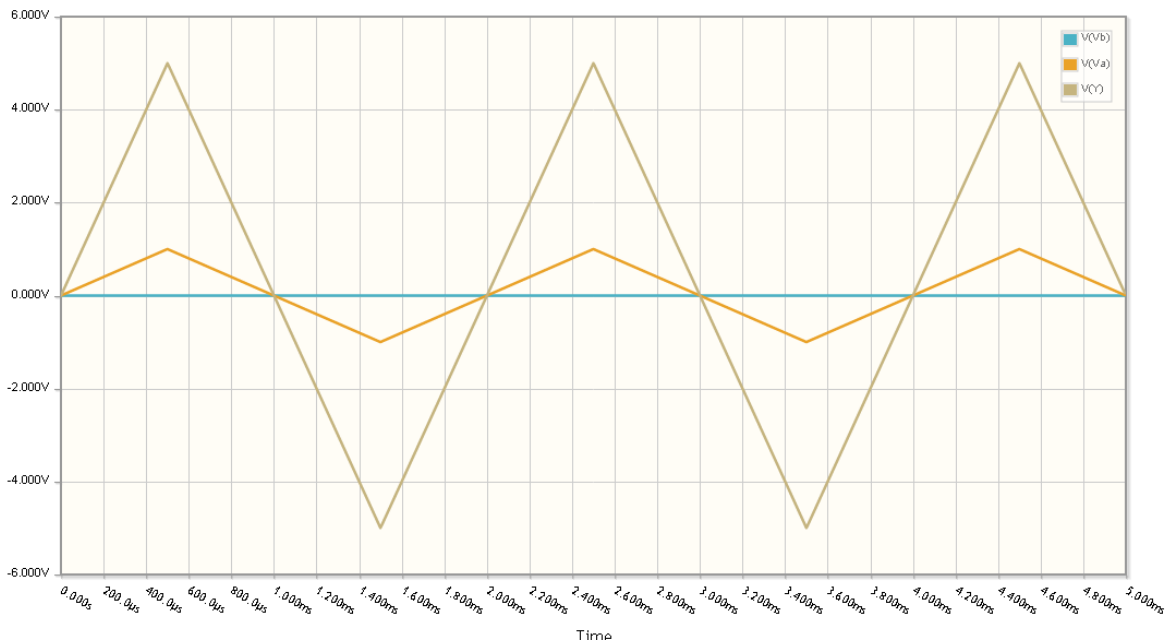

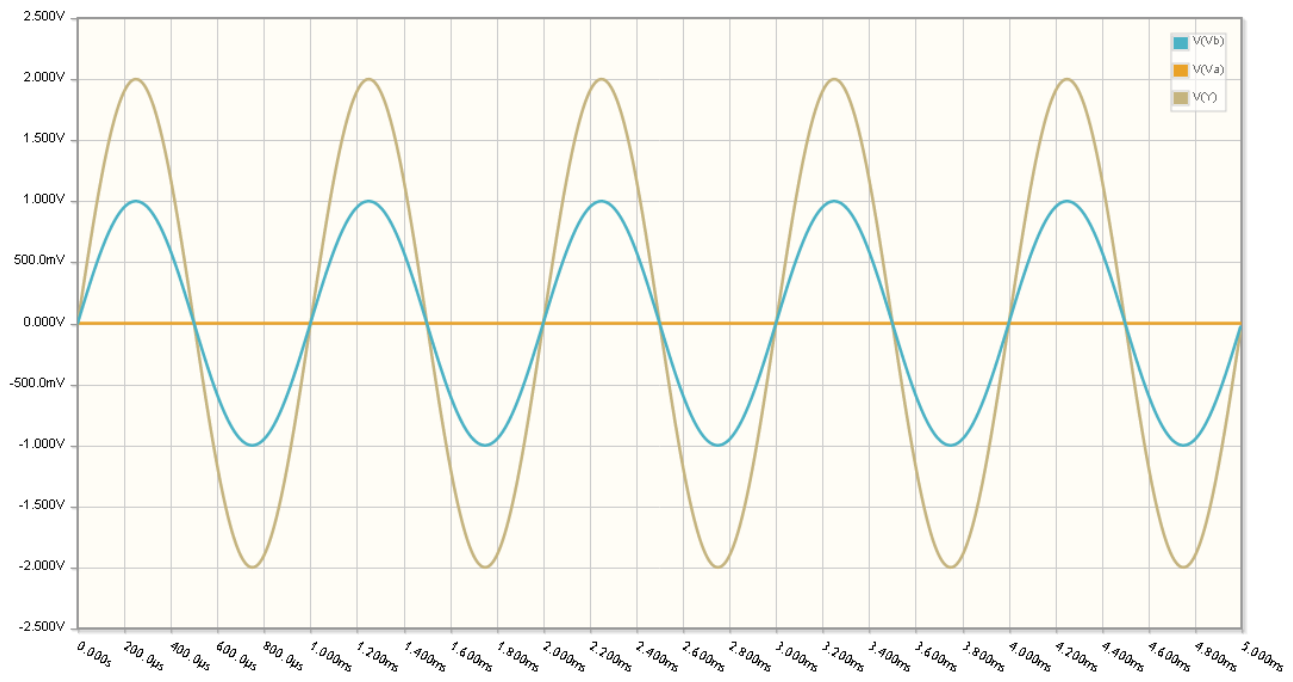

Problem 6) Verify the operation of your circuit in hardware: Apply a 1kHz sine wave to input A then B

Input A

- $V_{in} = 0.317V_{rms}$
- $V_{out} = 0.649V_{rms}$
- gain = 2.047

Input B

- $V_{in} = 0.317V_{rms}$
- $V_{out} = 1.500V_{rms}$
- gain = 4.73

