

# ECE 321 - Quiz #3 - Name \_\_\_\_\_

Filters

1) Assume X and Y are related by the following transfer function

$$Y = \left( \frac{200}{(s+4)(s+6)} \right) X$$

Find  $y(t)$  assuming


$$x(t) = 10 + 5 \cos(mt) + d \sin(mt)$$

where

- $m$  is your birth month (1..12), and
- $d$  is your birth date (1..31)

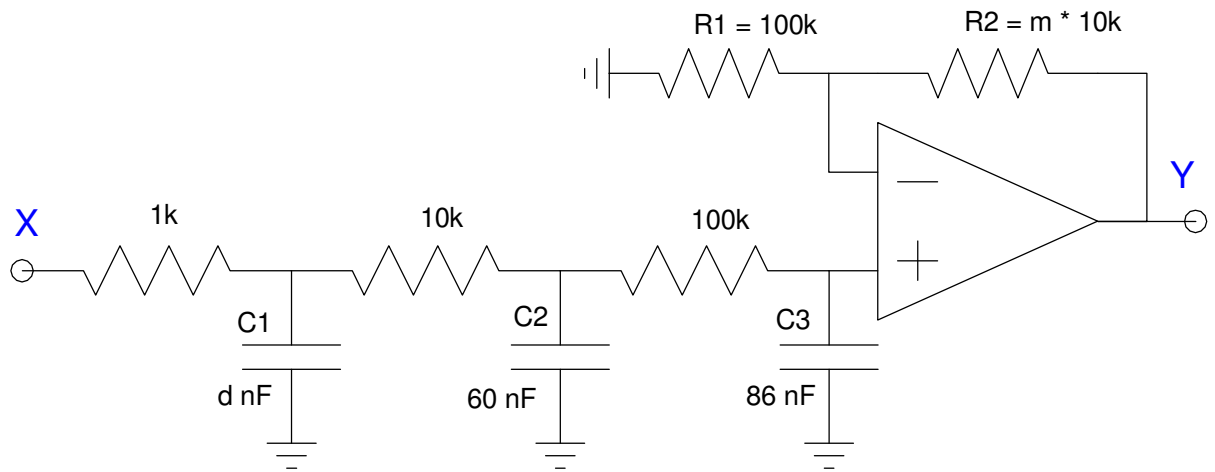
2) Determine the transfer function for the following filter. Assume

- $m$  is your birth month (1..12) ( $R_a = 10k \dots 120k$  Ohms)
- $d$  is your birth date (1..31) ( $C1 = 1nf \dots 31nF$ )



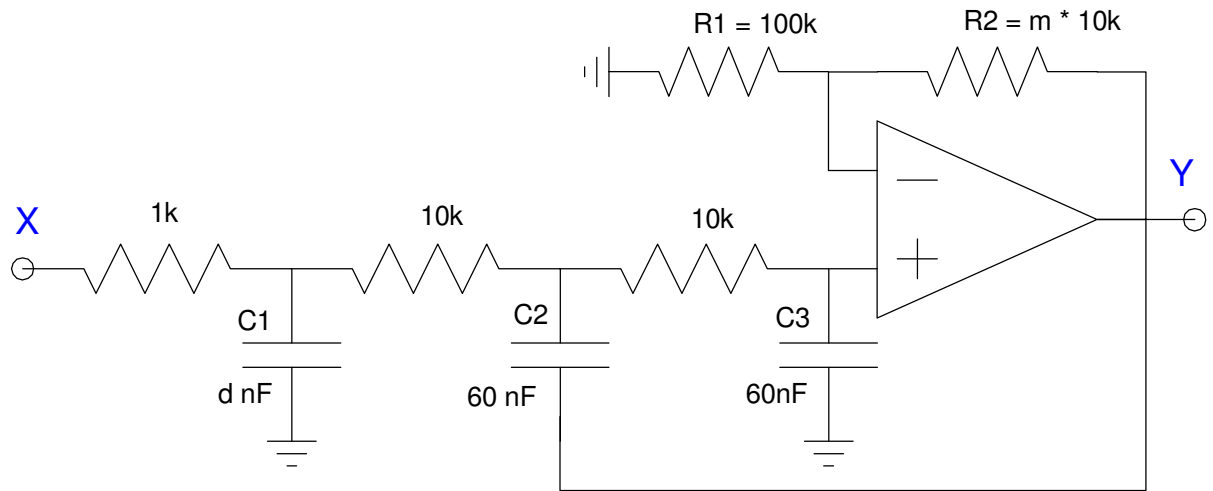3) Determine the transfer function for the following filter. Assume

- $m$  is your birth month (1..12) ( $R_a = 10k \dots 120k$  Ohms)
- $d$  is your birth date (1..31) ( $C1 = 1..31$  nF)



4) Give the transfer function for a filter which meets the following requirements


- $0.9 < \text{gain} < 1.1$  for frequencies below 30 rad/sec
- $\text{gain} < 0.2$  for frequencies above 50 rad/sec

5) Give the Matlab code for an m-file you would use to have Matlab's *fminsearch()* design a filter with the following gain vs. frequency

$$G(s) = \left( \frac{a(s^2+b)}{(s^2+cs+d)(s^2+es+f)} \right)$$

The m-file should

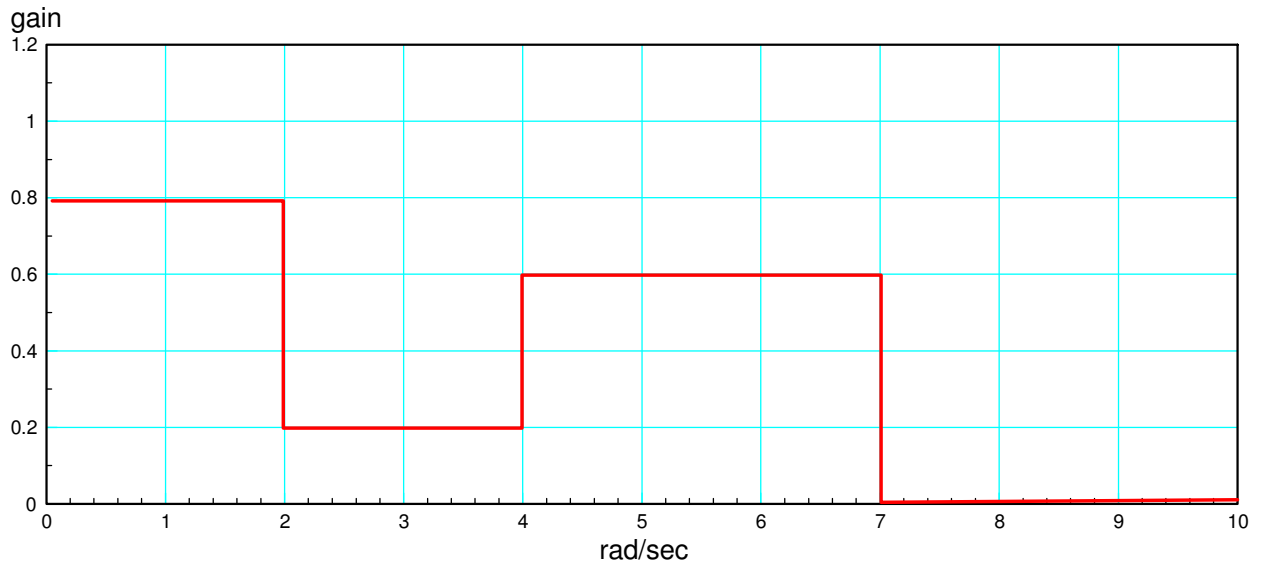- Receive parameters {a,b,c,d,e,f,g}
- Compute  $G(j\omega)$
- Return the sum squared error between  $G(j\omega)$  and the graph below



6) What is the transfer function for the following analog computer?

Assume

- $R1 =$  your birth month (1..12) k Ohms
- $R2 =$  your birth data (1..31) k Ohms

