

ECE 321 - Homework #1

Op Amp Amplifiers, Push-Pull Amplifiers. Due Monday, April 4th

Please make the subject "ECE 321 HW#1" if submitting homework electronically to Jacob_Glower@yahoo.com (or on blackboard)

1) Pick an amplifier to build for ECE 321 Analog Electronics. This amplifier needs to include

- A speaker and a push-pull amplifier (homework #1)
- An amplifier and/or mixer (homework #1),
- A sensor (light, audio, temperature / 555 timer) and
- A filter (homework #3 and #4),

Some suggestions are...




Lab (Hardware) -


Option #1 (single +5V power supply)

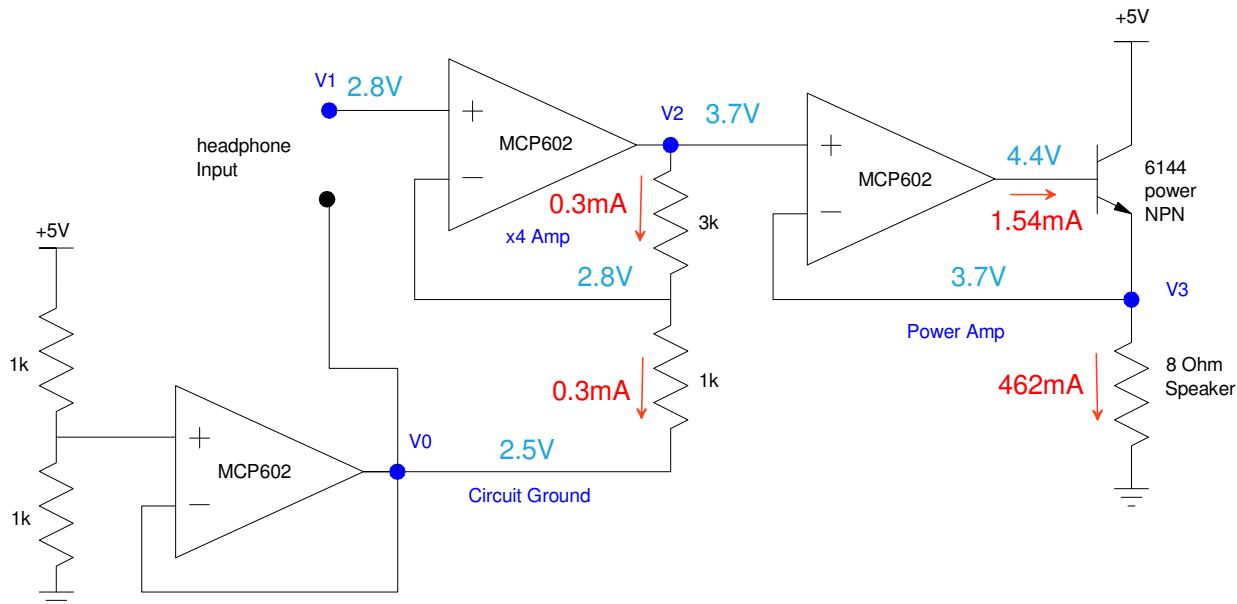6) Calculate the voltages and currents when


V_{in} = +0.3V relative to circuit ground (2.8V)



V₁ = circuit ground (2.5V)

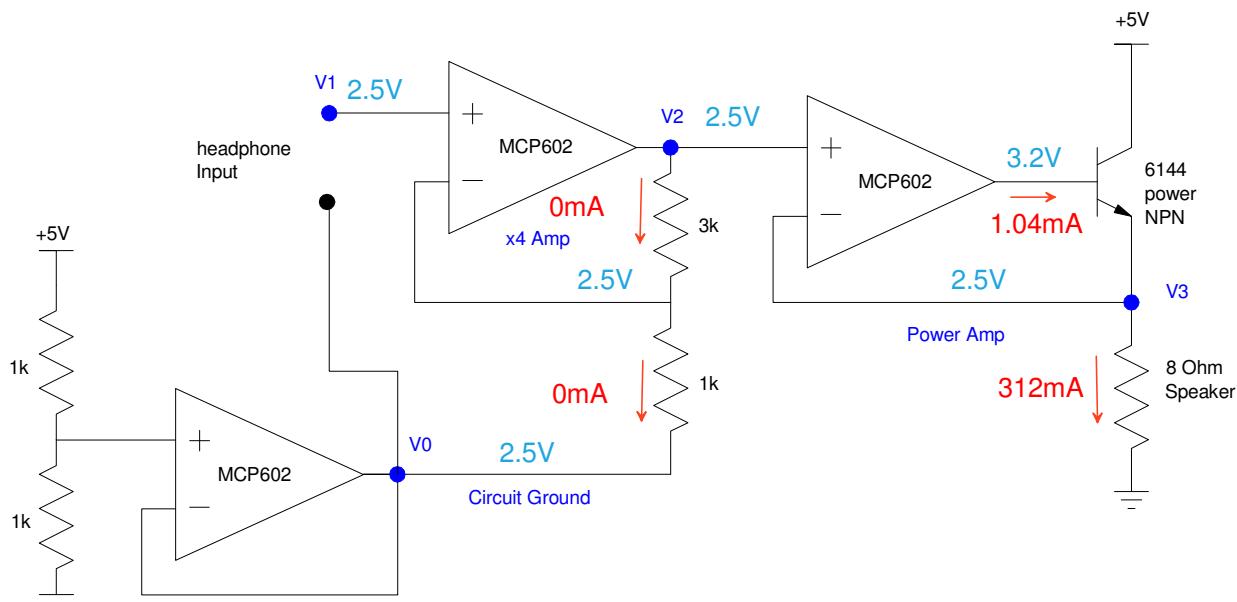


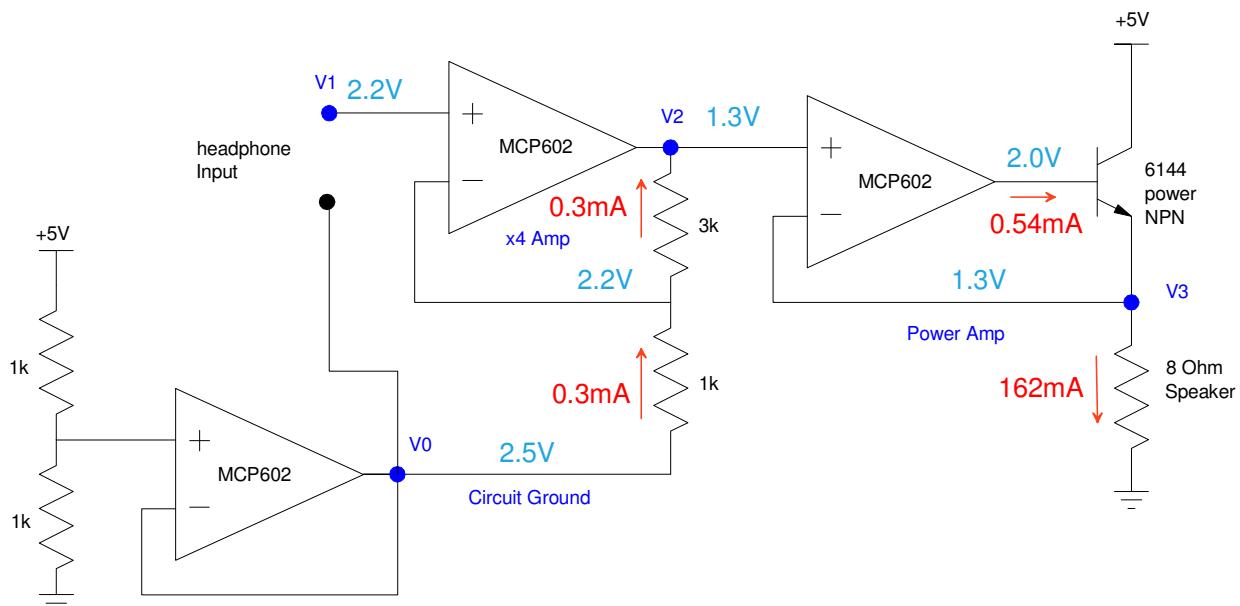$V_{in} = -0.3V$ relative to circuit ground (2.2V)



7) Simulate this circuit in CircuitLab with

- $V1 = 0.3V_p$, 1kHz sine wave

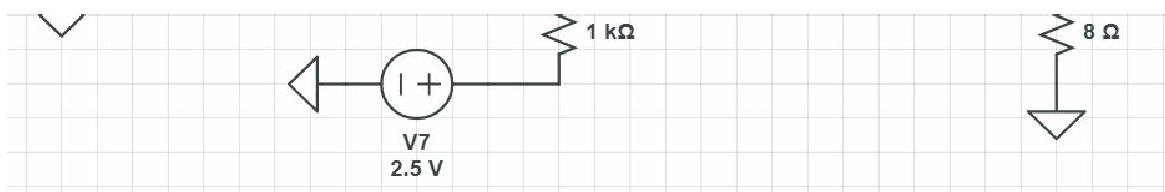


Option #2 (dual power supplies: +6V & -6V)


6) Calculate the voltages and currents when

$$V_{in} = \text{circuit ground} + 0.3V$$


- Assume $|V_{be}| = 1.4V$ (Darlington pair)

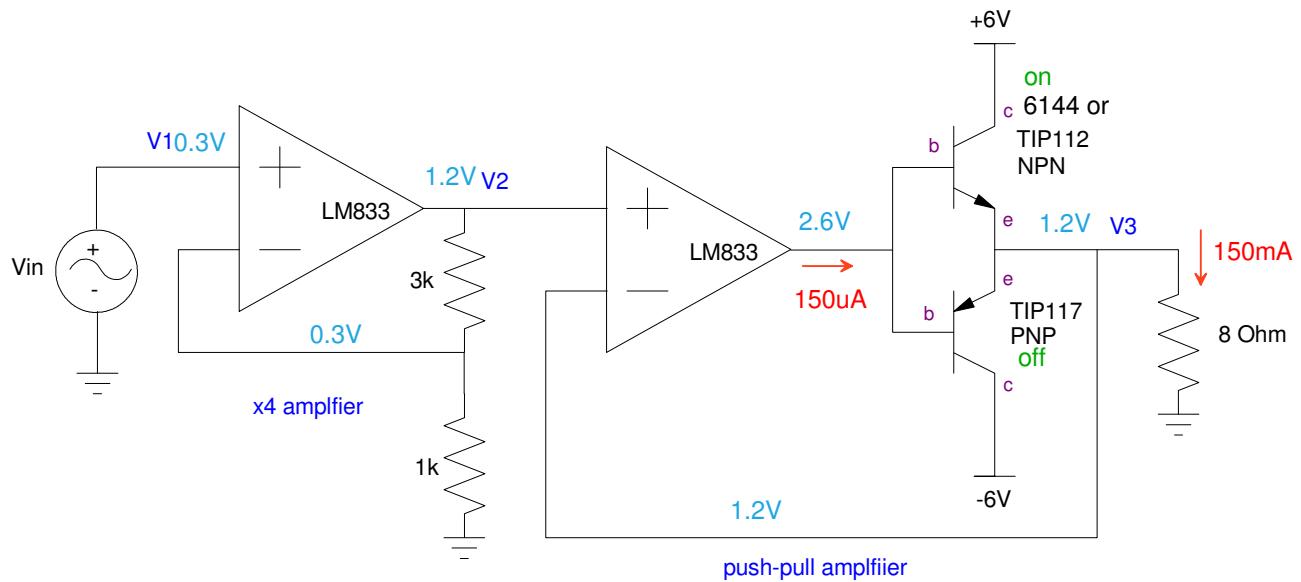

$$V_1 = \text{circuit ground}$$

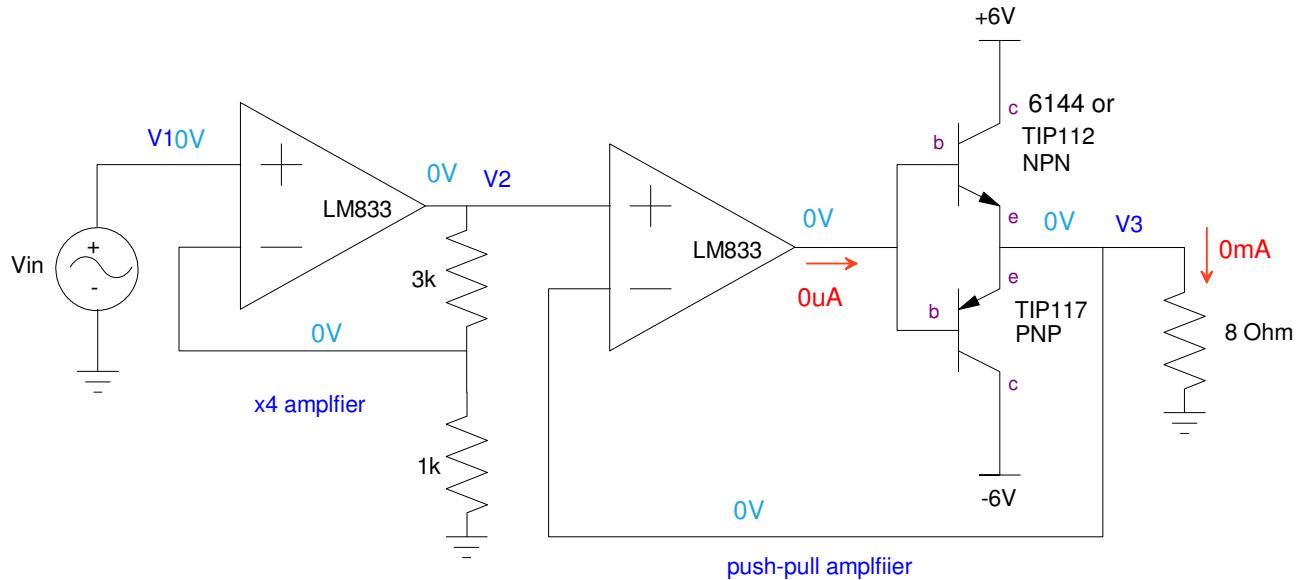

V1 = circuit ground - 0.3V

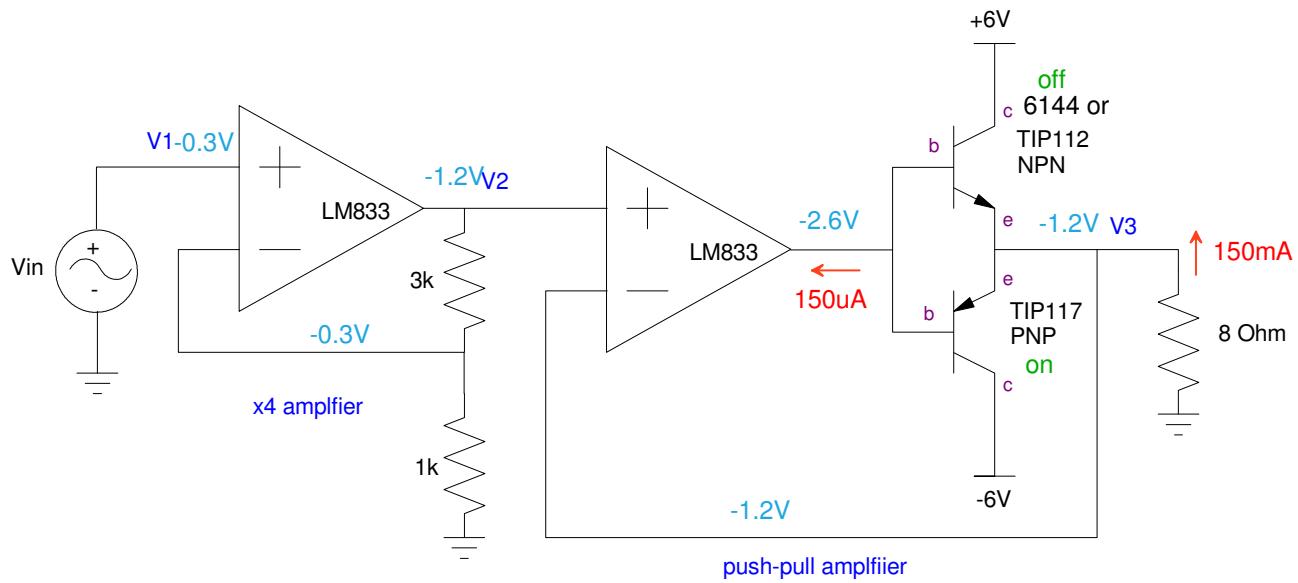

Hardware: @ 600Hz

$V_1 = 168\text{mVrms}$

$V_2 = 686\text{mVrms}$ (x11 amp)

$V_3 = 680\text{mVrms}$

7) Simulate this circuit in CircuitLab with

- $V_1 = 0.3V_p$, 1kHz sine wave

8) Build this circuit in hardware. With a sine wave input, (1kHz) verify that that

- $V2 = 4*V1$ (relative to circuit ground)
- $V3 = V2$ (relative to circuit ground)

8) Demo

- Replace V1 with an audio signal and verify the song plays on the speaker