


# ECE 321 - Final Exam - Name \_\_\_\_\_

Spring 2023

**1. OpAmp Circuits:** Determine  $y$  as a function of  $A$ ,  $B$ ,  $C$ , and  $D$ . Assume

- Ideal op-amps
- $R = 800 + 100 \times (\text{your birth month}) + (\text{your birth day})$ .

$R$ $800 + 100 \times \text{mo} + \text{day}$	$Y = aA + bB + cC + dD$
<b>1314</b>	$Y = -11.41A - 15.00B - 6.81C - 5.18D$

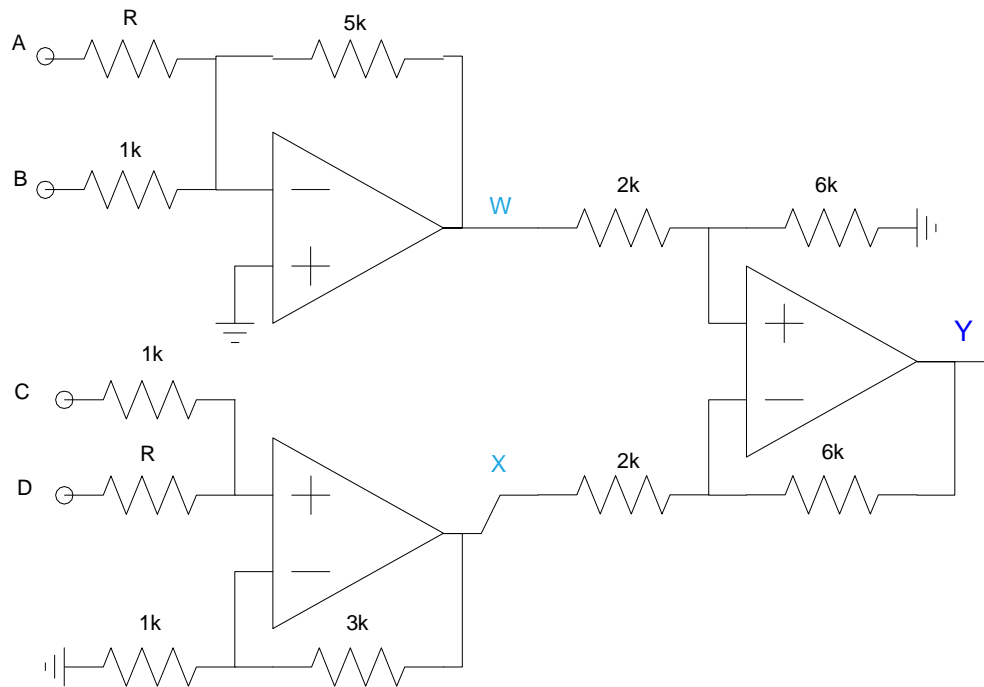

$$W = -\left(\frac{5k}{1314}\right)A - \left(\frac{5k}{1k}\right)B$$


$$X = \left(1 + \frac{3k}{1k}\right) \left( \left(\frac{1314}{1k+1314}\right)C + \left(\frac{1k}{1314+1k}\right)D \right)$$

$$Y = 6(W - X)$$

**2. Push-Pull:** Determine the voltages and currents for the following push-pull amplifier when  $X = -4V$ . Assume

- $R = 800 + 100 \cdot (\text{birth month}) + (\text{birth day})$ .
- $|V_{ce}| = 0.7V$  (ideal silicon diodes)
- $\beta = 30$

R	V1	V2	V3	I4	I5
$800 + 100 \cdot \text{mo} + \text{day}$					
<b>1314</b>	<b>-9.9560</b>	<b>-9.2560</b>	<b>-4.000</b>	<b>37.45mA</b>	<b>1.161A</b>

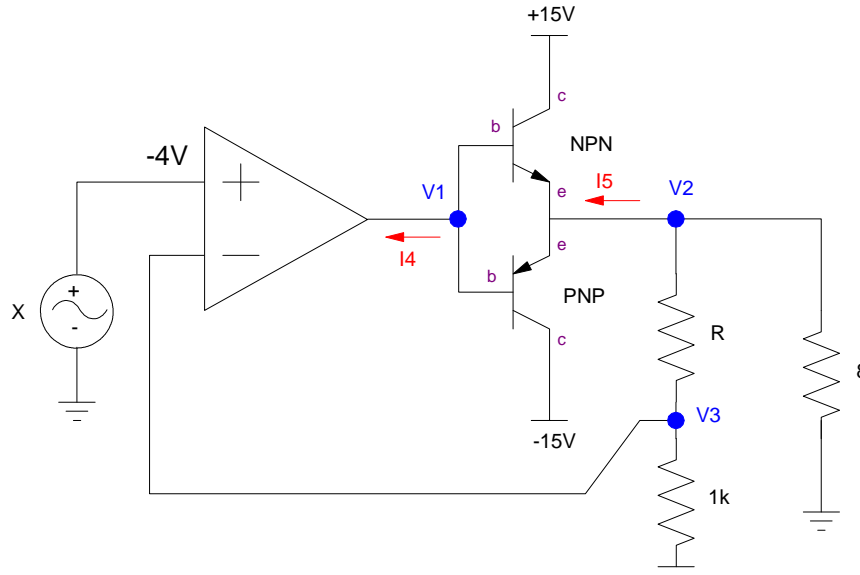

$$V_3 = -4V$$

$$V_2 = \left(1 + \frac{R}{1k}\right) V_3 = -9.256V$$

$$V_1 = V_2 - 0.7 = -9.9560V$$

$$I_5 = \frac{V_2}{8} + \frac{V_2}{1k+R} = 1.161A$$

$$I_4 = \frac{I_5}{\beta+1} = 37.45mA$$

**3. Instrumentation Amplifier:** Assume an RTD has the temperature - resistance relationship of


$$R_x = 1000 \cdot (1 + 0.0043T)\Omega$$

where T is the temperature in degrees C. Design a circuit which outputs

- +10V at +40C, and
- 0V at 0C

Assume

- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$

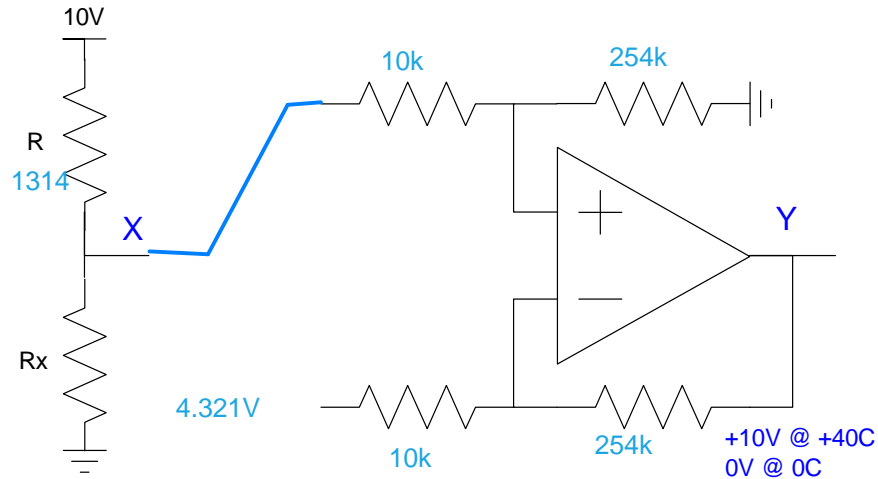

At 0C

$$R_x = 1000$$

$$X = \left( \frac{R_x}{R_x + 1314} \right) 10V = 4.321V$$

At 40C

$$R_x = 1172\Omega$$

$$X = \left( \frac{R_x}{R_x + 1314} \right) 10V = 4.7144V$$

Offset = 4.321V (where Y = 0)

Connect to the + input (Y goes up as X goes up)


$$gain = \left( \frac{10V - 0V}{4.7144V - 4.321V} \right) = 25.45$$

**4. Filters:** Let

- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$ .

Determine the poles and the DC gain

R 800 + 100*mo + day	Transfer Function $Y = G(s) * X$
<b>1314</b>	$\left( \frac{8.4621 \cdot 76.10 \cdot 38.05 \cdot 761.03^2}{(s+76.10)(s+38.05)(s+761.03 \angle \pm 51.72^\circ)} \right)$

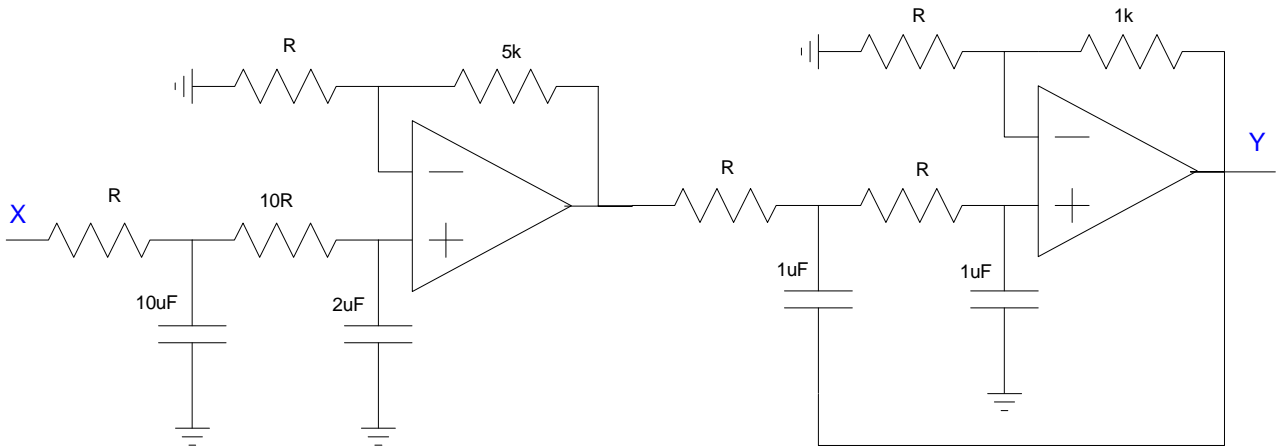

pole 1: 76.1035 38.0518 761.0350 51.7216 8.4621

$$pole = -\left(\frac{1}{RC}\right) = -\left(\frac{1}{1314 \cdot 10\mu F}\right) = -76.103$$

$$pole = -\left(\frac{1}{RC}\right) = -\left(\frac{1}{1340 \cdot 2\mu F}\right) = -38.0518$$

$$pole_3 = -\left(\frac{1}{RC}\right) = -\left(\frac{1}{1314 \cdot 1\mu F}\right) = -761.03$$

$$k = 1 + \frac{1k}{R} = 1.7610$$

$$3 - k = 2 \cos \theta$$

$$\theta = 57.721^\circ$$

$$DC = \left(1 + \frac{5k}{R}\right) \left(1 + \frac{1k}{R}\right) = 8.4621$$

**5) Filter Analysis:** Determine  $y(t)$  given

$$Y = \left( \frac{20s}{s^2 + 2s + 100} \right) X$$

$$x(t) = 4 + m \cos(10t) + d \sin(10t)$$

$$x(t) = 4 + 5 \cos(10t) + 14 \sin(10t)$$

where

- $m$  is your birth month(1..12) and
- $d$  is your birth date (1..31)

DC:

$$s = 0$$

$$X = 4$$

$$Y = \left( \frac{20s}{s^2 + 2s + 100} \right)_{s=0} \cdot (4)$$

$$Y = 0$$

AC:

$$s = j10$$

$$X = 5 - j14$$

$$Y = \left( \frac{20s}{s^2 + 2s + 100} \right)_{s=j10} \cdot (5 - j14)$$

$$Y = 50 - j140$$

$$y(t) = 50 \cos(10t) + 140 \sin(10t)$$

*real = cosine, -imag = sine*



*Total*

$$Y = 0 + 50 \cos(10t) + 140 \sin(10t)$$

**6. CE Amplifiers (DC analysis):** Determine the Q-point for the following circuit. Assume

- $R_2 = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$
- $\beta = 30$
- $|V_{be}| = 0.7V$  (ideal silicon diode)

R2	Vb	Rb	Vce	Ic
800 + 100*mo + day				
<b>1314</b>	<b>2.1559 V</b>	<b>1077.9 Ohms</b>	<b>8.8107 V</b>	<b>349.2uA</b>

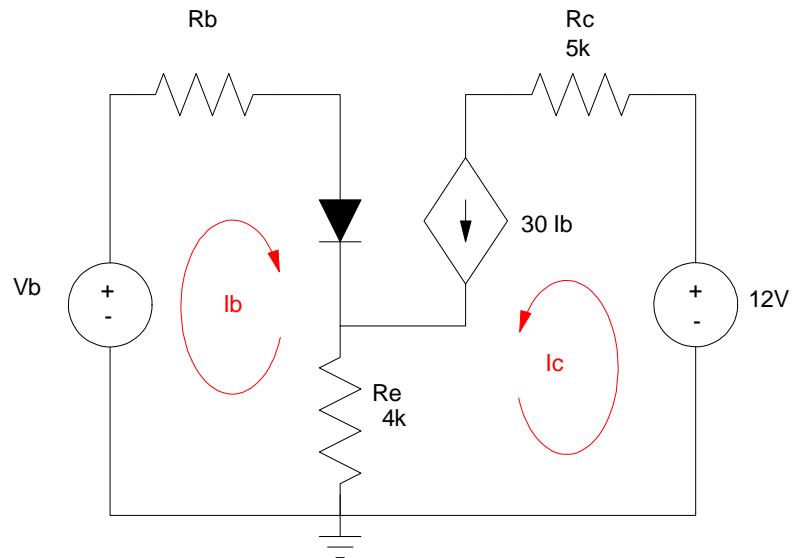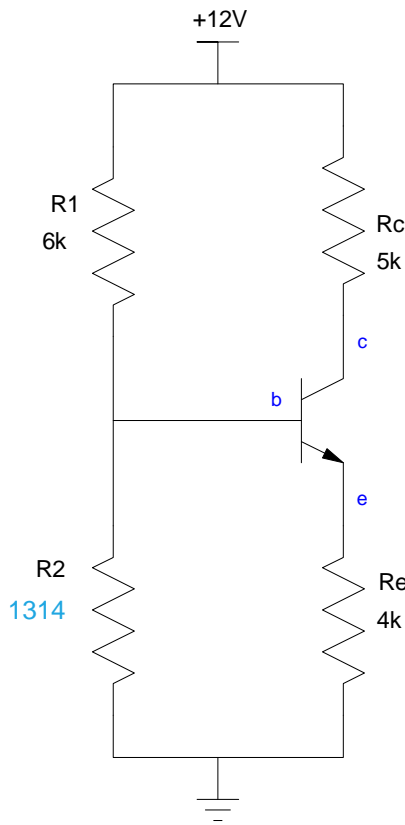

$$R_b = R_1 || R_2 = 1077.9\Omega$$

$$V_b = \left( \frac{R_2}{R_1 + R_2} \right) 12V = 2.1559V$$

$$I_b = \left( \frac{V_b - 0.7}{R_b + (1 + \beta)R_e} \right) = 11.64\mu A$$

$$I_c = \beta I_b = 349.2\mu A$$



$$V_{ce} = 12 - R_c I_c - R_e (I_b + I_c) = 8.8107V$$

**7. 2-Port model:** Determine the 2-port parameters for the following circuit. Assume

- $R = 800 + 100 * (\text{your birth month}) + (\text{your birth date})$  Ohms

R 800 + 100*mo + day	R <sub>in</sub>	A <sub>i</sub>	R <sub>out</sub>	A <sub>o</sub>
<b>1314</b>	<b>962.6 Ohms</b>	<b>0.7326</b>	<b>41.36 Ohms</b>	<b>0.9759</b>

0.9626 0.7326 41.3643 0.9759

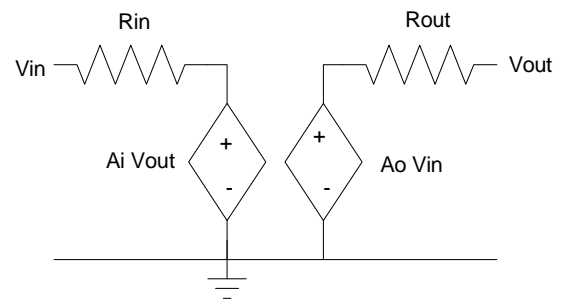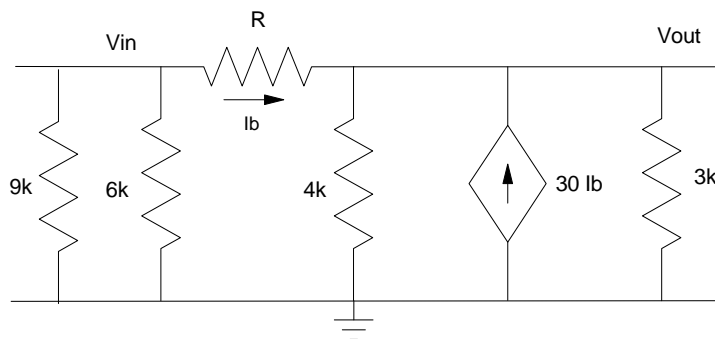

R<sub>in</sub>: Short V<sub>out</sub>, measure the resistance at the input.

$$R_{in} = 9k || 6k || R = 962.6\Omega$$

A<sub>in</sub>: Apply 1V at V<sub>out</sub>, measure V<sub>in</sub>. By voltage division

$$A_{in} = \left( \frac{9k || 6k}{9k || 6k + R} \right) = 0.7326$$

R<sub>out</sub>: Short V<sub>in</sub>. Apply 1V to V<sub>out</sub> and compute the current draw

$$I = \left( \frac{1}{3k} \right) + \left( \frac{1}{4k} \right) + \left( \frac{1}{R} \right) + 30 \left( \frac{1}{R} \right) = 24.18mA$$

$$R_{out} = \frac{1V}{24.18mA} = 41.36\Omega$$


A<sub>out</sub>: Apply 1V to V<sub>in</sub>, compute V<sub>out</sub>. Do a voltage node equation at V<sub>out</sub>

$$\left( \frac{V_o - 1}{R} \right) + \left( \frac{V_o}{4k} \right) + 30 \left( \frac{V_o - 1}{R} \right) + \left( \frac{V_o}{3k} \right) = 0$$

$$V_o = 0.9759V$$

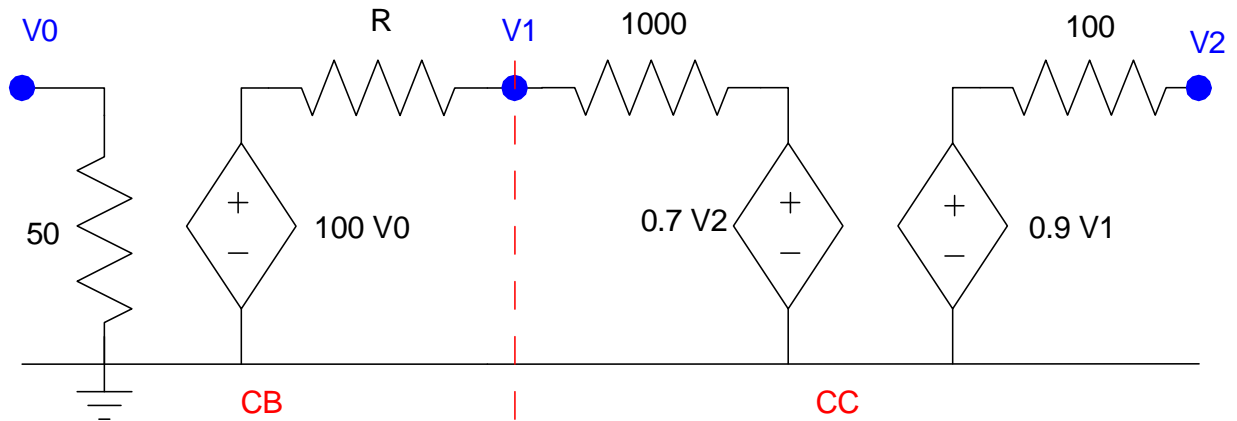**8. 2-Port model:** Determine the 2-port parameters for a Common-Base amplifier cascaded with a Common Collector amplifier. Assume

- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$  Ohms



R 800 + 100*mo + day	Rin	Ain	Rout	Aout
<b>1314</b>	<b>50</b>	<b>0</b>	<b>155.70 Ohms</b>	<b>60.55</b>

By inspection

$$R_{in} = 50$$

$$A_{in} = 0$$

Rout: Short V0, Apply 1V to V2. Compute the current draw

$$V_1 = \left( \frac{R}{R+1000} \right) 0.7V = 0.3975V$$

$$I = \left( \frac{1V - 0.9 \cdot 0.3975V}{100\Omega} \right) = 6.423mA$$

$$R_{out} = \frac{1V}{I} = 155.7\Omega$$