

Common Emitter Amplifier


Background:

Assume you have a transistor circuit set up so that the Q point is in the active region. Use this to amplify a small AC signal.

Assume the following circuit for now with the Q-point being

$$I_c = 6\text{mA}$$

$$V_c = 6\text{V}$$

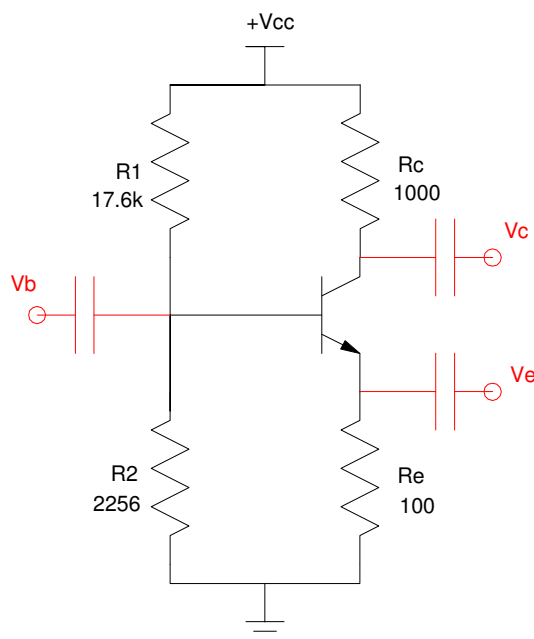

To prevent the outside world from messing up the Q-point, add capacitors to the base, emitter, and collector.

For a common-emitter amplifier, connect

- V_e to ground.
- The input to V_b
- The output to V_c .

If you apply an AC signal to V_b , this changes the voltage (and hence current) to the base. This current is amplified by β , which is converted to a voltage and amplified again by R_c . The net is an amplifier.

To analyze this amplifier, ignore the DC terms. The DC analysis set the Q point, and we don't want to mess with that. Besides, the capacitors block DC terms from getting to the amplifier.

Instead, analyze the AC terms. For a resistor, AC and DC look alike. For a diode, however, we need to find the small signal model. We need that AC model for the diode to model the base-to-emitter connection for the transistor.

Recall that for a silicon diode that


$$V_d = \eta V_T \cdot \ln(I_d/I_o + 1)$$

$$\eta \approx 2$$

$$V_T = 0.026$$

$$I_o \approx 10^{-10} \text{A}$$

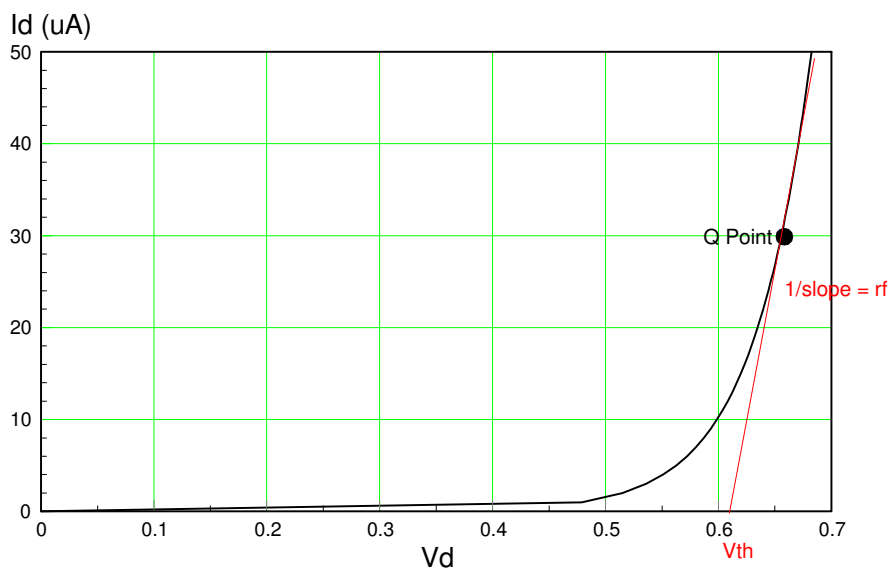which gives the following VI characteristic. Drawing the tangent to the VI curve at the Q point gives the small-signal model (a.k.a. the first two terms in the Taylor's series expansion.)



Taking the tangent results in the small-signal model:

$$V_d \approx V_{th} + i_d r_f$$

Taking the derivative:

$$r_f = \frac{dV_d}{dI_d} = \frac{d}{dI_d} \left(\eta V_T \cdot \ln \left(\frac{I_d}{I_o} + 1 \right) \right)$$

$$r_f = (\eta V_T) \left(\frac{1}{\frac{I_d}{I_o} + 1} \right) \left(\frac{1}{I_o} \right)$$

$$r_f = (\eta V_T) \left(\frac{1}{I_d + I_o} \right)$$

Since $I_o \ll I_d$ at the Q point,


$$r_f \approx \left(\frac{\eta V_T}{I_d} \right)$$

or with the Q point being 30uA (I_b),


$$r_f = \left(\frac{0.052 \text{V}}{30 \mu\text{A}} \right) = 1733 \Omega$$

There's also a DC term, but we're ignoring DC terms for AC analysis.

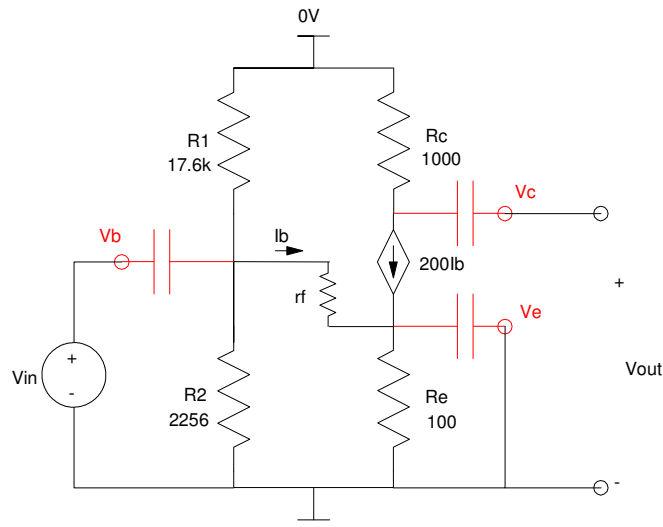
Now, let's look at the small signal model (i.e. the AC model). Note that $V_{cc} = +12V$, which has no AC term. Hence, for AC analysis, $V_{cc} = 0V$.



Redrawing this results in

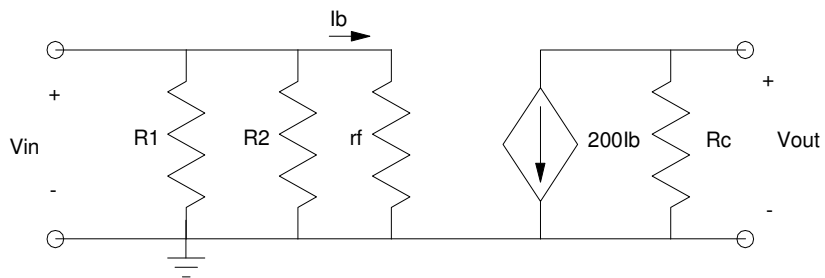

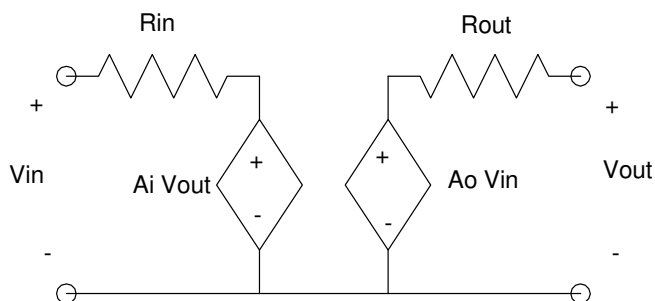To simplify this, use a generic Thevenin equivalent for a circuit with an input and output, termed a 2-port model:



To find the two port parameters, come up with a test to find all four parameters for the 2-port model. Do the same test on the CE amplifier circuit.

Rin: For the 2-port model, short V_o so that $V_o=0$ and $A_i V_{out} = 0$. Measure the resistance at the input. Doing the same for the CE amplifier, this results in

$$R_{in} = R_1 || R_2 || r_f$$

Ai: For the 2-port model, apply 1V to V_{out} . Measure the resulting voltage at V_{in} . Doing the same for the CE amplifier results in $V_{in} = 0V$, so

$$A_i = 0$$

Rout: For the 2-port model, short V_i so that $V_i=0$ and $A_o V_{in} = 0$. Measure the resistance at the output. Doing the same for the CE amplifier, this results in

$$R_{out} = R_c$$

Ao: For the 2-port model, apply 1V to V_{in} . Measure the resulting voltage at V_{out} . Doing the same for the CE amplifier results in

$$I_b = \frac{1}{r_f}$$

$$I_c = \beta I_b = \frac{\beta}{r_f}$$

$$V_{out} = -R_c I_c = -\frac{\beta R_c}{r_f}$$

so


$$A_o = -\frac{\beta R_c}{r_f}$$

The 2-port model for a CE amplifier is then

$$R_{in} = 928\Omega$$


$$R_{out} = 1k\Omega$$

$$A_o = -115$$

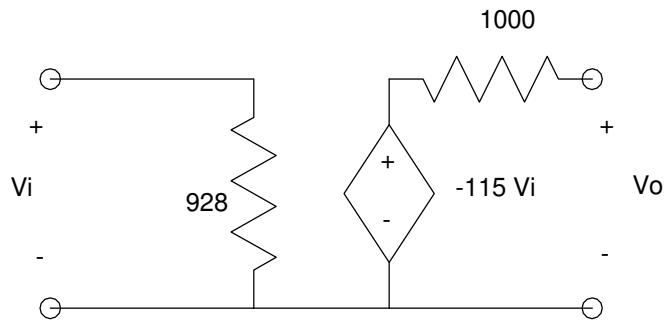


Problem: Simulate the response of this circuit to a 0.1mV, 1kHz sine wave input. Assume all capacitors are 100uF.

Using MultiSim:

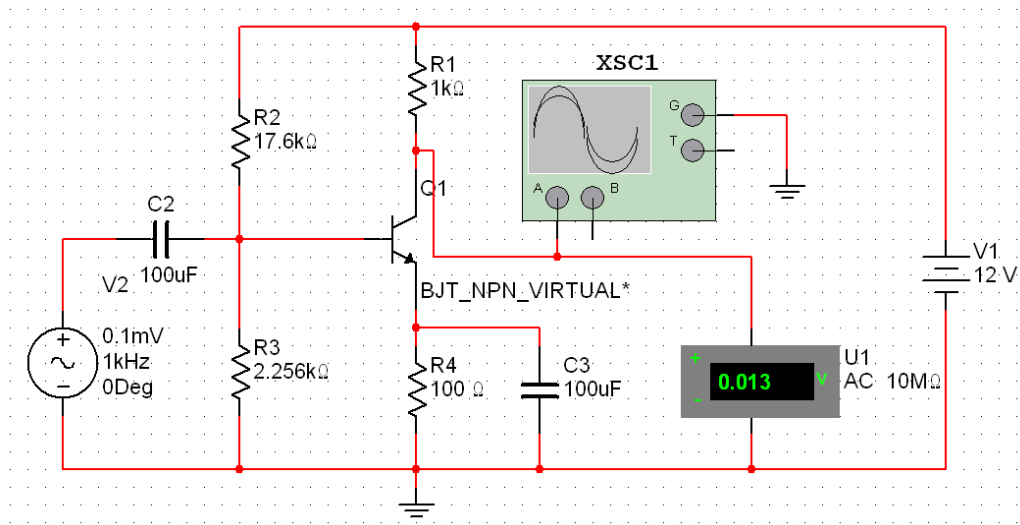


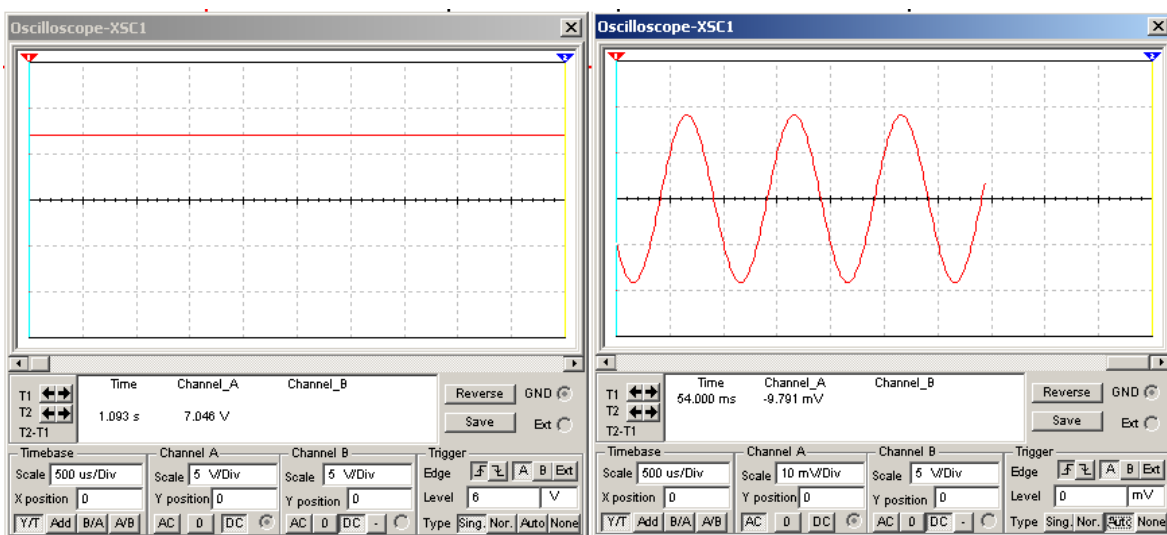If you use DC coupling on the oscilloscope (left), you see the small AC signal at Vc riding on top of a 6V DC offset. If you switch to AC coupling to remove the DC offset, you can see the AC signal is 13mV rms, resulting in an AC gain of 130. The gain is supposed to be 115, so this is pretty close to our analysis.




DC Coupling showing the DC offset of the Q-point (left) and AC coupling showing the gain (right)

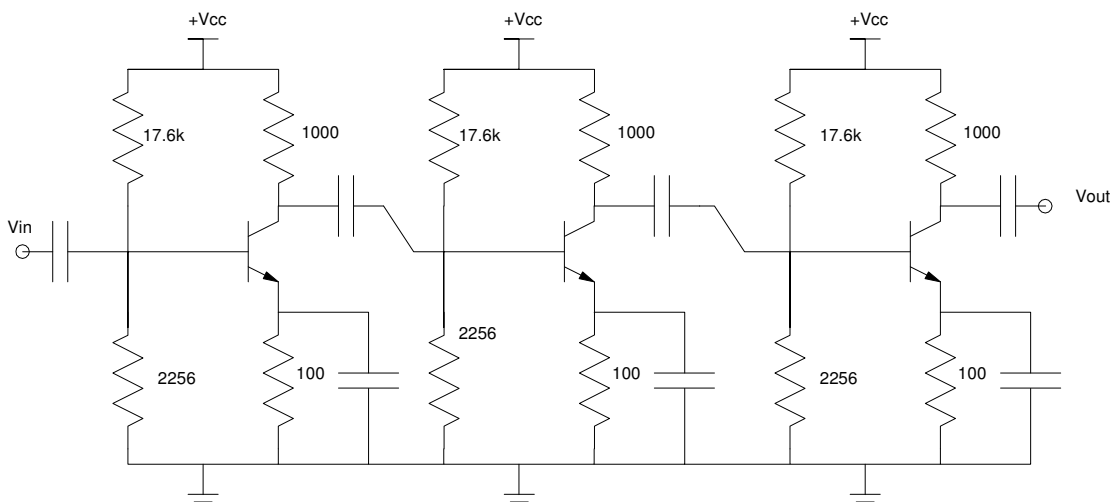Problem: Find the 2-port model for the following circuit:



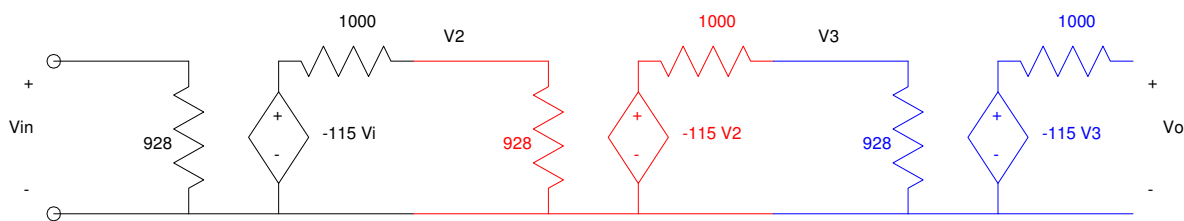Solution: This is the same circuit we've been analyzing, copied three times. The 2-port model will be the same for all three sections since they're identical. Using the 2-port model then,



Now go through the 2-port tests:

Rin: Set $V_o = 0V$ and measure the input resistance. $R_{in} = 928$ Ohms.

Ai: Set $V_o = 1V$ and measure the voltage at V_{in} . $A_i = 0$

Rout: Set $V_{in} = 0V$ and measure the resistance across V_o . $V_{in} = 0$ sets $V_2 = 0$ sets $V_3 = 0$ sets $-115V_3 = 0$. $R_{out} = 1000$ Ohms.


Ao: Apply 1V at V_{in} and measure V_{out} . If $V_{in} = 1V$,

$$V_2 = \left(\frac{928}{1000+928} \right) (-115V_i) = -55.35V$$

$$V_3 = \left(\frac{928}{1000+928} \right) (-115V_2) = 3063.9V$$

$$V_o = -115V_3 = -352,350$$

So the 2-port model is

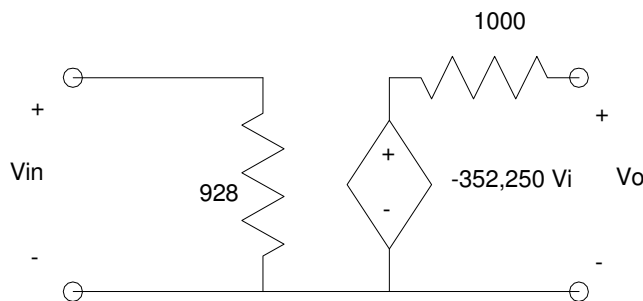

CE amplifiers are used to add gain.

In MultiSim, you can see the additional gain from adding stages. Using two stages results in the output still riding on a 6V offset, but now with an amplitude of 0.982V (rms), for a voltage gain of 9,790.

