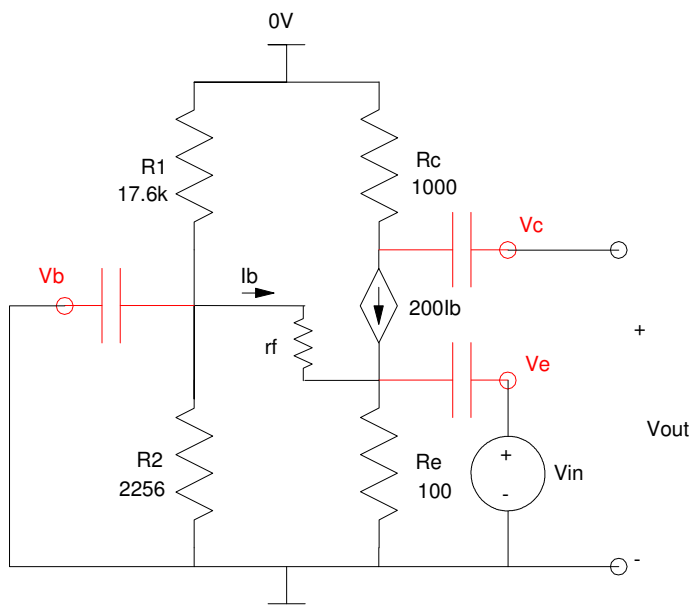



Common Base, Common Collector Amplifiers.

Common Base Amplifier:

- Connect the base to ground
- Connect the input to V_e
- Connect the output to V_c :



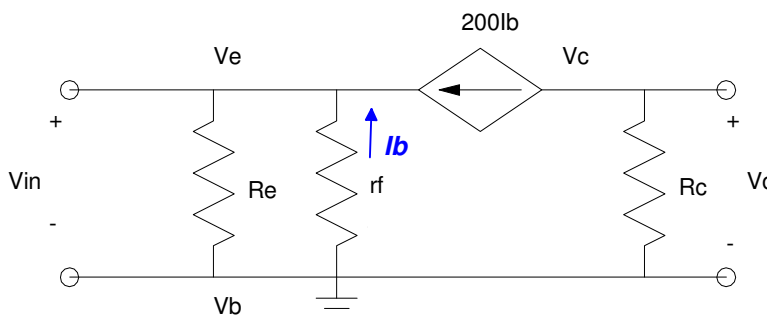Now find the 2-port model. To do this, let's first redraw the circuit:



Now let's find the 2-port parameters:

R_{in} : Set $V_o = 0V$ and measure the input resistance. In this case, it's not that obvious what the answer is. So, let's apply 1V to V_{in} and see how much current is drawn, $1/I_{in}$ is the input resistance.

$$I_{in} = \frac{1V}{R_e} + \frac{1V}{r_f} + \beta I_b$$

$$I_{in} = \frac{1V}{R_e} + \frac{1V}{r_f} + \frac{\beta}{r_f}$$

so

$$R_{in} = \left(\frac{1}{R_e} + \frac{1}{r_f} + \frac{\beta}{r_f} \right)^{-1}$$

Note that this is also

$$R_{in} = R_e \parallel r_f \parallel \frac{r_f}{\beta}$$

$$R_{in} = 8\Omega$$

Ain: Set $V_o = 1V$ and measure the voltage at the input. Again, this isn't obvious, but 0V works. If $V_{in} = 0V$, $I_b = 0$, $\beta I_b = 0$. So $A_{in} = 0$.

$$A_{in} = 0.$$

Rout: Set $V_{in} = 0V$ and measure the resistance at the output. If $V_{in} = 0V$, $I_b = 0$, $\beta I_b = 0$ and everything is turned off. The only thing you see at the output is R_c .

$$R_{out} = R_c.$$

Ao: Set $V_{in} = 1V$ and measure the voltage at the output.


$$I_b = \frac{1}{r_f}$$

$$I_c = \beta I_b$$

$$A_o = V_o = -\frac{\beta R_c}{r_f}$$

$$A_o = -115$$

So, the 2-port model is then

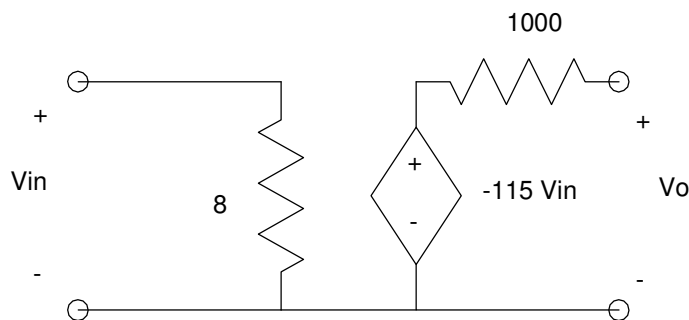


Note that the common-base amplifier has a low input impedance. It's used as the first stage in an amplifier where the sensor needs a low-impedance load, such as a phonograph (the current carries the signal.)


Common Collector Amplifier:

- Short the collector to ground
- Connect the input to the base

- Connect the output to the collector

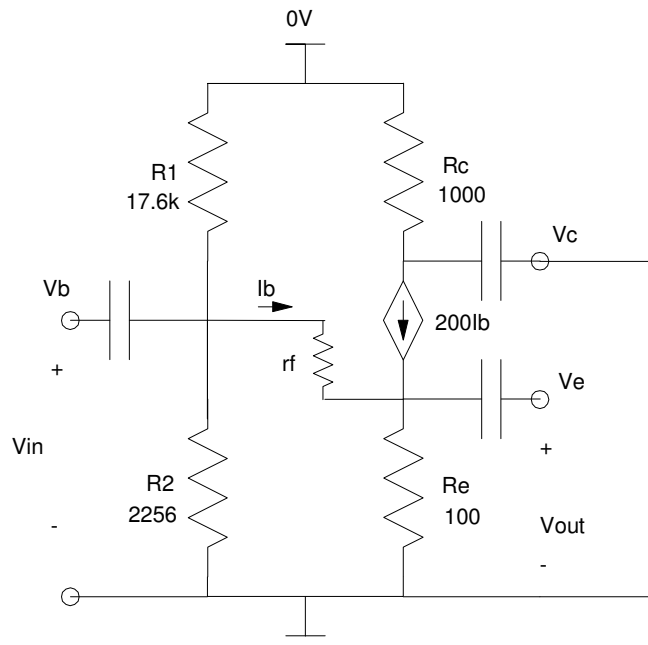

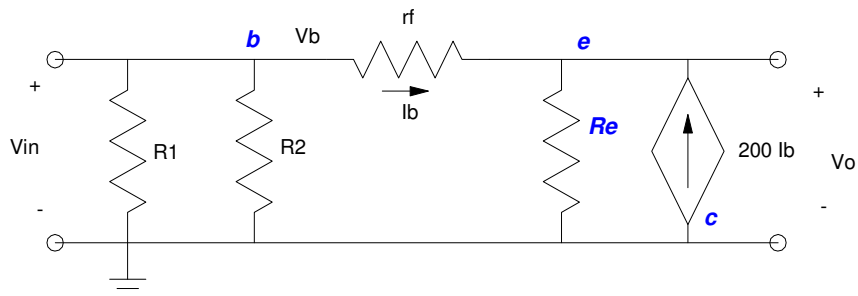To find the 2-port parameters, redraw the circuit:



Now, find the 2-port parameters:

Rin: Set $V_o = 0V$ and measure the resistance at the input.

$$R_{in} = R_1 || R_2 || r_f$$

$$R_{in} = 928\Omega$$

Ain: Set $V_o = 1V$ and measure the voltage at the input. By voltage division

$$A_{in} = \left(\frac{R_1 || R_2}{R_1 || R_2 + r_f} \right)$$

$$A_{in} = 0.5357$$

Rout: Set $V_{in} = 0V$ and measure the resistance across V_o . Again, this isn't obvious, so let's apply a 1V source to V_o and measure the current drawn:


$$I = \frac{1}{r_f} + \frac{1}{R_e} - \beta(-I_b)$$

$$I = \frac{1}{r_f} + \frac{1}{R_e} + \frac{\beta}{r_f}$$

so

$$R_{out} = \left(\frac{1}{r_f} + \right)$$

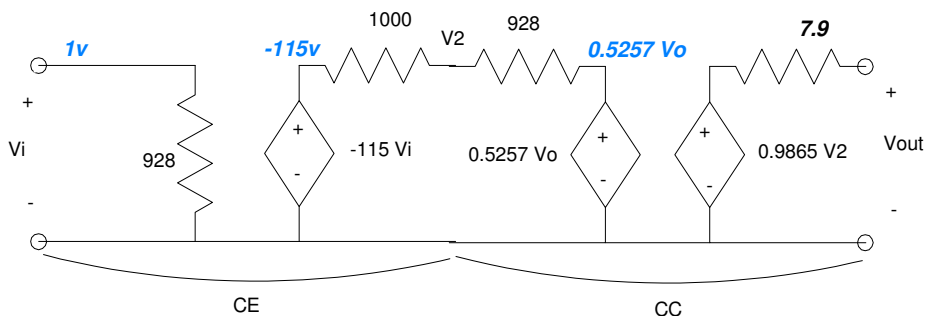Aout: Set $V_i = 1V$ and measure the voltage at the output. Using voltage nodes, at V_2 :



Solve for the voltage at V_2 . Using voltage nodes:

$$\left(\frac{V_2-0}{1000}\right) + \left(\frac{V_2-0.5257V_o}{928}\right) = 0$$

$$V_o = 0.9865V_2$$

$$\left(\frac{V_2-(-115)}{1000}\right) + \left(\frac{V_2-0.5257 \cdot 0.9865 \cdot V_2}{928}\right) = 0$$


$$\left(\left(\frac{1}{1000}\right) + \left(\frac{1-0.5257 \cdot 0.9865}{928}\right)\right) V_2 = -\left(\frac{115}{1000}\right)$$

$$V_2 = -75.72V$$

$$V_o = 0.9865V_2$$

$$V_o = -74.69$$

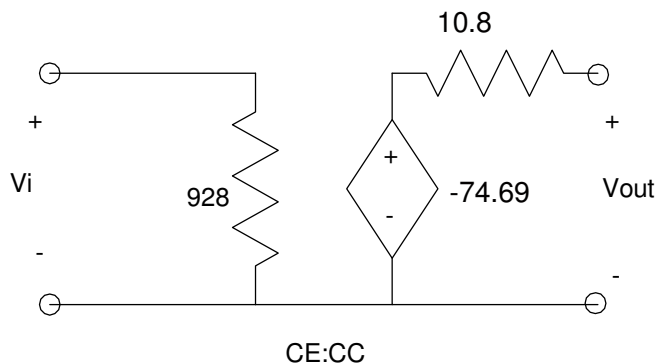So the 2-port model of a CE:CC amplifier is



Common collector amplifiers are used as the last stage for an amplifier when you need to drive a low-impedance load, such as an 8-Ohm speaker.

