
Amplifiers and Mixers

ECE 321: Electronics II

Please visit [Bison Academy](#) for corresponding lecture notes, homework sets, and solutions

Amplifiers and Mixers

With op-amps, you can build a wide variety of amplifiers and mixers. This covers some of the common ones we'll use.

Noninverting Amplifier

Writing the three voltage node equations


$$V_p = X$$

$$V_m = V_p$$

$$\frac{V_m - Y}{R_1} + \frac{V_m}{R_2} = 0$$

Solving
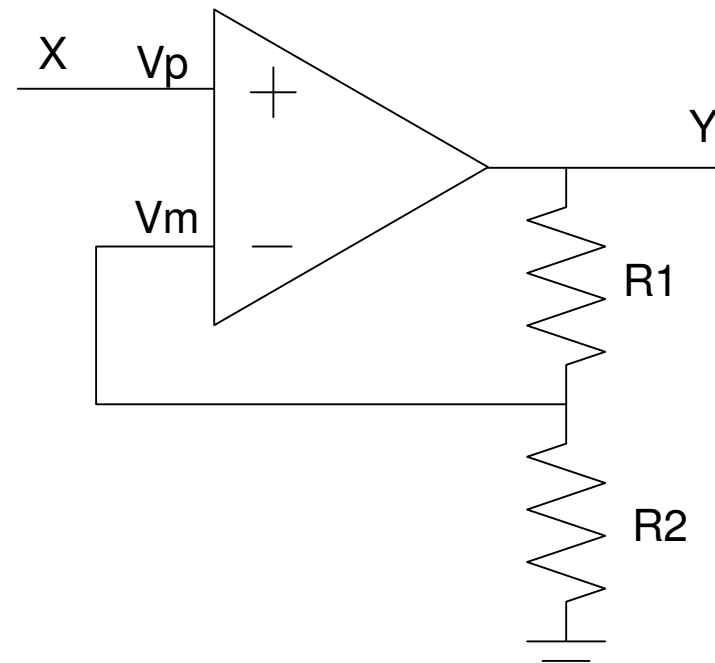
$$Y = \left(1 + \frac{R_1}{R_2}\right) X$$




Example: Design a circuit to implement


$$y = 1.5x$$

$$\text{gain} = 1 + \frac{R_1}{R_2} = 1.5$$

Let $R_1 = 500$, $R_2 = 1\text{k}$

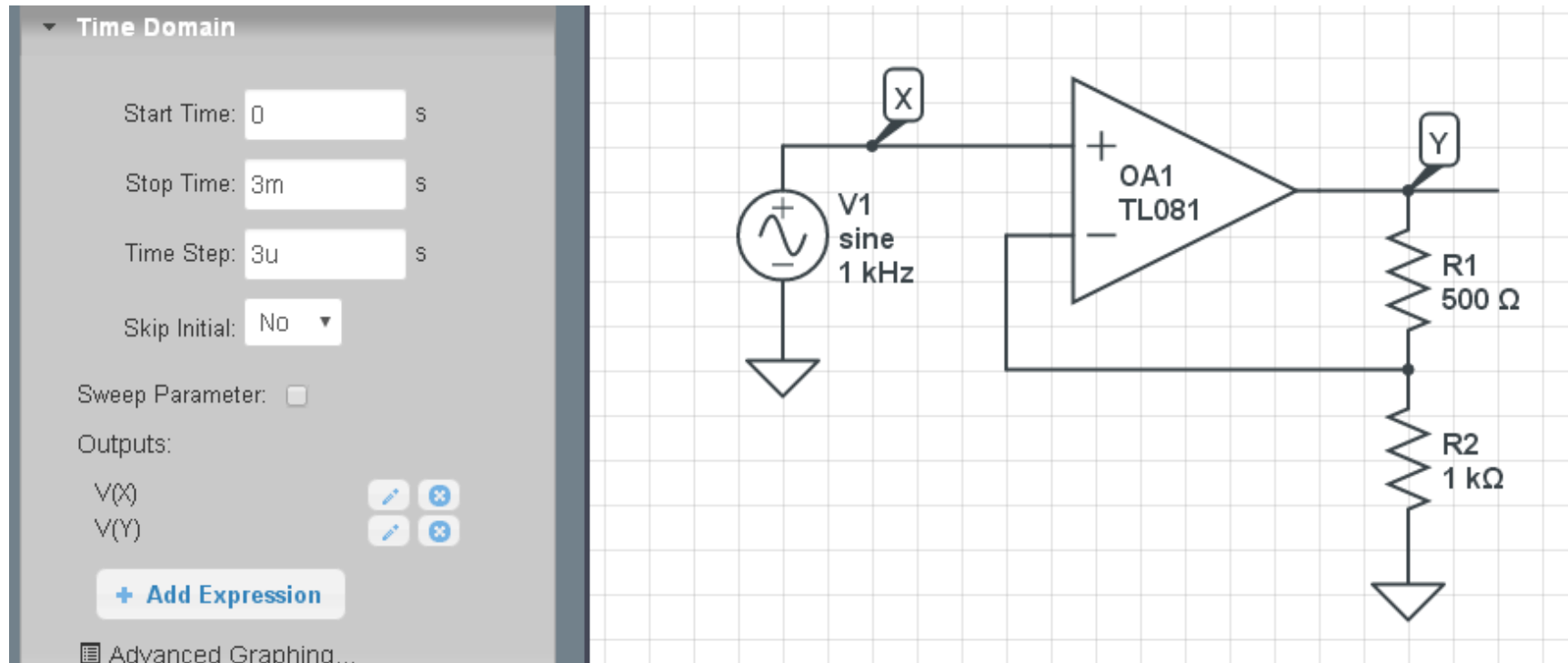

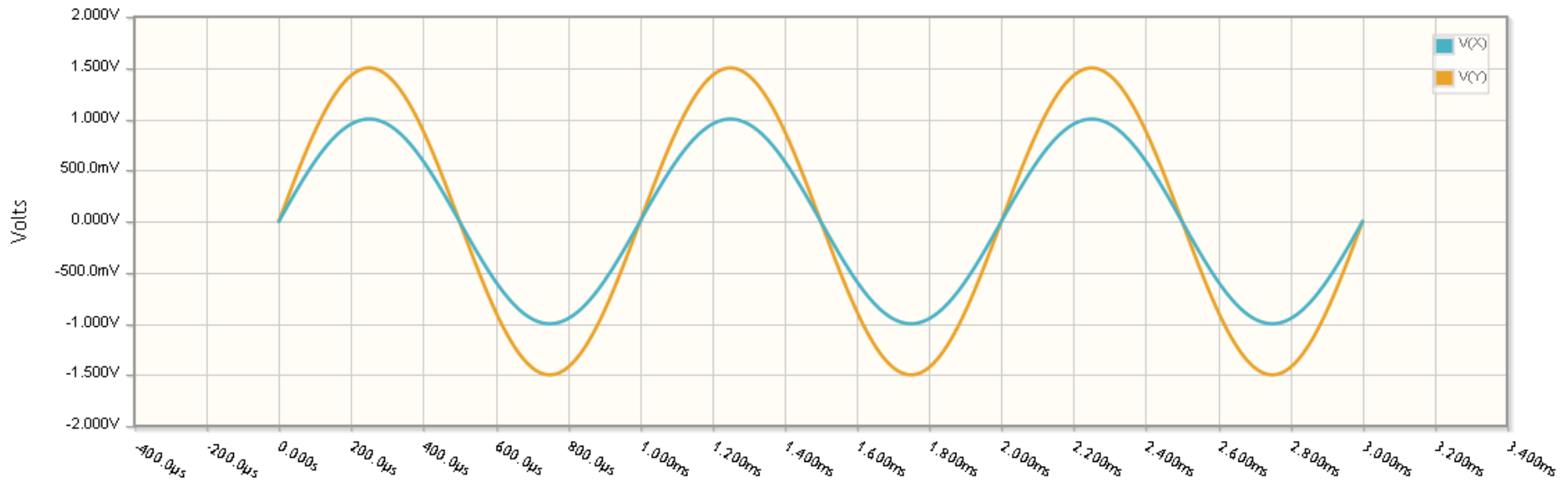Running a simulation for 3ms (3 cycles) gives the following result.



Note the following:

- The output is 1.5x the input ($Y = 1.5 X$)
 - They are in phase (the gain is positive)
 - A sine wave is used to show that the gain of 1.5 works from -1V to +1V
-


Non-Inverting Summing Amplifier:

Design a circuit to mix Katy Perry, Iron Butterfly, and Enya

$$Y = 3A + 4B + 5C$$


Rewrite this as

$$Y = \frac{3A+4B+5C}{12} \cdot 12$$

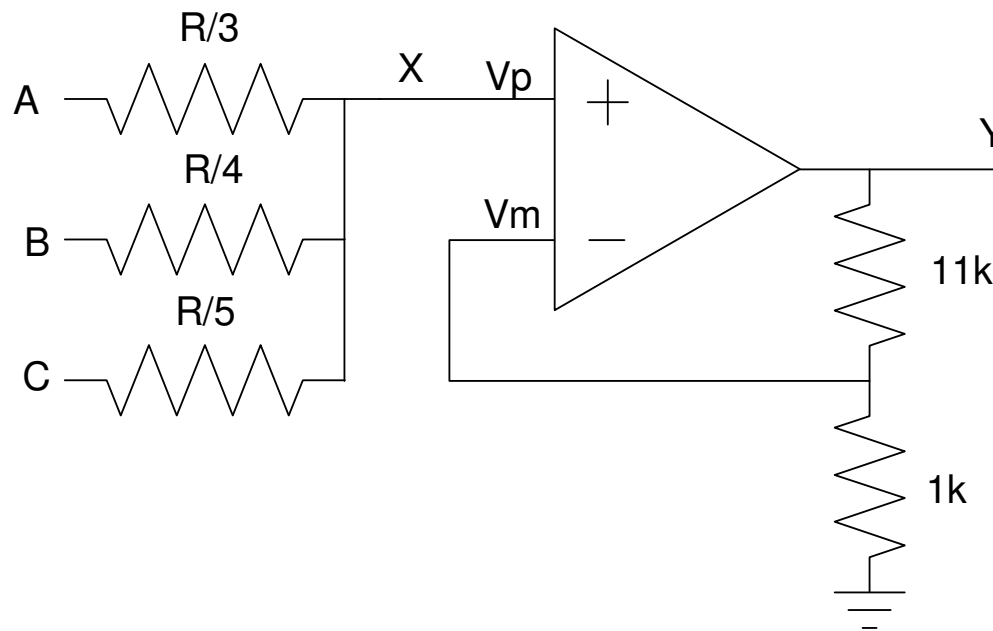

Checking in CircuitLab: Use three inputs

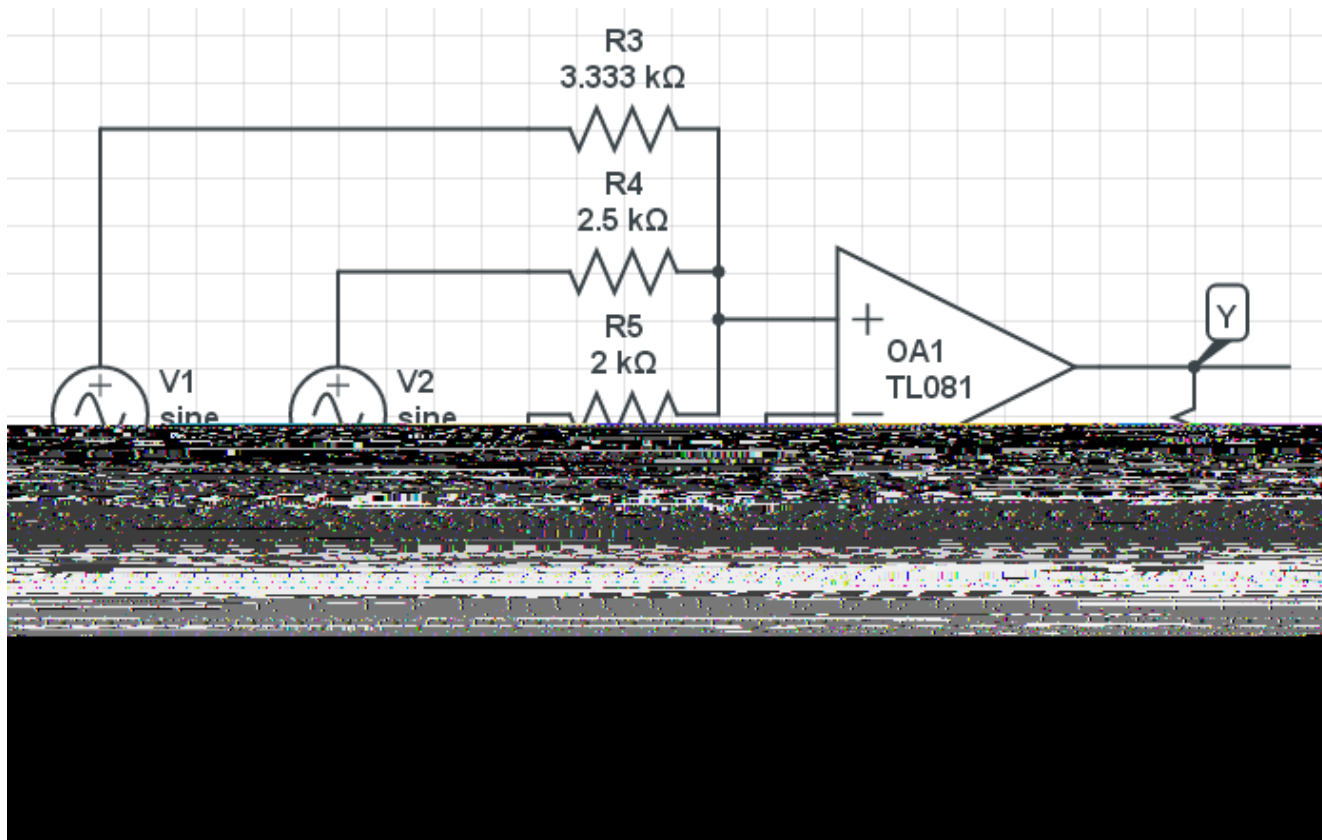- 1V @ 1kHz
- 1V @ 10kHz (10x different so you can see the difference at Y)
- 0V (getting too many signals to see what's going on)



Running a time-domain simulation for 3ms (3 cycles)

Here, you can see

- The 1kHz sine wave (envelope), mixed with
- A 10kHz sine wave.

Inverting Amplifier

3 nodes: Need 3 equations for 3 unknowns


$$V_p = 0$$

$$V_m = V_p = 0$$

$$\frac{V_m - V_{in}}{R_2} + \frac{V_m - V_o}{R_1} = 0$$

Solving:


$$V_o = -\frac{R_1}{R_2} V_{in}$$

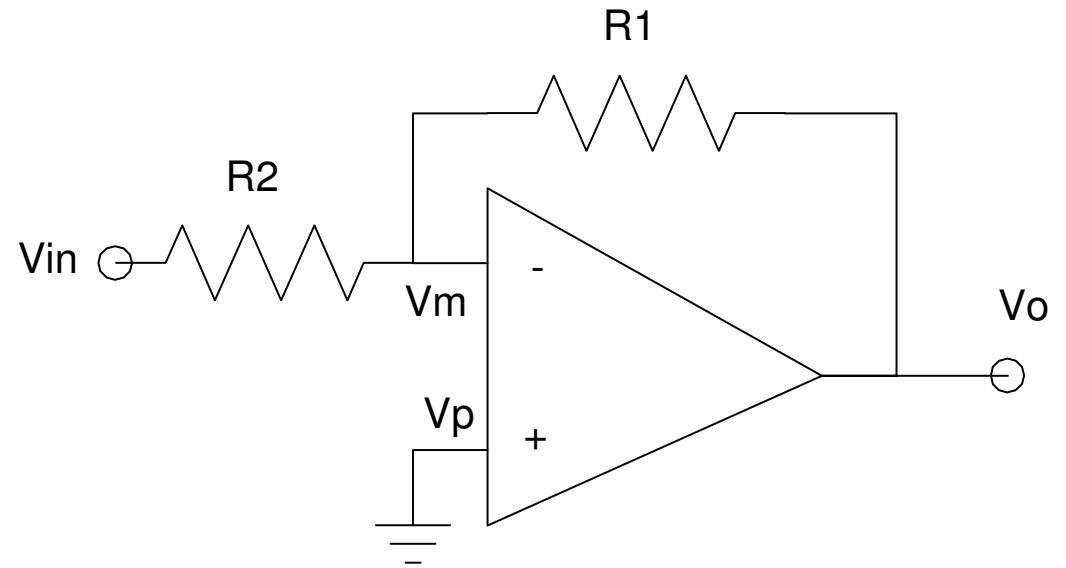

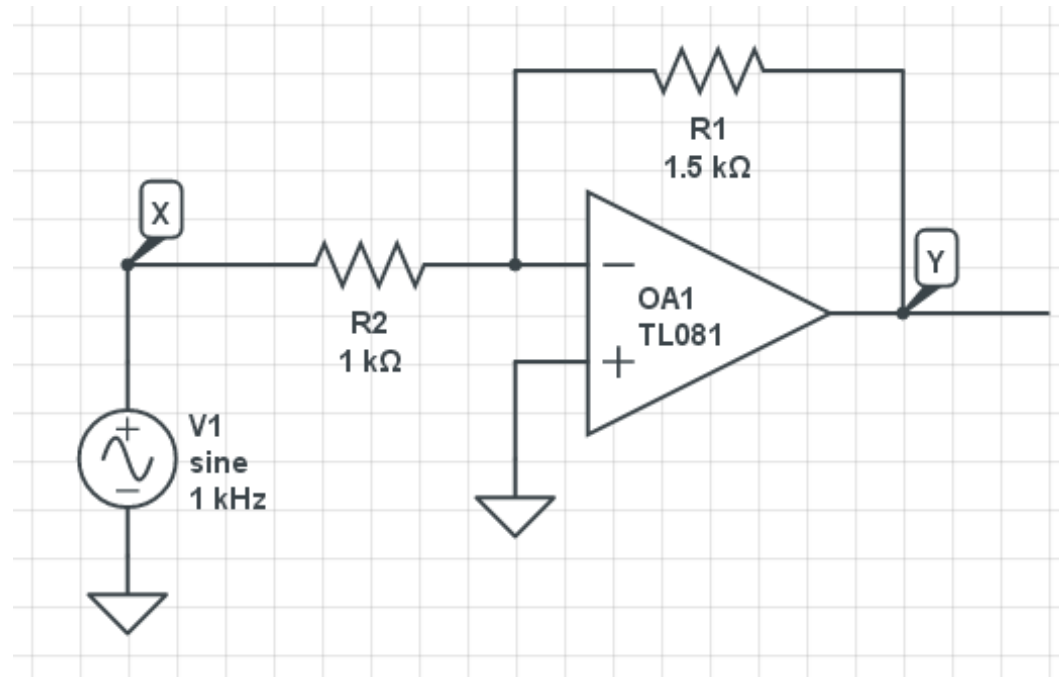
Example: Design a circuit with a gain of

$$y = -1.5x$$

Solution: Let $R1 = 1500$ and $R2 = 1000$ Ohms.



Simulation Results:

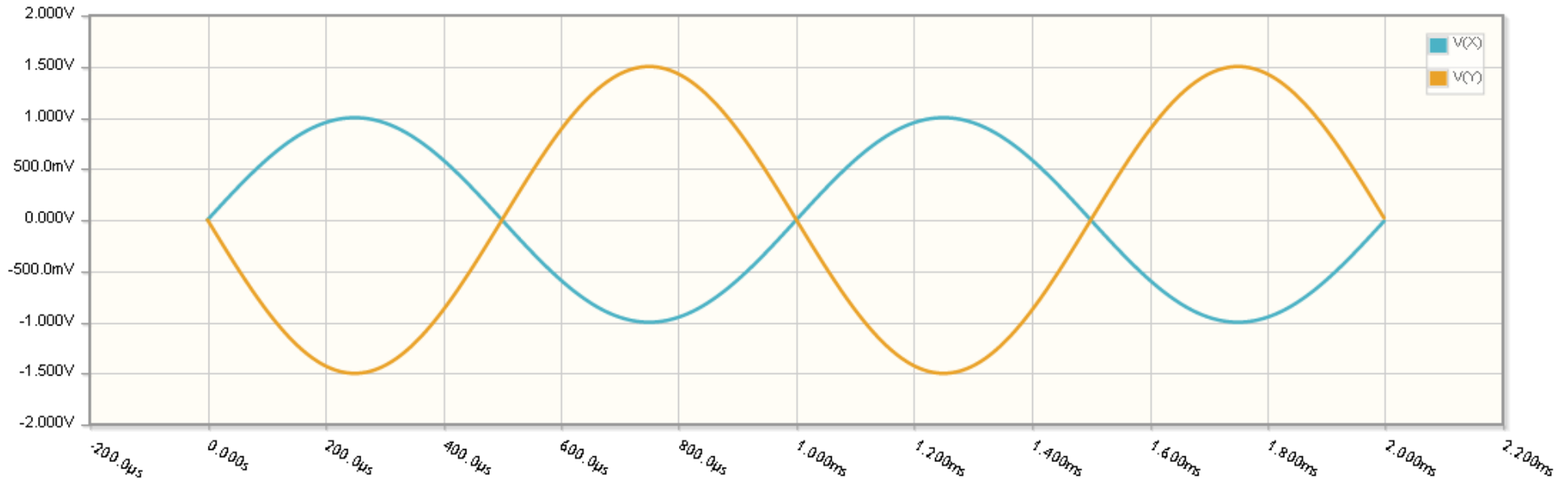

Note the following:

- The amplitude of Y is 1.5x the amplitude of X (as desired)
- Y is 180 degrees out of phase from X (the gain is -1.5)

Summing Inverting Amplifier:

A slight variation is the summing amplifier


$$V_p = 0$$

$$V_m = V_p = 0$$

$$\frac{V_m - V_a}{R_a} + \frac{V_m - V_b}{R_b} + \frac{V_m - V_o}{R_1} = 0$$

Solving:
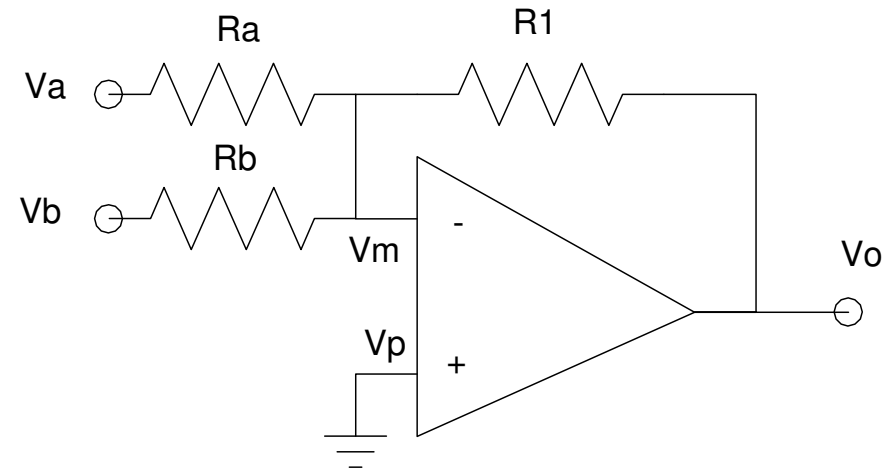
$$V_o = -\frac{R_1}{R_a} V_a + -\frac{R_1}{R_b} V_b$$



Instrumentation Amplifier:

3 Nodes: Need 3 equations for 3 unknowns


$$V_p = V_m$$

$$\frac{V_p - A}{R_2} + \frac{V_p}{R_1} = 0$$

$$\frac{V_m - B}{R_2} + \frac{V_m - Y}{R_1} = 0$$

Solving gives

$$Y = \frac{R_1}{R_2} (A - B)$$

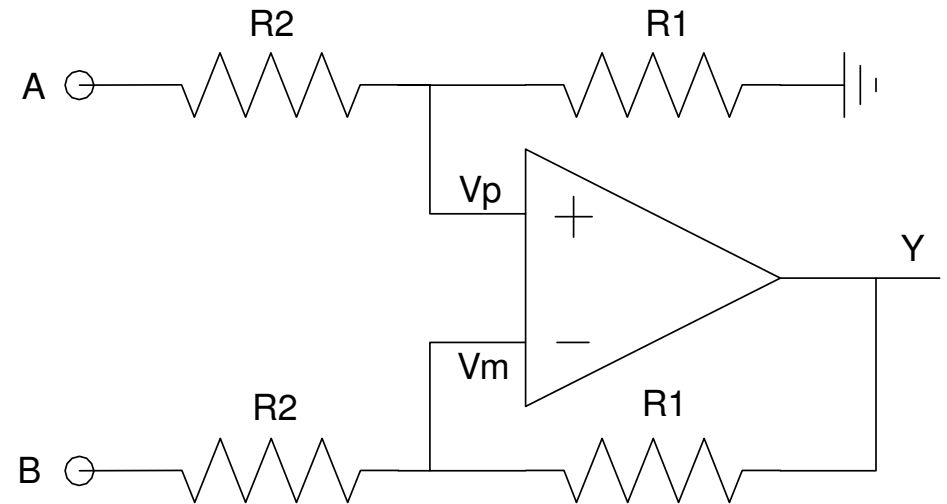


Example: Implement

$$Y = 10X - 4$$

Rewrite as

$$Y = 10(X - 0.4)$$

$$Y = \frac{R_1}{R_2} (A - B)$$

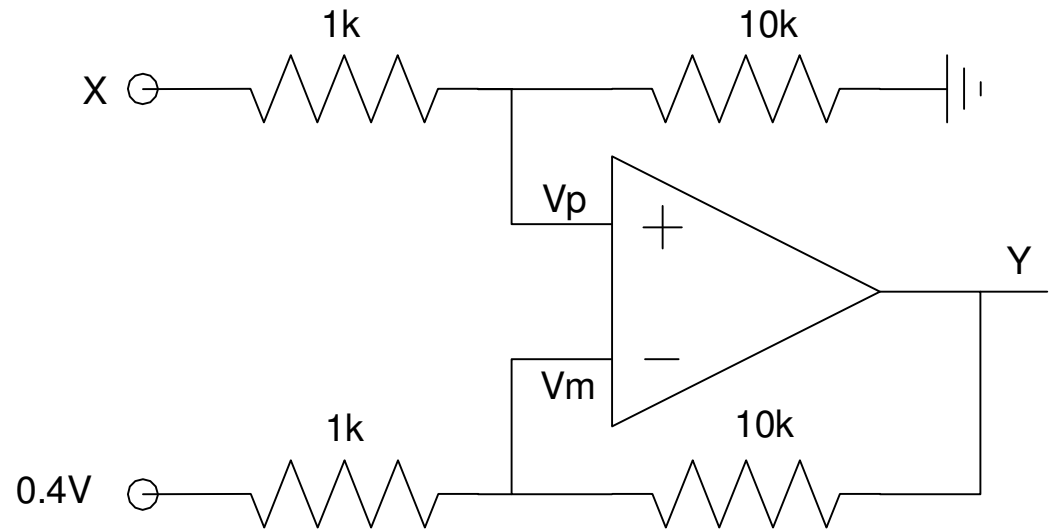

With this circuit, you can implement almost any function.
