
Push Pull Amplifiers

ECE 321: Electronics II


Lecture #3

Please visit [Bison Academy](#) for corresponding lecture notes, homework sets, and solutions

Class-A Amplifiers

Bias the transistors in the active region

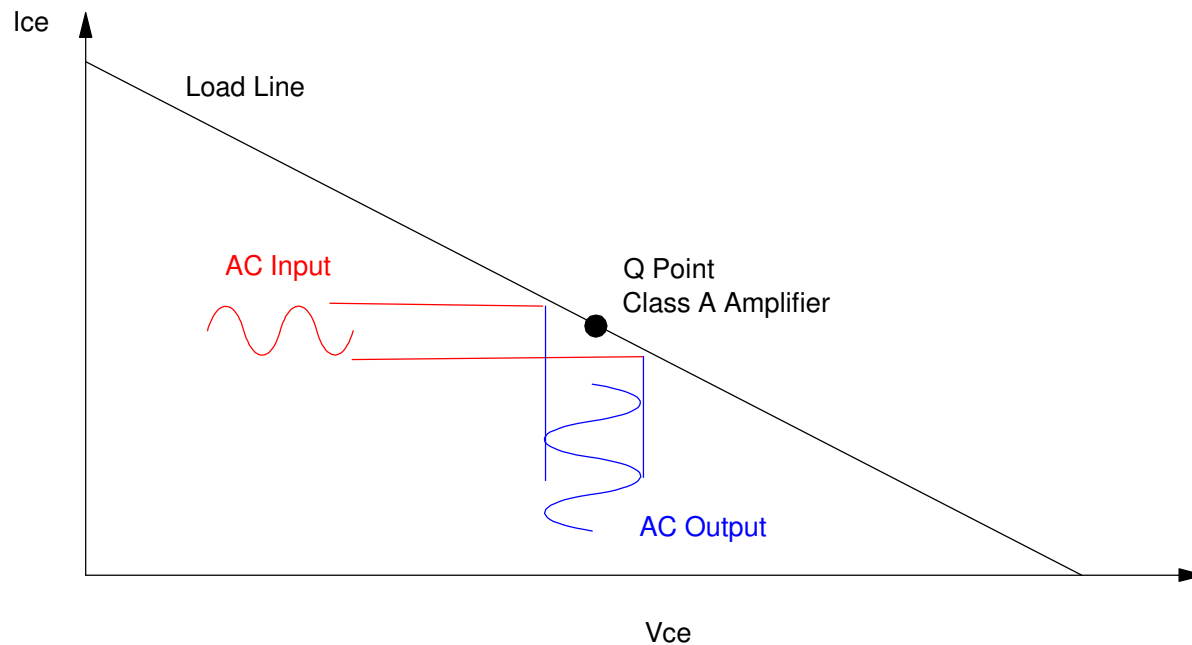
- Results in a large power drain even when there is no audio signal



Class-B Amplifiers (Push-Pull)

Biases the transistor so that it is off when there is no AC input.

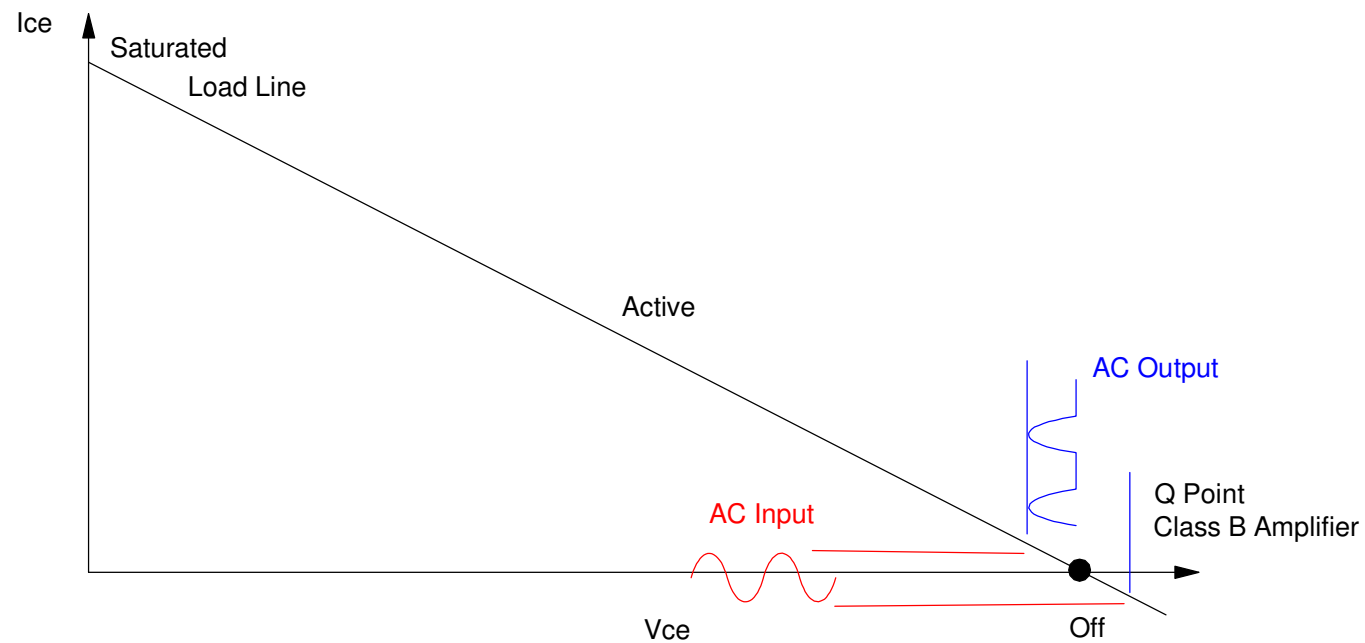- Less power consumption for small signals
- Results in clipping



Example: Drive an 8-Ohm Speaker

Input:

- 0..10V analog signal
- Capable of 20mA (i.e. a function generator)

Output:

- 8 Ohm speaker

Relationship:


- $Y = X$

Option 1: Use an op-amp capable of 1.25A

- OPA2544: \$18 each
- AMT 30A8T: \$200 each

Option 2: Use a push-pull amplifier

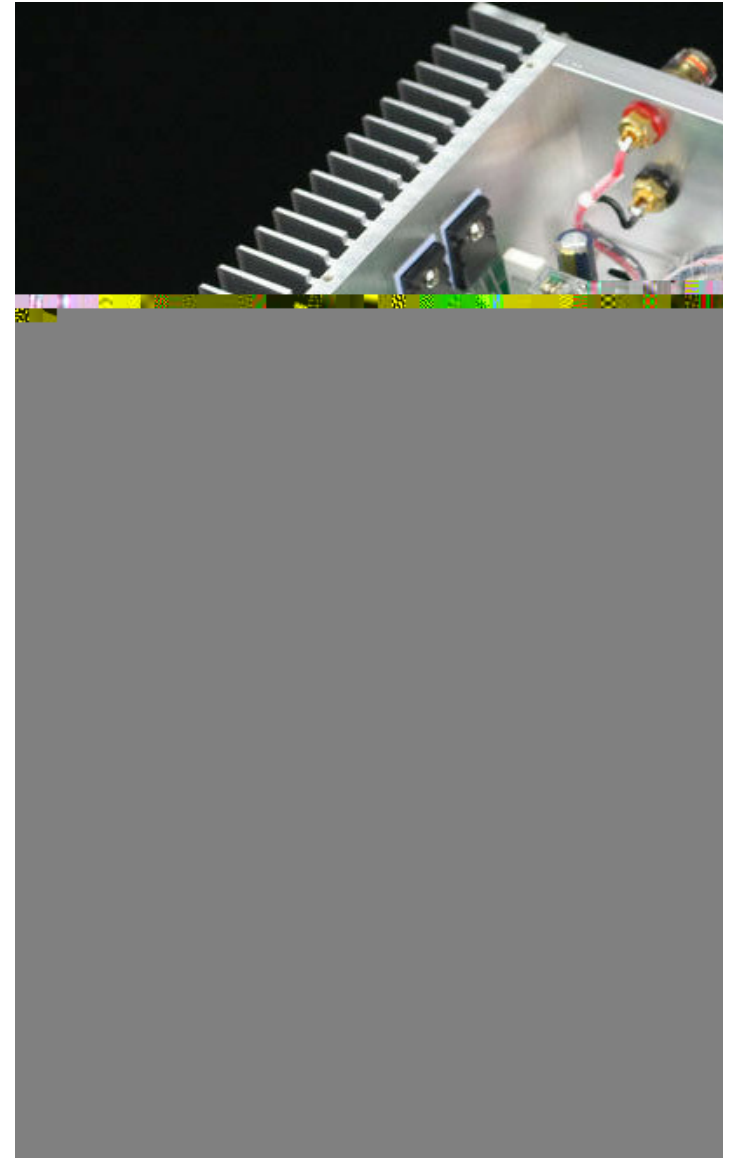- TIP112 or 6411 (NPN)
- TIP117 (PNP)
- \$1 solution





Solution (push):



- Use a transistor to amplify the current
- Place the load at the emitter

What this does is

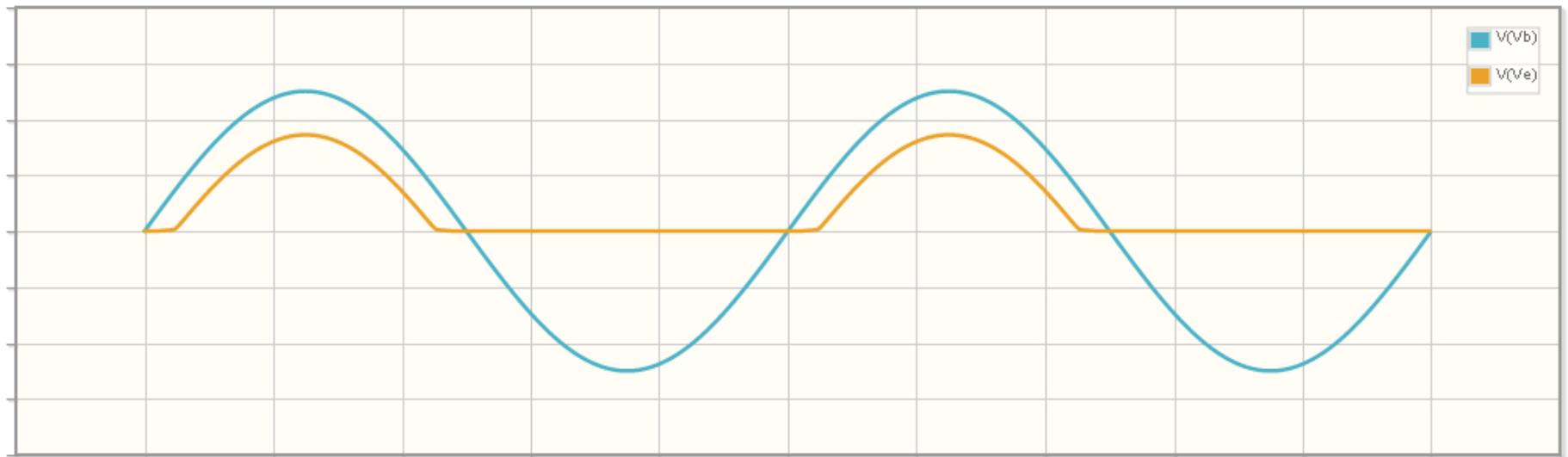
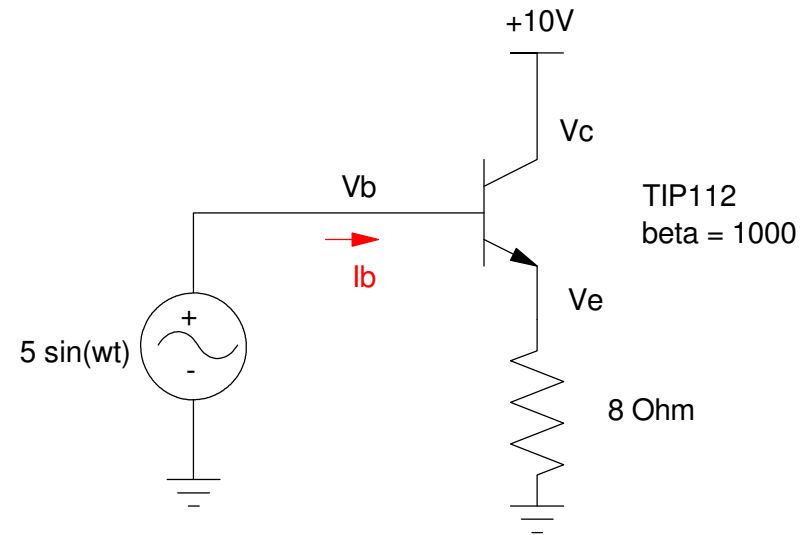
- When $V_b > 0$, V_e follows V_b
- When $V_b < 0$, the diode turns off and $V_e = 0$.



Solution: Push-Pull

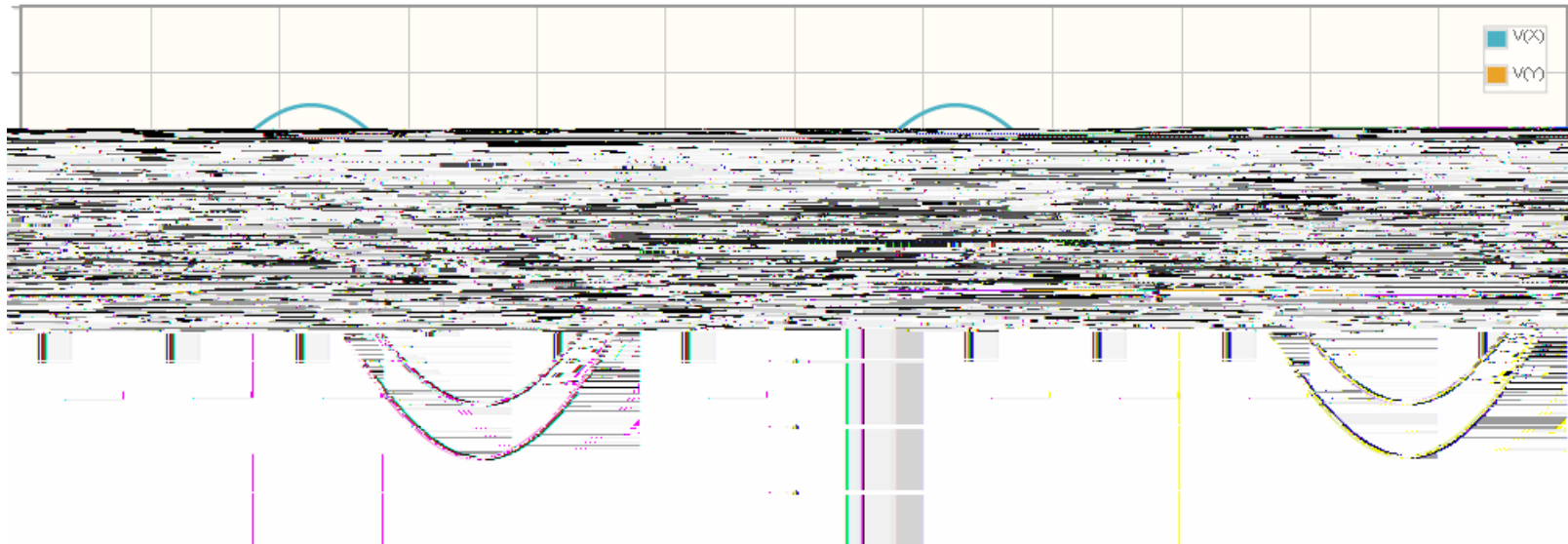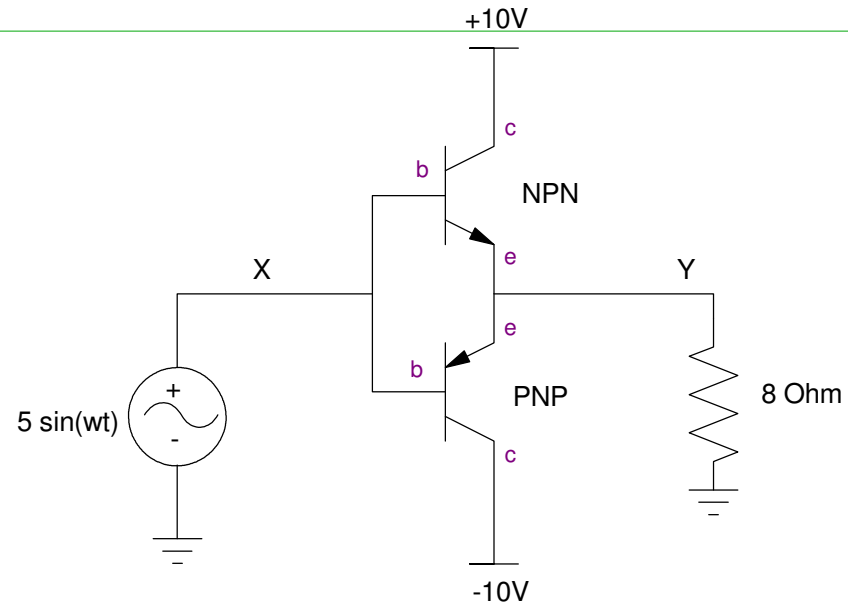

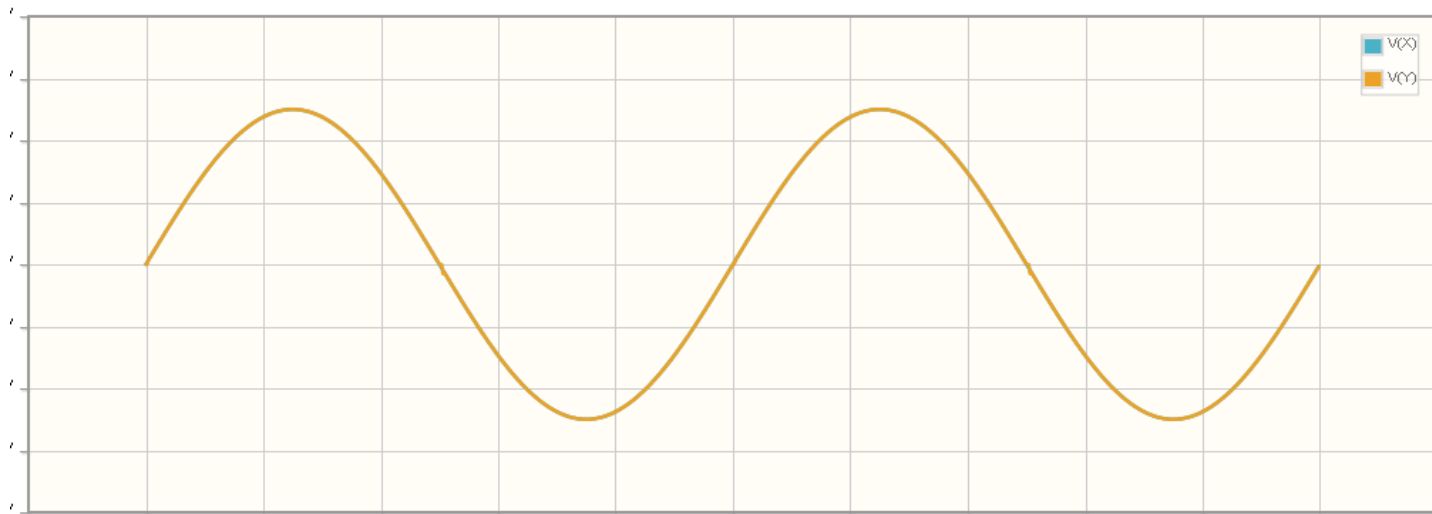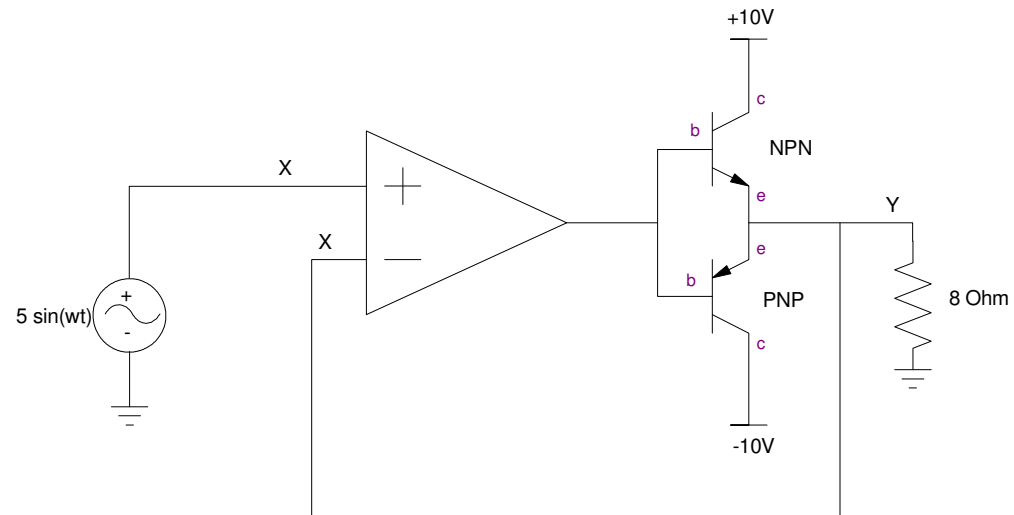Solution: Remove the cross-over distortion




Result: Power Amplifier

Voltage: Assume $X = 8V$

$$Y = X$$

Current:

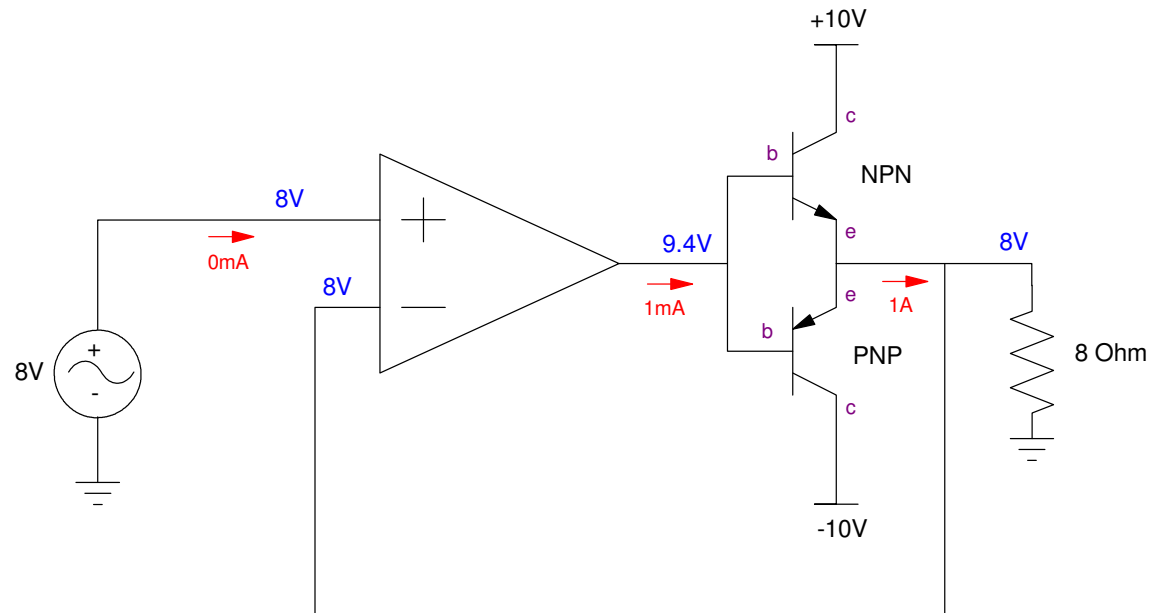
- $I_3 = 1.00A$ ($8V$ @ 8 Ohms)
- $I_2 = 1.00\text{ mA}$ ($\beta = 1000$)
- $I_1 = 0.00\text{ mA}$ (ideal op amp)



Variation: Voltage Output


For DC motors, voltage is speed (approximately).
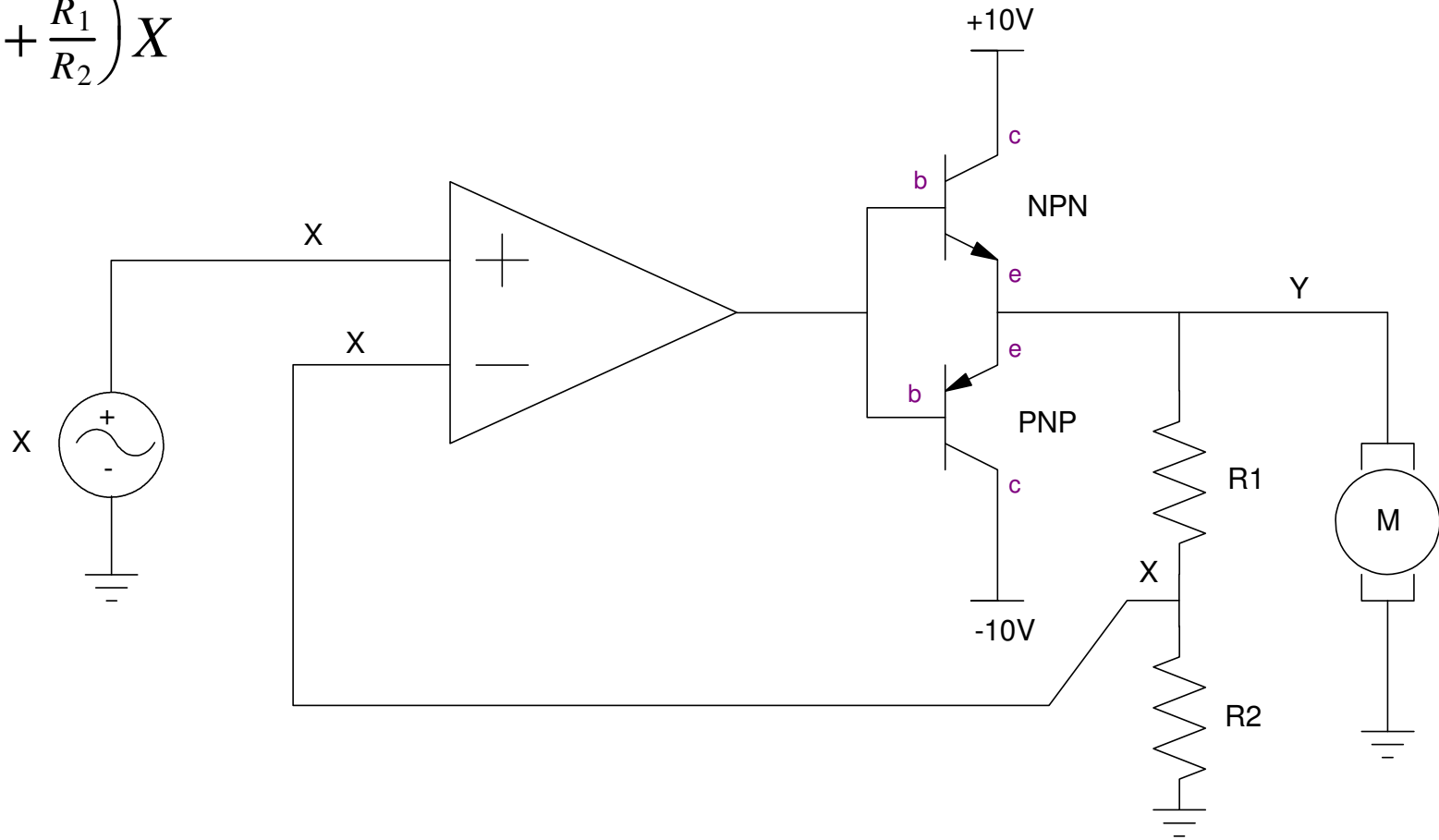
$$Y = \left(1 + \frac{R_1}{R_2}\right) X$$




Handout: Determine the voltages and currents

- $|V_{be}| = 0.7V$
- $\beta = 300$

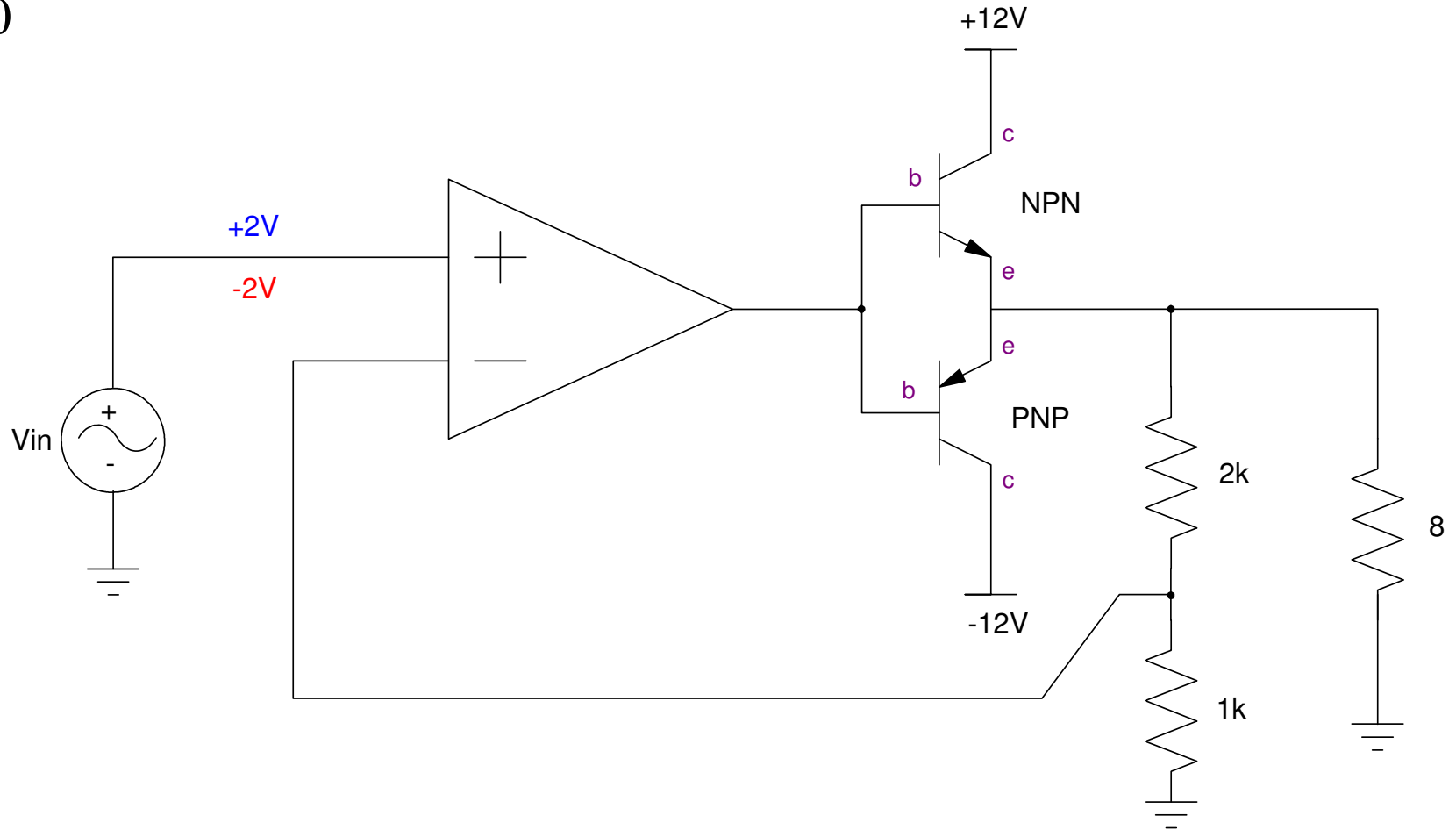

Solution

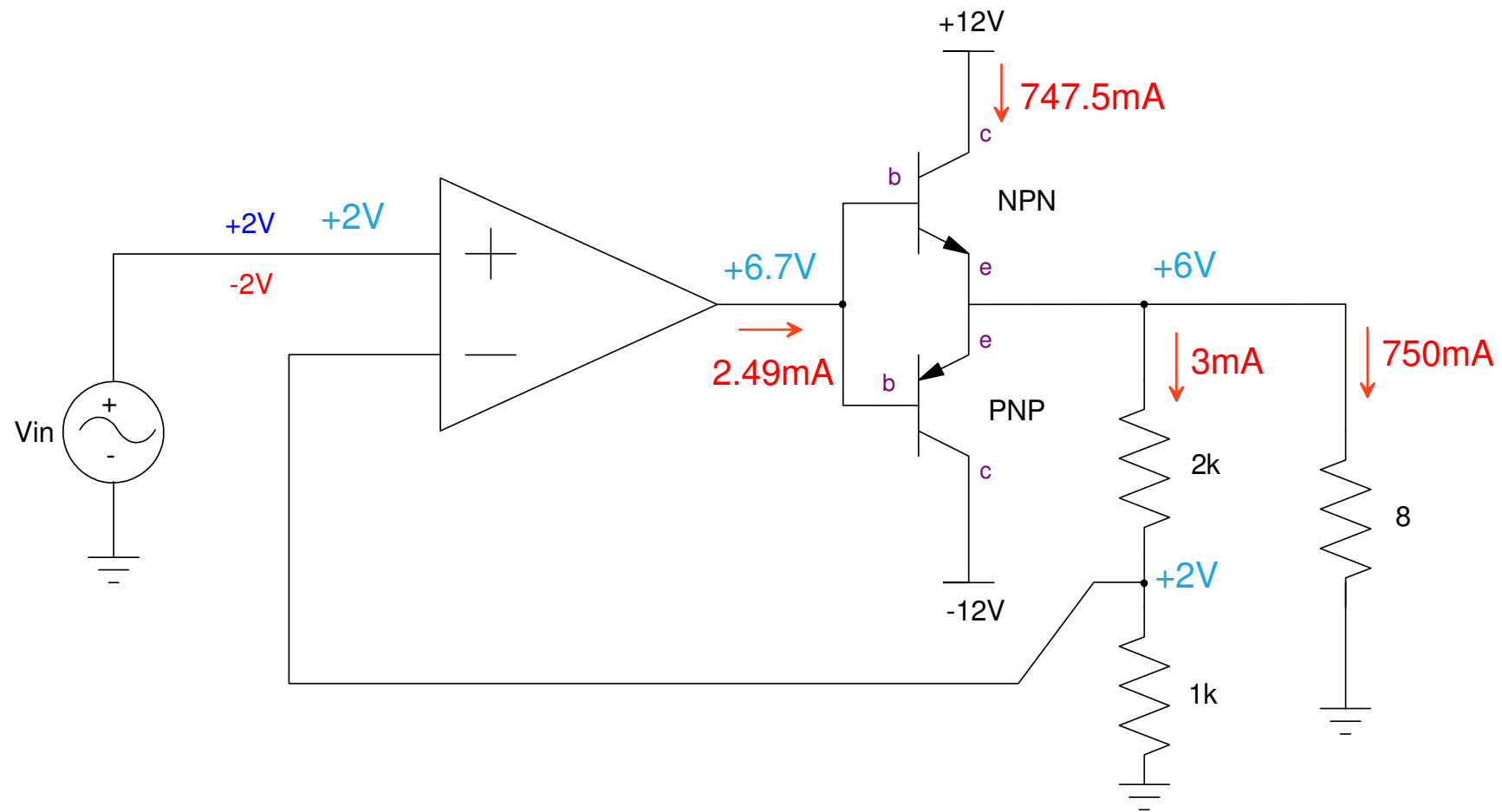


Variation: Current Output


For DC motors, current is torque.


For LED's, current is brightness.

$$I_m = \frac{X}{1\Omega}$$

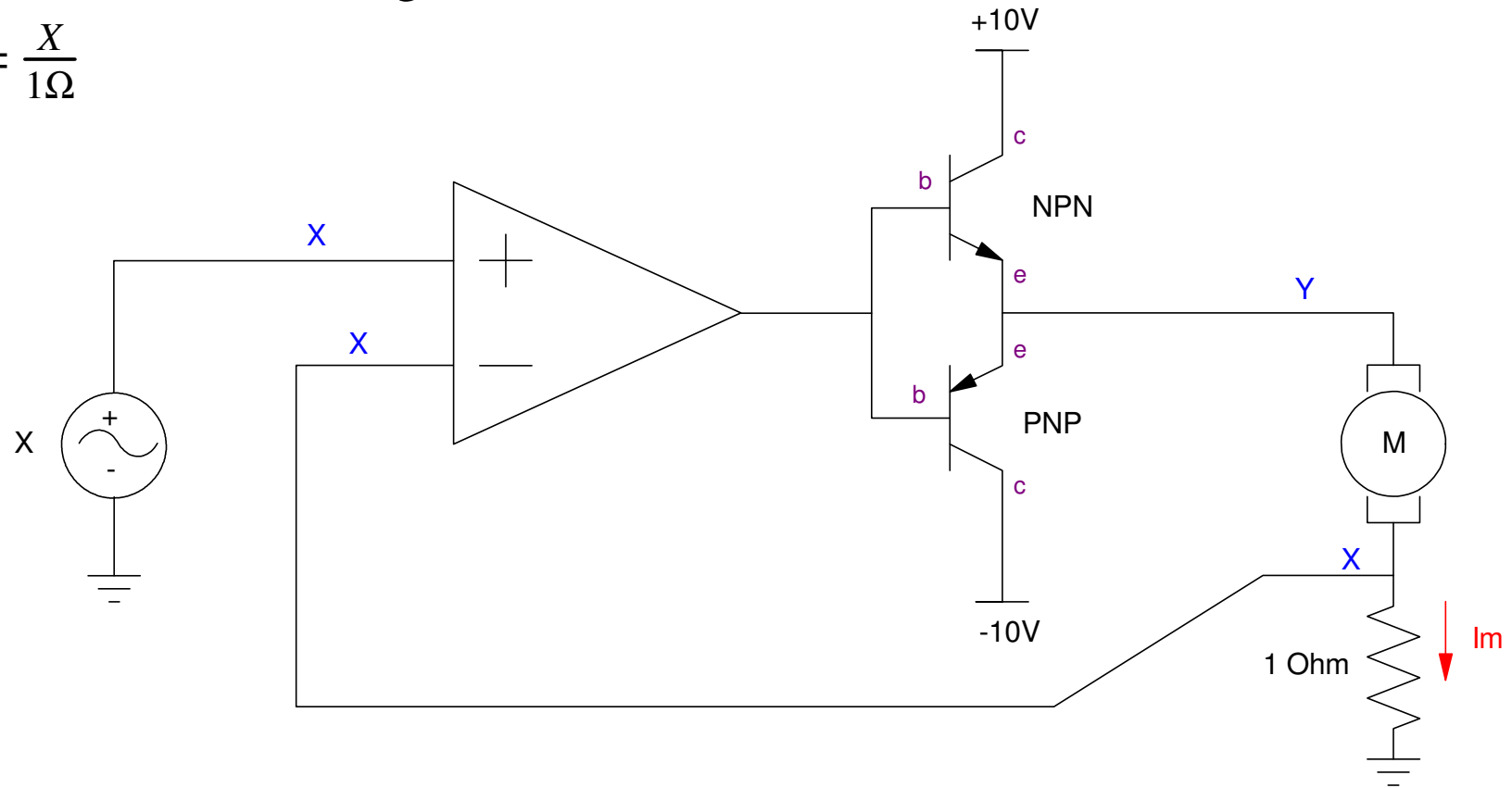

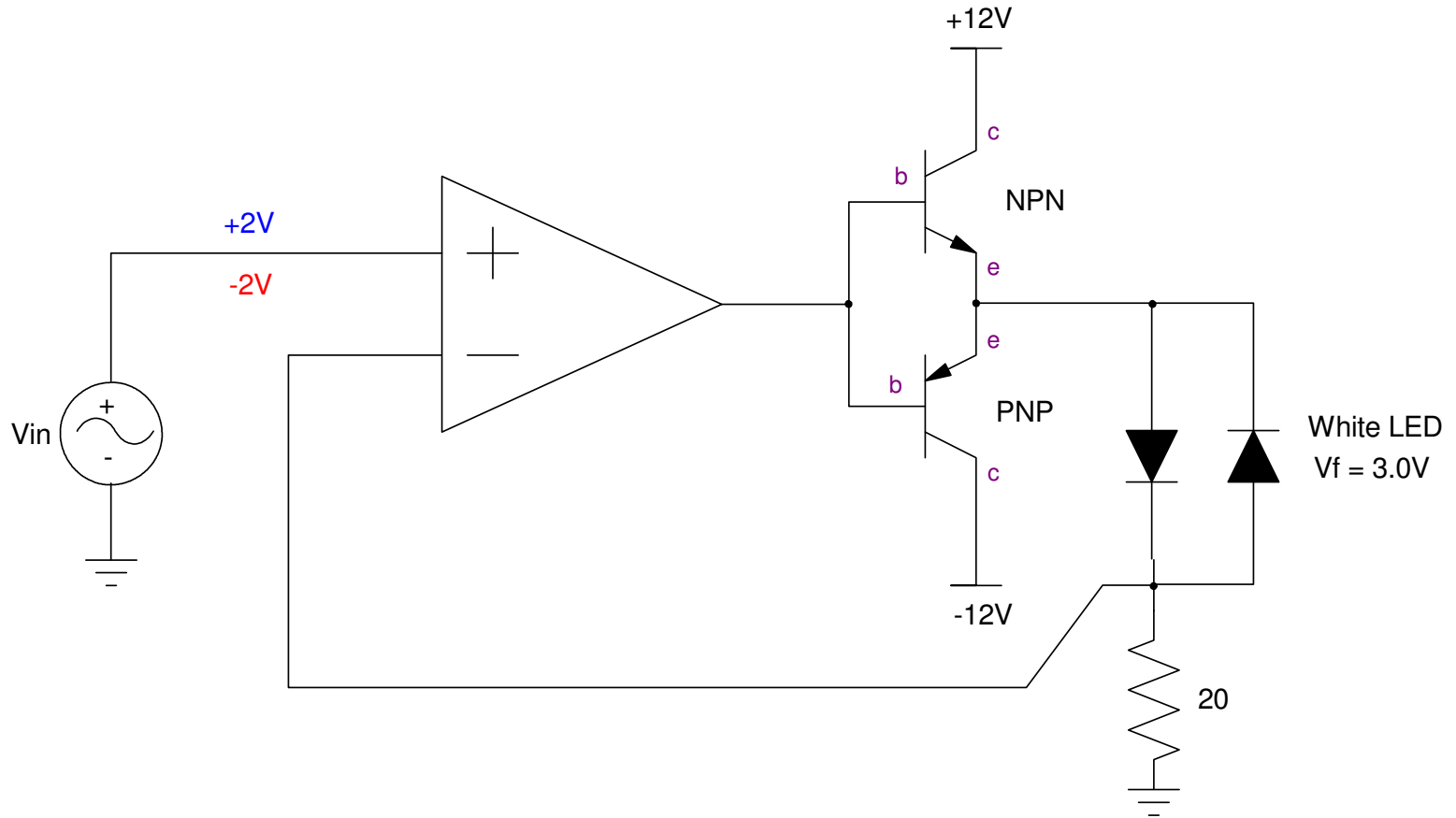
Handout: Determine the voltages and currents



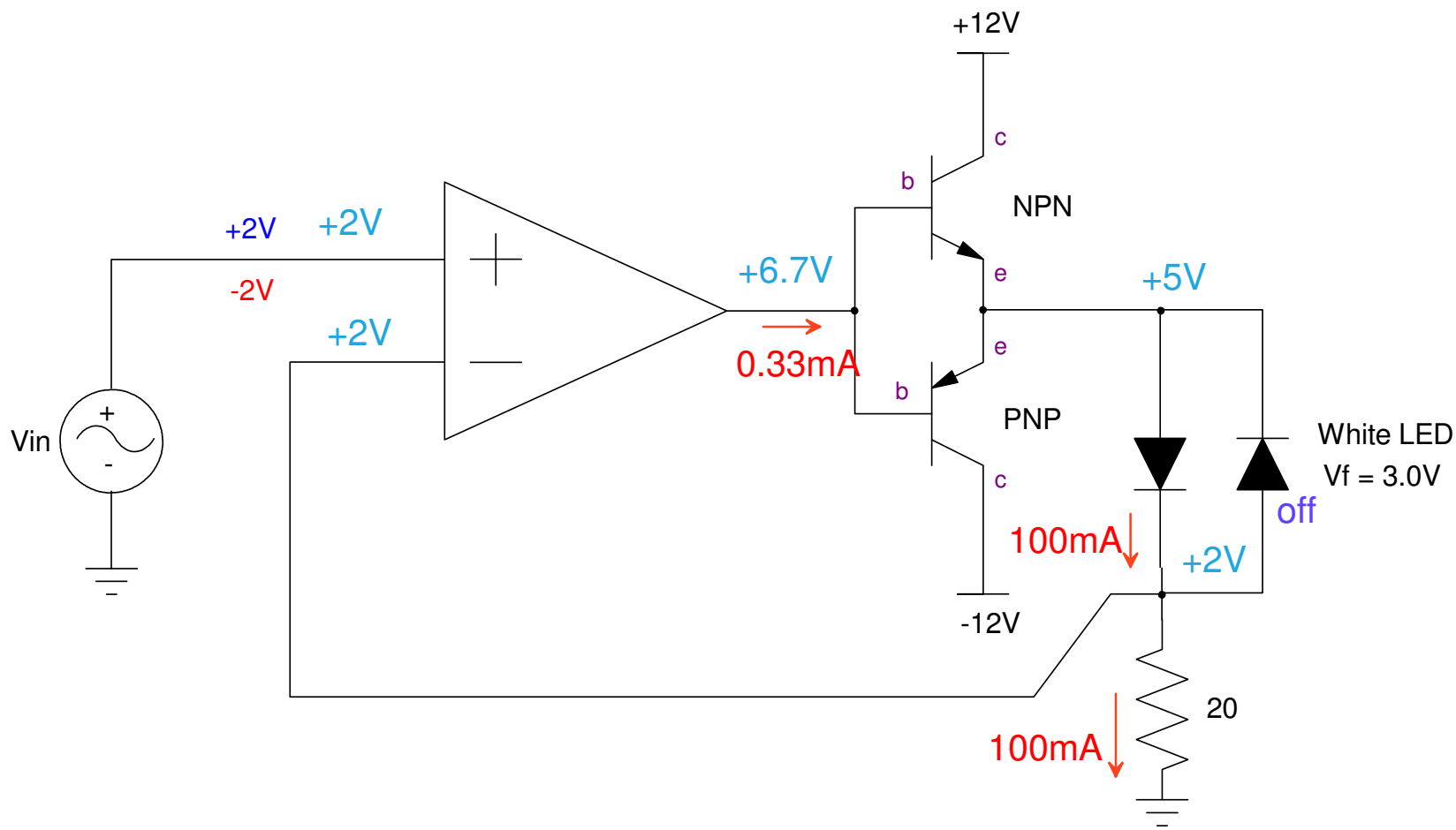


Variation: Single Sided Supply

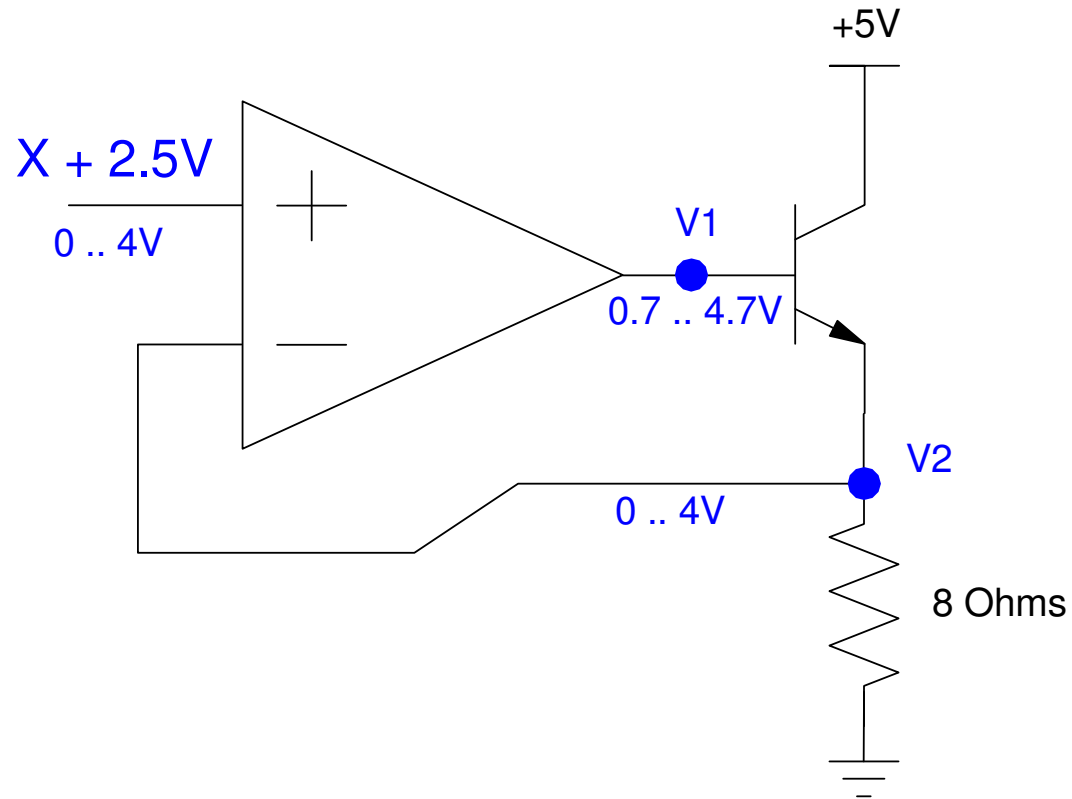- 0 .. +4V Out
- Class A Amplifier (inefficient)




Handout: Determine the voltages and Currents

- $V1 = 2.8V$ (circuit ground + $0.3V$)

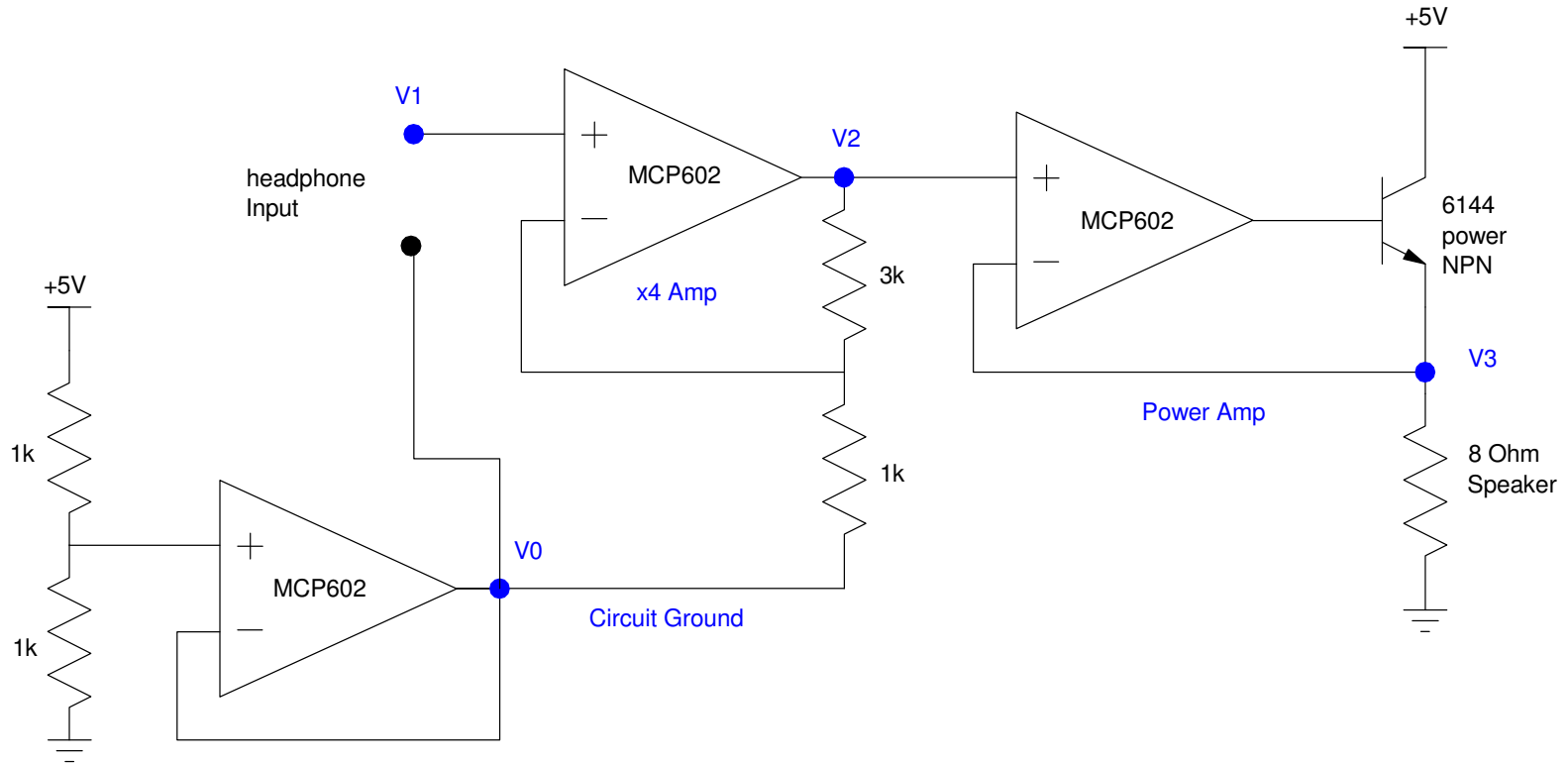


Solution

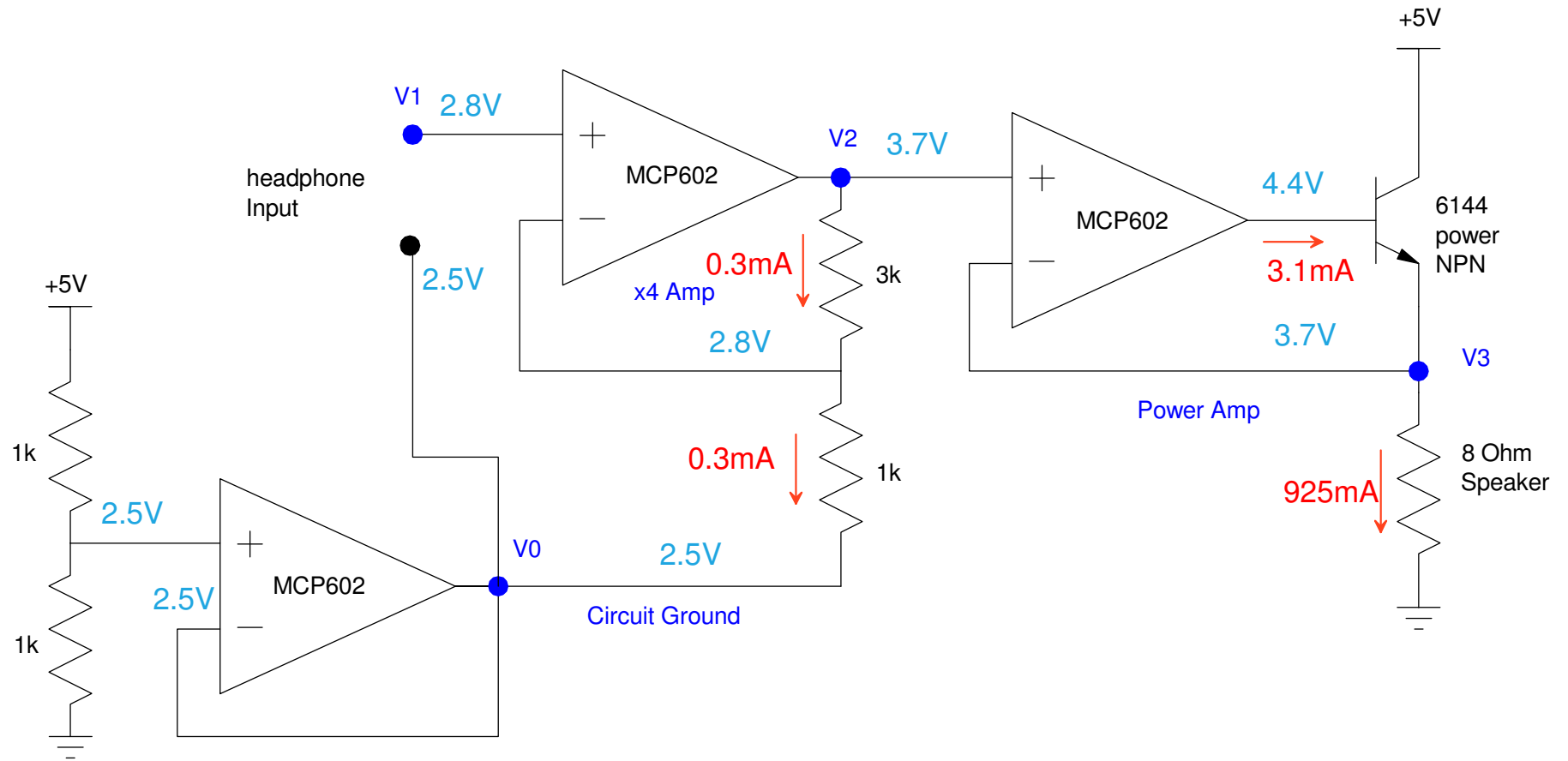


Variation: Single-Sided Supply

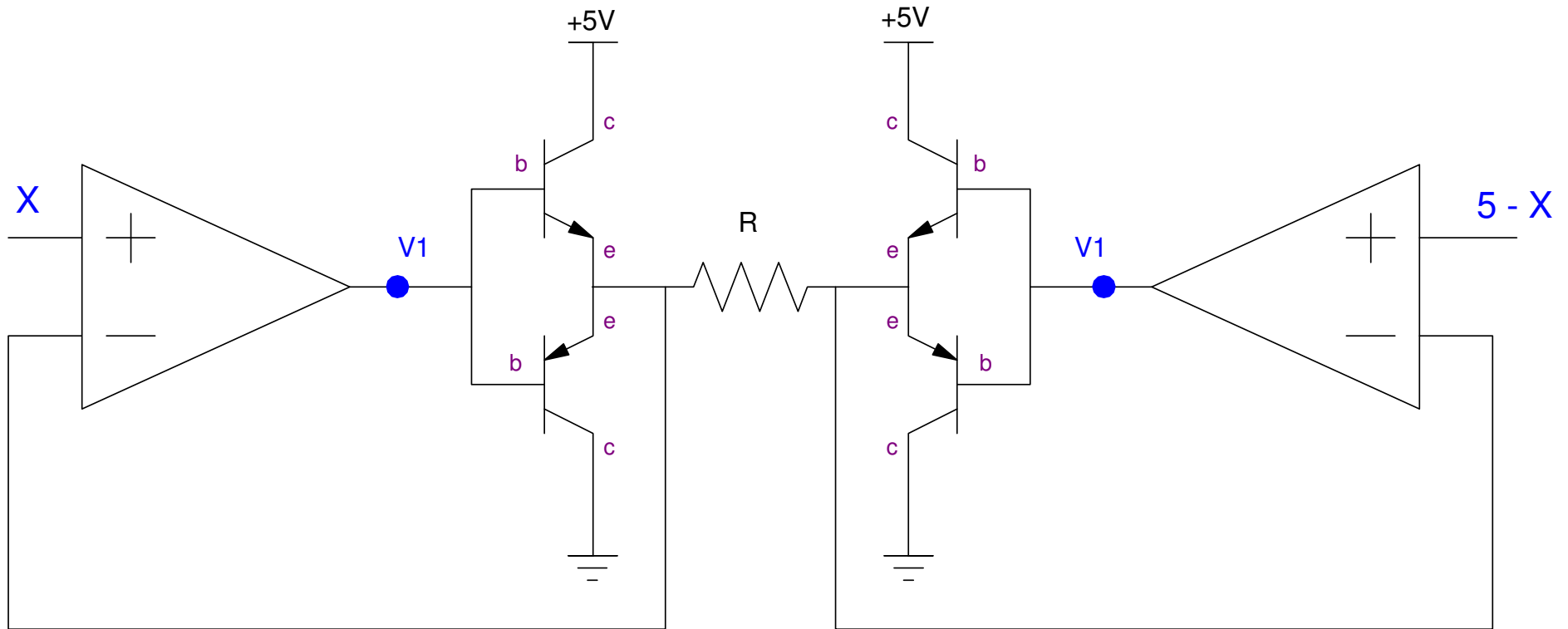
- +3V .. -3V Out
- Class AB Amplifier (more efficient)



+3V Out

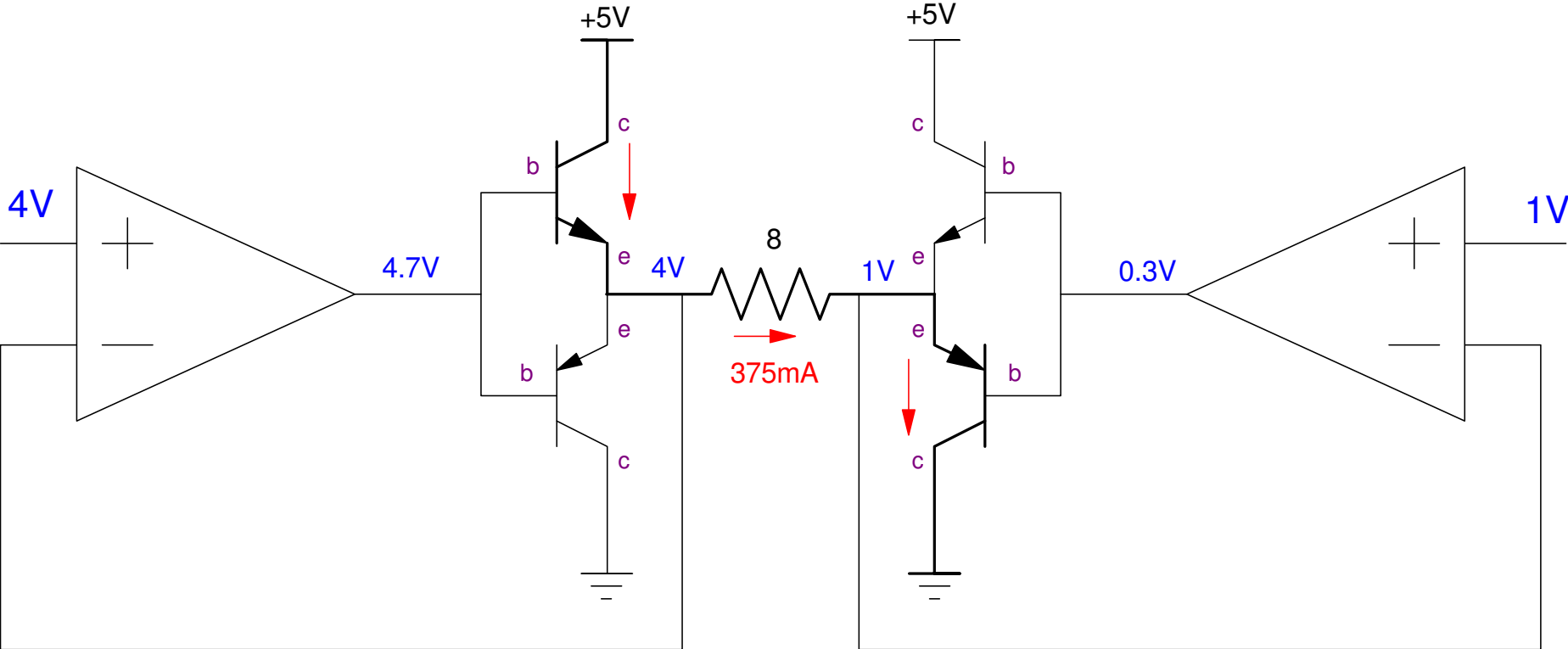

-3V Out

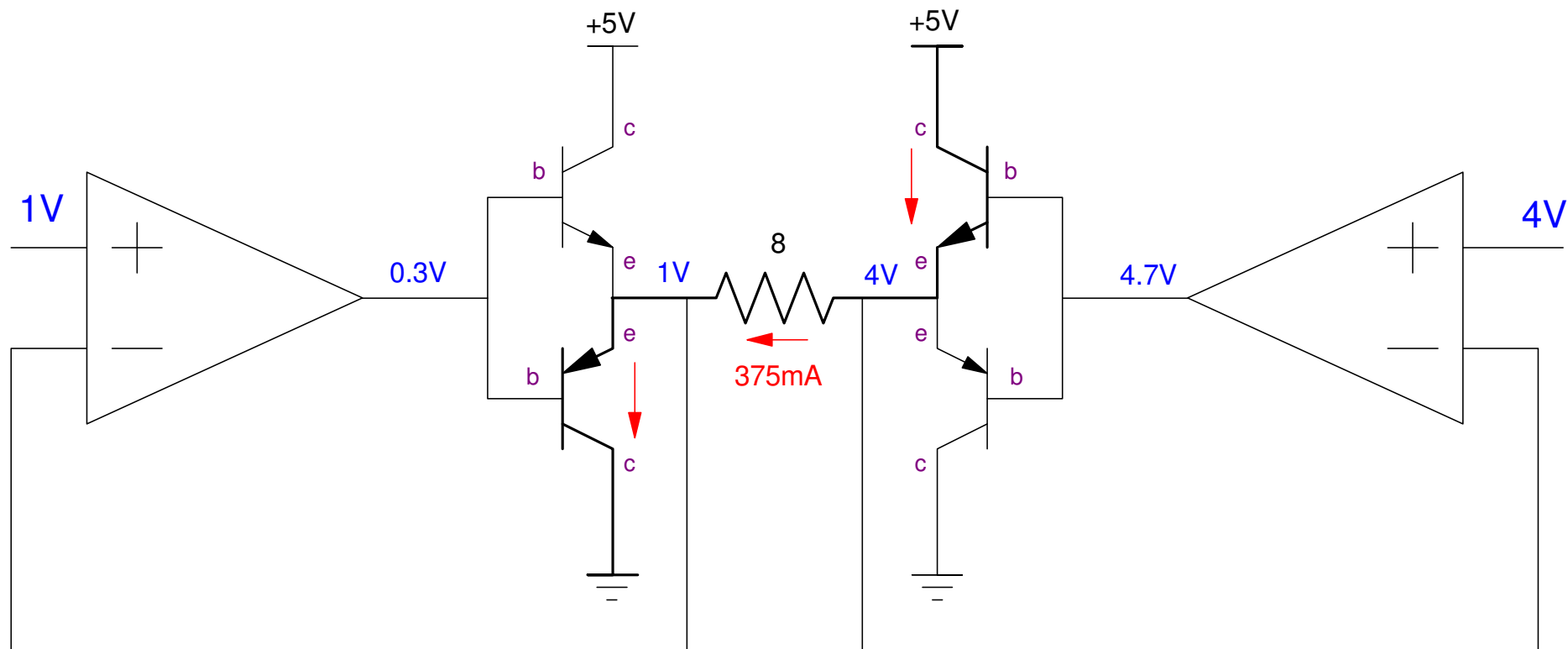

Summary

A push-pull amplifier allows an op-amp circuit to drive a low-impedance load

- DC motor
- Speaker

Voltage Amplifier:

- Drive a speaker
- Control the speed of a DC motor

Current Amplifier

- Drive a power LED
 - Control the torque of a DC motor
-

