

---

# **2-Port Models**

**ECE 321: Electronics II**

**Lecture #13:  
Jake Glower**

Please visit Bison Academy for corresponding  
lecture notes, homework sets, and solutions


---

# 2-Port Models

Generalized Thevenin Equivalent



Thevenin Equivalents

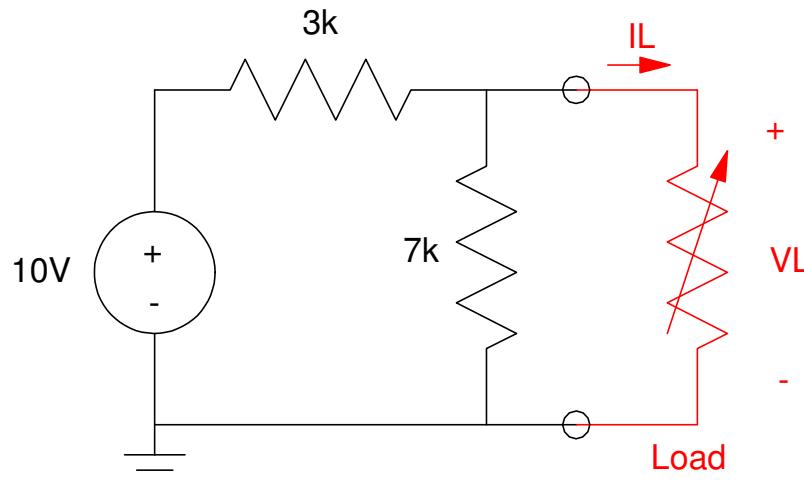- The output of a circuit follows a load line
- Any circuit with the same load line behaves the same
- The Thevenin Equivalent is the simplest circuit to obtain the same load line


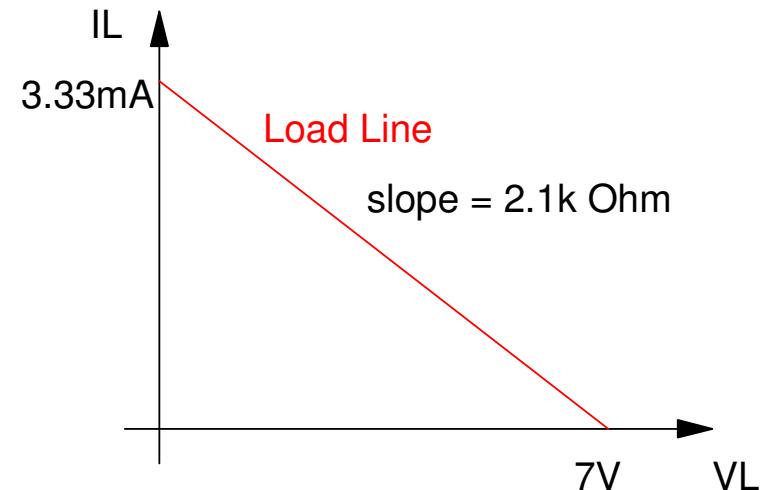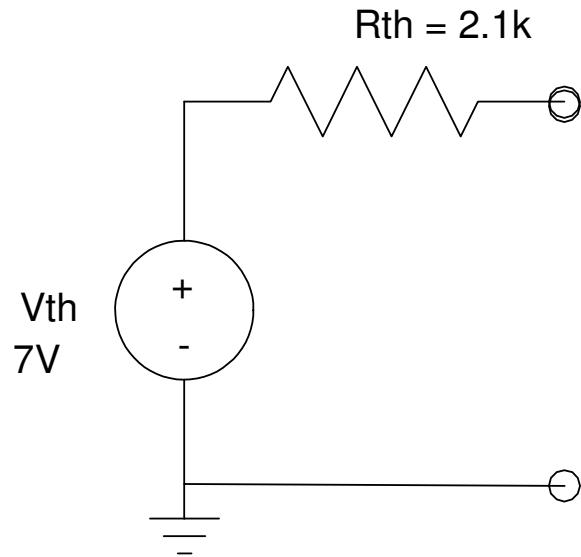
## Thevenin Example:

- $V_{th}$ : The voltage at the load with  $R_L = \text{infinity}$  (7V)
- $R_{th}$ : The resistance looking in with sources turned off:  $3\text{k}\parallel 7\text{k} = 2.1\text{k}$
- $I_{short}$ : The current  $I_L$  when  $R_L = 0$ .  $I_{short} = V_{th} / R_{th}$ :  $I_{short} = 10\text{V}/3\text{V} = 3.33\text{mA}$




Thevenin Equivalent for Previous Circuit along with its Load Line

## 2-Port Models

Thevenin equivalent for circuits with


- An input
- An output

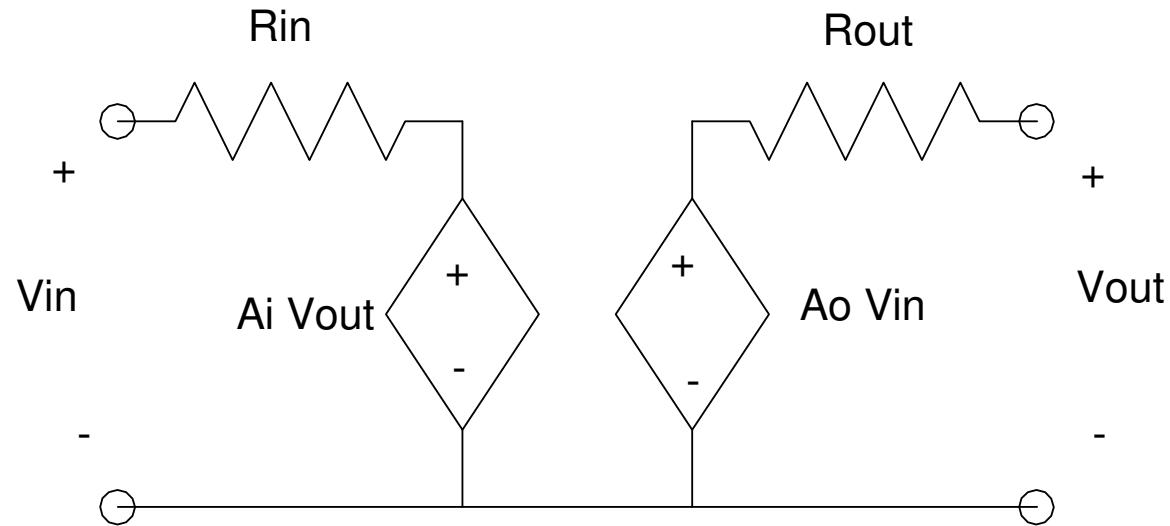
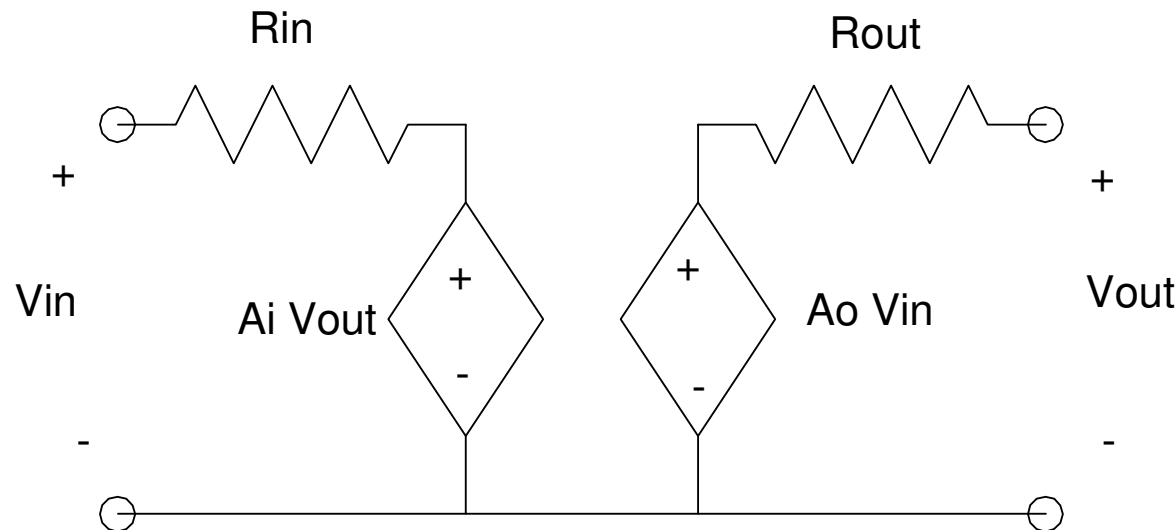
## 2-Port Parameters:


To determine each of the four 2-port model parameters, four tests are run:

- $A_i$ : Set  $V_{out} = 1V$  and measure  $V_{in}$ .  $A_i = V_{in}$
- $A_o$ : Set  $V_{in} = 1V$  and measure  $V_{out}$ .  $A_o = V_{out}$
- $R_{in}$ : Set  $V_{out} = 0V$  and measure the resistance seen at the input
- $R_{out}$ : Set  $V_{in} = 0V$  and measure the resistance seen at the output





---

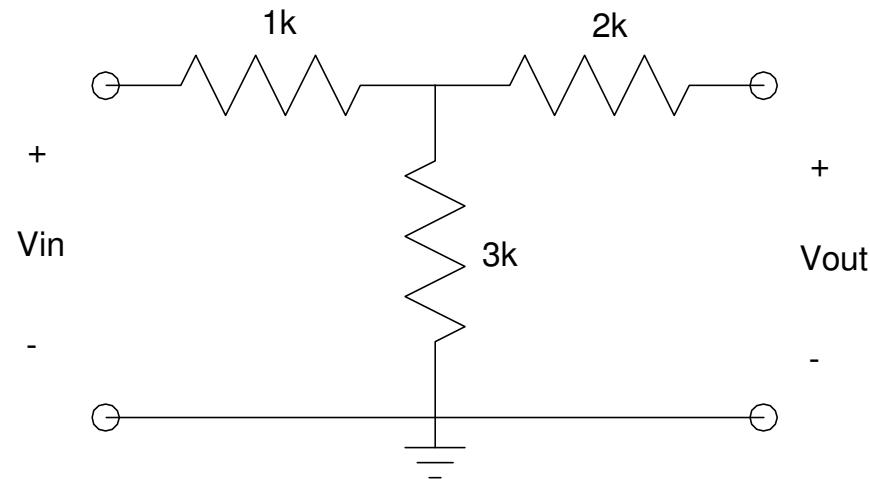Example: Determine the 2-port model for the following circuit:





**Ai:** Set  $V_{out} = 1V$ , measure the voltage at  $V_{in}$ .  $A_i = V_{in}$

- $A_i = 0.6$

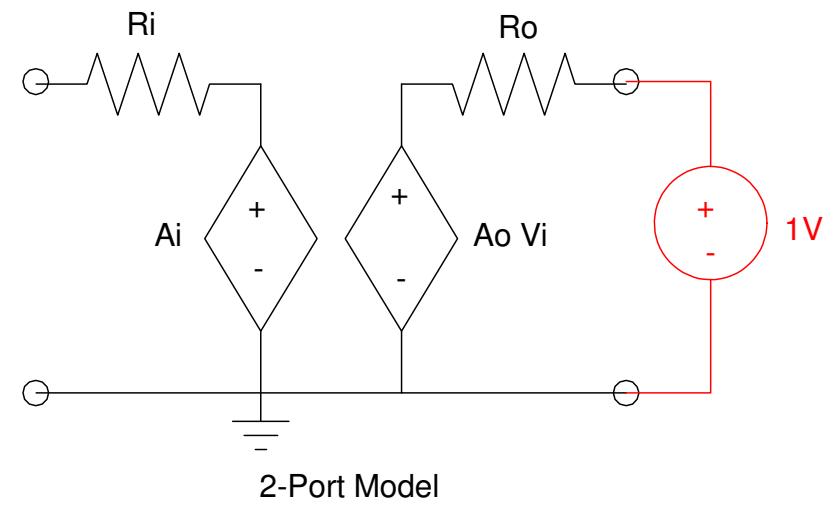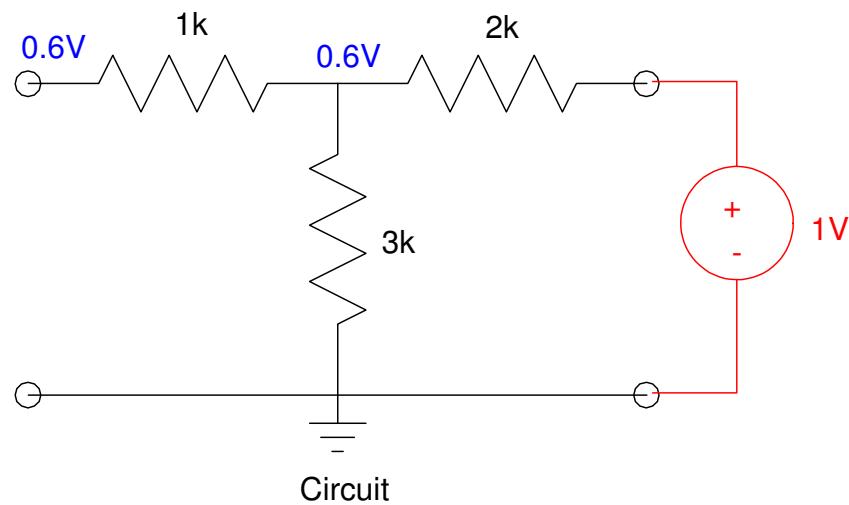



**Ao:** Set  $V_{in} = 0V$ , measure the voltage at  $V_{out}$ .  $A_o = V_{out}$

- $A_o = 0.75$

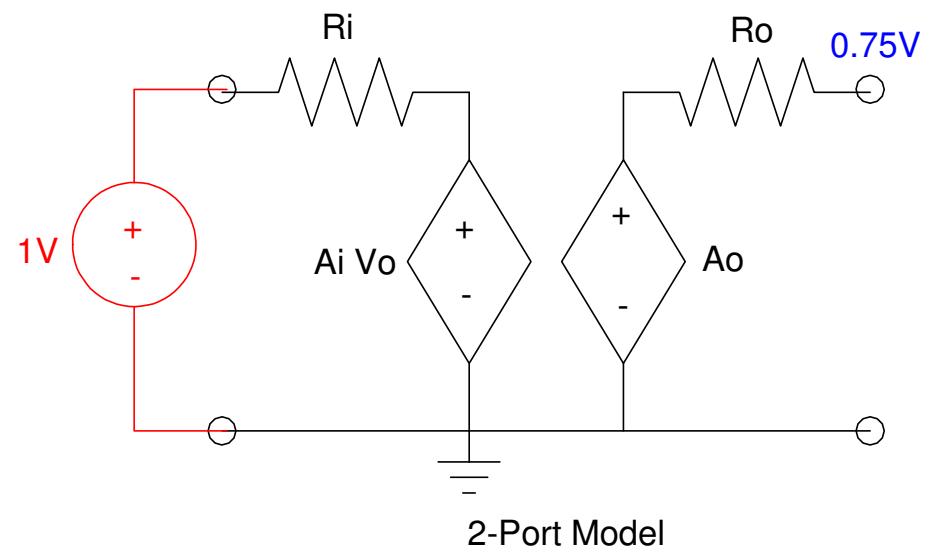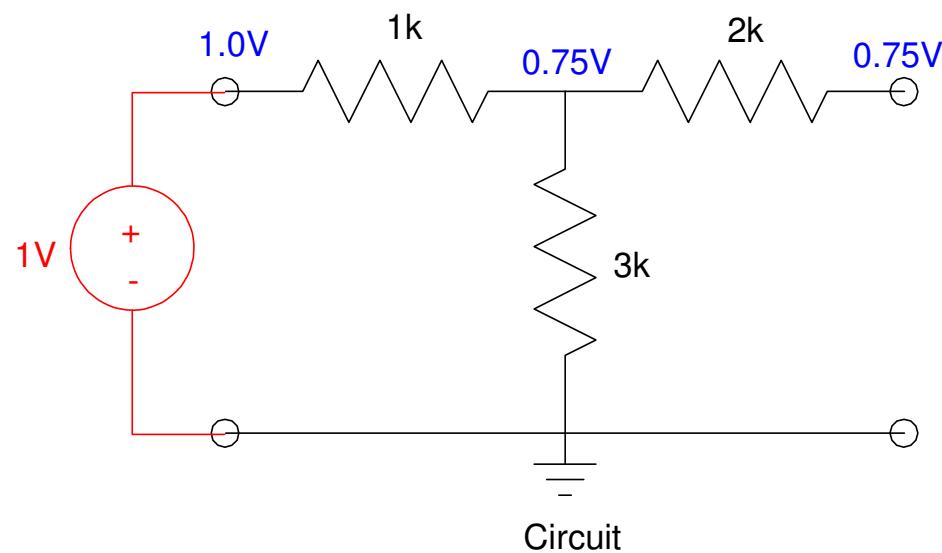



**Rin:** Set Vout = 0V, measure the resistance at Vin.

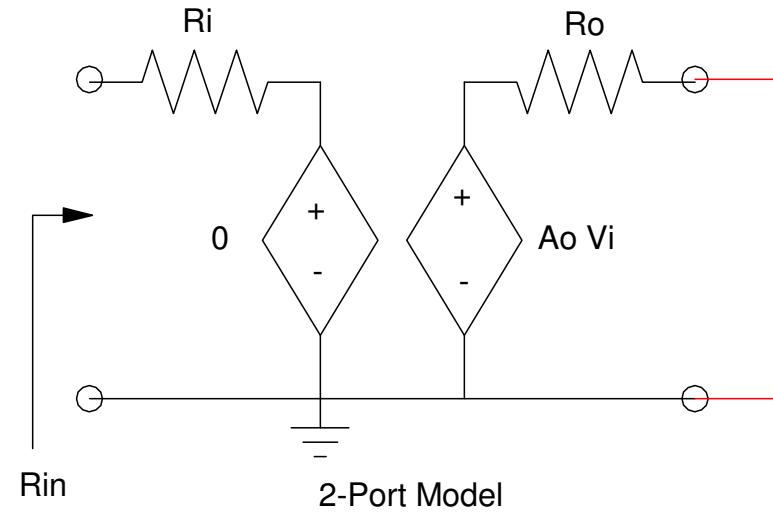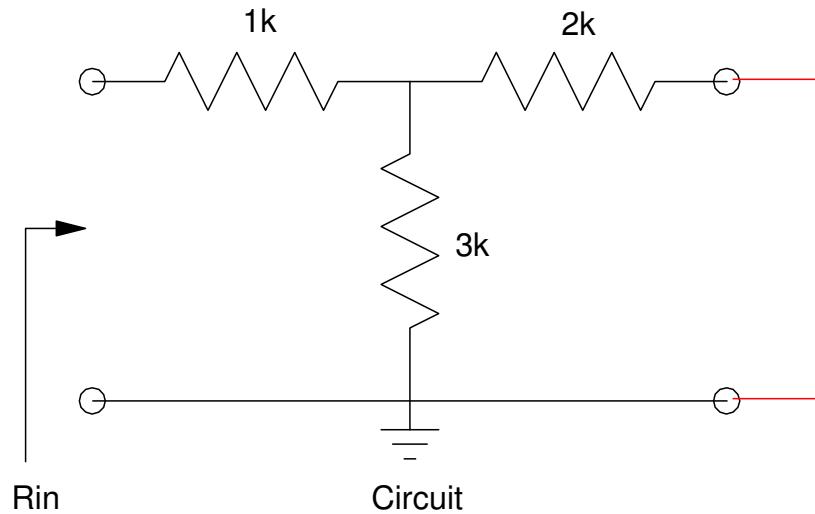- $R_{in} = 1k + 3k \parallel 2k = 2.2k\Omega$




**Rout:** Set  $V_{in} = 0V$ , measure the resistance at  $V_{out}$

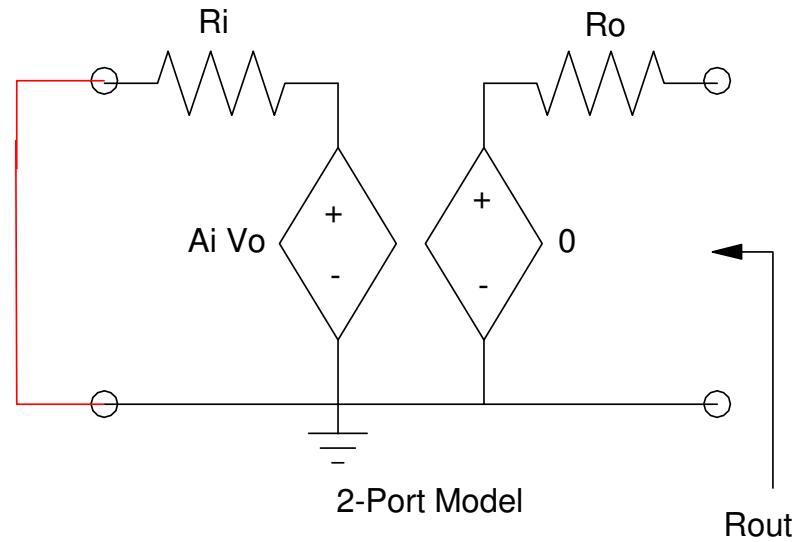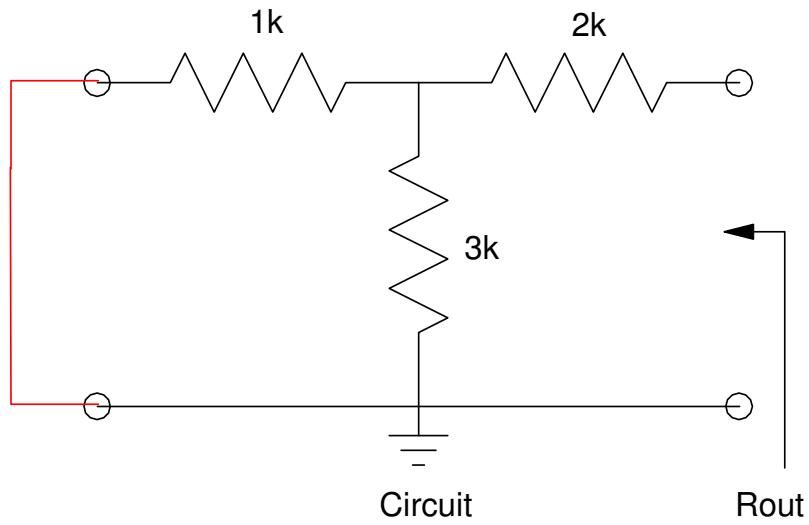- $R_{out} = 2k + 1k \parallel 3k = 2750\Omega$



---


So, the 2-port model is:

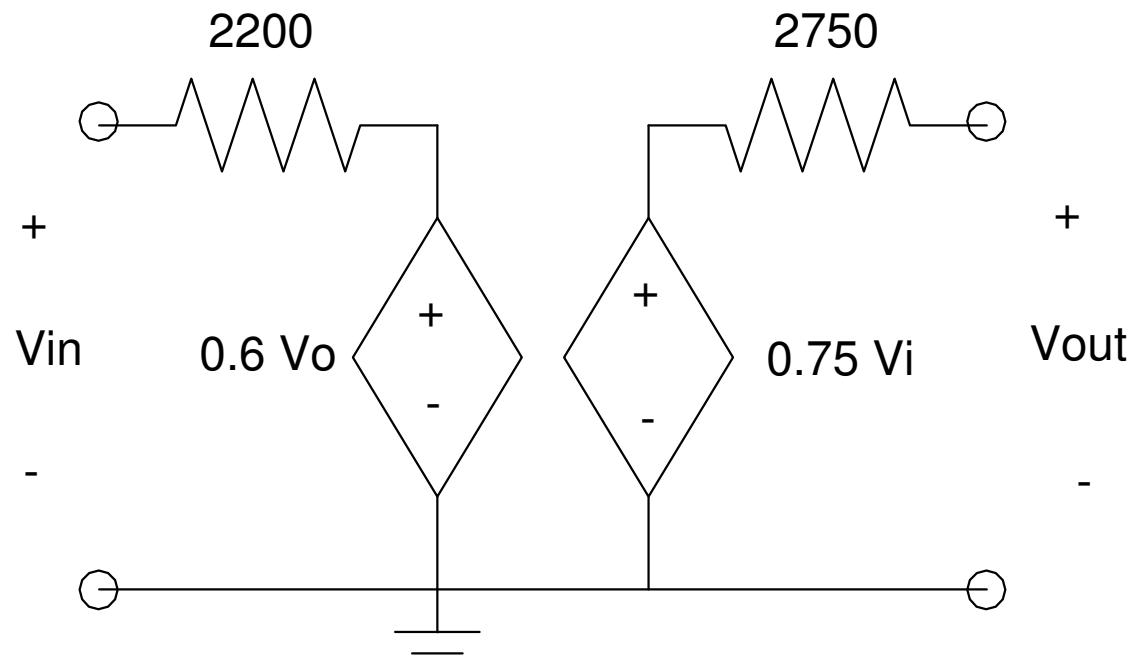


---
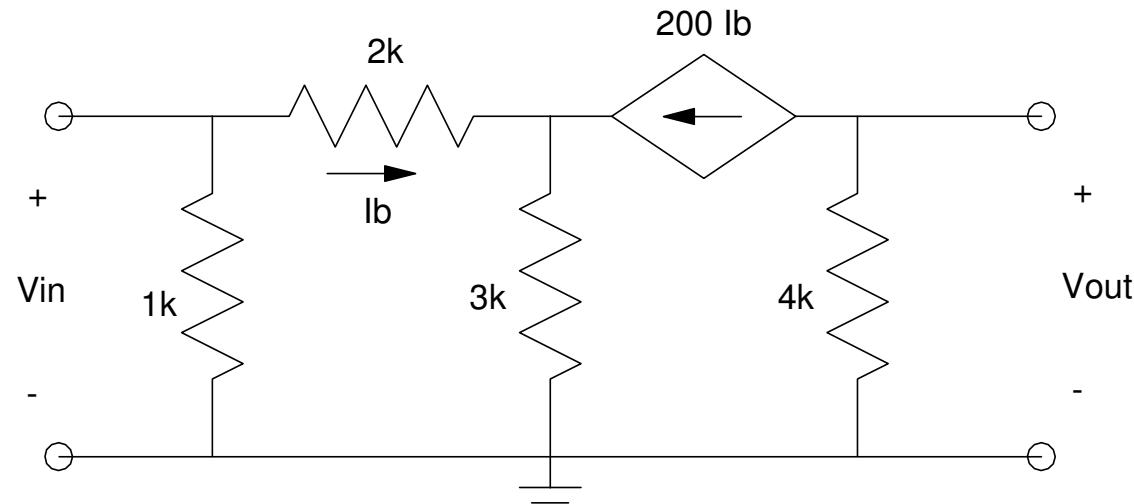
## Example 2: When R isn't obvious

- Apply a test voltage (1V typical)
- Compute the current draw
- $R = 1V / I$



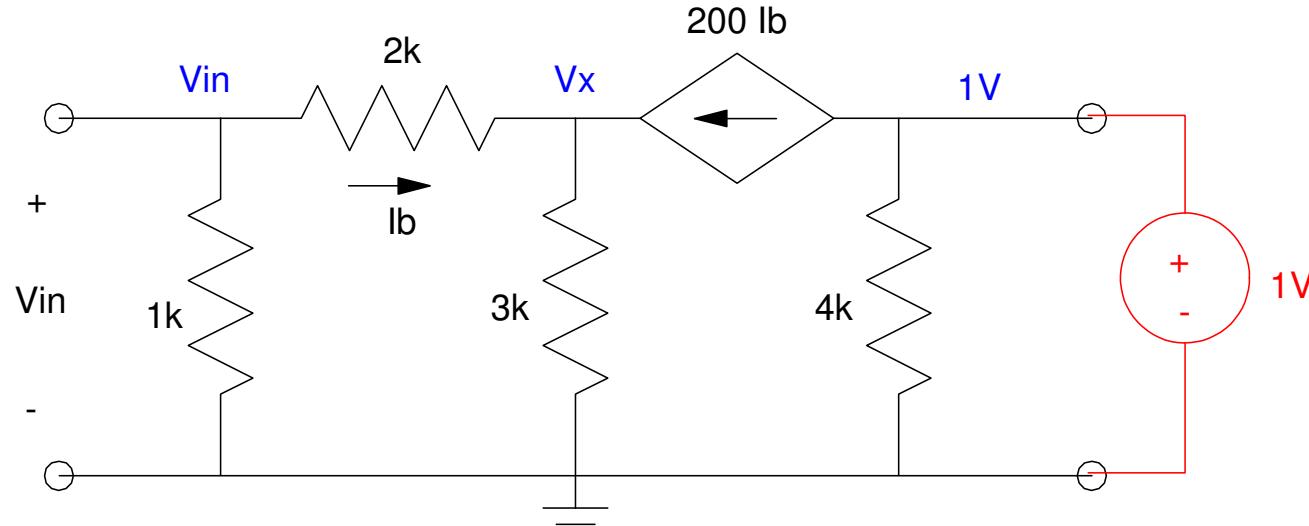Ai: Set  $V_{out} = 1V$ , measure  $V_{in}$



Compute  $V_x$  using voltage nodes:

$$\left(\frac{V_x}{1k+2k}\right) + \left(\frac{V_x}{3k}\right) - 200\left(\frac{0-V_x}{3k}\right) = 0$$

$$V_x = 0 \quad \Rightarrow \quad \mathbf{Ai} = \mathbf{0}$$

---

**Ao:** Set Vin = 1V, measure the voltage at Vo


Find Vx using voltage nodes:

$$\left(\frac{V_x - 1}{2k}\right) + \left(\frac{V_x}{3k}\right) - 200\left(\frac{1 - V_x}{2k}\right) = 0$$

$$V_x = 0.9951V$$

$$I_b = \left(\frac{1 - V_x}{2k}\right) = 2.469\mu A$$


$$V_o = -(200I_b)4k = 1.9753V$$

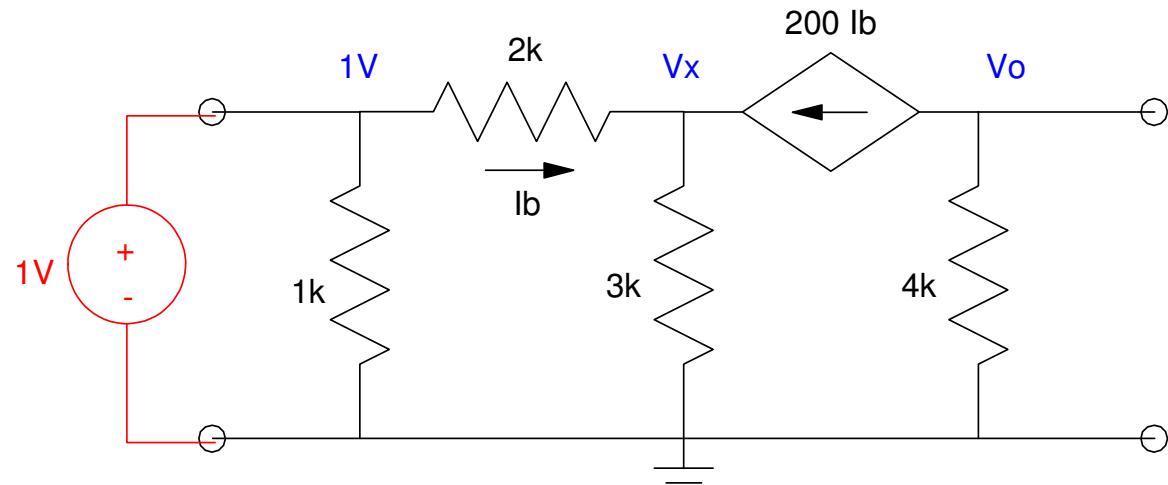

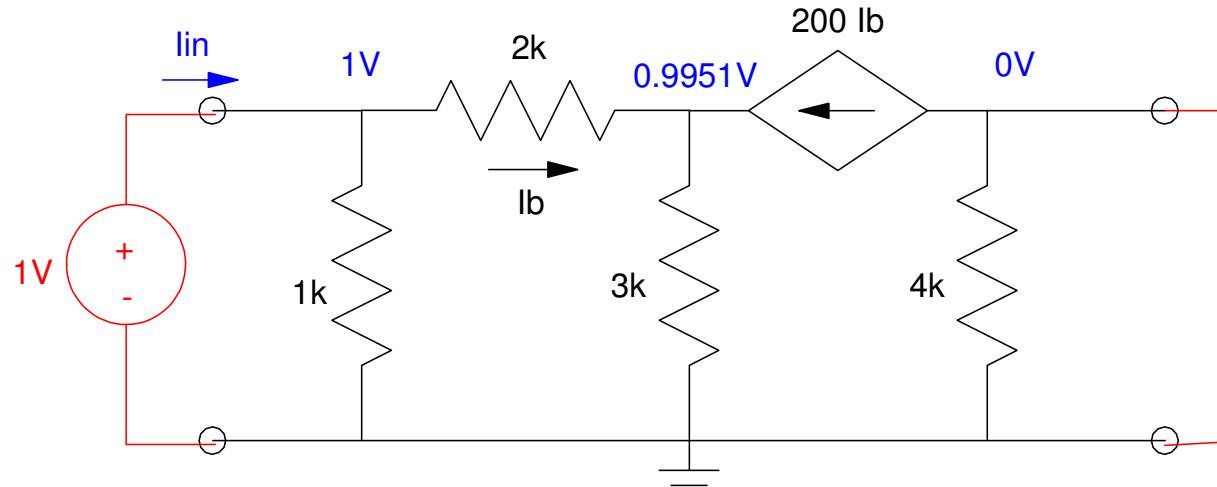**Ao = 1.9753**

---

**Rin:** Set  $V_o = 0V$ , measure the resistance at the input.



From the previous analysis,  $V_x = 0.9951V$ ,

$$I_{in} = \left( \frac{1V - 0.9951V}{2k} \right) + \left( \frac{1V}{1k} \right) = 1.0017mA$$

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{1V}{1.0017mA} = 998\Omega$$

**R<sub>out</sub>:** Set V<sub>in</sub> = 0V, measure the resistance at V<sub>out</sub>.

This isn't obvious, so add a 1V source at the output and compute the resulting current

Solve for V<sub>x</sub>:


$$\left(\frac{V_x - 0}{2k}\right) + \left(\frac{V_x}{3k}\right) - 200\left(\frac{0 - V_x}{2k}\right) = 0$$




$$V_x = 0$$

$$I_{out} = 0 + \left(\frac{1V}{4k}\right) = 250\mu A$$

so

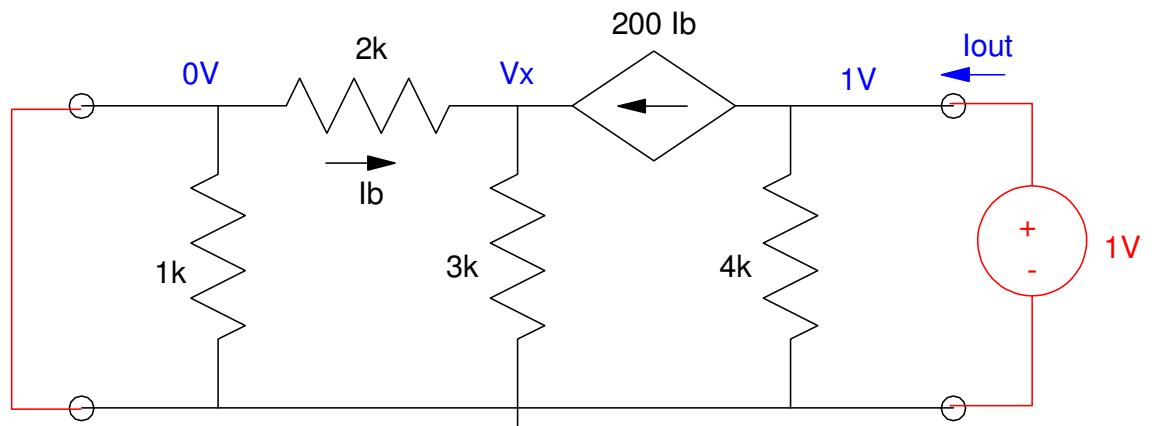
$$R_{out} = \frac{V_{out}}{I_{out}} = \frac{1V}{250\mu A} = 4k\Omega$$



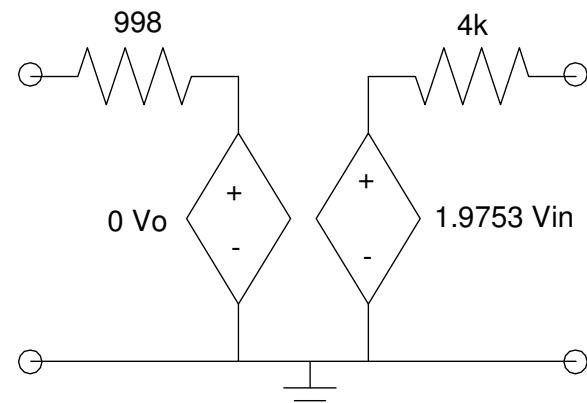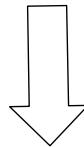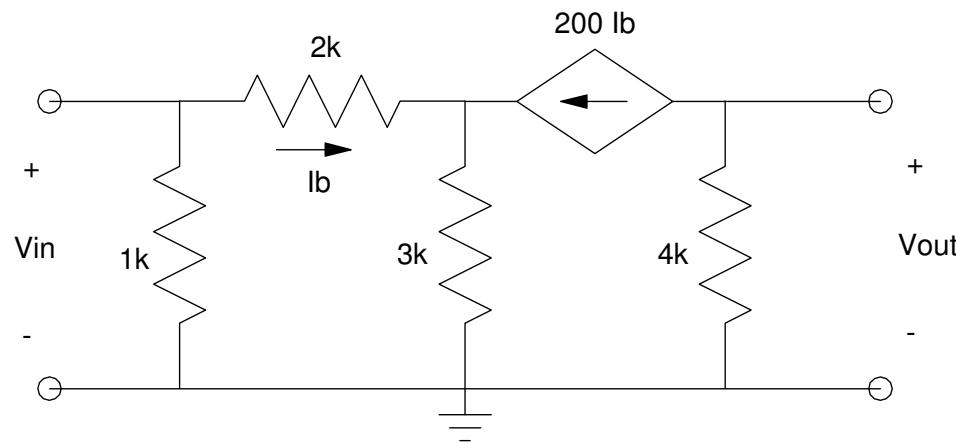
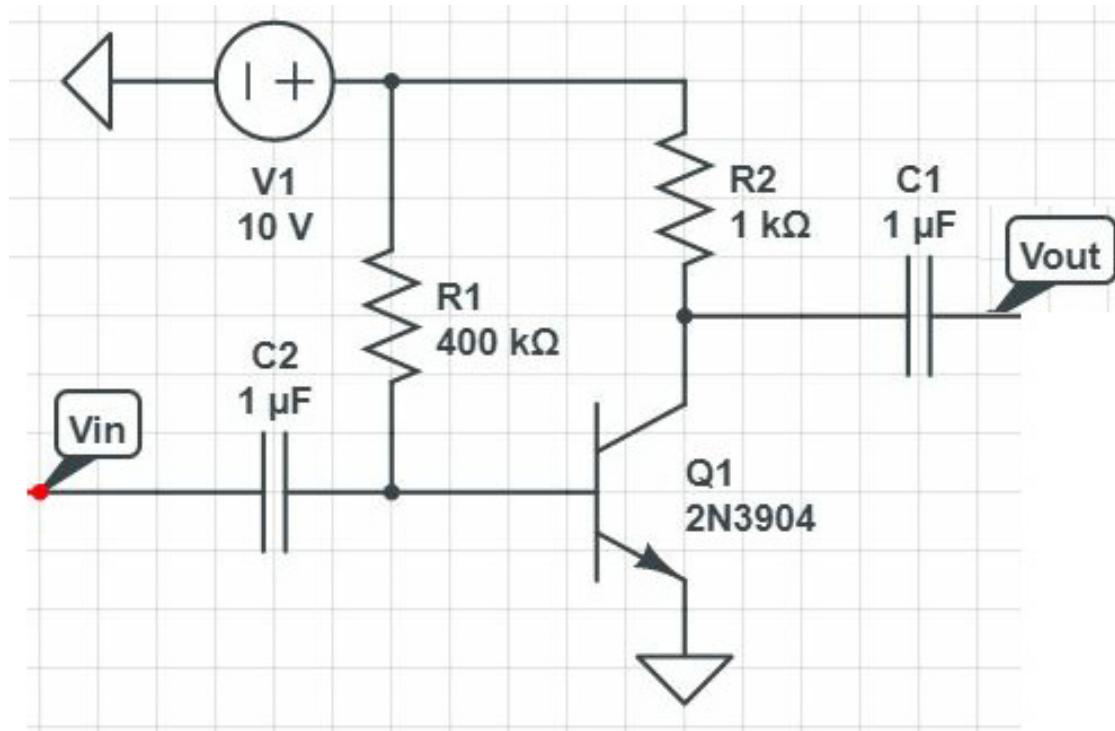
## 2-Port Model: Experimental

- Actually CircuitLab
- Determine the 2-port model at 1kHz





## Ao:

- Open Vout (set Rout = 10M)
- Apply 1mV @ 1kHz at Vin
- Measure Vout

$$V_{out} = 137.5 \text{ mV}_p$$

- out of phase with Vin
- Ao = -137.5

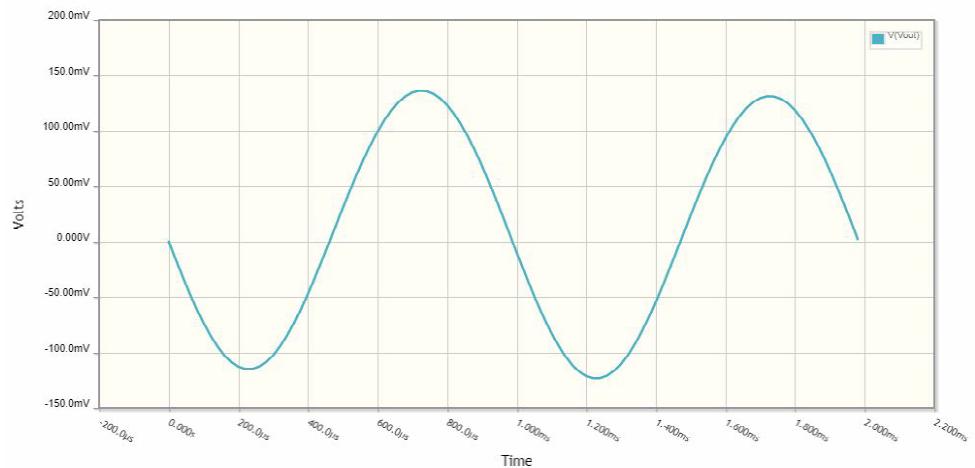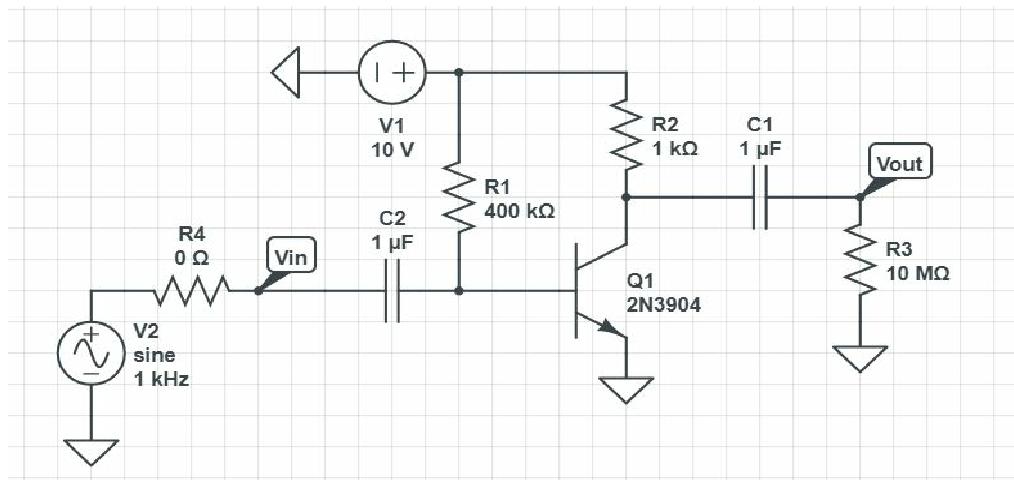

## Rout:

- Apply 1mV @ 1kHz to Vin
- Add a 1k resistor to Vout
- Measure Vout



$$V_{out} = 70.3 \text{ mV}_p$$

Ao = 135.7mV from before

$$70.3 \text{ mV} = \left( \frac{1000}{1000 + R_{out}} \right) 135.7 \text{ mV}$$

$$R_{out} = \left( \frac{135.7 \text{ mV} - 70.3 \text{ mV}}{70.3 \text{ mV}} \right) 1k$$

$$R_{out} = 930.3 \Omega$$

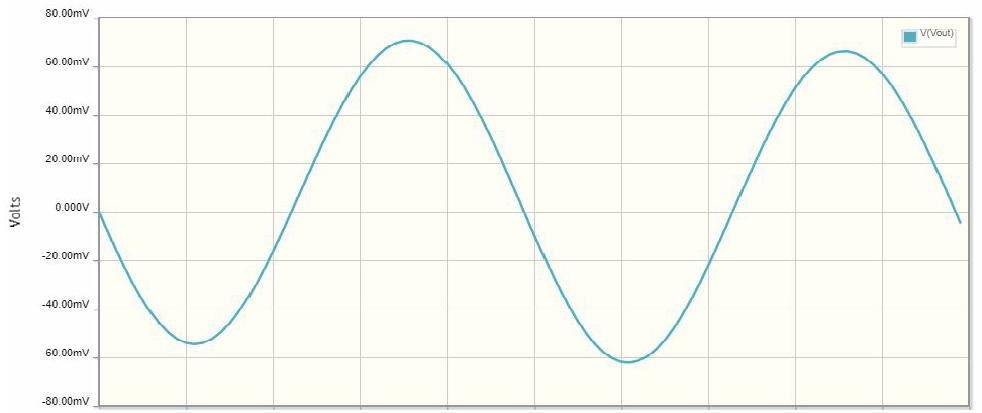
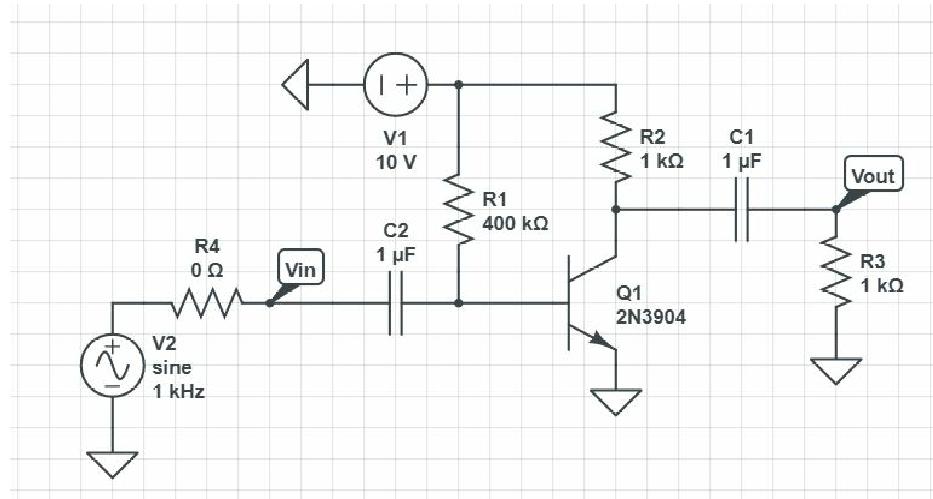


## Ain:

- Apply 1mV 1kHz sine wave at Vout
- Measure Vin

$$Vin = 9.25\text{nV}$$

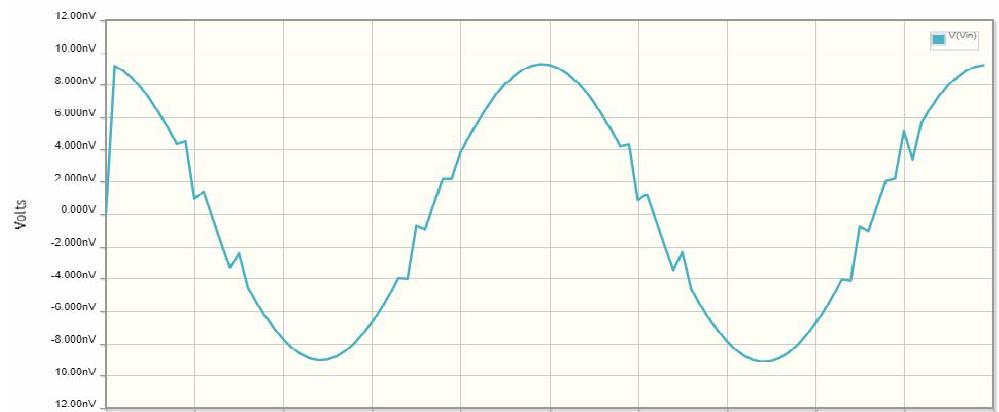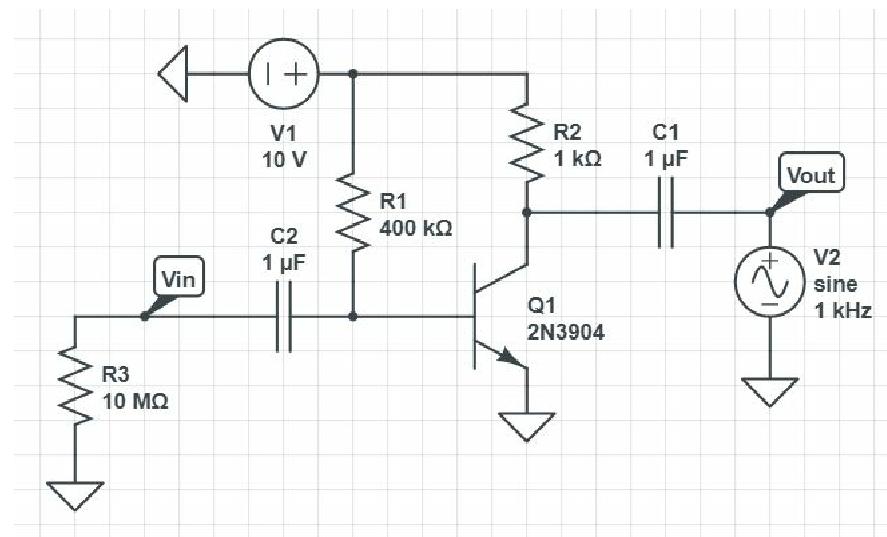- $A_{in} = 0.00925$
- $A_{in}$  is about zero



# Rin



- Since  $A_{in} = 0$
- Apply 1mV 1kHz sine wave to  $V_{in}$
- Add a 1k resistor in series
- Measure  $V_{out}$

$$V_{out} = 71.66\text{mV}$$

$$\left( \frac{R_{in}}{R_{in}+1k} \right) 135.7\text{mV} = 71.66\text{mV}$$

$$R_{in} = \left( \frac{71.66\text{mV}}{135.7\text{mV}-71.66\text{mV}} \right) 1k$$

$$R_{in} = 1119.0\Omega$$

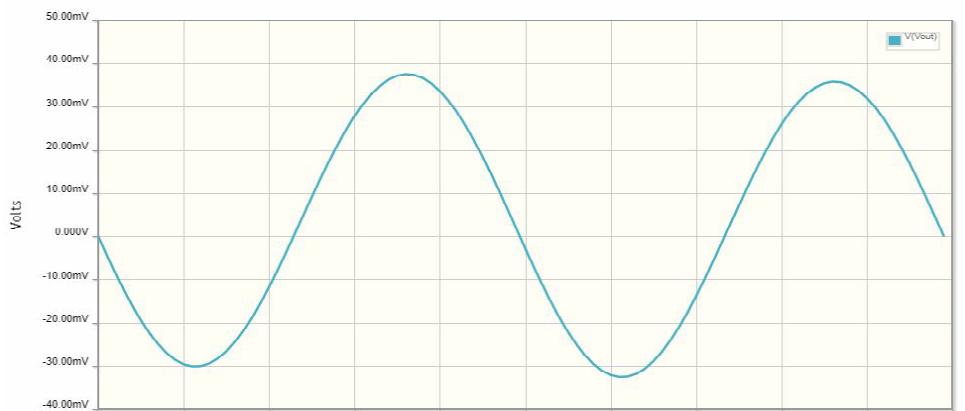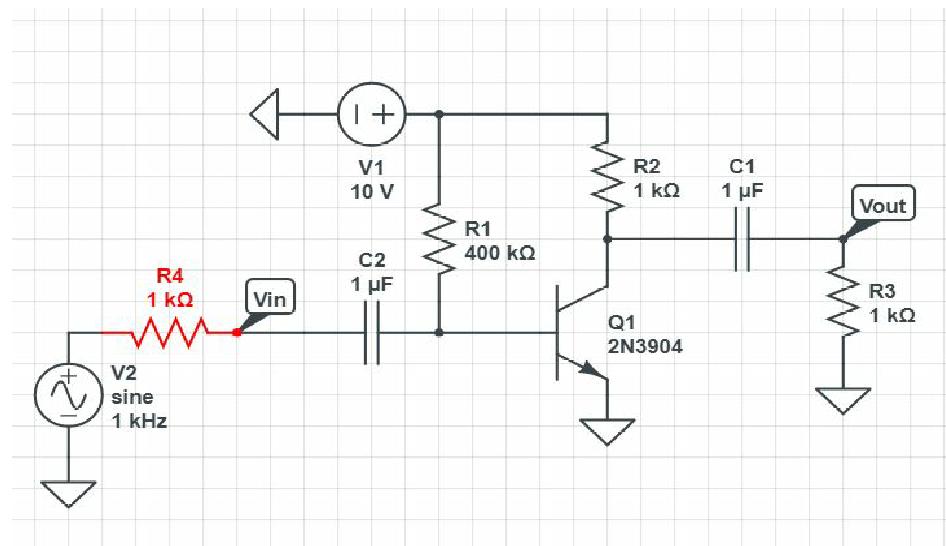

# Summary

2-Port models are a generalized Thevenin equivalent

- Thevenin equivalent at the input ( $V_{out} = 1V$ )
- Thevenin equivalent at the output ( $V_{in} = 1V$ )

With four tests, you can determine

- $A_{in}$
- $R_{in}$
- $A_{out}$
- $A_o$

