
Op-Amps & 555 Timers

ECE 401 Senior Design I

Week #4

Please visit Bison Academy for corresponding lecture notes,
homework sets, and videos
www.BisonAcademy.com



Operational Amplifiers (Op-Amps)

One of the requirements for your 401 project is it must include an integrated circuit (IC). Usually, this is an op-amp, a 555 timer, or a PIC processor.

Op-amps are really useful devices that can do all sorts of things. With op-amps, you can build

- Comparitors
- Schmitt Triggers
- Half-wave and full-wave rectifiers,
- Envelope detectors
- Amplifiers
- Filters

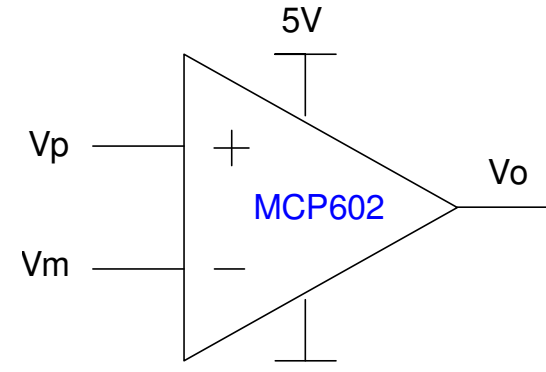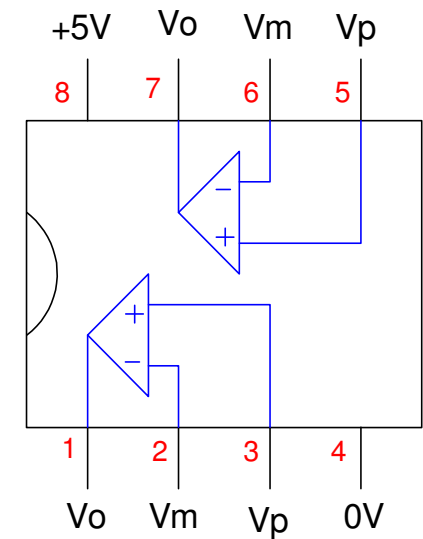to name just a few. Op-amps are just darn useful.





MCP602 Op-Amp

- The heart of a comparitor

Use an MCP602:

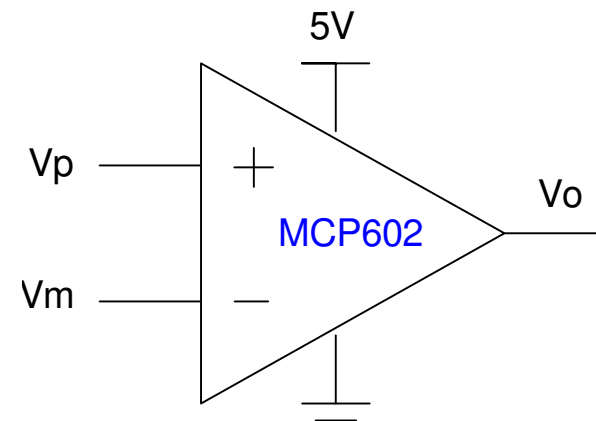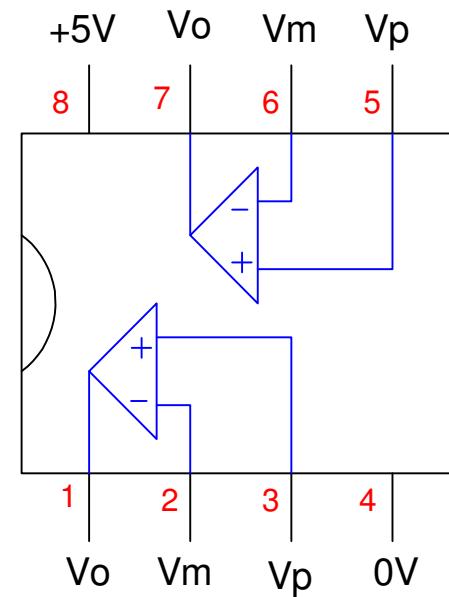- It can operate from a single 5V power supply
 - range is 3V to 6V
- It's a rail-to-rail op-amp.
 - Output can go all the way up to 5.00V
 - Output can go all the way down to 0.00V
- It's a dual op-amp
 - you get two op-amps in each IC




The MCP602 is a high-gain differential amplifier,
where

$$V_o = 200,000(V_p - V_m)$$

What this means is

- $V_p > V_m$
 - The output rails at the upper power supply (5V)
- $V_p < V_m$
 - The output rails at the lower power supply (0V)

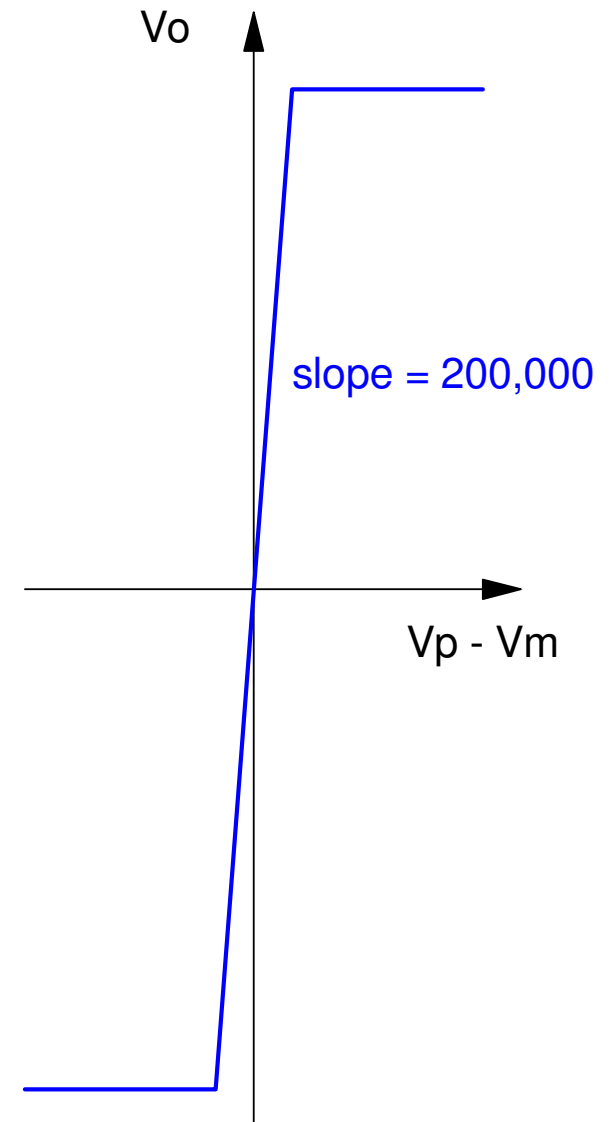This allows you to build several different circuits.




Comparator: $Y = (V_{in} > 2.3V)$

Turn on an LED when $V_{in} > 2.3V$

- Connect V_{in} to V_p
- Connect $2.3V$ to V_m
- This produces the function: $Y = V_{in} > 2.3V$

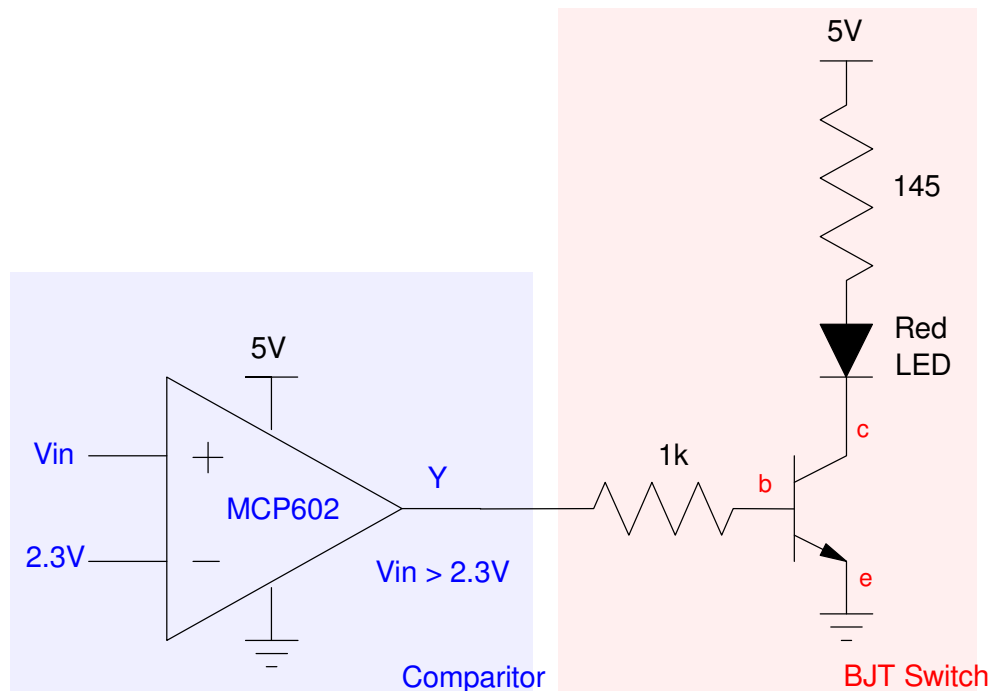If you swap V_p and V_m , you get the opposite ($V_{in} < 2.3V$)



Comparitor: $Y = (T > 20C)$

First, convert temperature to resistance

$$R = 1000 \cdot \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$

Convert resistance to voltage


$$V_x = \left(\frac{R}{R+1000}\right) 5V$$

Connect V_x to V_m

- As T goes up
- R goes down
- V_x goes down
- Y goes up


Connect V_p to $V_x(20C)$

- $R = 1250.59$ Ohms
- $V_x = 2.778V$

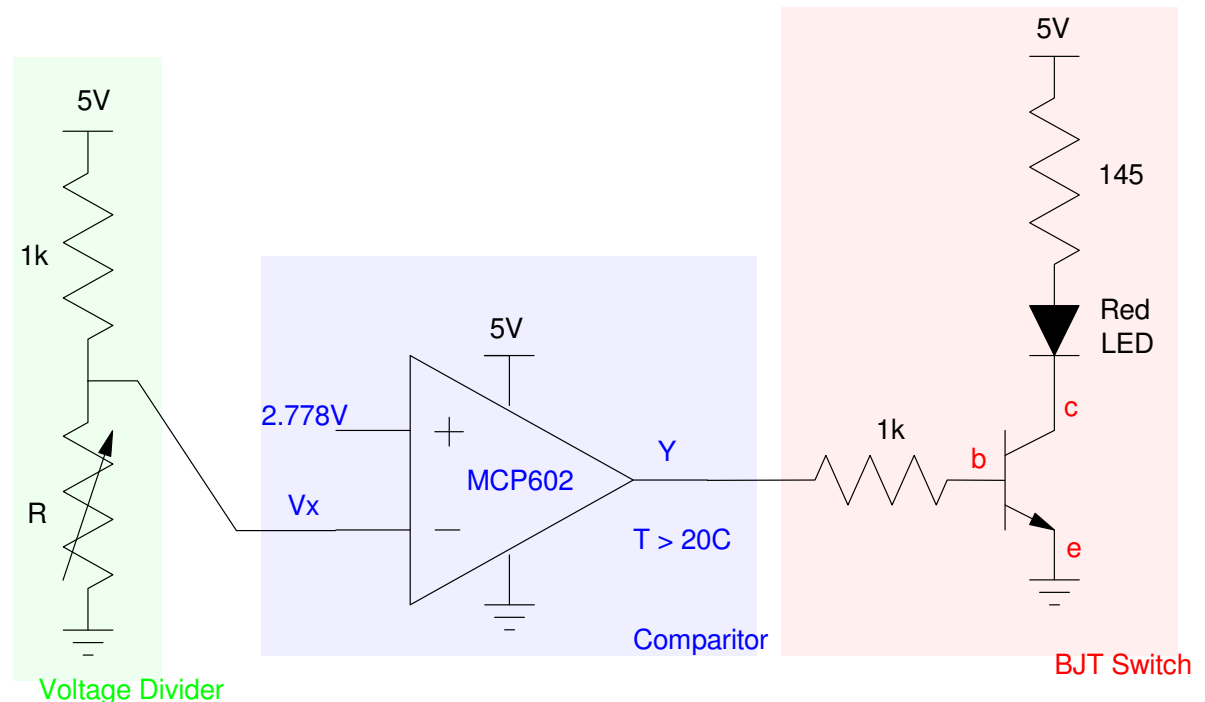

Note

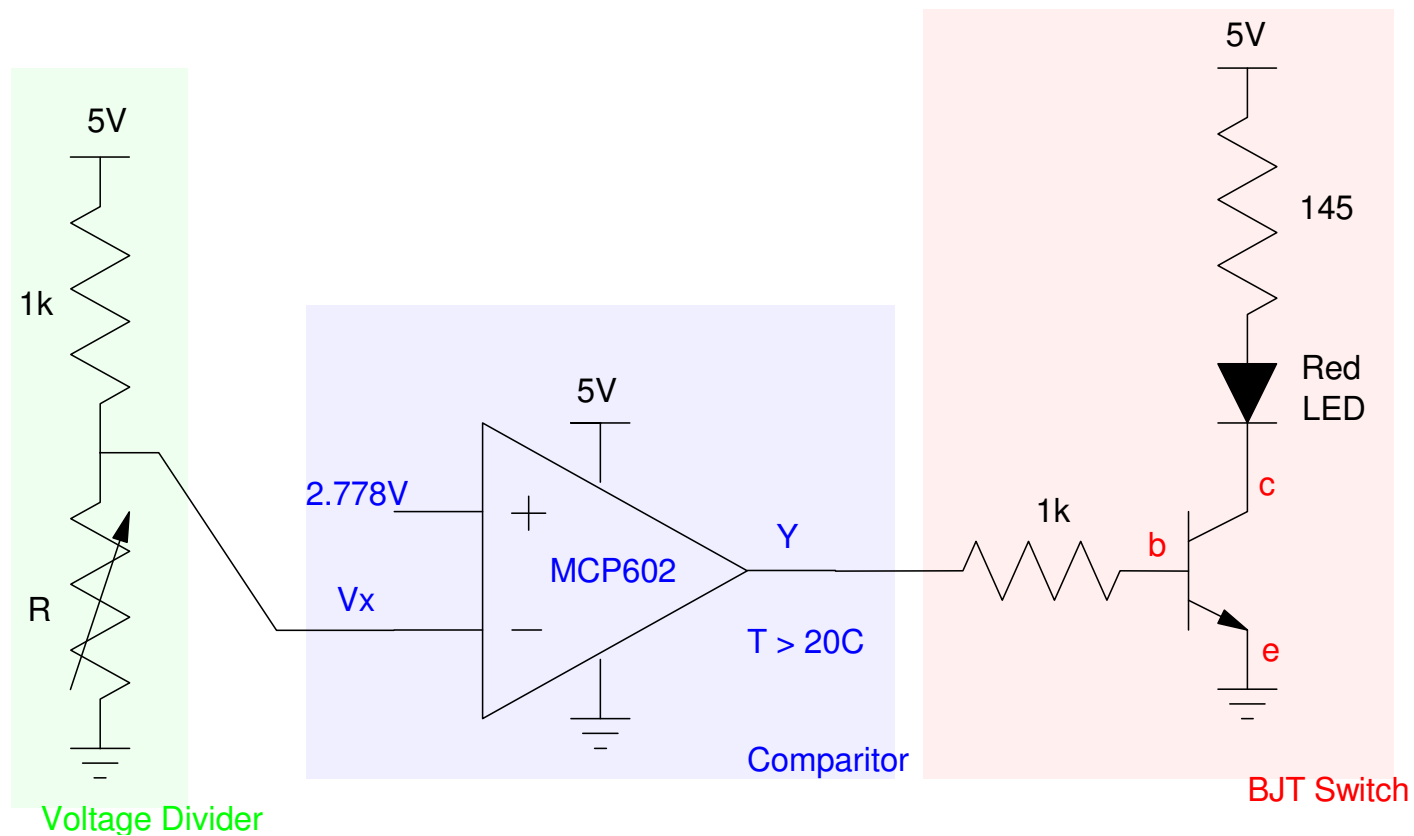- If you swap V_p and V_m , you get the opposite (light is on when $T < 20C$).
- If you change R to a light sensor, the LED turns on and off with light level
- If you change R to a magnetic field sensor, the LED turns on and off with magnetic field strength



Schmitt Triggers


To avoid the chatter you get with comparitors, add hysteresis

- V_{on} and V_{off} are different

The positive feedback on a Schmitt trigger provides this feedback

Schmitt Trigger: $V_{on} > V_{off}$

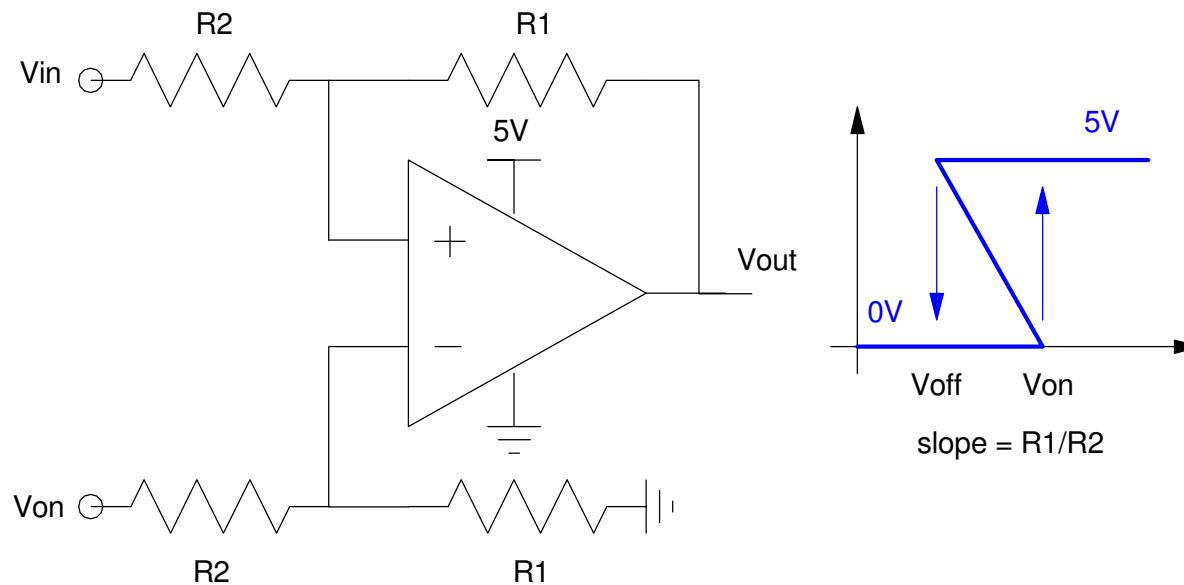- Swap V_{in} and V_{on} if $V_{on} < V_{off}$



Schmitt Trigger when $V_{on} > V_{off}$

Example: design a circuit which turns an LED

- On when $T > 25\text{C}$ and
- Off when $T < 20\text{C}$

When $20\text{C} < T < 25\text{C}$, the LED remains unchanged (on or off).

Step 1: Convert temperature to resistance

- Use a thermistor

$$R = 1000 \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$

Step 2: Convert resistance to voltage

- Use a voltage divider with a 1k resistor

$$V_x = \left(\frac{R}{R+1000}\right) 5V$$

20C

$$R = 1250$$

$$V_x = V_{\text{off}} = 2.778V$$

25C


$$R = 1000$$

$$V_x = V_{\text{on}} = 2.500V$$

Since $V_{on} < V_{off}$, connect to the minus input

$$gain = \left(\frac{\text{change in output}}{\text{change in input}} \right)$$
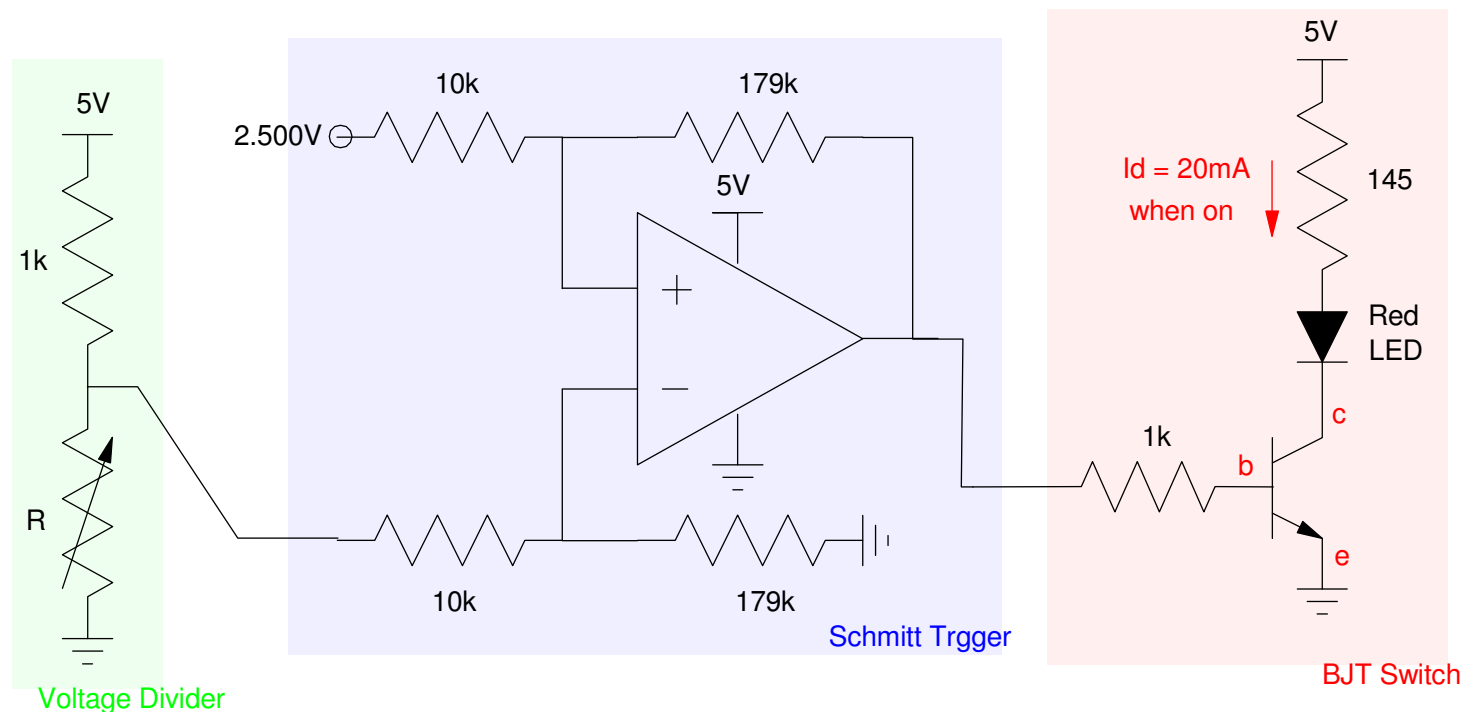
$$gain = \left(\frac{5V - 0V}{2.778V - 2.500V} \right) = 17.96$$




555 Timers

Really useful IC that can make

- An oscillator
 - Keep track of time, make lights blink, etc.
- An light controlled oscillator
 - Frequency varies with light level
 - Or temperature, magnetic field strength, etc.
- A voltage-controlled oscillator
 - Allowing you to make siren noises, and
- A one-shot
 - Output a single pulse

This course looks at an oscillator

- See ECE 320 for other circuits

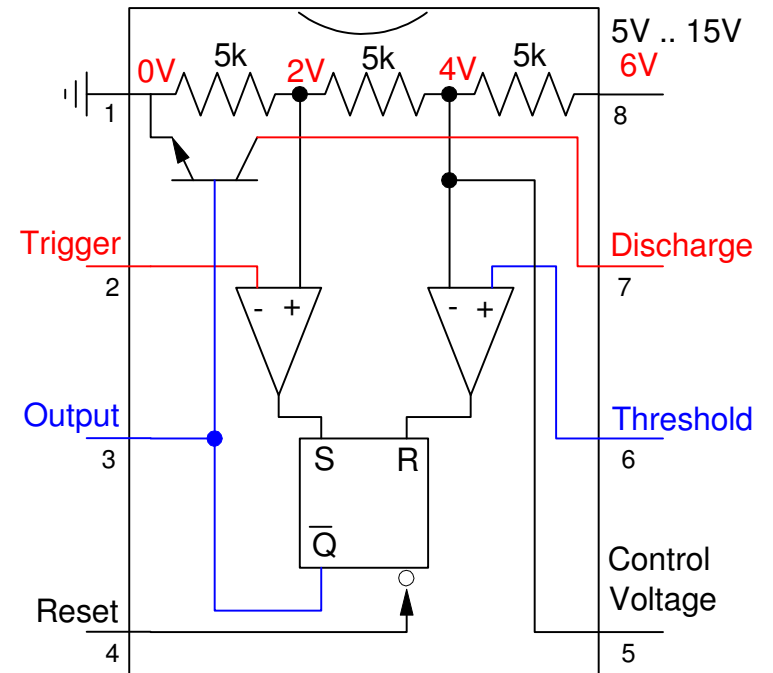


555 Timer:

Name comes from three 5k resistors

Function of Pins:

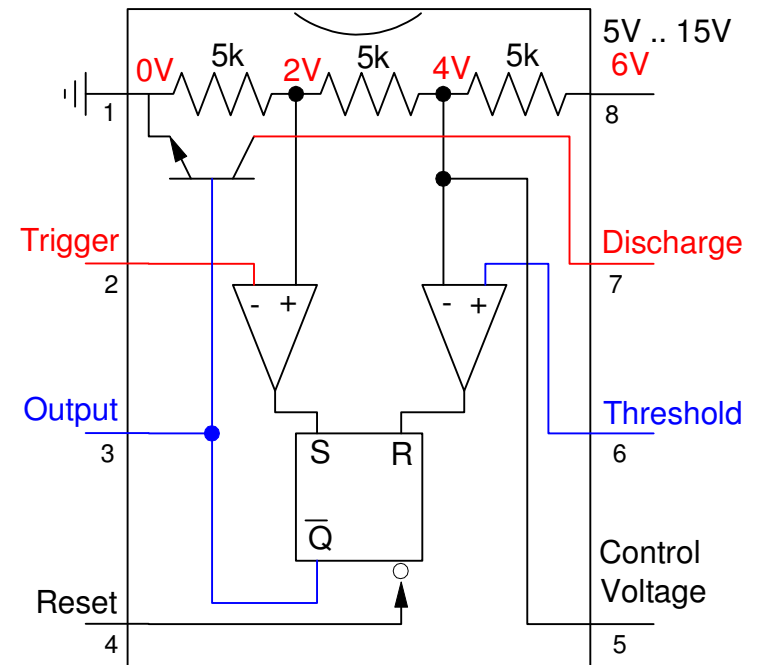- Power and Ground: 0V and 5V
- Trigger: Set the SR flip-flop $> 2V$
- Threshold: Clear the SR flip-flop when $> 4V$
- Control Voltage: Change the threshold voltage
- Discharge:
 - When the output is low, Discharge is shorted to ground through a transistor.
 - Otherwise, Discharge is a floating pin.



555 Oscillator (take 1):

When V2 reaches 1/3 of 5V





- Discharge is floating,
- C charges up to 2/3 of 5V through R1 and R2.

When V2 reaches 2/3 of 5V

- Discharge is grounded
- C discharges down to 1/3 of 5V through R2

Repeat

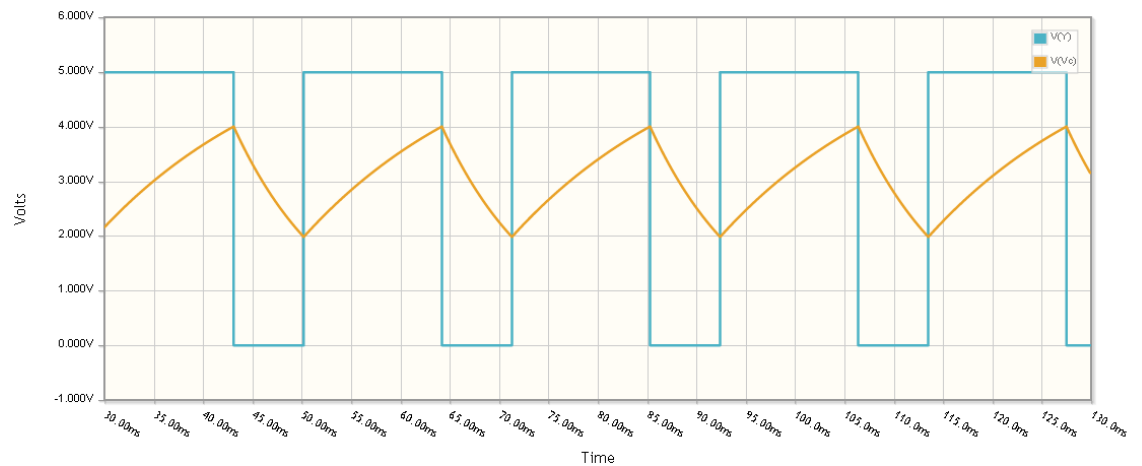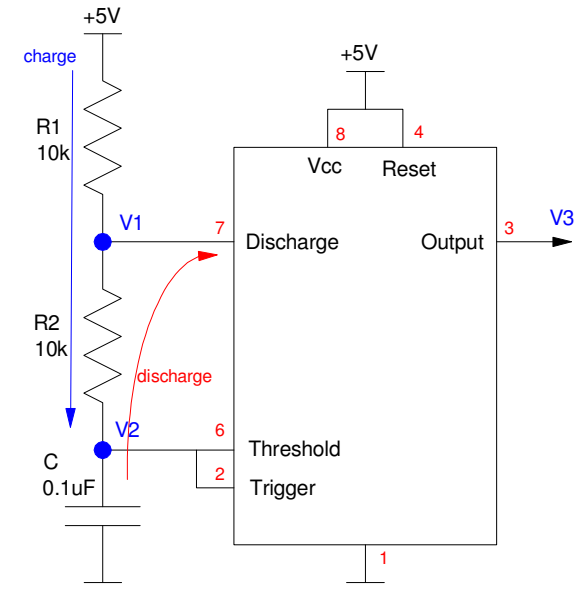

Calculations:

$$T_{on} = (R_1 + R_2) \cdot C \cdot \ln(2)$$

$$T_{off} = R_2 \cdot C \cdot \ln(2)$$

$$T = \text{Period} = T_{on} + T_{off} = (R_1 + 2R_2) \cdot C \cdot \ln(2)$$


For the values given, this works out to

$$T_{on} = 1.386ms$$

$$T_{off} = 0.693ms$$


$$T = \text{Period} = 2.079ms$$

$$f = \frac{1}{T} = 480.9Hz$$

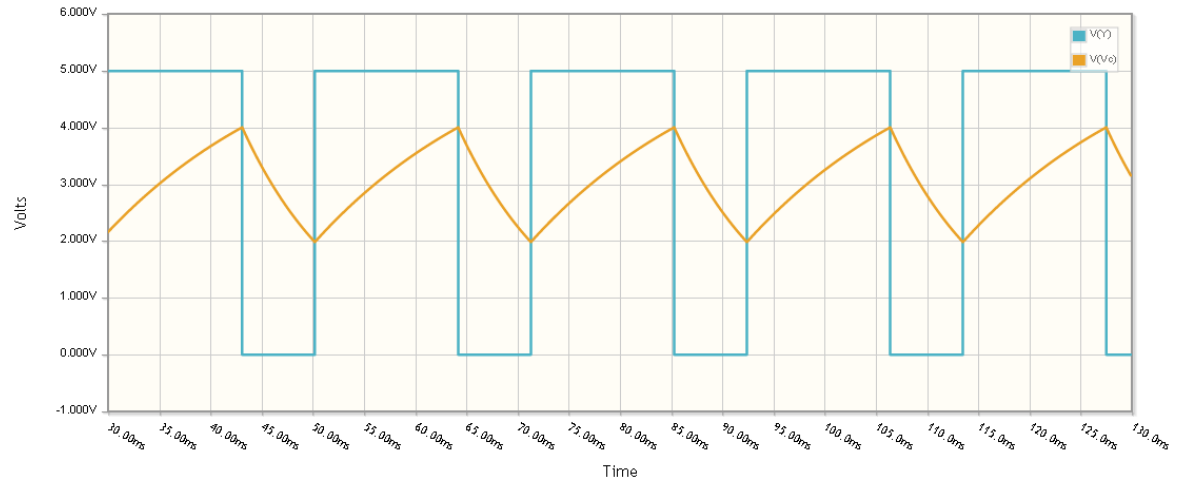

Note

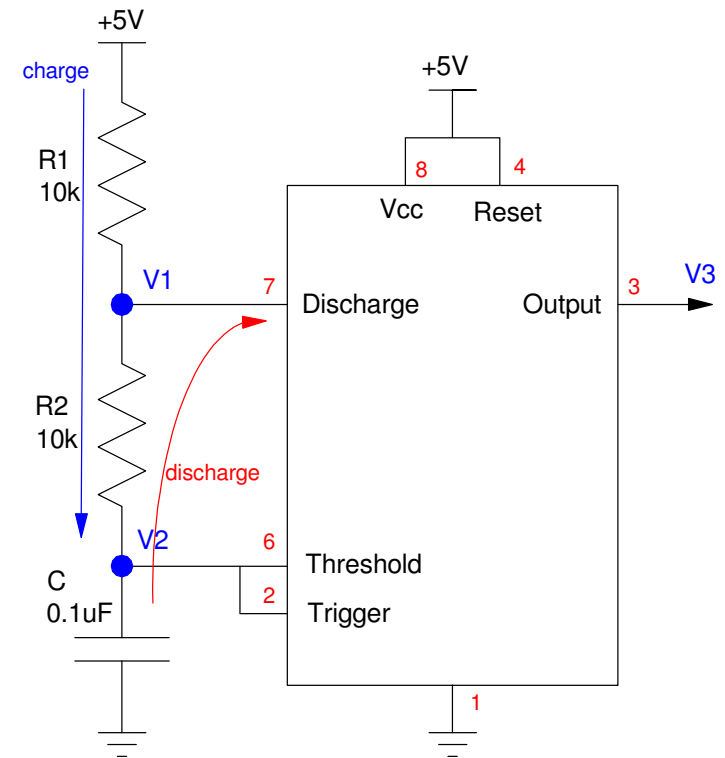
- The on time is twice as large as the off time. This is due to C charging through R1 and R2, while discharging through R2.
- If you replace either resistor with a thermistor or a photo-resistor, the period (and frequency) will change with temperature or light.



555 Oscillator (take 2):

A slight improvement is to add a diode as follows. This results in

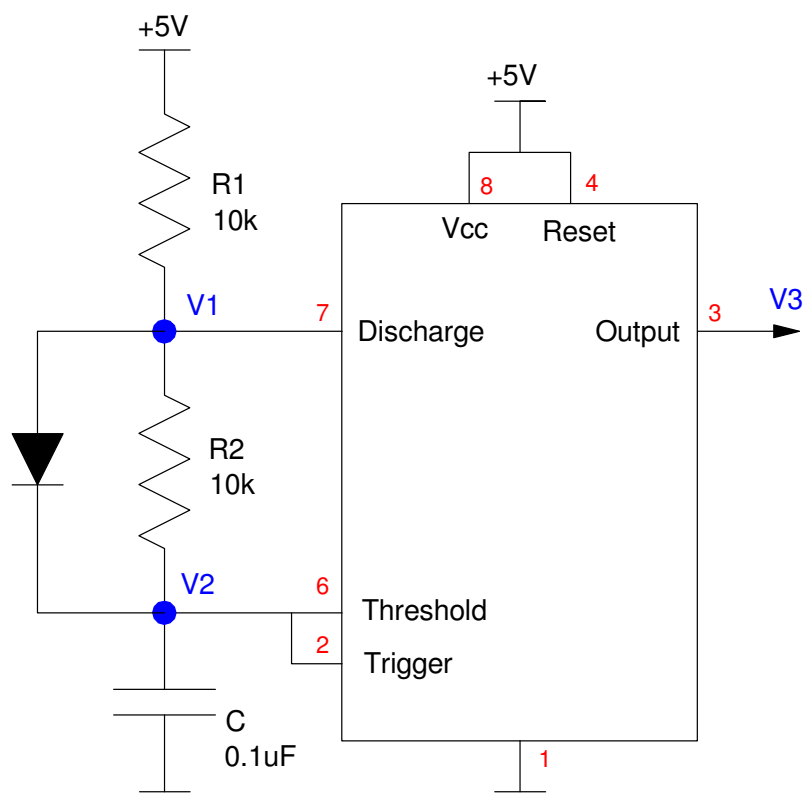- C charging through R1 (R2 is bypassed by the diode), and
- C discharging through R2 (when pin 7 of the 555 timer is grounded).



Calculations

$$T_{on} \approx R_1 \cdot C \cdot \ln(2)$$

$$T_{off} = R_2 \cdot C \cdot \ln(2)$$

If $R_1 = R_2 = 10k$

$$T_{on} \approx 0.693ms$$

$$T_{off} = 0.693ms$$

$$T = T_{on} + T_{off} = 1.386ms$$

$$f = \frac{1}{T} = 721.3Hz$$

note: $T(on)$ is approximate due to ignoring V_d in the calculations for T_{on}

