


ECE 461/661 Handout #16

Rotational Systems with Gears

Draw the circuit equivalent for the following mass-spring system. Assume

- $J = 1\text{kg}$, $B = 0.2\text{ Nms/rad}$, $K = 10\text{N/rad}$

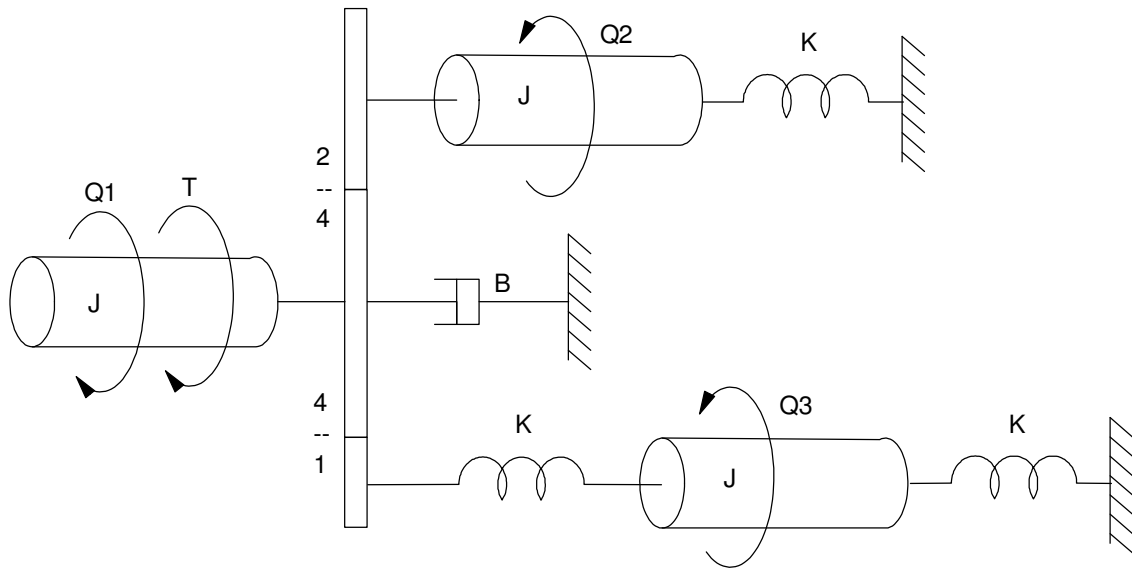Write the equations of motion (i.e. write the voltage node equations)



Rotational Systems with Gears - Solution


ECE 461/661 - Handout for Lecture #16

Draw the circuit equivalent for the following mass-spring system. Assume


- $J = 1\text{kg}$, $B = 0.2\text{ Nms/rad}$, $K = 10\text{N/rad}$

Write the equations of motion (i.e. write the voltage node equations)

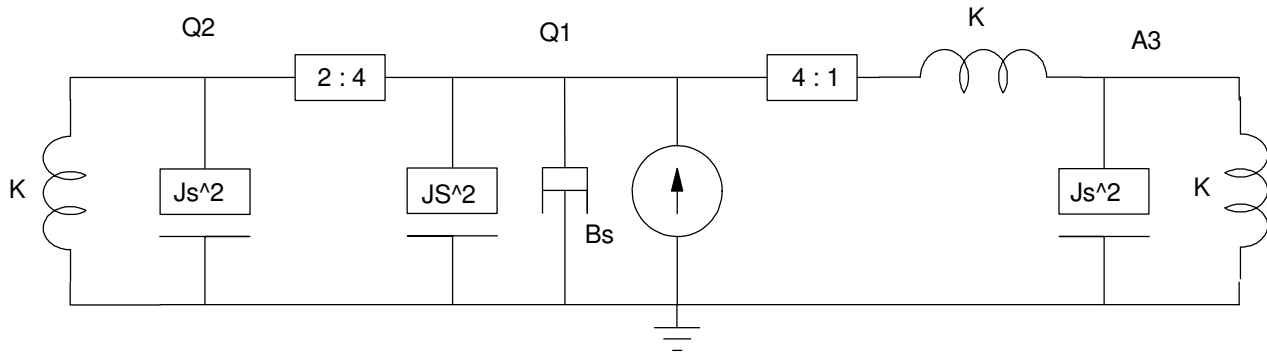First, draw the circuit equivalent with the gears included



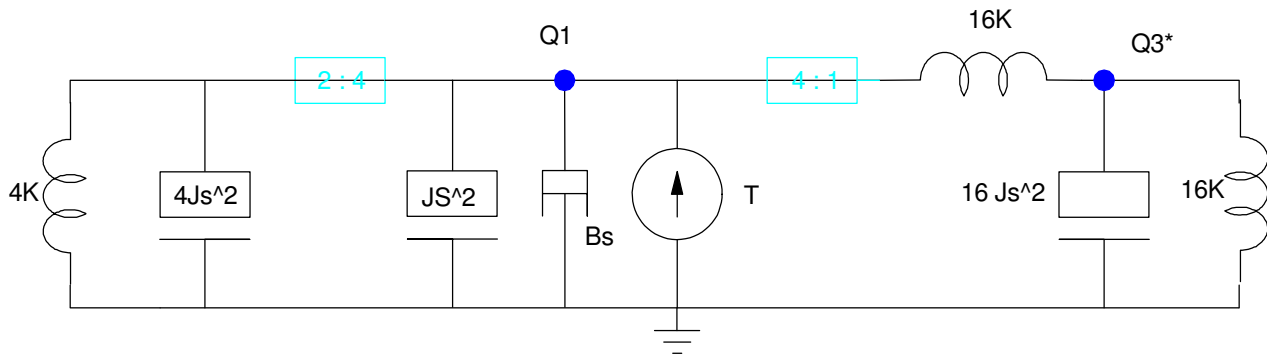next, remove the gears. Take everything to node Q1



Write the node equations (only two nodes)

$$(5Js^2 + Bs + 20K)\theta_1 - (16K)\theta_3^* = T$$

$$(16Js^2 + 32K)\theta_3^* - (16K)\theta_1 = 0$$